

DIGITALS

NOTES

GATE 2009

JANARDHANARAO

Digitals

SUN.

17/08/08

Number Systems:

	<u>Base/Radix</u>	<u>Numbers</u>
1. Decimal	10	0, 1, ..., 9
2. Binary	2	0, 1
3. Octal	8	0, 1, ..., 7
4. Hexadecimal	16	0, 1, ..., 9, A, B, C, D, E, F.

Each Hexa digit $\rightarrow$ 4 bits,

$$3f_{16} \rightarrow 0011\ 1111_2$$

Each octal digit $\rightarrow$ 3 bits

$$316_8 \rightarrow 011\ 001\ 110_2$$

Q. $110010_2 = x_{16}$

$$\begin{array}{r} 0011\ 0010 \\ \hline 3\quad\quad 2 \end{array}$$

$$= 32_{16}$$

Q. $11011.01_2 = x_{16}$

$$\begin{array}{r} 0001\ 1011\ .\ 0100 \\ \hline 1\quad\quad B\quad\quad 4 \end{array}_{16}$$

Q. $6728_{10} = x_2$

$$6728_{10} \rightarrow 6728_8 \rightarrow x_2$$

$$\Rightarrow 16 \overline{) 6728}$$

$$16 \overline{) 420} - 8$$

$$16 \overline{) 26} - 4$$

$$\boxed{1} - 10(A) \uparrow$$

$$1A48_{16}$$

$$= 0001\ 1010\ 0100\ 1000_2$$

Q. Determine the possible bases of the following relations.

(1). $\sqrt{41} = 5$

max. digit is ≤ 5

$\downarrow$ so min value of base is 6, so base ≥ 6

Let base = b.

$$\sqrt{4 \times b^1 + 1 \times b^0} = 5 \times b^0_{10}$$

$$\Rightarrow \sqrt{4b+1} = 5$$

$$\Rightarrow 4b+1 = 25$$

$$\Rightarrow b = 6.$$

Q. $\frac{302}{20} = 12.1$

Let base = b .

$$\Rightarrow \frac{3b^2 + 2}{2b} = b + 2 + \frac{1}{b}$$

Base ≥ 4 b'coz max digit is 3.

$$\Rightarrow \frac{3b^2 + 2}{2b} = \frac{b^2 + 2b + 1}{b}$$

$$\Rightarrow b = 4.$$

Q. $\frac{44}{4} = 11$

Let base = b . Observed base ≥ 5 , b'coz maximum value of digit = 4.

$$\frac{4b+4}{4} = b+1 \Rightarrow b+1 = b+1$$

The above relation is valid in all the no. system with base ≥ 5 .

Q. In a positional weight system x & y are two successive digits and $xy = 25_{10}$ & $yx = 31_{10}$. Determine the values of base x & y .

Here $b = ?$, $x = ?$ & $y = ?$

and $y = x+1$.

$$(x)(x+1) = 25_{10} \quad ((x+1)b + x) = 31_{10} \quad (1)$$

$$\Rightarrow [x \times b + (x+1) = 25]_{10} \Rightarrow x(b+1) + b = 31 \rightarrow (2)$$

$$\Rightarrow x(b+1) + 1 = 25 \rightarrow (1)$$

$$(1) - (2) \Rightarrow b = 7. \text{ Then from (1) } \Rightarrow x = 3, y = 4.$$

Complementary Number Representation :-

Base = 2

$\Rightarrow (2-1)$'s Complement

$\Rightarrow 2$'s complement

Decimal system ($2=10$).

$$9\text{'s complement of } 168_{10} \Rightarrow \begin{array}{r} 999 \\ - 168 \\ \hline 831_{10} \end{array}$$

$$10\text{'s complement of } 168_{10} \Rightarrow 9\text{'s comp} + 1$$

$$\Rightarrow \begin{array}{r} 999 \\ - 168 \\ \hline 831 \end{array} + 1 = 832_{10}$$

Q. 862_{10}

$$\begin{array}{r} 491_{10} \\ (-) \hline ? \end{array} = 862_{10} + (-491_{10})$$

$$(i). \begin{array}{r} 862 \\ + (9\text{'s of } 491) \\ \hline \end{array} \Rightarrow \begin{array}{r} 862 \\ + 508 \\ \hline 1370 \\ \text{(+1)} \rightarrow \text{EOC} \\ \hline 371 \end{array}$$

$$(ii). \begin{array}{r} 862 \\ + (10\text{'s of } 491) \\ \hline \end{array} = \begin{array}{r} 862 \\ + 509 \\ \hline 1371 \end{array}$$

EOC (1) ignore

Q. 491_{10}

$$\begin{array}{r} 491_{10} \\ - 862_{10} \\ \hline ? \\ - 371_{10} \end{array} = \begin{array}{r} 491 \\ + (-862) \\ \hline \end{array} = \begin{array}{r} 491 \\ + 138 \leftarrow 10\text{'s} \\ \hline \end{array}$$

NO EOC
↓
629
↓ 10's
371

Digital System ($2=2$)

1's complement of $1011 \Rightarrow 0100_2$

2's complement of $1011 \Rightarrow 1\text{'s of } 1011 + 1$

$$\Rightarrow 0100 + 1 = 0101$$

Q. $x = 1000111\underline{000}$

2's complement of $x = 011100\underline{1000}$

Q. $x = 1011$

2's of $x = 0101$

Q. $11010_2 - 01110_2 = +(-01110)$

(i). $11010 + (1's \text{ of } 01110) = 11010 + 10001$

(ii). $11010 + (2's \text{ of } 01110)$

$$\begin{array}{r} 11010 \\ + 01011 \\ \hline 100101 \end{array}$$

EOC ① 01011
→ +1
01100

$11010 = 10010$

$$\begin{array}{r} 11010 \\ + 10010 \\ \hline 101100 \end{array}$$

EOC ignore ① 01100

Q. $01110_2 - 11010_2 = + (2's \text{ of } 11010)$

$01110 = 00110$

NO EOC → 10100
↓ 2's
01100

$2^4 = 16$
 $16 - 2 = 14$

$16 - 1 = 15$

1's comp

2's comp

$+0 = 0000$

$+0 = 0000$

$-0 = 1's \text{ comp of } +0$

$-0 = 2's \text{ comp. of } +0$

$= 1's \text{ of } 0000$

$= 0000$

$= 1111$

(Disadv. of 1's complement)

* Range of numbers represented using

'n' bits

Go represent
(16)
numbers

$$1's \text{ comp. form} \Rightarrow + (2^{n-1} - 1) \text{ to } - (2^{n-1} - 1)$$

$$\text{Let } n=4 \Rightarrow +7 \text{ to } -7 \rightarrow (14)$$

$$2's \text{ comp. form} \Rightarrow + (2^{n-1} - 1) \text{ to } -2^{n-1}$$

$$\text{Let } n=4 \Rightarrow +7 \text{ to } -8 \rightarrow (15)$$

Q. How many bits are required to represent -64_{10} in a). 1's comp. form b). 2's form

$$1's \text{ form} \Rightarrow + (2^{n-1} - 1) \text{ to } - (2^{n-1} - 1)$$

$$\text{Let } n=7 \Rightarrow +63 \text{ to } -63$$

$$\checkmark n=8 \Rightarrow +127 \text{ to } -127$$

$$2's \text{ form} \Rightarrow + (2^{n-1} - 1) \text{ to } -2^{n-1}$$

$$\checkmark \text{Let } n=7 \Rightarrow +63 \text{ to } -64$$

Q. 10's comp for $(731)_{10}$


$$\begin{array}{r} A \ A \ A \\ 7 \ 3 \ 1 \\ (-) \hline 3 \ 7 \ 9 \end{array}$$

Q. 9's comp of $(731)_{10}$

$$\begin{array}{r} 9 \ 9 \ 9 \\ (-) \ 7 \ 3 \ 1 \\ \hline 2 \ 6 \ 8 \end{array}$$


Binary Numbers:

(a). Unsigned Numbers $\rightarrow$

 

(b). Signed Numbers

$\downarrow$ represented by

 

(i). sign magnitude

(ii). 1's comp form

(iii). 2's comp form

0 $\Rightarrow$ +ve

1 $\Rightarrow$ -ve

These

three representations are same for unsigned (+ve Numbers).

(i). sign magnitude $\Rightarrow +3 = \underline{011}$
 $-3 = \underline{111}$

(ii). 1's comp. form $\Rightarrow +3 = 011$
 $-3 = \underline{1's \text{ comp of } +3}$
 $= 100$

(iii). 2's comp. form $\Rightarrow +3 = 011$
 $-3 = \underline{2's \text{ comp of } +3}$
 $= 101$

Q. Decimal equivalent of 2's number 101 is -?
 $\swarrow \downarrow 2's$
 $\downarrow$
 $\underline{011}$
 $= -3_{10}$

Q. Decimal equivalent of sign mag. no. 111 is -?
 -3_{10}

Q. Represent $+53_{10}$ & -53_{10} in all the 3 forms of signed no. representation.

$53_{10} \rightarrow$

2	53	
2	26 - 1	$= 110101_2$
2	13 - 0	
2	6 - 1	$+53 = 0110101$
2	3 - 0	
	1 - 1	

Sign mag. form 0110101
 $\downarrow$
 1110101

$+53_{10}$ 1's form 0110101 2's form 0110101

-53_{10} $-53 = 1's \text{ of } +53$ $-53 = 2's \text{ of } +53$
 $= 1001010$ 1001011

Q. What are the decimal equivalents of the following signed no.s in all the 3 forms.

	Sign mag. form	1's form	2's form
01101	$+13_{10}$	$+13_{10}$	$+13_{10}$
101010	$\begin{array}{r} 101010 \\ -10_{10} \end{array}$	$\begin{array}{r} 101010 \\ \downarrow 1's \\ -010101 \\ = -21_{10} \end{array}$	$\begin{array}{r} 101010 \\ \downarrow 2's \\ -010110 \\ = -22_{10} \end{array}$
111111	$\begin{array}{r} 111111 \\ -1_{10} \end{array}$	$\begin{array}{r} 111111 \\ \downarrow 1's \\ -0 \end{array}$	$\begin{array}{r} 111111 \\ \downarrow 2's \\ -1 \end{array}$

Q. Decimal equivalent of 2's no. 1000 is - ?

$$\begin{array}{r} 1000 \\ \downarrow 2's \\ -1000 \\ = -8_{10} \end{array}$$

Q. Decimal equivalent of 2's no. 10000 is - ?

$$\begin{array}{r} 10000 \\ \downarrow 2's \\ -10000 \\ = -16_{10} \end{array}$$

Q. What is the equivalent 2's comp representation of a 2's comp. no. 1101 is - ?

(a). 001101 (b). 011101 (c). 101101 (d). 111101

$$+6 = 0110$$

$$-6 = 2's \text{ of } +6 = 2's \text{ of } 0110$$

$$= 1010$$

$$= 2's \text{ of } 00110 = 11010$$

$$= 2's \text{ of } 000110 = 111010$$

Q. A Register contains a 2's comp. no. 10110
 what is the content of the register if
 it is divided by 2.


decimal equi. of 10110 = -01010

$$= -\frac{10_{10}}{2} = -5$$

-5 = 2's of +5

= 2's of 00101 = 11011


(or).

 

Binary codes:-

a). Alpha numeric { ASCII code
 [7 bits, $2^7 = 128$ Alpha numerals]
 EBCDIC
 [8 bits, $2^8 = 256$ Alpha numerals]

 b). Numeric { BCD $\rightarrow$ each decimal digit $\rightarrow$ 4 bits



Excess-3 : self complementary code, Sequential code.

8421 : Sequential code.

Dec. digit	Natural BCD	Self comple			
		EXCESS-3	2421	631-1	Gray
0	0000	0011	0000	0000	0000
1	0001	0100	0001	0010	0001
2	0010	0101	0010	0101	0011
3	0011	0110	0011	0100	0010
4	0100	0111	0100	0110	0100
5	0101	1000	1011	1001	0101
6	0110	1001	1100	1011	0100
7	0111	1010	1101	1010	0100
8	1000	1011	1110	1101	1100
9	1001	1100	1111	1111	1101

743₁₀ in (1). BCD $\rightarrow$ 0111 0100 0011_{BCD}

(2). 3321 $\rightarrow$ 1101 0101 0011₃₃₂₁

3
↓
1000 } Self
0100 } complementary
0011 }
(3321)
7
→ 2 = 0010
(3321)
Now 7 → comp. of 0010
= 1101.

(3). Binary $\rightarrow 2^n \geq 743$, $n = 10$.

16 | 743
16 | 46 - 7
16 | 2 ↗ 14 (E)

$2E7_{16} = 0010 1110 0111_2$

Gray code: (reflective code, unit distance code)

1-bit 2-bit 3-bit

0 00 000

1 01 001

0+0=0
0+1=1
1+0=1
1+1=0
Modulo-2
Addition
(Exclusive OR)

Binary: 10110

Gray: 11101

Binary: 10110

differ by 1-bit

permits: 20A

2FI
458
0001

BCD Addition :-

$$\begin{array}{r} 6_{10} = 0110_{BCD} \\ + 2_{10} = 0010_{BCD} \\ \hline 1000_{BCD} \\ \downarrow 8_{10} \end{array}$$

$$\begin{array}{r} 8_{10} = 1000_{BCD} \\ + 6_{10} = 0110_{BCD} \\ \hline 1110 \rightarrow \text{not a valid BCD.} \\ + 0110 \\ \hline 0001 \quad 0100_{BCD} \\ \hline 14_{10} \end{array}$$

$$\begin{array}{r} 9_{10} = 1001_{BCD} \\ + 8_{10} = 1000_{BCD} \\ \hline 1 \quad 0001 \\ + 0110 \\ \hline 1 \quad 0111_{BCD} \\ \hline 17_{10} \end{array}$$

Decimal Binary/Hexa

0	0
1	1
2	2
3	3
4	4
5	5
6	6
7	7
8	8
9	9
10	A
11	B
12	C
13	D
14	E
15	F
16	10

Q. In the following BCD additions how many BCD corrections are required.

$$\begin{array}{r} 49_{10} = 0100 \quad 1001 \\ + 57_{10} = 0101 \quad 0111 \\ \hline 1010 \quad 0000 \\ + 0110 \quad 0110 \\ \hline 1 \quad 0000 \quad 0110 \\ \hline 1 \quad 0 \quad 6_{10} \end{array}$$

Ans: 2 times

$$\begin{array}{r} 176_{10} \\ + 824_{10} \end{array}$$

Ans: 3 times

$$\begin{array}{r} 176 \\ 824 \\ \hline 1000 \end{array}$$

$$\begin{array}{r} 0001 \quad 0111 \quad 0110 \\ 1000 \quad 0010 \quad 0100 \\ \hline 1001 \quad 1001 \quad 1010 \\ + 0110 \\ \hline 1001 \quad 1010 \quad 0000 \\ + 0110 \\ \hline 1010 \quad 0000 \quad 0000 \\ + 0110 \\ \hline 1 \quad 0000 \quad 0000 \quad 0000 \end{array}$$

* SUNDAY. 31. Aug. 2008 *

Boolean Algebra:

AND Law

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A \cdot A = A$$

$$A \cdot \bar{A} = 0$$

Identity element

OR Law

$$A + 0 = A$$

$$A + 1 = 1$$

$$A + A = A$$

$$A + \bar{A} = 1$$

Identity element.

(1). Commutative Law:

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$


* AND, OR operations are commutative & Associative

(2). Associative Law:

$$(A + B) + C = A + (B + C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

 Q find the commutative & Associative operations of NAND.



$$(a) \cdot \bar{A} \cdot B = \bar{B} \cdot A$$

$$(b). (\bar{A} \cdot B) \text{ NAND } C = \overline{\bar{A} \cdot B \cdot C}$$

$$A \text{ NAND } (B \text{ NAND } C) = A \text{ NAND } (\bar{B} \cdot C)$$

$$= \overline{A \cdot \bar{B} \cdot C}$$

$$\Rightarrow \overline{\bar{A} \cdot B \cdot C} \neq \overline{A \cdot \bar{B} \cdot C}$$

* NAND operation is commutative but not associative.

(3). Distribution law:

$$A \cdot (B + C) = AB + AC$$

$$A + (BC) = (A + B)(A + C)$$

$$(i). A + \bar{A}B = (A + \bar{A})(A + B) \\ = (A + B).$$

$$(ii). \quad \bar{A} + AB = (\bar{A} + A)(\bar{A} + B) \\ = (\bar{A} + B)$$

(4). Consensus Law:

$$AB + \bar{A}C + BC = AB + \bar{A}C$$

Eg: $yx + \bar{y}z + pwxyz = yx + \bar{y}z$

proof: $AB + \bar{A}C + BC(A + \bar{A})$

$$= AB + \bar{A}C + ABC + \bar{A}BC$$

$$= AB(1 + C) + \bar{A}C(1 + B)$$

$$= AB + \bar{A}C$$

$$(A + B) \cdot (\bar{A} + C) \cdot (B + C) = (A + B) \cdot (\bar{A} + C)$$

(5). Transposition Law:

$$AB + \bar{A}C = (A + C)(\bar{A} + B)$$

Eg: $xy + \bar{y}z = (x + \bar{y})(y + z)$

RHS: $(x + \bar{y})(y + z) = xy + \bar{y}z + xz$
 $= xy + \bar{y}z$

$$(A + B) \cdot (\bar{A} + C) = AC + \bar{A} \cdot B$$

(6). De Morgan's Law:

$$\overline{A + B + C + \dots} = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \dots$$

$$\overline{A \cdot B \cdot C \cdot \dots} = \bar{A} + \bar{B} + \bar{C} + \dots$$

Additional Laws:

(1). $x \cdot f(x, \bar{x}, w, y, \dots, z)$

$$= x \cdot f(1, 0, w, y, \dots, z)$$

$$x + f(x, \bar{x}, w, y, \dots z) \\ = x + f(0, 1, w, y, \dots z)$$

(7). Duality :

All the boolean expressions resulting from interchanging of operators and identity elements are valid.

Eg: $A \cdot 1 = A$

$$\Rightarrow A + 0 = A$$

Adv: To findout complement of a function +.

Step 1: find dual of f ie f_D .

Step 2: Compliment of all var.s $\rightarrow \bar{F}$.

Eg: $A + B + CD$

$$\bar{F} = \overline{A + B + CD}$$

$$f_D = A \cdot B \cdot (C + D)$$

$$= \bar{A} \cdot \bar{B} \cdot (\bar{C} + \bar{D})$$

$$\bar{F} = \bar{A} \cdot \bar{B} \cdot (\bar{C} + \bar{D})$$

$$= \bar{A} \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot \bar{B} \cdot \bar{D}$$

$$= \bar{A} \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot \bar{B} \cdot \bar{D}$$

Q. Simplify following Boolean functions.

(1). $f = AB + \bar{A}C + \bar{C}D + \bar{B}C$

$$= AB + C(\bar{A} + B) + \bar{C}D$$

$$= \underbrace{AB}_x + \underbrace{\bar{A}B}_x C + \bar{C}D$$

$$= AB + (C + \bar{C}D)$$

$$= AB + C + D$$

✓(2). $f = AB\bar{C} + A\bar{B}C + \bar{A}BC + ABC$

$$= AB\bar{C} + A\bar{B}C + \bar{A}BC + ABC + ABC + ABC$$

$$= AB(\bar{C} + C) + BC(\bar{A} + A) + AC(\bar{B} + B)$$

$$= AB + BC + AC$$




$$\begin{aligned}
 (3). \quad f &= \bar{x}\bar{y}z + \bar{x}y\bar{z} + \underline{\bar{x}yz} + xyz \\
 &= \bar{x}\bar{y}z + \bar{x}y\bar{z} + \bar{x}yz + \bar{x}yz + \bar{x}yz + xyz \\
 &= \bar{x}z(\bar{y}+y) + \bar{x}y(\bar{z}+z) + yz(\bar{x}+x) \\
 &= \bar{x}z + \bar{x}y + yz.
 \end{aligned}$$

Q. How many two input NAND's are required to implement the following

$$\begin{aligned}
 (i). \quad f(A, B, C) &= A + AB + ABC. \\
 &= A + AB(1+C) \\
 &= A + AB = A.
 \end{aligned}$$


Ans: zero NAND gates.

$$(ii). \quad f = ABC.$$

   

Each AND is replaced by two NAND's. So the total no. of NAND gates = 4.

 Q. Complement EX-OR using min. no. of NAND gates.




$$\underline{A \oplus B} = \bar{A}B + A\bar{B}$$

$$= (\bar{A} + \bar{B})A + (\bar{A} + \bar{B})B$$

$$= A\bar{A}B + B\bar{A}B$$

$$Y = \bar{Y} = \overline{(A\bar{A}B + B\bar{A}B)}$$
 
$$= (\overline{A\bar{A}B}) \cdot (\overline{B\bar{A}B}) \Rightarrow \underline{5 \text{ NAND's.}}$$



Here NAND's are replaced by NOR's
then we get Ex-NOR gate:

$$\begin{aligned}
 & \overline{A + \overline{A+B}} + \overline{B + \overline{A+B}} \\
 &= (A + \overline{A+B}) (B + \overline{A+B}) \\
 &= (A + \overline{A} \cdot \overline{B}) (B + \overline{A} \cdot \overline{B}) \\
 &= (A + \overline{B}) (B + \overline{A}) \\
 &= \overline{AB} + \overline{A}\overline{B} = A \odot B
 \end{aligned}$$

Operator precedence:

- (1). paranthesis ()
- (2). NOT $\neg$
- (3). AND $\cdot$
- (4). OR $+$

Literal = variable (or) complement of a var.

Implement x-NOR using min. no. of NOR's.

minterms & maxterms :

Let $f(A, B, C)$.

containing all variables

minterms

$$\bar{A} \cdot \bar{B} \cdot \bar{C}$$

$$\bar{A} \cdot \bar{B} \cdot C$$

$$\textcircled{8} \quad \bar{A} \cdot B \cdot \bar{C}$$

⋮

$$A \cdot B \cdot \bar{C}$$

$$A \cdot B \cdot C$$

maxterms

$$\bar{A} + \bar{B} + \bar{C}$$

$$\bar{A} + \bar{B} + C$$

$$\textcircled{8} \quad \bar{A} + B + \bar{C}$$

⋮

$$A + B + \bar{C}$$

$$A + B + C$$

* for 'n' var. function $\rightarrow 2^n$ minterms
 2^n maxterms

* Sum of all minterms = 1. $\sum_{i=0}^{2^n-1} m_i = 1$

* product of all maxterms = 0. $\prod_{i=0}^{2^n-1} M_i = 0$

* product of any two minterms = 0.

$$m_i \cdot m_j = 0, \text{ if } i \neq j$$

$$= m_i, \text{ if } i = j$$

* Sum of any two maxterms = 1.

$$M_i + M_j = 1, \text{ if } i \neq j$$

$$= M_i, \text{ if } i = j$$

Let $f(x, y)$

1 = var

0 = $\bar{\text{var}}$

x y

minterm

0 0

$$\bar{x} \cdot \bar{y} \quad m_0$$

0 1

$$\bar{x} \cdot y \quad m_1$$

1 0

$$x \cdot \bar{y} \quad m_2$$

1 1

$$x \cdot y \quad m_3$$

max term

$$x + y \quad M_0$$

$$x + \bar{y} \quad M_1$$

$$\bar{x} + y \quad M_2$$

$$\bar{x} + \bar{y} \quad M_3$$

$\Rightarrow$ complement of min-term = max-term
and vice-versa.

$$M_j = \bar{m}_j$$

Q. If $f(A, B, C, D, E)$. what is $m_{23} = ?$

$$m_{19} = ? \quad m_{28} = ? \quad , \quad M_{23} = ?$$

$$23 \rightarrow 10111$$

$$19 \rightarrow 10011$$

$$m_{23} = A \cdot \bar{B} \cdot C \cdot D \cdot E$$

$$m_{19} \rightarrow A \cdot \bar{B} \cdot \bar{C} \cdot D \cdot E$$

$$28 \rightarrow 11100$$

$$23 \rightarrow 10111$$

$$M_{28} \rightarrow \bar{A} + \bar{B} + \bar{C} + D + E \quad M_{23} = \bar{A} + B + \bar{C} + \bar{D} + \bar{E}$$

$$M_{23} = \bar{m}_{23} = \overline{A \cdot \bar{B} \cdot C \cdot D \cdot E}$$

$$= \bar{A} + B + \bar{C} + \bar{D} + \bar{E}$$

Q. $A \oplus A \oplus A \dots \oplus A = ?$

$$A \oplus A \oplus A \oplus A, \text{ if even no. of } A\text{'s.}$$

$$= 0 \oplus 0 = 0$$

$$A \oplus A \oplus A, \text{ if odd no. of } A\text{'s.}$$

$$= 0 \oplus A = A$$

$$* \therefore A \oplus A \oplus A \dots \oplus A = 0, \text{ if no. of terms} = \text{even}$$

$$= A, \text{ if } " = \text{odd}$$

$$* \bar{A} \oplus \bar{A} \oplus \bar{A} \oplus \dots \oplus \bar{A} = 0, \text{ if no. of terms} = \text{Even}$$

$$= \bar{A}, \text{ if } " = \text{odd}$$

Q. How many Boolean fun^s are possible, using 'n'-var^s

Using n-var^s $\rightarrow \underset{(x)}{2^n}$ min terms

x min terms can be arranged in 2^x ways.

ie 2^{2^n} boolean functions are possible.
 for 2 var. $\rightarrow 2^{2^2} = 16$ functions.
 $f(x, y)$.

	x	y	f_1	f_2	f_3	...	f_{16}
m_0	0	0	0	0	0		1
m_1	0	1	0	0	0		1
m_2	1	0	0	0	1		1
m_3	1	1	0	1	0		1

$\emptyset$ AND (Inhibition)
 $\bar{x}y = x|y$ 1

Algebraic forms of Boolean functions:

- ①. Standard form $\begin{cases} \text{stand SOP form} \\ \text{stand. POS form} \end{cases}$
- ②. Canonical form $\begin{cases} \text{Cano. SOP form (or) Sum of minterms} \\ \text{Cano. POS form (or) product of maxterms} \end{cases}$

$$f_1(A, B, C) = (A+B+\bar{C})(\bar{A}+\bar{B}+\bar{C}) \rightarrow \text{Cano. POS}$$

$$f_2(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}BC + \bar{A}\bar{C} \rightarrow \text{stand. SOP form}$$

* SAT. 11 | 10 | 08 *

Q. Convert the following boolean eq. into canonical SOP form.

$$1). f(A, B, C) = \bar{A} + \bar{A}\bar{B}C + B\bar{C} \text{ — Std. SOP}$$

$$\Rightarrow \bar{A}(B+\bar{B})(C+\bar{C}) + \bar{A}\bar{B}C + B\bar{C}(A+\bar{A})$$

$$= \begin{matrix} 011 & 010 & 001 & 000 & 101 & 110 \\ \bar{A}BC & \bar{A}\bar{B}\bar{C} & \bar{A}\bar{B}C & \bar{A}\bar{B}\bar{C} & A\bar{B}C & A\bar{B}\bar{C} \\ + & \bar{A}BC & & & & \end{matrix}$$

$$= m_3 + m_2 + m_1 + m_0 + m_5 + m_6$$

$$= \sum m(0, 1, 2, 3, 5, 6).$$

(OR)

$\bar{A}$	A	B	C		A	B	C		$\bar{A}\bar{B}\bar{C} \rightarrow m_5$
$\downarrow$	0	$-$	$-$		0	1	0	$B\bar{C}$	
	0	0	$0 \rightarrow m_0$		0	1	$0 \rightarrow m_2$		
	0	0	$1 \rightarrow m_1$		1	1	$0 \rightarrow m_6$		
	0	1	$0 \rightarrow m_2$						
	0	1	$1 \rightarrow m_3$						

$$f = \sum m(0, 1, 2, 3, 5, 6) \rightarrow \text{cano. SOP}$$

$$f = \pi M(4, 7) \rightarrow \text{cano. POS}$$

Q. Convert the following boolean eq. into cano. pos form.

$$f(A, B, C) = \bar{A} \cdot (\bar{B} + \bar{C}) \cdot (\bar{A} + \bar{B} + \bar{C}) \rightarrow \text{std. pos form}$$

$$f = (\bar{A} + B\bar{B} + C\bar{C}) (\bar{B} + \bar{C} + A\bar{A}) \cdot (A + B + \bar{C})$$

$$= (\bar{A} + B\bar{B} + C) (\bar{A} + B\bar{B} + \bar{C}) (\bar{B} + \bar{C} + A) (\bar{B} + \bar{C} + \bar{A}) (A + B + \bar{C})$$

$$= (\bar{A} + B + C) (\bar{A} + \bar{B} + C) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + \bar{C}) (A + \bar{B} + \bar{C}) (\bar{A} + B + \bar{C}) (A + \bar{B} + C)$$

$$= M_4 \cdot M_6 \cdot M_5 \cdot M_7 \cdot M_3 \cdot M_7 \cdot M_1$$

$$= \pi M(1, 3, 4, 5, 6, 7) \rightarrow \text{cano. POS}$$

$$= \sum m(0, 2) \rightarrow \text{cano. SOP}$$

[OR]

A	B	C	
$\downarrow$	0	0	$\rightarrow M_4$
0	0	$1 \rightarrow M_5$	
0	1	$0 \rightarrow M_6$	
0	1	$1 \rightarrow M_7$	

A	B	C	
0	1	$1 \rightarrow M_3$	
1	1	$1 \rightarrow M_7$	

Q. convert the following into cano. pos form.

$$f(x, y, z) = \bar{x}y + \bar{x}z \rightarrow \text{std. SOP}$$

$$\Rightarrow f = (x+z)(\bar{x}+y)$$

x	y	z
0	0	0
1	0	0

$$m_0 \quad 000 \quad 100 \quad m_4$$

$$m_2 \quad 010 \quad 101 \quad m_5$$

$$f = \Pi M(0, 2, 4, 5) \rightarrow \text{cano. POS}$$

K-maps :-

2-variable k-map

A \ B	0	1
0	0	1
1	2	3

neighbours

$$m_0 \rightarrow m_1, m_2$$

$$m_2 \rightarrow m_0, m_3$$

4 var. k-map

AB \ CD	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

neighbours:

$$m_0 \rightarrow m_1, m_4, m_2, m_8$$

$$m_9 \rightarrow m_8, m_{11}, m_{13}, m_1$$

3-var. k-map

A \ BC	00	01	11	10
0	0	1	3	2
1	4	5	7	6

neighbours

$$m_0 \rightarrow m_1, m_4, m_2$$

$$m_6 \rightarrow m_2, m_4, m_4$$

To make neighbours differ by only one bit

group of 8 $\rightarrow$ octet

group of 4 $\rightarrow$ quad

group of 2 $\rightarrow$ pair

$\rightarrow$ single minterm

In 3-var. k-map: Qvads: 0145, 1357,

3276, 0246, 0132, 4576 : Total = 6.

Q. Simplify $f(A, B, C) = \sum m(0, 2, 3, 4, 5, 6)$
[That is from cano sop into std sop].

A \ BC	00	01	11	10
	1		1	1
0	1		1	1
1	1	1		1

$$= \bar{A}B + A\bar{B} + C$$

In 4-var. k-map:

Total Octets = 8 ; Columns 12, 23, 34, 41
Rows 12, 23, 34, 41

Q. Simplify $f(A, B, C, D) = \sum m(0, 2, 3, 5, 6, 10, 4, 11, 12, 13, 15)$.

AB \ CD	00	01	11	10
	1	1	1	1
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$$\Rightarrow f = B\bar{C} + \bar{A}\bar{D} + \bar{B}C + ACD$$

Simplified k-map eq. is a minimal eq. but not unique.

Q. Simplify $f(w, x, y, z) = \sum m(0, 1, 2, 4, 5, 8, 9, 10, 12, 14, 15)$

wx \ yz	00	01	11	10
	1	1	1	1
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$$f = \bar{y}\bar{z} + w\bar{y} + \bar{x}\bar{z} + \bar{x}\bar{y} + wxy$$

Q. $f(A, B, C) = \pi M(0, 1, 2, 4, 5, \text{---}) \rightarrow \text{cano. pos}$

A \ BC	00	01	11	10
0	0	0	1	0
1	0	0	1	0

{ convert it into
std pos form }

$$f = B \cdot (A + C)$$

Q. $f(w, x, y, z) = \pi M(0, 1, 2, 4, 5, 9, 11, 13, 14, 15)$

wx \ yz	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	0	0	1	0
10	0	0	1	0

$$f = (w + y)(\bar{w} + \bar{z})(\bar{w} + \bar{x} + \bar{y})$$

$$(\bar{x} + w + \bar{z})$$

Implicant: It indicates the set of all adjacent minterms.

Prime Implicant: It is an implicant which is not a subset of another implicant.

Essential PI: It is a PI which covers minterms exclusively.

Minimal expressions = EPI's + PI's (optional)

Eg: $f(A, B, C) = \sum m(1, 2, 5, 6, 7)$

A \ BC	00	01	11	10
0	0	1	1	0
1	0	1	1	1

All are PI's.

$$\text{EPI's} = \textcircled{1}, \textcircled{4}$$


Minimal expressions

$$= \textcircled{1} + \textcircled{4} + \textcircled{2}$$

$$(\text{or}) \textcircled{1} + \textcircled{4} + \textcircled{3}$$

Q. find EPI's and minimal expressions for the following boolean functions.
 
$$f(A, B, C) = \sum m(0, 1, 2, 5, 6, 7)$$



$$EPE'f = 0 \text{ (Nil)}$$


Minimal expressions

$$= \textcircled{1} + \textcircled{3} + \textcircled{5}$$

$$\text{(or)} \textcircled{2} + \textcircled{4} + \textcircled{6}$$

Don't care conditions:-

 for non-occurring i/p's the o/p can be assumed as 0 or 1. and this is called as Don't care condition.



valid BCD i/p's

$$0 - 0000$$

$$1 - 0001$$

:

$$9 - 1001$$

non-occurring
i/p's. o/p

$$10 - 1010 \rightarrow x$$

$$11 - 1011 \rightarrow x$$


$$12 - 1100 \rightarrow x$$

$$13 - 1101 \rightarrow x$$

$$14 - 1110 \rightarrow x$$

$$15 - 1111 \rightarrow x$$

} don't care's

 


Don't care's : 0000 $\rightarrow x$

$$0001 \rightarrow x$$

$$0010 \rightarrow x$$
 
$$Q. f(A, B, C, D) = \sum m(0, 1, 3, 6, 10, 13, 15) + d(2, 5, 8, 11)$$



$$f = \bar{A}\bar{B} + \bar{B}C + ABD$$

$$+ \bar{A}C\bar{D}$$

signal level over

$$Q. f_1 = \sum m(0, 2, 4, 7); f_2 = \sum m(1, 2, 4, 6)$$

$$f = f_1 \cdot f_2 \Rightarrow f = ?$$

$$f = \sum m(2, 4)$$


Similarly $f_3 = f_1 - f_2 \Rightarrow f_3 = ?$

$$f_3 = \sum m(0, 7)$$

$$f_4 = f_2 - f_1 \Rightarrow f_4 = ?$$

$$f_4 = \sum m(1, 6)$$

 Q. Determine the function f_3 in the following logic ckt.



where $f = \sum m(0, 1, 3, 5)$

$$f_1 = \sum m(2, 3, 6, 7)$$

$$f_2 = \sum m(0, 1, 5)$$

$$f = \overline{f_1 f_2} \cdot \overline{f_3}$$

$$= f_1 f_2 + f_3$$

$$\Rightarrow f_3 = f - f_1 f_2$$

But $f_1 f_2 = \emptyset$

$$\Rightarrow f_3 = f = \sum m(0, 1, 3, 5)$$

Q. $f = f_1 \cdot f_2$ where $f_1 = \sum m(0, 1, 5) + d(2, 3, 7)$

$$f_2 = \sum m(1, 2, 4, 5) + d(0, 7)$$

$$f = f_1 \cdot f_2 = \sum m(1, 5)$$

$$+ d(0, 2, 7)$$

minterm
in one
fun. ↓
don't care
in another
fun.

$$1 \cdot d = d$$


$$0 \cdot d = 0$$

$$1 + d = 1$$

$$0 + d = d$$


Two level logic :-

SOP form $\rightarrow Y = AB + A\bar{C}$

 

AND - OR logic $\equiv$ NAND - NAND

 pos form : $\rightarrow y = (A + \bar{B})(A + C)$




OR - AND logic $\equiv$ NOR - NOR.

Q. How many two i/p NOR gates are required to implement the following k-map.


AB \ CD	00	01	11	10
00	0	1	1	0
01	1	1	1	1
11	1	1	1	1
10	0	1	1	0

$$Y = B + D.$$

 
$$\Rightarrow Y = \overline{\overline{B + D}}$$



combinational circuits:-

 

Sequential circuits:-

 


Q. Design a BCD to 3321 code converter.


BCD	3321
0	3
1	4
2	5
3	6
4	7
5	8
6	9
7	0
8	1
9	2

BCD	3321
0	3
1	4
2	5
3	6
4	7
5	8
6	9
7	0
8	1
9	2


BCD	3321
0	3
1	4
2	5
3	6
4	7
5	8
6	9
7	0
8	1
9	2

 

 
$$Z = \overline{B}D + CD + B\overline{C}\overline{D}$$


 
$$Y = A + \overline{B}C + B\overline{C}\overline{D}$$




$$X = A + BC + B\overline{D}$$

 

$$W = A + BD + BC$$

Arithmetic combi. circuit :-

Half Adder :-

 

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = A\overline{B} + A\overline{B}$$


$$\Rightarrow A \oplus B$$

$$C = AB$$

1 HA $\rightarrow$ { 1 EX-OR gate
1 AND gate }

* SUNDAY. 12.10.08 *

Full Adder :-

 

A	B	Ci	S	Ci+1
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

for S

	00	01	11	10
0	0	1	0	1
1	1	0	1	0

diagonal Adjacency

$$S = \overline{B} (A \oplus C_i) + B (A \oplus \overline{C_i})$$

$$= B \oplus x = B \oplus A \oplus C_i$$

$$\Rightarrow S = A \oplus B \oplus C_i$$

$$C_{i+1} = \overline{A} B C_i$$


$$+ A \overline{B} C_i + A B \overline{C_i} + A B C_i$$

$$= A B + B C_i + C_i A$$

(or)

$$C_i (A \oplus B) + A B$$

Half Subtractor:-

 


(borrow) (Difference)

A	B	D	b
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$D = A \oplus B$$

$$b = \overline{A} B$$

Full Subtractor:-

 

A	B	b _i	D	b _{i+1}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$D = A \oplus B \oplus b_i$$

	00	01	11	10
0	0	1	1	1
1	0	0	1	0


$$\Rightarrow b_{i+1} = \overline{A} b_i + B b_i + \overline{A} B$$

for b_{i+1}

$$= (\overline{A} + B) b_i + \overline{A} B$$



$$= (\overline{A} + B) b_i + \overline{A} B$$

 Q. Implement a FA by using HA's and logic gates.



FA requires, one OR gate and two HA's.

Q. Convert the following FA into a fs.

  

Q. Implement the following boolean exp-s using only HA's.

$$D = ABC\bar{C} + \bar{A}C + \bar{B}C$$


$$E = \bar{A}BC + A\bar{B}C$$

Sol: $D = ABC\bar{C} + (\bar{A} + \bar{B})C$

$$= ABC\bar{C} + \bar{A}\bar{B}.C = \bar{A}\bar{B} \oplus C$$

$$E = (\overline{A}B + A\overline{B})C$$

$$= (A \oplus B)C$$

 

(i) 4-bit parallel Binary Adder:-


$A \rightarrow A_4 \ A_3 \ A_2 \ A_1$

$B \rightarrow B_4 \ B_3 \ B_2 \ B_1$

(combi. circuit)

Required: 3 FA's + 1 HA

(or) 4 FA's

 

Adv:

Simple to construct

Drawback:

Speed of operation is less if the size of the adder increases.



FA $\rightarrow$ $\begin{cases} 32 \text{ ns} \rightarrow \text{sum} \\ 14 \text{ ns} \rightarrow \text{carry} \end{cases}$

Then the total time required for the operation

Ans: $42 + 32$ for S_4 ; for $C_5 \Rightarrow 42 + 14 = 56$
 $= 74 \text{ ns.}$

$\therefore$ To complete addition
 Total time = 74 ns.

  (2) Carry Look Ahead Adder :- (combi. circuit)



$$C_{i+1} = C_i (A \oplus B) + AB$$

(1). $C_{i+1} = 1$ if $AB = 1$

→ Carry Generation $G_i = AB$

(2). when $C_{i+1} = C_i$ then $A \oplus B = 1$

→ Carry propagation $P_i = A \oplus B$

Now,

$$C_{i+1} = C_i P_i + G_i$$

$$\Rightarrow C_2 = C_1 P_1 + G_1$$

$$C_3 = C_2 P_2 + G_2$$

$$= [C_1 P_1 + G_1] P_2 + G_2$$

$$= C_1 P_1 P_2 + G_1 P_2 + G_2$$


$$C_4 = C_3 P_3 + G_3$$

$$= C_1 P_1 P_2 P_3 + G_1 P_2 P_3 + G_2 P_3 + G_3$$

Adv: speed is more

Dis Adv: More hardware complexity

(3). Serial Adder:-

 

Adv: (1) easy to construct


(2) only one fA is used.

Dis-Adv:

speed of operation is less.


4 Bit parallel Binary Adder (74 LS 83)

LS $\rightarrow$ Low power Schottky

 

Switching speed is more.

 
BCD + 0011 = Ex-3 code
(BCD to Ex-3 converter)



Ex-3 + 2's no 1101

= Ex-3 + (-0011)

= BCD code

 


1001 + BCD in 2's comp-form

= 1001 + (-BCD)

= 2's comp of BCD = B

(-x = 2's comp of +x.)

 

$$\begin{aligned}
 & A + (\text{if of } B + 1) \\
 &= A + 2^{\text{if of } B} \\
 &= A + (-B) \\
 &= A - B
 \end{aligned}$$


BCD Adder:-

	$S_4 S_3$	00	01	11	10
$S_2 S_1$	00				
	01				
	11	1	1	1	1
	10			1	1


$$\begin{array}{r}
 \text{BCD 1} \\
 \text{BCD 2} \\
 (+) \quad \quad \quad \\
 \hline
 \quad \quad \quad > 9 \\
 \rightarrow \text{add 6}
 \end{array}$$

Invalid BCD =
 
$$\begin{aligned}
 Y &= S_4 S_3 + S_4 S_2 \\
 &+ C_5
 \end{aligned}$$




3-bit magnitude Comparator:-

 

$$A = A_3 A_2 A_1$$

$$B = B_3 B_2 B_1$$

 

$$\begin{aligned}
 (a) \quad A = B & \text{ if } A_3 = B_3 \& A_2 = B_2 \& A_1 = B_1 \\
 \text{ie } A = B & \text{ if } x_3 = 1 \& x_2 = 1 \& x_1 = 1 \\
 \text{ie } A = B & \text{ if } x_3 x_2 x_1 = 1
 \end{aligned}$$

(b). $A > B$ if $A_3 > B_3$ (or) $A_3 = B_3$ and $A_2 > B_2$


(or) $A_3 = B_3$ and $A_2 = B_2$ and $A_1 > B_1$

$A > B$ if $A_3 \bar{B}_3 + x_3 A_2 \bar{B}_2 + x_3 x_2 A_1 \bar{B}_1 = 1$

(c). $A < B$ if $\bar{A}_3 B_3 + x_3 \bar{A}_2 B_2 + x_3 x_2 \bar{A}_1 B_1 = 1$


(1). decoder (2). demultiplexer (3). Encoder (4). Multiplexer

Decoder :-

 

Q. Implement the following sum of minterm eq by using a decoder and logic gates.

$$f(A, B, C) = \sum m(0, 2, 3, 7)$$

 


Q. Implement a fA by using decoder and logic gates,


A	B	C _i	C _{i+1}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = \sum m(1, 2, 4, 7)$$

$$C_{i+1} = \sum m(3, 5, 6, 7)$$

 



Demultiplexer:-

 

A 2 to 4 decoder [with active low o/p's] can be converted to a 1 to 4 demux by choosing A & B as selection lines and the enable pin as the serial i/p.

* 29/11/08 *


ENCODER:

  

PRIORITY ENCODER: (74 LS 148)


D_7 - highest priority

D_0 - lowest priority

 

x - ignored

MULTIPLEXER:

 


A	B	f
0	0	d_0
0	1	d_1
1	0	d_2
1	1	d_3

for 4:1 MUX,

$$f = \bar{A}\bar{B}d_0 + \bar{A}Bd_1 + A\bar{B}d_2 + ABd_3$$


$$= m_0d_0 + m_1d_1 + m_2d_2 + m_3d_3$$

 

for 2:1 MUX,

$$f = \bar{A}d_0 + Ad_1$$

Q.

 


$$f(A, B) = \sum m(1, 3)$$

← decoder


Q. Implement the following sum of minterms exp. by using multiplexer.

(sum of minterms)

$$f(A, B) = \sum m(1, 3).$$

 

Q. Implement a FA by using multiplexers:


 



A	B	C _i	S	C _{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

FA $\rightarrow$ MUX
 (sum of minterms)

$$S = \sum m(1, 2, 4, 7)$$

$$C_{i+1} = \sum m(3, 5, 6, 7)$$

  

 

Given that



$$a_0 = a_1 = C$$

$$a_2 = a_3 = \bar{C}$$

$$\begin{aligned} f &= \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C} \\ &= \bar{A}C(\bar{B}+B) + A\bar{C}(\bar{B}+B) \\ &= A \oplus C. \end{aligned}$$

Q. Determine the o/p's of the following Mux's?

1). Switching speed is 50 ns.

  

$$f_1 = \bar{A}a_0 + Aa_1$$

$$f_1 = \bar{x}_1 \cdot 1 + x_1 \cdot 0 = \bar{x}_1$$



$$f = \bar{A}a_0 + Aa_1$$

$$= \bar{x}_2 \cdot \bar{x}_1 + x_2 \cdot x_1$$

$$= x_2 \odot x_1$$

Q. How many 4:1 mux's are required to construct a 16:1 MUX.

Ans: 5

  


Q. Implement sum of minterm exp. $f(A, B, C)$

$= \sum m(0, 2, 3, 5, 6, 7)$ by using 4:1 MUX.

8:1 MUX

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$\phi, 1, C, \bar{C}$

 


[OR]

	00	01	10	11
	d_0	d_1	d_2	d_3
0 $\bar{C}$	0	2	4	6
1 C	1	3	5	7

	<u>AB</u>	d_0	d_1	d_2	d_3
$\bar{C}$		0	2	4	6
C		1	3	5	7
		$\bar{C}$	1	C	1


Implement above problem by choosing B & C as selection lines.

		<u>BC</u>	d_0	d_1	d_2	d_3
			00	01	10	11
0	$\bar{A}$		0	1	4	6
1	A		4	5	6	7
			$\bar{A}$	A	1	1

 

* Using 4:1 MUX, we can implement all 2 variable functions and some 3 variable functions. $f(A, B)$ $f(A, B, C)$

Require some logic gates like NOT GATE.

 

If $z=0$, MUX is enabled and with $z=1$, MUX is disabled.

$$S_1 = \bar{y}$$

$$S_0 = z$$

x	y	z	$\bar{y}$ s_1	$\bar{z}$ s_0	f
0	0	0	1	0	$\bar{z} = y = 0$
0	1	0	0	0	$\bar{z} = x = 0$
1	0	0	1	0	$\bar{z} = y = 0$
1	1	0	0	0	$\bar{z} = x = 1$

$1 \rightarrow$ disabled

$f = x y \bar{z}$

ANOTHER WAY :

$$f = \bar{A}\bar{B} \bar{z}_0 + \bar{A}B \bar{z}_1 + A\bar{B} \bar{z}_2 + AB \bar{z}_3$$

where $s_1 A = \bar{y}$ $\bar{z}_0 = \bar{z}_1 = x$
 $s_0 B = z$ $\bar{z}_2 = y; \bar{z}_3 = \bar{y}$

$$\Rightarrow f = \bar{y} \bar{z} x + \bar{y} z x + y \bar{z} y + \bar{y} z \bar{y}$$


$$= x y \bar{z} + \cancel{x y z} + 0 + \cancel{\bar{y} z}$$


$x=1$	$x=1$	$y=0$
$y=1$	$y=1$	$\bar{z}=1$
$z=0$	$\bar{z}=1$	

$$\Rightarrow f = x y \bar{z}$$

ROM [READ ONLY MEMORY]

 ROM $\Rightarrow$ DECODER + Programmable OR gates



 

Size of the ROM indicates the no. of fuses at the beginning

PLA : programmable AND gates & programmable OR gates.

PAL : Programmable AND gates & fixed OR gates.

Decoder }
MUX } $\leftarrow$ Sum of minterms is $\Sigma m(\dots)$
ROM } (canonical SOP form).

PLA $\leftarrow$ Std. SOP form. is sufficient.

Determine the size of the ROM for the following

(i). $f_1(x, y, z) = \Sigma m(0, 1, 3)$.


$$f_2(x, y, z) = x\bar{y} + \bar{x}\bar{y}\bar{z} + \bar{y}z$$

$$f_3(x, y, z) = \bar{x}yz.$$

$$n = 3 \text{ \& } m = 3.$$

$$\text{ROM Size} = 2^3 \times 3 = 24.$$

(ii). 3 bit binary Multiplier

 

$$111 \times 111$$

$$7_{10} \times 7_{10} = 49_{10}$$


$$\Rightarrow 2^m \geq 49$$

$$\Rightarrow m = 6.$$

$$\therefore \text{Size} = 2^6 \times 6$$

$$=$$

SEQUENTIAL CIRCUITS:

 


$$\text{Outputs} = f(\text{present i/p's, past o/p's})$$

or

$$+ (\text{present state})$$

1 Bit Memory Element:


(SR LATCH)

 


S	R	Q
1	0	1
0	0	1



S	R	Q
0	0	No change in o/p
0	1	0
1	0	1
1	1	Impractical state

 Even i/p's are removed the o/p will be 1 i.e. it stored the o/p. $\rightarrow$ ^{1 bit} memory unit



CLOCKED S-R FLIP FLOP:

 

  

CLK wave form.

TRUTH TABLE :

S	R	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	(Ambiguous state)

CHAR. TABLE :


S	R	$Q(t)$	$Q(t+1)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	x
1	1	1	x

	RQ	00	01	11	10
0		0	1	0	0
1		1	1	x	x

$Q(t+1) = S + RQ$

CLOCKED D-FLIP FLOP :

D - DELAY

 

TRUTH TABLE

D	Q(t+1)
0	0
1	1

$S=0$
 $R=1$
 $S=1$
 $R=0$

CHAR. TABLE :

D	Q(t)	Q(t+1)
0	0	0
0	1	0
1	0	1
1	1	1


$$Q(t+1) = D\bar{Q} + DQ$$

$$= D.$$

CLOCKED JK FLIP FLOP :

$$S = J\bar{Q}$$

$$R = KQ$$

 

TRUTH TABLE :

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q-bar(t)

CHAR. TABLE:


J	K	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$Q(t+1) = J\bar{Q} + \bar{K}Q$

	00	01	11	10
0	0	1	0	0
1	1	1	0	1

CLOCKED T- FLIP FLOP:

T - TOGGLE

 

TRUTH TABLE:-

T	Q(t+1)
0	Q(t)
1	$\bar{Q}(t)$



$J=K=0 \leftarrow 0$
 $J=K=1 \leftarrow 1$

CHAR. TABLE:-

T	Q(t)	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

$$Q(t+1) = T \oplus Q$$

  Q. Determine the fun. table of the following logic ckt.



x	y	Q
0	0	$Q=1, \bar{Q}=1$
0	1	1
1	0	0
1	1	No change

Q. Obtain char. eq. of x-y flip flop whose truth table as shown below—

x	y	$Q(t+1)$
0	0	1
0	1	$\bar{Q}(t)$
1	0	$Q(t)$
1	1	0

char. table becomes :-



x	y	$Q(t)$	$Q(t+1)$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

	yQ			
x	00	01	11	10
0	1	1	0	1
1	0	1	0	0



$$Q(t+1) = \bar{x}\bar{Q} + yQ$$

TYPES OF TRIGGERING:


(1). LEVEL TRIGGER

  

(2). EDGE TRIGGERED

  


Q.

 


$$Q(t) = 0$$

$$Q(t+1) = 1$$

 Q. Determine the clk freq. of the following fls - ?



 
$$\begin{array}{c} J \quad K \\ 1 \quad 1 \Rightarrow Q(t+1) \\ = \overline{Q(t)} \end{array}$$




$$T_0 = 2T$$

$$f_0 = \frac{1}{T_0}$$

 
$$f_0 = \frac{f}{2} = \frac{1 \text{ kHz}}{2} = 500 \text{ Hz}$$



 NOTE: If the flip is in toggle mode, the o/p freq. is half of the clk freq.



米 SUN. 07/12/08 米

 

clk	pr	cr	Q
0	0	1	1
0	1	0	0
1	1	1	J, K i/p's.

RACE AROUND CONDITION:

RAC occurs when $t_p \gg \Delta t$ and $j=k=1$.

$t_p \Rightarrow$ applied clk pulse width


$\Delta t \rightarrow$ propagation delay of flt.


Asynchronous / direct

8/19

presct (pr)


clear (cr)

 

 


TO AVOID RAC:

$$t_p \leq \Delta t < T$$

 


RAC occurs only in level triggered f/f but not in edge triggered f/f.

MASTER-SLAVE JK f/f:

 


SHIFT REGISTER $\rightarrow$ D-f/f's.

 


N-bit shift Register	
(1). SIPO	'N' CLK's.
(2). SISO	$N + (N-1) = (2N-1)$ CLK's.
(3). PIPO	NO CLK's.
(4). PISO	$(N-1)$ CP's.

3 bit shift REGISTER

CLK	Serial i/p	Q_2	Q_1	Q_0	MSB 1 0 1 LSB ($Q_2 Q_1 Q_0$)
0	—	0	0	0	
1	1 (LSB)	1	0	0	
2	0	0	1	0	
3	1 (MSB)	1	0	1	
4	x	x	1	0	parallel o/p
5	x	x	x	1	serial o/p

 


 Q. what is the value of following shift reg. after 4 cp's.



CLK	Serial i/p (Q_0)	Q_4	Q_3	Q_2	Q_1	Q_0
0	—	1	0	1	1	0
1	0	0	1	0	1	1
2	1	1	0	1	0	1
3	1	1	1	0	1	0
4	0	0	1	1	0	1
5	1	1	0	1	1	0

 
Q. In the following shift reg. how many CP's are required to make shift reg. content to have all one's.



CLK	Serial i/p ($Q_3 \oplus Q_0$)	Q_3	Q_2	Q_1	Q_0
0	—	0	1	1	0
1	1	1	0	1	1
2	0	0	1	0	1
3	1	1	0	1	0
4	1	1	1	0	1
5	1	1	1	1	0
6	1	1	1	1	1


APPLICATIONS OF SHIFT REG'S:

 - (1). Serial to parallel & parallel to serial conversion
- (2). Time delays - SISO
- (3). Sequence Generator
- (4). Counter — RING
JOHNSON.



... 011101110111.

RING COUNTER:

 

CLK	Serial i/p (Q_0)	Q_2 Q_1 Q_0
0	—	1 0 0
1	0	0 1 0
2	0	0 0 1
3	1	1 0 0


N-bit Ring Counter:

$\Rightarrow$ 3:1 COUNTER

→ Counting capacity = $N:1$

→ Output frequency = f/N .

JOHNSON COUNTER: [TWISTED RING COUNTER].

 

CLK	Serial i/p ($\bar{Q}_0$)	Q_2 Q_1 Q_0
0	—	0 0 0
1	1	1 0 0
2	1	1 1 0
3	1	1 1 1
4	0	0 1 1
5	0	0 0 1
6	0	0 0 0

$\Rightarrow$ 6:1 COUNTER.

N-Bit Johnson Counter:

→ Counting capacity = $2N:1$

→ Output frequency = $f/2N$.

Q. what is the o/p freq. of a 3bit Johnson counter if its clk freq is 18 kHz. The initial content of the reg. is 101.

CLK	Serial i/p ($\bar{Q}_0$)	Q_2	Q_1	Q_0
0	—	1	0	1
1	0	0	1	0
2	1	1	0	1

⇒ 2:1 COUNTER.

$$2N = 6$$


$$\therefore f_0 = \frac{f}{2} = 9 \text{ kHz}$$

$$f/2N = f/6$$

COUNTERS:

- (1). Asynchronous / Rattle. → T' f/f.
- (2). Synchronous / parallel.

3-bit Asynchronous / Rattle counter:

 

CLK	(LSB) Q_0	Q_1	(MSB) Q_2
0	0	0	0
1	1	0	0
2	0	1	0
3	1	1	0
4	0	0	1
5	1	0	1
6	0	1	1
7	1	1	1
8	0	0	0

← UP COUNTER

{ CLK PULSE is given to LSB flip }

8:1 COUNTER

→ N-bit Asynchronous counter:

→ $2^N : 1$ counter

→ final o/p freq = $f/2^N$.

Let $t_{pd/ff} = 10 \text{ ns}$.


Then Max. conversion time = 30 ns .

⇒ $T \geq 30 \text{ ns}$.

$$f = \frac{1}{T} \leq \frac{1}{30 \text{ ns}}$$

⇒ $f_{\max} = \frac{1}{30 \text{ ns}}$.

 
∴ $f_{\max} = \frac{1}{N \cdot t_{pd/ff}}$ no. of fl's



CLK	(LSB) Q_0	Q_1	(MSB) Q_2
0	0	0	0
1	1	1	1
2	0	1	1
3	1	0	1
4	0	0	1
5	1	1	0
6	0	1	0
7	1	0	0
8	0	0	0

← DOWN COUNTER.

2- Bit Asynchronous up/down counter:

 

$x=1, \rightarrow Q_0 \rightarrow CLK \rightarrow$ up counter. (00, 01, 10, 11, 00..)

$X = 0, \rightarrow Q_0 \rightarrow CLK \rightarrow \text{DOWN counter. } (00, 11, 10, 01, 00, \dots)$

MODULUS OF A COUNTER:

→ It is the no. of cp's required to bring the counter to the initial state.


→ A Mod-N counter counts from 0 to $(N-1)$.

and o/p freq. = $\frac{f}{N}$

Q. Construct Mod-6 Asy. counter.

MOD - 6 ASY. COUNTER:
 
$$2^N \geq \text{mod} \Rightarrow 2^N \geq 6 \Rightarrow N = 3 \text{ f/f'}$$



UP COUNTER

CLK	LSB Q_0	Q_1	MSB Q_2
0	0	0	0
1	1	0	0
2	0	1	0
3	1	1	0
4	0	0	1
5	1	0	1
6	0	1	1
7	0	0	1




Q. Construct a Asy. decade counter?

Mod - 10

$$2^N \geq 10 \Rightarrow N = 4 \text{ flf's.}$$

CLK	LSB Q_0	Q_1	Q_2	MSB Q_3
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
...				
10	0	1	0	1

 

Excitation Tables :


J K $Q(t+1)$

~~0 0~~ $Q(t)$

~~0 1~~ 0

1 0 1

1 1 $\overline{Q(t)}$

 


J K

1 0

1 1

1 x

S R f/f :

 

S R

0 1

0 0

0 x

$Q(t)$	$Q(t+1)$	J	K	S	R	T	D
0	0	0	x	0	x	0	0
0	1	1	x	1	0	1	1
1	0	x	1	0	1	1	0
1	1	x	0	x	0	0	1

Q. Obtain excitation table of x-y f/f :-


x	y	$Q(t+1)$
0	0	1
0	1	$\overline{Q(t)}$
1	0	$Q(t)$
1	1	0

$Q(t)$	$Q(t+1)$	x	y
11 10 1x	0	1	x
00 01 0x	1	0	x
11 01 x1	0	x	1
00 10 x0	1	x	0

Q. Design a mod-6 syn. counter using JK flip's.

mod-6 $\Rightarrow$ 0 to 5.

state diagram

 

self starting counter.

state transition table:

present state			Next state			FF inputs		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	J_2, K_2	J_1, K_1	J_0, K_0
0	0	0	0	0	1	0x	0x	1x
0	0	1	0	1	0	0x	1x	x1
0	1	0	0	1	1	0x	x0	1x
0	1	1	1	0	0	1x	x1	x1
1	0	0	1	0	1	x0	0x	1x
1	0	1	0	0	0	x1	0x	x1

$J_0 = k_0 = 1$

J_1

$Q_2 \backslash Q_1 Q_0$	00	01	10	11
0	0	1	x	x
1	0	0	x	x


$$J_1 = \bar{Q}_2 Q_0$$

and $k_1 = Q_0$, $k_2 = Q_0$

J_2


$Q_2 \backslash Q_1 Q_0$	00	01	10	11
0	0	0	1	0
1	x	x	x	x

$$J_2 = Q_1 Q_0$$

 

$$f_{\max} = \frac{1}{t_{pd} / ff}$$

unused states

 

present state			flip flops						Next state		
Q_2	Q_1	Q_0	J_2	k_2	J_1	k_1	J_0	k_0	Q_2	Q_1	Q_0
1	1	0	0	0	0	0	1	1	1	1	1
1	1	1	1	1	0	1	1	1	0	0	0

Q. Design a syn. counter using T flip/f's.

which counts to 0, 3, 5, 6, 0, ...


Is it a self starting counter?

state diagram


→ Not a self starting counter.

"LOCK OUT"

Unused states:

 

①, ②, ④, ⑦

 

(1).

P.S.

N.S

f/f i/p's

$Q_2 Q_1 Q_0$

$Q_2 Q_1 Q_0$

$T_2 T_1 T_0$


(2).

P.S

f/f i/p's


N.S.

 Q. Draw the state diagram of following digital circuit (i.e. 2 bit syn. up/down counter).



(ii). JK - f/f

 present i/f { J, k } → branches of each state.
P.S { Q } → states




(iii). T - f/f


T → present i/p

Q → P.S.

T	Q(t+1)
0	Q(t)
1	$\overline{Q(t)}$

 

CONVERSION OF f/f's:

 

Q. Convert SR - f/f into T - f/f.

SR f/f → T - f/f
Exci. table char. table

T	Q(t)	Q(t+1)	S	R
0	0	0	0	x
0	1	1	x	0
1	0	1	1	0
1	1	0	0	1


	$\bar{Q}$	Q
$T=0$	0	x
$T=1$	1	0

$$S = T\bar{Q}$$


	$\bar{Q}$	Q
$T=0$	x	0
$T=1$	0	1

$$R = TQ$$

$\Rightarrow T\text{-f/f}$

 

Q Identify the following f/f.

 

x	$Q(t)$	$x \oplus Q$	D	$Q(t+1)$
0	0	0	0	0
0	1	1	1	1
1	0	1	1	1
1	1	0	0	0


$Q(t+1)$	0	1	1	0
D	0	1	1	0
x	0	0	0	0
$Q(t)$	0	1	1	0
$\bar{Q}(t)$	1	0	0	1

x	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$

$\Rightarrow T\text{-f/f}$

Q Convert D-f/f into JK-f/f.

Q2. Identify the following f/f.

 

Q. In which of the following counters
lockout doesn't occur.

(1). Mod - 13 counter (2). Mod - 30 counter

(3). Mod - 32 " (4). Mod - 36 "

$$2^4 - 13 = 3 \text{ unused states}$$

$$2^5 - 32 = 0 \text{ unused states}$$

$$2^5 - 30 = 2 \text{ unused states}$$

$$2^6 - 36 = 28 \text{ unused states}$$

MULTI VIBRATORS USING LOGIC GATES:

1. ASTABLE MV:

→ 2 quasi stable states

→ Square wave Generator.

2. BISTABLE MV:


→ 2 stable states


→ 1-bit memory element

3. MONOSTABLE MV: [one shot]

→ 1 quasi & 1 stable


→ pulse generator

 

 


(2). flip flop

MONO STABLE :

 


Q. Identify the following MV's.

 


→ NO trigger ; Ans: ASTABLE MV.

DATA CONVERTERS :

 - (1) . DAC [Digital to Analog]
- (2) . ADC [Analog to Digital].



CLK	count	V_o
0	0000	0V
1	0001	1V
2	0010	2V
...	...	...
15	1111	15V
16	0000	0V

 

no. of steps = 15

fso (full scale o/p) = 15V

Resolution = step size (V)

It is the smallest possible change at the o/p of DAC for any change in i/p.

'N' Bit DAC $\rightarrow (2^N - 1)$

= no. of steps $\times$ step size $\leftarrow$ fso

= $(2^N - 1) \times$ step size

$$\rightarrow \% \text{ Resolution} = \frac{\text{step size}}{\text{fso}} \times 100$$

$$= \frac{1}{2^N - 1} \times 100$$

Q. The o/p of a 8-bit DAC is 0.15V when the i/p is 00000001.

Determine (1). % resolution

(2). FSO

(3). DAC o/p for a digital i/p of 10101010.

Sol: (1). $\frac{1}{2^8 - 1} \times 100$


(2). $\therefore \text{FSO} = (2^N - 1) \times \text{step size}$
 $= (2^8 - 1) \times 0.15 \text{ V}$

(3). $1010 \ 1010 \xrightarrow{2} 170_{10}$


$\therefore \text{o/p} = 170 \times 0.15 \text{ V.}$

Resolution $\left\{ \begin{array}{l} \text{Voltage (should be less)} \\ 0.1 \text{ V} \\ 0.5 \text{ V} \\ 1 \text{ V} \end{array} \right.$
 8 bit DAC
 16 "
 32 "


(1). BINARY WEIGHTED DAC:

 

 (1). If $a_{N-1} = 1; a_{N-2} = \dots = a_1 = a_0 = 0$



 (2). If $a_0 = 1, a_{N-1} = \dots = a_1 = 0$.



Resolution

$$V_0 = \left(a_{N-1} 2^{-1} + a_{N-2} 2^{-2} + \dots + a_1 2^{-(N-1)} + a_0 2^{-N} \right) V_R$$


Eg: for a 3 bit DAC.


$$V_0 = \left(a_2 2^{-1} + a_1 2^{-2} + a_0 2^{-3} \right) V_R$$

$$\text{Resolution} = \frac{V_R}{2^3}$$


Draw back $\rightarrow$ for 32 bit DAC $\rightarrow 2^{31} \times R$ is required $\dots$ and so.

R - 2R LADDER DAC:

 

 

 Q: Determine I_1 & V_0 in the following circuit.



$$I = \frac{V}{R} = \frac{10}{1k} = 10mA$$

$$I_1 = \frac{I}{16} = \frac{10mA}{16}$$





$$V_0 = -I_2(2k)$$

$$= -\left[\frac{I}{4} + \frac{I}{16}\right](2k)$$

ADC'S:

1. counter type
2. Successive approximation type.
3. flash type
4. dual slope.

COUNTER TYPE:-

    


$$\text{Max. conversion time} = (2^N - 1) \cdot T;$$

T - clock period


$$T_s \geq \text{Max. conversion time}$$

$$T_s = \text{Sampling period}$$

SUCCESSIVE APPROXIMATION ADC

 


3-bit SAR

 

Max. conversion time
= $N \cdot T$


where
 $T = \text{clk period}$

 Q. The final value of a 5-bit SAR is 01011. what are its intermediate values?



FLASH TYPE ADC : [PARALLEL ADC]

(3-bit)

 

$$\text{let } \frac{4V_R}{8} < V_{in} < \frac{5V_R}{8}$$

$$\Rightarrow \text{Digital o/p} = 100$$

$$\text{let } V_R = 8$$

$$4V < V_{in} < 5V$$

$$\Rightarrow 100$$


$$\text{let } \frac{1 \cdot V_R}{8} < V_{in} < \frac{2V_R}{8}$$

$$\Rightarrow 001$$

Draw back:-

A N-bit flash type ADC requires $2^N - 1$ comparators.

DUAL SLOPE [INTEGRATING ADC]:

 

polarities of V_{in} , V_R have to be opposite.

$$V_o = -\frac{1}{RC} \int v dt$$

$$\Rightarrow V_o = -\frac{V}{RC} t$$


(1). $V_o > 0$, counter counts

$V_o \leq 0$, counter stops.

(2). control circuitry:

$S \rightarrow V_{in}$ for fixed time ' T_1 '

$S \rightarrow V_R$ and counter starts.

 

→ Max. Conversion time = $(2^N - 1) T$.

Conversion time depends on the magnitude of i/p .

$$T_2 = \frac{|V_{in}| T_1}{|V_R|}$$

Advantages:

1. It is very accurate and used in digital voltmeters.
2. The integrator at the i/p eliminates the power supply noise.

Draw back:

It is very slow in conversion.

Q. 8-bit ADC, i/p voltage range is -10 to $+10$

Resolution = ?


$$\begin{aligned} \text{Resolution} &= \frac{+10 - (-10)}{2^8} \\ &= \frac{20}{256} \end{aligned}$$

Q. To convert $V_{in} = 5V$ into digital, a SAR ADC takes 10s and dual slope takes 10ns.

Then for $V_{in} = 2.5V$, what is time required.?

$V_{in} = 2.5V$
 SAR ADC → 10s
 Dual ADC → 5s.

 Q. what is sampling rate of 8 bit dual slope if its clk freq. is 5 MHz.



$$f = 5 \text{ MHz}$$

$$T = \frac{1}{f} = 0.2 \mu\text{sec}$$



$T_s \gg$ max. conversion time

$$\text{ie } T_s \gg (2^8 - 1) T$$


$$T_s \gg (255 * 0.2 \mu\text{sec})$$

$$T_s = 51 \mu\text{sec}$$
  
$$\begin{aligned} \text{Sampling rate } f_s &= \frac{1}{T_s} \\ &= \frac{1}{51 \mu} \text{ samples/sec.} \end{aligned}$$



 Q. Identify the following logic gate in -ve logic - ?



A	B	Y
0	0	0
0	+5	$4.3V \approx 5V$
+5	0	$4.3V \approx 5V$
+5	+5	$4.3V \approx 5V$


A	B	Y
1	1	1
1	0	0
0	1	0
0	0	0

← AND gate


* The OR gate in +ve logic is equal to AND gate in -ve logic.

+ve logic	-ve logic
NAND	NOR
NOR	NAND
Ex-OR	Ex-NOR
Ex-NOR	Ex-OR

WIRED-AND LOGIC :-

 


WIRED-OR LOGIC:

 

MICRO PROCESSORS

Micro computer.

 

8085 MP :-

(1). 16 Adr. lines $\rightarrow A_0$ to A_{15}

$$\begin{aligned}\text{Memory capacity} &= 2^{16} \\ &= 2^6 \cdot 2^{10} \\ &= 64 \cdot 1\text{KB} \\ &= 64\text{KB}.\end{aligned}$$

(2). 8 Data lines $\rightarrow D_0$ to D_7 .

(3). freq of MP = ~~3.072~~ 3.072 MHz.

(f).

(4). Clock freq 'f',


$$\text{Clock period } T = \frac{1}{f} = 320\text{ ns}.$$

'NMOS' Tech :

Von Neumann Architecture $\rightarrow$ Data & program stored in the same

Harvard Architecture $\rightarrow$

Data & program are stored separately

 

8 Bit Registers : (7)

B
C
D
E
H
L
ACC

16 Bit Registers : (3)


PSW₁₆ = program status word
= ACC₈ + Flag reg₈

BC
DE

HL $\rightarrow$ Memory pointer


PC:

Program Counter

 

It indicates memory location from where μp has to fetch its next instr.

FLAG REGISTER:

 

S - Sign flag $\Rightarrow S=1$, if MSB of ALU result = 1.

Z - Zero flag $\Rightarrow Z=1$, if ALU result = 0.

P - Parity flag $\Rightarrow P=1$, if ALU result has even parity.

Cy - Carry flag $\Rightarrow Cy=1$, if carry occurs during ALU operations.

AC - Auxiliary Carry flag $\Rightarrow AC=1$, if carry occurs from D_3 to D_4 bit.

↳ Can't be accessed by the programmer.

→ used in BCD arithmetic operations.

1	1	0	1	1	1	0	1
1	1	1	1	1	1	0	0
1	1	1	0	1	1	0	0

$S=1, P=0, Z=0, Cy=1, AC=1$.

Over flow flag → Signed Addition

+ 011 (+3) (or) 110 (-2)

+ 010 (+2) 101 (-3)

101

011

↑ -ve number.

← +ve number

101

↓ 2's

-011 ← -3

→ So over flow flag will set in this case.

MEMORY 8C's:


1 kB Memory
 $= 1024 \times 8$

03ff ← 16 bit Address


$= 0000 \ 0011 \ 1111 \ 1111$

$$\begin{array}{r} 8fff \\ - 03ff \\ \hline 8c00 \end{array}$$

$$2^n \geq 1024$$

 

8fff

 


$$\begin{array}{r} 03ff \\ 3800 \\ \hline 3bff \end{array}$$

4 kB Memory

$$\begin{aligned} 4 \text{ kB} &= 2^2 \cdot 2^{10} \\ &= 2^{12} \\ &= 4 \times 1024 \times 8 \end{aligned}$$

$$\begin{aligned} (2^n \geq 4096) & \xrightarrow{12} \\ n=12 & \text{ } A_0-A_{11} \end{aligned}$$

$$= 4096 \times 8$$

 

$$\begin{array}{r} f = 15 \\ 8 \quad 8 \\ \hline 1f \quad 23 \end{array}$$


$$\begin{array}{r} 0fff \\ 3800 \\ \hline 47ff \end{array}$$

Q. for a 32 kB memory the ending location address is "Afff". what is its starting address. ?


Ans: 3000H

$$\begin{array}{l} \text{EPROM} \\ \boxed{2716} = 2 \text{ kB} \leftarrow \boxed{6116} \text{ RAM} \\ \boxed{2732} = 4 \text{ kB} \leftarrow 6132 \\ \boxed{2764} = 8 \text{ kB} \leftarrow 6164 \\ \boxed{27128} = 16 \text{ kB} \leftarrow 61128 \end{array}$$

 Q. Construct a 4 kB memory using 2716 memory IC's.



 Q. Construct a 1 kB memory using 1024 x 4 memory IC's.




Q. The add. lines of 64 memory IC having capacity of 256 x 2 are connected together. What is the size of resulting memory.

64 Memory IC's

$$256 \times 2$$
 
$$256 \times (64 \times 2) \\ = \underline{256 \times 128}$$



Q. How many 256×4 memory IC's are required to construct a 32 KB memory.

$$\text{No. of IC's required} = \frac{\text{Required size}}{\text{Given size}}$$

$$128 \left\{ \begin{array}{l} \text{2 columns} \\ \text{rows} \end{array} \right\} = \frac{32 \times 1024 \times 8}{256 \times 4} \\ = 256 \text{ IC's.}$$


8085 HP $\rightarrow$ 40 pins

$A_8 - A_{15} \rightarrow 8$


$A_0 - A_7$ } $A_0 - A_7 \rightarrow 8$
 $D_0 - D_7$ }
16

16
 8
24

 * Ready pin used to interface μp with slow speed peripherals.



 when μp is reset,
all the reg.s get cleared
including the program counter.



Masking


TRAP (RST 4.5) — NMI

RST 7.5 } Masked ← selectively disabling
 RST 6.5 } or
 RST 5.5 } Disabled

INTR — Disabled

MEMORY INTERFACING:

 Q In the following memory interfacing diagram identify addr. ranges of memory bc's.



2 kB Memory Internal access


chip select

$A_{15} A_{14} A_{13} A_{12} A_{11} A_{10} \dots A_0$

1 0 1 0 0 0 $\dots$ 0 = $A000_{\#}$

1 0 1 0 0 1 1 $\dots$ 1 = $A7FF_{\#}$

Q.

 

8085 MP

2 kB

Internal access

$A_{15} A_{14} A_{13} A_{12} A_{11} A_{10} A_9 \dots A_0$

1 0 1 0 1 0 0 $\dots$ 0 = $A800_{\#}$

1 0 1 0 1 1 1 $\dots$ 1 = $Afff_{\#}$

8/0 INTERFACING:

1. Memory mapped 8/0 $\rightarrow$ 8/0 devices are considered as memory etc.
2. 8/0 mapped 8/0. $\rightarrow$ 8/0 & Memory are considered separately.


	Memory mapped I/O		I/O mapped I/O	
1). NO. of addr. lines	16	16	16	8
2). Control signals	$\overline{MEMR}$ $\overline{MEMW}$	$\overline{MEMR}$ $\overline{MEMW}$	$\overline{MEMR}$ $\overline{MEMW}$	$\overline{IOR}$ $\overline{IOW}$
3). NO. of peripherals	60 KB $\rightarrow$ 4 KB 50 KB $\rightarrow$ 14 KB 64 KB $\rightarrow$ Nil			2^8 $= 256$ I/O devices

Control signals:

$\overline{MEMR}$ $\overline{IOR}$
 $\overline{MEMW}$ $\overline{IOW}$

Q. A peripheral is interface to the μP as shown below. Determine —

 - (1). Mode of interfacing
- (2). Addr.s of internal reg.s.



Ans: (1). I/O mapped I/O mode.

(2). peripheral has 8 reg.s., peripheral is I/O device b'coz


	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0	
R_1	1	1	1	1	0	0	0	0	$= F0$
R_2									
R_3									
R_4									
R_5									
R_6									
R_7									
R_8	1	1	1	1	0	1	1	1	$= F7$

INSTRUCTION CYCLE:

Time required to execute an instr.

Range: 1 machine cycle to 5 m/c.

MACHINE CYCLE:

 


Time required to complete one operation of accessing memory, accessing I/O devices & sending an acknowledgement.

Range: 3 T states to 6 T.

T-STATE:

 
It is sub task performed in one clock period



$T = 320 \text{ ns}$

TYPES OF MACHINE CYCLES:

 1. Opcode fetch m/c $\rightarrow 4T$
2. Memory Read m/c $\rightarrow 3T$
3. Memory write m/c $\rightarrow 3T$
4. I/O Read m/c $\rightarrow 3T$
5. I/O write m/c $\rightarrow 3T$
6. Hold Ack m/c
7. Interrupt Ack m/c




Opcode fetch m/c $\rightarrow 4T = 3T + 1T$

decoding
↓


↑ fetching

①. MOV C, A $\rightarrow$ ②. opcode

$= 01001111_2 = 4F_{16}$

 


 1 - Byte Instruction: $\rightarrow$ MOV C, A




2 - Byte Instruction:

$\rightarrow$ ~~MOV~~ MOV C, 32
let xx

 

3 - Byte Instruction:

$\rightarrow$ LDA 7250
xy

 

XTHL $\rightarrow$ 1B

ANI f2 $\rightarrow$ 2B

LDA XB $\rightarrow$ 1B

LXI H, 1122 $\rightarrow$ 3B

STACK:


SP: Stack pointer

LIFO:

Last in first out

(1). PUSH. xp

$\uparrow$ reg. pair

 


Eg
PUSH B
PUSH D
PUSH H

$\hookrightarrow$ decrement sp + push higher reg.
decrement sp + push lower reg.


Eg: Let SP = ffff

HL = 2550


1). PUSH H
SP $\rightarrow$ ffff

 

2). PUSH H $\frac{SP}{fffB}$

 


POP RP:

 

Get 1 Byte into lower reg + increment sp

 Get 1 Byte into higher reg + increment sp




Q what are the contents of acc & flag reg. after executing following instructions.

(i). SP = ffff

(ii). push H

HL = 2100

(iii). POP PSW

 

The above program is used to clear the flag register.

1) push H
2) push B
pop H
pop B } X

2) push H
push B
pop B
pop H } ✓

INSTRUCTIONS :

1. Data Transfer
2. Arithmetic } flags Affected.
3. Logical }
4. Branching
5. Machine related, & I/O
6. Additional

MP
BC = 8250
HL = 8252

Memory	
data	Addr.
11	8250
22	8251
33	8252
44	8253

(BC) = (8250)
= 11

(HL) = (8252)
= 33.

M = (HL) = 33.

HL = 8252

M = (HL)

= (8252) = 22.

ARITHMETIC INTRNS:

m/c → get the instr + operation

(X) 1 + 0
1 + 1
ADL 47 2 + 0

Instruction Operation Bytes/Mbc/r Types of Mbc Flags affected.

1). ADD ^{B, C, D, E, H, L, A.} R	$A + R \rightarrow A$	1/1/4	r	ALL
ADD M	$A + (HL) \rightarrow A$	1/2/7	r, R	ALL
ADD 8bit data	$A + (8bit\ data) \rightarrow A$	2/2/7	r, R	ALL
2). SUB R				
SUB H				
SUB 8bit data				
3). ADC R	$Cy + A + R \rightarrow A$	1/1/4		
ADC M	$Cy + A + (HL) \rightarrow A$	1/2/7		
ADC 8bit data	$Cy^A + (8bit\ data) \rightarrow A$	2/2/7		
4). SBB R				
SBB M	$A - (HL) - Cy \rightarrow A$	1/2/7		
SBB 8bit data				

ALL
except 'cy' flag

f

f

1/1/4

1/1/4

R+1 → R

R-1 → R

5). INR R

DCR R

f, R, W

1/2/10

(HL)+1 → (HL)

1/2/10

(HL)-1 → (HL)

S = opcode fetch m/c (GT)

B = Bus idle m/c (3T) No FLAGS

1/1/6

SP+1 → SP

1/1/6

SP-1 → SP

INX SP

DCX SP

BC = 8250,

INR B

INX B

BC = 8251.

B = 83

f, B, B

1/3/10

HL+SP → HL

6). DAD SP

only 'cy' flag.

LOGICAL INSTRUCTIONS:

A VR → A

ORA R

A VR (HL) → A

ORA M

A VR 8bit data → A

ORI 8bit data

ALL

but cy = 0.

2). ANA R

$A \leftarrow A \text{ (HL)} \rightarrow A$

ANA H

ANL

XRA R


$A \oplus R \rightarrow A$

XRA H

XRL 8bit data

RAL

(with cy)

 

RLC

(without cy)



RAR


(with cy)



Affects only cy.

RRC
(without c_y)

ACC. =

 

CHP R

A - R

1 / 1 / 4

$c_y = 0, Z = 0$
 $c_y = 1, Z = 0$
 $c_y = 0, Z = 1$
 S, P, AC affected.

f { $A > R$
 $A < R$
 $A = R$

CHP M

A - (HL)

1 / 2 / 7

f, R { - do -
 exp. R $\rightarrow$ (HL)

CPH 8 bit data

A - (8 bit data)

2 / 2 / 7

f, R { - do -

CMA

$\bar{A} \rightarrow A$

No flags

CMC

$c_y \rightarrow c_y$

only 'cy'

STC

$c_y = 1$

only 'cy'

A = f2
 Masking
 A = 3
 02

ANI OF

A $\rightarrow$ 1111 0010
 0000 1111
 0000 0010

DATA TRANSFER INSTR.S:

1). MOV R_d, R_s $R_s \rightarrow R_d$

MOV R, M $(HL) \rightarrow R$

MOV M, R $R \rightarrow (HL)$

MVL ~~MOV~~ $R, 8\text{bit data}$ 8bit data $\rightarrow R$

MVL $M, 8\text{bit data}$ 8bit data $\rightarrow (HL)$

2). LXI $sp, 16\text{bit data}$ 16 bit data $\rightarrow sp$

(Load Immediate)

3). LDA 16 bit address (16 bit addr.) $\rightarrow A$

(Load Accumulator)

4). STA 16 bit address $A \rightarrow (16\text{bit addr.})$

(Store Accumulator)

5). LDAX sp $(sp) \rightarrow A$

STAX sp $A \rightarrow (sp)$

$\uparrow$ fR, W
 $\uparrow$ $2+1$
2/3/10

$\uparrow$ fR, W
 $\uparrow$ $3+0$
3/3/10

fR, R

fR, W

fR

fW

31 5 | 16
↓
3+2
FRR RR

31 5 | 16
↓
3+2
FRR RR

(16 bit addr.) → L
(16 bit addr + 1) → H

LHLD 8252 ie (8252) → L

(8253) → H

L → (16 bit addr.)
H → (16 bit addr. + 1)

(H) = 8090

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

6). LHLD 16 bit addr.

LHLD 8252

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

SHLD 8254

jnrao.k@gmail.com

Contact: 09966715471