

260

260

-: HAND WRITTEN NOTES:-
OF
ELECTRICAL ENGINEERING

-: SUBJECT:-
POWER SYSTEM - I

POWER SYSTEM

→ Section 1:

- Generating station ✓
- Economic aspects of generating stations ✓
- Tariff
- Economic dispatch of G/R station
- Operational and control concepts of G/R station.

→ ** Section 2:

- Calculation of resistance, inductance and capacitance of transmission line.
- Performance of short T.L.
- Performance of medium T.L.
- Performance of long T.L.
- Concept of travelling waves in T.L.
- Insulators and string efficiency
- Calculation of sag for various configurations
- Performance of underground cables

→ * Section 3:

- Circuit Breakers
- Performance of Relays
- Protection of Power system equipment

→ Section 4: (Most Imp)

- Per unit System Analysis.
- Concept of symmetrical components in power system.
- Evaluation of Positive sequence n/w, negative sequence n/w and zero sequence n/w.
- Fault analysis.
- Load flow analysis.
- Power s/n stability analysis.

PER UNIT SYSTEM ANALYSIS

#



→ The performance of a power system network consisting of several power system equipments like: a

- * Alternator — 11 kV
- * Transformers 11/132 kV
- * Transmission lines 132 kV
- * Busbars 11 kV, 33 kV
- * loads etc.

→ These can be obtained by means of Per unit s/n.

→ Before 1980 the performance of a power system network is obtained by using ABSOLUTE SYSTEM.

→ Absolute System:

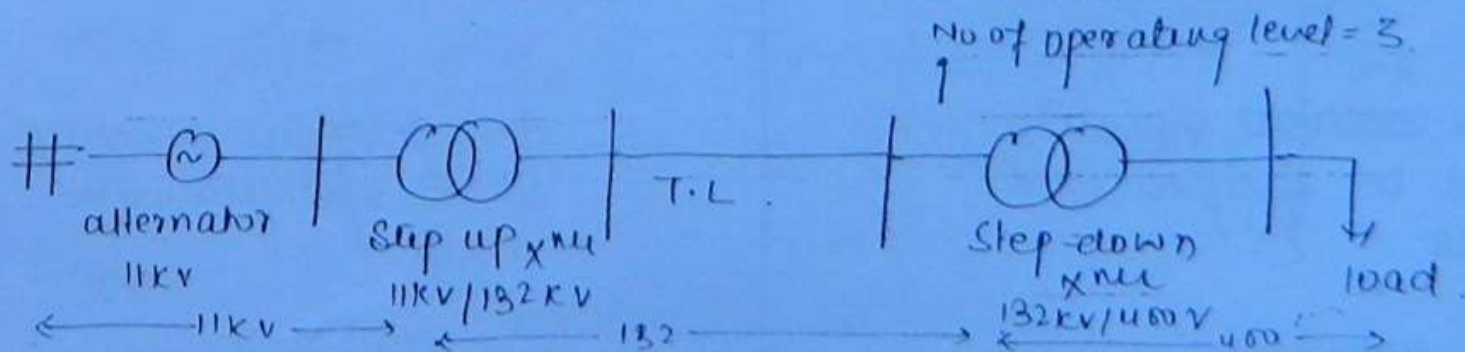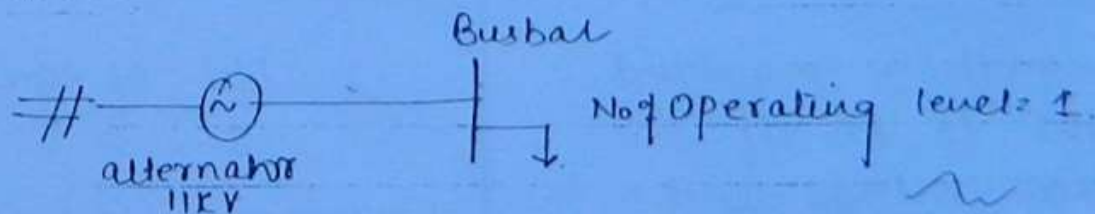

→ Consider a power system network as shown in fig (a). In absolute s/n no of equation required to analyse the performance of power system n/w is equal no no of operating level = 1.

Consider a power s/m network shown in figure (2) above. No. of equation required to analyse the performance of power s/m network is equal. no. of operating voltage level = 3.

→ A modern power system network operates at many voltage level. Therefore time required to analyse the performance of power system network increases. Due to these limitation ABSOLUTE SYSTEM is replaced with per unit s/m.

• ABSOLUTE SYSTEM

1) No. of equations required is equal to no. of operating voltage level.

2) An electrical quantity must be specified with units.

3) The performance of power s/m equipment is evaluated one after another equipment.

• PER UNIT SYSTEM

1) No. of equation required = 1.

2) An electrical quantity is not specified with units.

3) The performance of all the equipments are evaluated simultaneously.

$$\frac{\text{Actual}}{\text{Base}} = \frac{\text{Absolute}}{\text{reference}}$$

4) the evolution time is less more	4) the evolution time is less.
------------------------------------	--------------------------------

Per unit system:

$$\text{Per unit of an electrical quantity} = \frac{\text{Actual value of an electrical quantity exprd in}}{\text{Base value of same electrical quantity exprd in}}$$

→ Actual value is also known as Absolute value.
Base value is also known as a reference value.

→ The selection of base value is optional

→ Per unit value ranges from 0 to ∞

→ Base values are always considered as positive value.

		Base value = 100	Base value = 0.
Test 1	99	$P.U_1 = \frac{99}{100} = 0.99$	$p.u = \frac{99}{0} = \infty$
Test 2	103	$P.U_2 = \frac{103}{100} = 10.3$	$P.U_2 = \infty$
Test 3	135	$P.U_3 = \frac{135}{100} = 1.35$	$P.U_3 = \infty$

As resistance is negligible to reactance in a winding.

Relation b/w ABSOLUTE S/M AND PER UNIT S/M :-

Consider two machines in power s/m network.

Machine 1: V_1 (VOLT), I_1 (Ampere)

Machine 2: V_2 (VOLT), I_2 (Ampere)

let $V_b = V_1$; $I_b = I_1$

p.u. current

$$\bullet I_{1p.u.} = \frac{I_1}{I_b} = I_1 / I_1 = 1 p.u.$$

$$\bullet I_{2p.u.} = \frac{I_2}{I_b} = I_2 / I_1 p.u.$$

p.u. voltage

$$\bullet V_{1p.u.} = \frac{V_1}{V_b} = \frac{V_1}{V_1} = 1 p.u.$$

$$\bullet V_{2p.u.} = \frac{V_2}{V_b} = \frac{V_2}{V_1} p.u.$$

A winding in a equipment consist a negligible resistance and significant reactance. Therefore resistance is neglected and reactance is only considered to analyse a power system in/w.

As the resistance is neglected. the error introduced in s/m is less than 5% and is neglected.

Since resistance is neglected. $X = V/I$

Reactance measured in Ω .

$$X_1 \text{ in } \Omega = \frac{V_1 \text{ in volts}}{I_1 \text{ in Ampere}} = \frac{V_B}{I_B} = X_B \text{ in } \Omega$$

$$X_2 \text{ in } \Omega = \frac{V_2 \text{ in volts}}{I_2 \text{ in Ampere}}$$

* P.u Reactance :-

$$\bullet X_{1 \text{ p.u}} = \frac{X_1 \text{ in } \Omega}{X_B \text{ in } \Omega} = \frac{X_1 \text{ in } \Omega}{X_1 \text{ in } \Omega} \cdot 1 \text{ p.u.}$$

$$\bullet X_{2 \text{ p.u}} = \frac{X_2 \text{ in } \Omega}{X_B \text{ in } \Omega} = \frac{X_2 \text{ in } \Omega}{X_1 \text{ in } \Omega} \text{ p.u.}$$

$$X_{\text{p.u}} = \frac{X \text{ in } \Omega}{X_B \text{ in } \Omega} \quad \text{--- (1)}$$

now from eq (1)

$$X_{\text{p.u}} = \frac{X \text{ in } \Omega}{V_B / I_B}$$

$$X_{\text{p.u}} = X \text{ in } \Omega \left(\frac{I_B}{V_B} \right) \quad \text{--- (2)}$$

Equation (2) expressed per unit reactance in terms of base current and base voltage.

Using equation (2) per unit reactance of all the equipments cannot be determined.
A X_{rel} is specified with VA rating

And voltage rating.

Expressing per unit reactance in terms of base MVA and base KV:-

$$X_{pu} = X_{in} \Omega \left(\frac{I_b}{V_b} \right)$$

$$= X_{in} \Omega \left(\frac{V_b \cdot I_b}{V_b \cdot V_b} \right)$$

$$= X_{in} \Omega \left(\frac{V_b \cdot I_b}{V_b^2} \right)$$

$$= X_{in} \Omega \left(\frac{V_b I_b / 10^6}{V_b^2 / 10^6} \right)$$

$$= X_{in} \Omega \left(\frac{\text{MVA base}}{(V_b / 10^3)^3} \right)$$

$$\boxed{X_{pu} = X_{in} \Omega \left(\frac{\text{MVA base}}{Kv_b^3} \right)} \quad \text{--- (3)}$$

When a new generating station is commissioned to the grid the per unit reactance of the power s/n network changes.

Expressing new per unit reactance in terms of old p.u reactance

$$X_{p.u. \text{ new}} = X_{\text{in } \Omega} \left(\frac{MVA_{B, \text{ new}}}{KV_{B, \text{ new}}^2} \right)$$

$$X_{p.u. \text{ old}} = X_{\text{in } \Omega} \left(\frac{MVA_{B, \text{ old}}}{KV_{B, \text{ old}}^2} \right)$$

$$\frac{X_{p.u. \text{ (new)}}}{X_{p.u. \text{ (old)}}} = \left(\frac{MVA_{B, \text{ (new)}}}{MVA_{B, \text{ (old)}}} \right) \left(\frac{KV_{B, \text{ old}}^2}{KV_{B, \text{ new}}^2} \right)$$

$$X_{p.u. \text{ (new)}} = X_{p.u. \text{ (old)}} \left(\frac{MVA_{B, \text{ (new)}}}{MVA_{B, \text{ (old)}}} \right) \left(\frac{KV_{B, \text{ old}}^2}{KV_{B, \text{ new}}^2} \right) \quad \text{--- (4)}$$

Trick

$$X_{p.u. \text{ (new)}} = X_{p.u. \text{ old}} \left(\frac{MVA_{B, \text{ (new)}}}{MVA_{B, \text{ old}}} \right) \left(\frac{KV_{B, \text{ old}}^2}{KV_{B, \text{ new}}^2} \right)$$

$\downarrow$
 10^6

$\downarrow$
 10^3

$M \rightarrow N(\text{new})$

$n(\text{numerator})$

Question :-

A Generating station has base values 30MVA, 11KV, 1.2
 what is the new per unit reactance if the base
 of generating station is selected as 75MVA, 13.2KV

$$MVA_{\text{old}} = 30 \text{ MVA}$$

$$KV_{\text{old}} = 11 \text{ K}$$

$$MVA_{\text{new}} = 75 \text{ MVA}$$

$$KV_{\text{new}} = 13.2 \text{ KV}$$

$$X_{pu(new)} = 1.2 \left(\frac{75}{30} \right) \left(\frac{11}{13.2} \right)^2$$

$$X_{pu(new)} = 2.08 \text{ pu} \quad \underline{\text{Ans}}$$

Ques:-

the pu reactance of an alternator with base values 30MVA, 11KV with 6Ω reactance is

$$X_{pu} = X \left(\frac{MVA_{base}}{KV_b^2} \right)$$

$$X_{pu} = 6 \cdot \left(\frac{30}{(11)^2} \right)$$

$$X_{pu} = 1.49 \text{ pu}$$

Ques:-

What is the per unit reactance, if the capacity (MVA) is doubled and voltage is double.

$$MVA_b(new) = 2 MVA_b(old)$$

$$KV_b(new) = 2 KV_b(old)$$

$$X_{pu(new)} = X_{pu(old)} \left(\frac{2 MVA_{old}}{MVA_{old}} \right) \left(\frac{2 KV_b(old)}{2 KV_b(new)} \right)^2$$

$$X_{pu \text{ new}} = \frac{1}{2} X_{pu \text{ old}} \quad \underline{\text{Ans}}$$

Questions

What is the pu reactance if capacity and voltage are reduced to 50% of original value..


$$X_{pu(\text{new})} = 1 \times \left[\frac{1 \text{ MVA (old)}}{2 \text{ MVA (old)}} \right] \left[\frac{\frac{2KV_B(\text{old})}{KV_B(\text{new})}}{1} \right]^2 \text{ p.u.}$$

Default per unit

$$X_{pu(\text{new})} = 2 X_{pu(\text{old})}$$

* the default value of per unit quantity is also always 1.

Definition of Per unit Reactance:

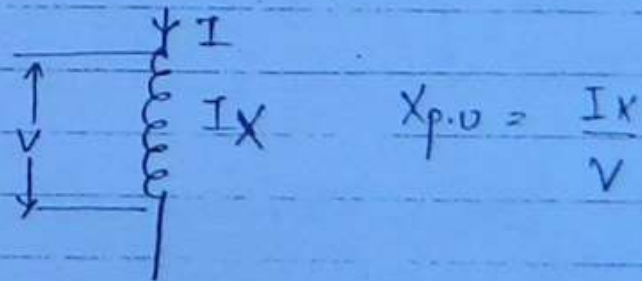

With full load current I flowing through the winding the ratio of the reactive drop to the rated voltage applied across the winding gives the per unit reactance of the winding.

$$X_{pu} = IX/V$$

Percentage reactance:

$$\left. \begin{aligned} \% X &= 100 \cdot X_{pu} \\ \% X &= 100 \cdot \frac{IX}{V} \end{aligned} \right\} \text{--- (6)}$$

substitute (5) in equation (6).

$$\% X_{pu} = 100 \cdot X_{pu}$$

$$\% X = 100 \cdot X_{in \Omega} \left(\frac{\text{MVA base}}{KV_D^2} \right) \text{--- (7)}$$

from equation (6).

$$\% X = \frac{IX}{V} \cdot 1000$$

$$\text{now } X_{in \Omega} = \frac{\% X \cdot V}{100 \cdot I} \text{--- (8)}$$

Expressing base reactance in terms of base MVA and base KV:

$$X_b = V_b / I_b$$

$$= \frac{V_b \cdot V_b}{10^6}$$

$$\frac{V_b^2}{10^6} \cdot I_b$$

$$\frac{V_B^2}{10^6}$$

$$\frac{V_B I_B}{10^8}$$

$$= \frac{(V_B/10^3)^2}{(V_B I_B/10^8)}$$

$$\boxed{X_{pu} = \frac{KV_B^2}{base \cdot MVA(B)}} \quad - (9)$$

* DIRECT EQUATION :-

$$\bullet \quad X_B = \frac{KV_B^2}{MVA_B}$$

$$\bullet \quad X_{pu} = \frac{X \times MVA_B}{\Omega \times KV_B^2}$$

checking units

$$\frac{V \cdot I}{I} = \frac{I \cdot X}{V}$$

$$\bullet \quad \% X = 100 \times X \text{ in } \Omega \left(\frac{MVA_B}{KV_B^2} \right)$$

$$\bullet \quad X_{pu(new)} = X_{pu(old)} \left(\frac{MVA_{old}}{MVA_{new}} \right) \left(\frac{KV_B^2(old)}{KV_B^2(new)} \right)$$

Short circuit current And short ckt MVA :-

$$I_{sc} = \frac{V_{in \text{ volt}}}{X_{ig} \Omega}$$

$$\frac{\%X}{100} \cdot \frac{V}{I}$$

$$\%X = 100 \cdot \frac{X_{p0}}{V}$$

$$\%X = 100 \frac{XI}{V}$$

$$X = \frac{\%X}{100} \cdot \frac{V}{I}$$

$$I_{sc} = \frac{100}{\%X} \cdot I \quad \text{--- (10)}$$

I - full load current.

I is the full load current flowing through the winding / circuit.

Imp

to limit the short circuit current increase $\%X$ or increase reactance of the winding measured in Ohms.

from equation (10)

$$\frac{I_{sc} \cdot V}{10^6} = \frac{100}{\%X} \cdot \frac{I \cdot V}{10^6}$$

$$MVA_{sc} = \frac{100}{\%X} MVA$$


$$= \boxed{MVA_{sc} = MVA \times \left(\frac{100}{\%X} \right)} \quad \text{--- (11)}$$

In above formulae MVA corresponds to full load

current flowing through the winding.

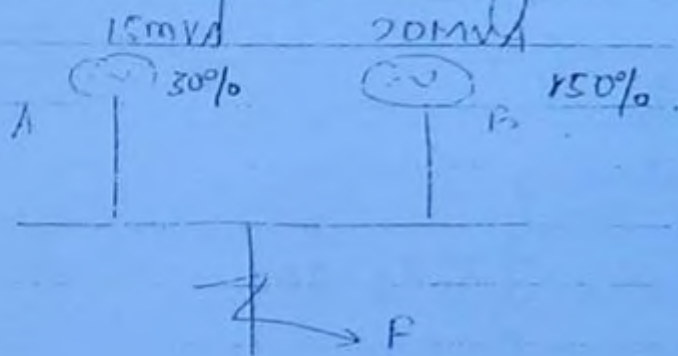Question:-

The single line diagram of a 3 ϕ system is shown below. The % reactance of each alternator is based on its own capacity. Find the short circuit current flowing in the n/w due to 3 ϕ S.C at point F. Evaluate by considering base MVA as 35 MVA.



STEP 1: reactance diagram

→ In the reactance diagram the %age reactance of the power s/n equipment calculated w.r.t base MVA are represented.

% X_A w.r.t Base MVA

is 30% — 15 MVA

$X_A\%$ —→ 35 MVA

$$= \frac{35}{15} \times 30$$

$$X_A\% = 70\%$$

∴ more value
will be found
as a proportion


* To protect the alternator always connected to ground through Y connection this must be shown in Reactance diagram
 $\%X_B$ w.r.t Base 20 MVA

$$15\% \text{ --- base 20 MVA}$$

$$X_B\% = \frac{25 \times 15}{20} = 87.5\%$$

$$X_B\% = 87.5\%$$

Reactance Diagram:



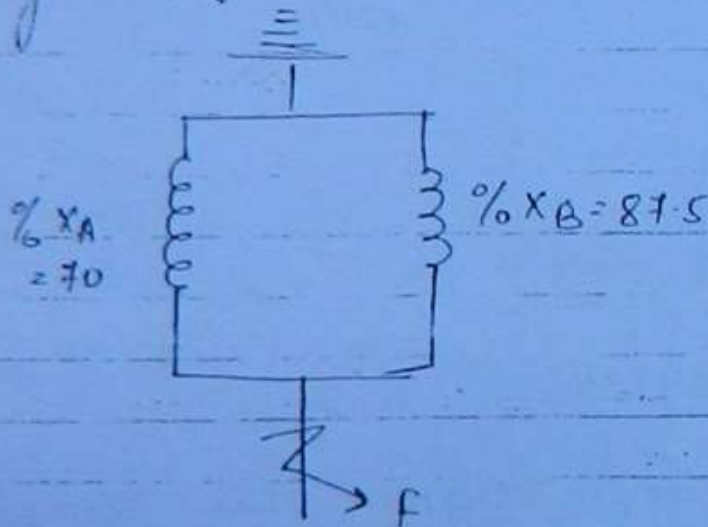


$$\%X = (\%X_A) \parallel (\%X_B)$$

$$= \frac{70 \times 87.5}{70 + 87.5}$$

$$X\% = 38.8\%$$

* Method of Grounding:

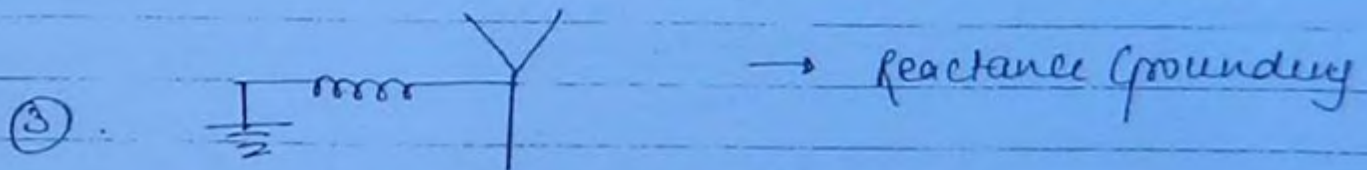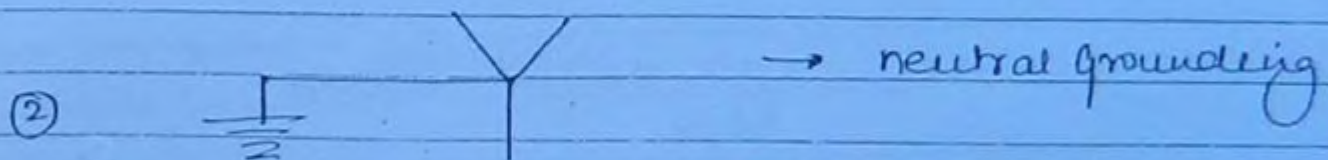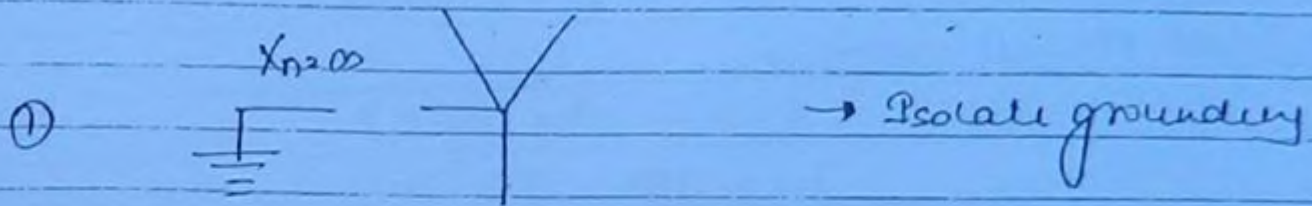

STEP 2: To find short circuit full load current flowing through the n/w's.

$$1\phi \text{ VA} = V_{ph} \cdot I_{ph}$$

$$3\phi \text{ VA} = 3 \cdot V_{ph} \cdot I_{ph}$$

$$3\phi : \Delta : \text{VA} = \frac{3 V_L \cdot I_L}{\sqrt{3}} = \sqrt{3} V_L I_L$$

$$3\phi : \nabla : \text{VA} = \frac{3 \cdot V_L \cdot I_L}{\sqrt{3}} = \sqrt{3} V_L I_L$$

→ full load current is calculated w.r.t base MVA

$$35 \times 10^6 = \sqrt{3} \times 12 \times 10^3 \times I_L$$

$$I_L = I_{ph} = I = 1684 \text{ A}$$

Step B: Short circuit current.

$$I_{sc} = \frac{100}{\%X} \cdot I$$

$$\frac{100}{38.89} \times 1684 = 4330 \text{ A}$$

$$I_{sc} = 4330 \text{ A}$$

Question 5:-

A 3 ϕ 20MVA, 10KV alternator has internal reactance of 5% and negligible resistance. Find the external reactance per phase to be connected in series with the alternator so that steady current on short circuit does not exceed 8 times the full load current.

$$I_{sc} = 8I$$

$$\frac{I_{sc}}{I} = 8 \quad \text{--- (1)}$$

$$I_{sc} = \frac{100}{\%X} \cdot I$$

$$\frac{I_{sc}}{I} = \frac{100}{\%X} = 8$$

$$\%X = 100/8 = 12.5\%$$

$$\%X_{\text{existing}} = 5\%$$

$$\%X_{\text{required}} = 12.5 - 5 = 7.5\%$$

$$\boxed{\%X_{\text{req}} = 7.5\%}$$

For per phase reactance:-

Reactance per phase can be obtained

$$\%X = 100 \cdot X_{pu}$$

$$\%X_{\text{req}} = 100 \cdot \frac{I X}{V}$$

$$\boxed{X_{in \Omega} = \frac{\%X_{\text{req}} \cdot V}{100 \cdot I}}$$

Full load current I:

I is calculated as

$$VA = \sqrt{3} V_L I_L$$

$$= \frac{20 \times 10^8}{\sqrt{3} \times 10 \times 10^3} = I_L$$

$$I_L = 1154.7 \text{ A}$$

→ Reactance is per phase so current and voltage must be per phase

$$\text{per phase reactance in ohms} = \frac{7.5 \times 10 \times 10^3 / \sqrt{3}}{100 \times 1154.7}$$

∴ Alternator % React Base MVA = 10 MVA.

% X_{alt} wrt Base MVA.

$$10\% \rightarrow 10 \text{ MVA}$$

$$\% X_{alt} \rightarrow 10 \text{ MVA.}$$

$$\% X_{alt} = \frac{10 \times 10}{10} = \boxed{10\% = X_{alt}\%}$$

∴ Transformer % reactance wrt base MVA.

% X_{Tf} wrt Base MVA.

$$5\% \rightarrow 5 \text{ MVA.}$$

$$\% X_{Tf} \rightarrow 10 \text{ MVA}$$

$$\% X_{Tf} \rightarrow \frac{10 \times 5}{5} = \boxed{10\% = X_{Tf}\%}$$

∴ Transmission line % reactance wrt MVA_b, KV_b.

$$\% X = 100 \cdot X_{p.u}$$

$$\% X = 100 \cdot X_{in \Omega} \left(\frac{\text{MVA}_b}{\text{KV}_b^2} \right)$$

$$\% R = 100 \cdot R_{in \Omega} \left(\frac{\text{MVA}_b}{\text{KV}_b^2} \right)$$

Single line diagram starts at G/R end to load.

* 98% of fault occur on the T.L and coz 98% of working is on T.L.

$$X_{line} = 0.375 \Omega$$


Question:-

A 3 ϕ T.L operating at 10KV and having resistance of 1Ω and reactance 4Ω is connected to G/R station busbar through 5MVA step up xmer. having a reactance of 5%. The bus bar are supplied by a 10MVA alternator having 10% reactance determine the short circuit kVA of a symmetrical fault b/w the phases if it occurs.

a) At the load end of T.L.

b) High voltage terminal of xmer.

Step 1:-

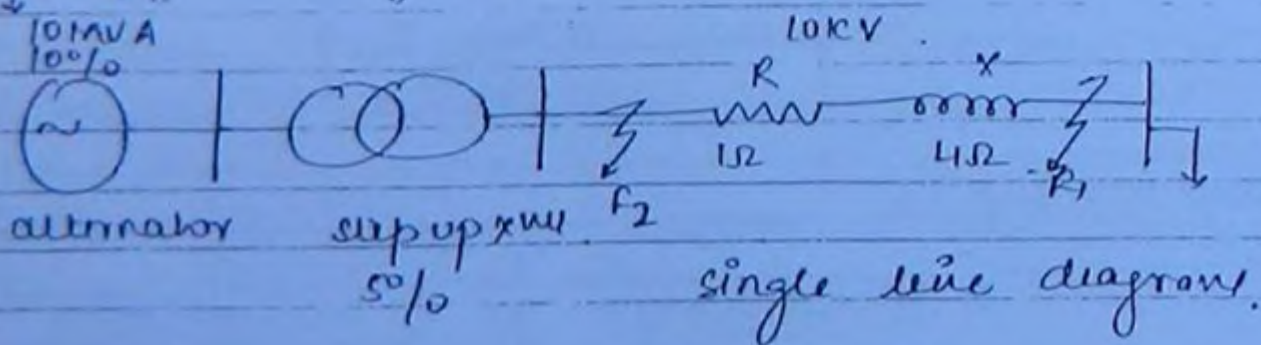

Step 2:- Reactance diagram: Here % reactance of all the equipment are listed.

* When horizontal line diagram is given base MVA is taken as the MVA of first equipment i.e. alternator.

Since T.L operates at 10kV select base KV as 10kV.


$$\%X_{TL} = \frac{100 \times 4 \times 10}{100} = 40\%$$

$$\boxed{\%X_{TL} = 40\%}$$

% resistance of T.L w.r.t MVA_B, KV_B.

$$\%R_{TL} = \frac{100 \times 1 \times 10}{(10)^2} = 10\%$$

$$\boxed{\%R_{TL} = 10\%}$$

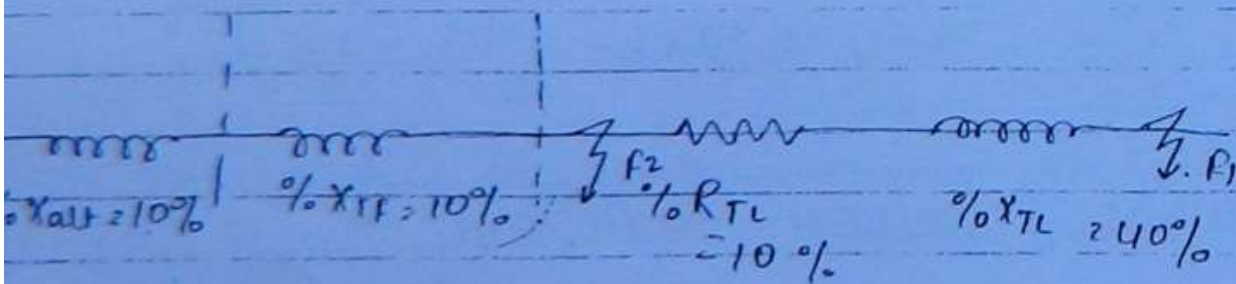

Step 3: Short circuit MVA w.r.t fault point F_1

Total $\%X$ upto fault point F_1

$$\%X_T = 10 + 10 + 40 = 60\%$$

Total $\%R$ upto fault point $F_1 = 10\%$.

* As we move away from ORIGINATING STATION
S.C. MVA DECREASE.

$$\% Z_{F1}^2 = \% X_{F1}^2 + \% R_{F1}^2$$

$$= 60^2 + 10^2$$

$$\boxed{\% Z_{F1} = 60.83\%}$$

Short circuit MVA upto fault point F_1 .

$$MVA_{SC} = \frac{100 (MVA_{base})}{\% Z_{F1}}$$

$$= \frac{100 \times 10}{60.83}$$

$$\boxed{MVA_{SCF1} = 16.44 MVA}$$

Step 4: Short circuit MVA upto fault point F_2 .

Total Reactance upto F_2

$$\% X_T = 20\%$$

$$\% R_T = 0$$


$$MVA_{SC} = \frac{100}{20} \times 10 = 50 MVA$$

$$\boxed{MVA_{SCF2} = 50 MVA}$$

→ The short circuit MVA DECREASES as we move away from originating station.

Question:-

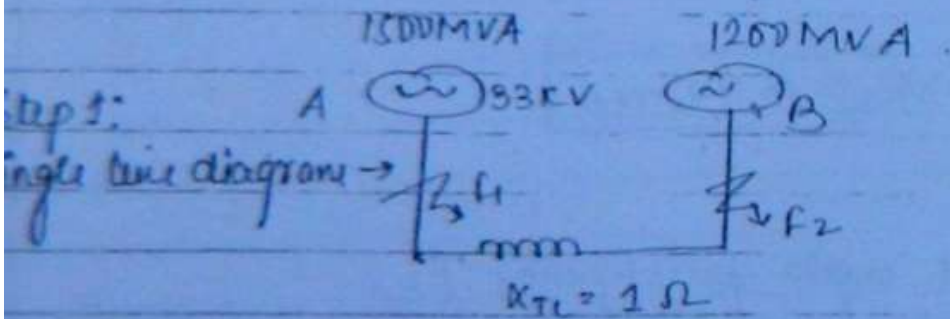3. estimated short circuit MVA at Busbar of generating station A and B are 1500 MVA and 1200 MVA. The generated voltage at each station is 33 kV. If the generating stations are interconnected through a T.L having a reactance 1 Ω and negligible resistance. Calculate the short circuit MVA at both generating stations with base MVA equal 100.



Base MVA = 100.

Step 2: Reactance diagram.

% Reactance of alternator w.r.t MVA_B

$$MVA_{SC} = \frac{100 \times 10 \text{ MVA}_B}{\%X_A}$$

$$\%X_{all} = \frac{100 \times 100}{1500} = 6.67$$

$$\%X_{\text{a.u.B}} = 100$$

→ $\%X_{\text{a.u.B}}$ @ W.T. 11 VAB : 2

$$\%X_{\text{a.u.B}} = \frac{100 \times \text{MVA}_B}{\text{MVA}_{SC}}$$



$$= \frac{100 \times 100}{1200} = 8.34\%$$

$$\boxed{\%X_{\text{a.u.B}} = 8.34}$$


→ $\%X_{TL}$ W.T. MVA_B and KV_B

$$\rightarrow 100 \times 1 \times \frac{100}{(33)^2} = 9.18\%$$

$$\boxed{\%X_{TL} = 9.18\%}$$

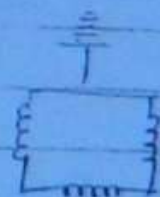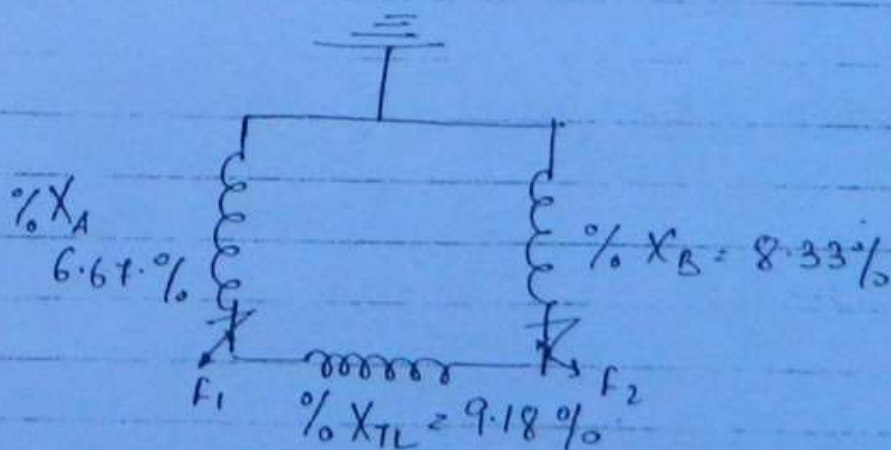

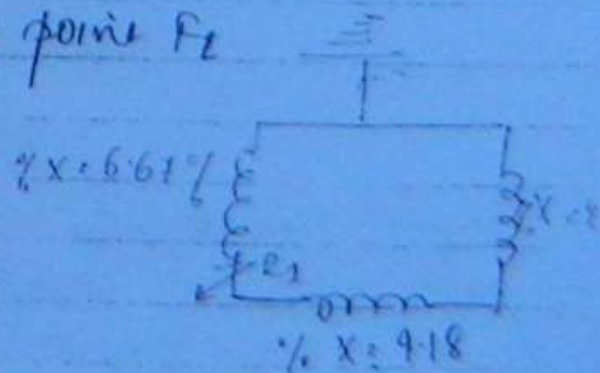Sup: Short circuit MVA upto fault point F_2



$\% X_A$
6.67



$$\% X = \% X_{TL} + \% X_B \text{ (series)}$$

$$17.51\%$$

$$\% X_{P_1} = \% X_A \parallel (\% X_B + \% X_{TL})$$

$$6.67\% \parallel (17.51)$$

$$= \frac{6.667 \times 17.51}{6.67 + 17.51} = 4.8\%$$

$$MVA_{sc} = \frac{100 \times 100}{4.8} = 2070 \text{ MVA}$$

Step → Total reactance upto fault F₂:

$$\% X = 6.67 + 9.18 = 15.85\%$$

$$\frac{8.33 \times 15.85}{8.33 + 15.85} = 5.46\%$$


$$MVA_{sc} = \frac{100 \times 100}{5.46} = 1831.39 \text{ MVA}$$

TEXT BOOK:- Electrical Power s/m "C.L. Wadhwa"
 : Power system by Stevenson
 : Power system by Anderson & Foud


Symmetrical Components:-

Necessity of symmetrical components:-

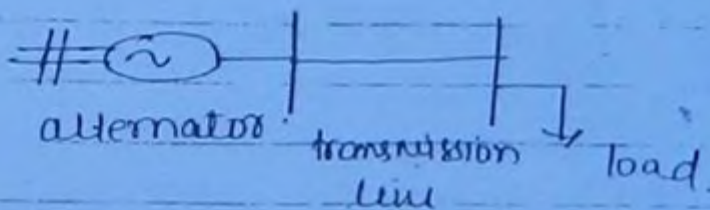Consider a power system n/w as represented by single line diagram



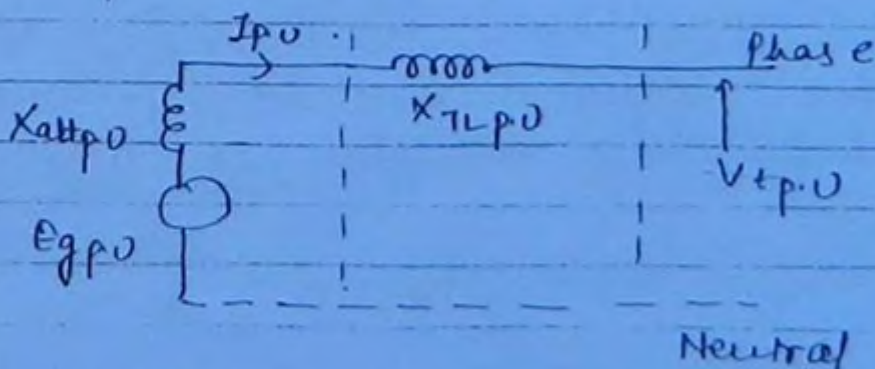→ The performance of power s/m network can be obtained by representing per phase reactance diagram in per unit value!



→ Per phase reactance diagram is drawn b/w PHASE AND NEUTRAL. phase is indicated by thick line and neutral is indicated by dotted line.

* When s/m is balance draw reactance for only one phase.

→ Reactance drop in alternator :-

$$I_{pu} X_{alt.p.u}$$

$$I_{pu} X_s$$

→ Reactance drop in T.L :- $I_{pu} X_{TL.p.u}$

→ total reactance drop $= I_{pu} (X_{alt.p.u} + X_{TL.p.u})$
 $I_{pu} (X_{eq.p.u})$

→ Terminal voltage

$$V_{tpu} = E_{gp.u} - I_{pu} X_{eq.p.u}$$

The above equation represent the performance of power system n/w.

→ For balanced s/m reactance diagram is represented for a single phase. When system is unbalance reactance diagram must be represented for all the 3 ϕ 's separately resulting in 3 eqⁿ.

$$R \text{ phase : } V_{R.p.u} = E_{gR.p.u} - I_{R.p.u} X_{eqR.p.u}$$

$$Y \text{ phase : } V_{Y.p.u} = E_{gY.p.u} - I_{Y.p.u} X_{eqY.p.u}$$

$$B \text{ phase : } V_{B.p.u} = E_{gB.p.u} - I_{B.p.u} X_{eqB.p.u}$$

* Regulation $\rightarrow$ speed $\rightarrow$ stationary (voltage) $\rightarrow$ T.L
 % efficiency $\rightarrow$ speed (rotatory)

By solving the above three equatⁿ the performance of power s/m network can be obtained

Unbalanced System :-

• Internal Unbalance s/m	• External Unbalanced s/m
• Internal unbalance occur due to mis operation of the power s/m equipment • $I_n \leq 10\% I_{FL}$ • The phase voltage $\vec{V}$ are approximately equal to each other. $V_R \approx V_Y \approx V_B$ • The phase voltages are with in regulation level.	• External unbalance occur due to faults • $I_n > 10\% I_{FL}$ • The phase voltages are not equal. $V_R \neq V_Y \neq V_B$ • Phase voltages are not with in regulatⁿ level.

In an unbalance system each and every unbalanced quantity can be represented by a set of 3-balanced quantities.

** sign of angle +ve $\rightarrow$ direction Anticlock.

[A.P]

$\rightarrow$ The set of balanced quantities are known as symmetrical components.

The above concept is formulated by 'FORIECQUE'

3-unbalanced $\quad$ 9-balanced.

$$V_R = V_{R0} + V_{R1} + V_{R2}$$


$$V_Y = V_{Y0} + V_{Y1} + V_{Y2}$$

$$V_B = V_{B0} + V_{B1} + V_{B2}$$

$\rightarrow$ The nine symmetrical component can be represent by 3.

OPERATOR K : (K or a or α).

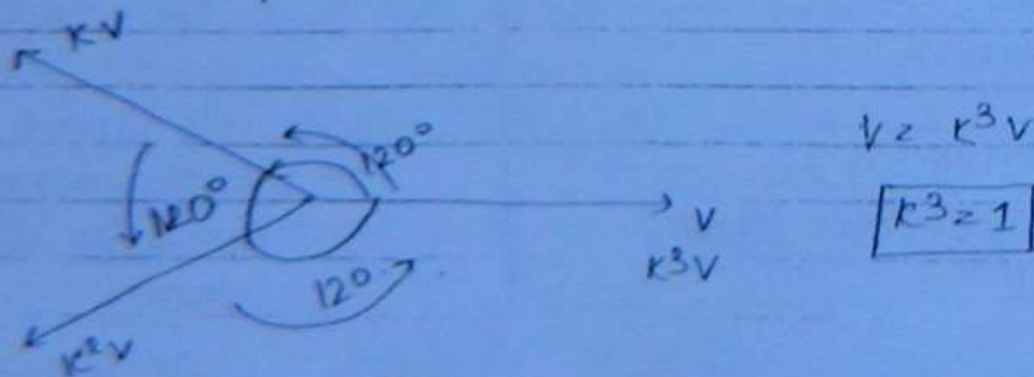Operator K rotates a vector in ANTI-CLOCKWISE direction by 120° .



$\rightarrow$ Operator K has magnitude equal 1.

As, operator k rotates a vector in Anticlockwise direction, phase angle $(+120^\circ)$

$$K = 1 \angle 120^\circ$$
$$= 1 \{ \cos 120^\circ + j \sin 120^\circ \}$$
$$= 1 \cdot \left\{ -\frac{1}{2} + j \frac{\sqrt{3}}{2} \right\}$$

$$\boxed{K = -0.5 + j 0.867}$$

$$K^2 = K \cdot K$$

$$1 \angle 120^\circ \cdot 1 \angle 120^\circ$$

$$1 \angle 240^\circ$$

$$= 1 \{ \cos 240^\circ + j \sin 240^\circ \}$$

$$= 1 \left\{ -\frac{1}{2} - j \frac{\sqrt{3}}{2} \right\}$$

$$\Rightarrow \boxed{K^2 = -0.5 - j 0.867}$$

$$K + K^2 = -0.5 + j 0.867 - 0.5 - j 0.867$$
$$= -1$$

$$\boxed{K + K^2 + 1 = 0}$$

$$\Rightarrow \boxed{K^3 + K^2 + K + 1 = 0}$$

FAULT ANALYSIS

→ Main purpose of fault analysis is design circuit breaker. (switch gear)

$I_f \rightarrow$ Fault current


$I_f \times V_f =$ Fault MVA (Circuit Breaker rating).

Fault Analysis

Symmetrical Fault Analysis

balanced
main
during fault


3 ϕ phase fault

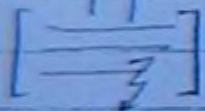


Unsymmetrical Fault Analysis

under fault
unbalanced condition


Single line to
ground (SLG)

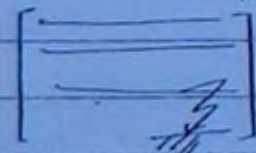

Double
line fault
(LL)

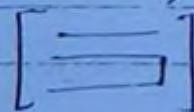

Double line
to ground
(LLG)

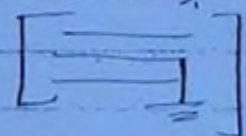

• Most severe fault is 3 ϕ fault and least is SLG.

• During design of circuit breaker, 3 ϕ fault is counted.

SLG fault is used in relay design (proper setting)

The unsymmetrical fault analysis is also an important

* Single line diagram: - indicates that original P.S is 3 ϕ and working at a balanced condition.

study since coz the knowledge of all types of fault is important to provide proper setting for the relay.

PER UNIT Analysis: -

Per unit value is unitless value.

$$\text{p.u value} = \frac{\text{Actual value in some unit}}{\text{Base/reference value in same unit}}$$

Advantage of p.u Method: -

- It simplifies power sys calculation.
- It avoids the discontinuity problem posed by presence of xmr in power system n/w. (Chief advantage)

* Single line diagram:

Neutral of

$$I_N = I_r + I_r + I_b = 0$$

$$V_n = I_n Z_n = 0$$

$$S_n = V_n I_n^* = 0$$

Single line diagram is called as zero power bus

finally we have




* Single line diagram: the single line diagram represents of

* circuit breaker rating should be high

power system indicates that original p.p.s. is 3 ϕ and its working under balanced condition. When s.p.s. work under balanced condition, the advantage is by working on single phase basis (by adopting p.u. method), we can claim that we have completed 3 ϕ analysis.

Explanation of point (3):-

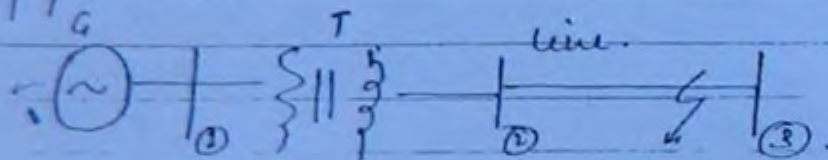

Assumption 4 Short circuit calculation?

- ① Capacitance of circuit neglected (mA $\rightarrow$ kV)
- ② resistance of ~~individual equipment~~ ~~line~~ neglected.

Ans: By neglecting the resistance and capacitance the only parameter which limit s.c. current is the inductance.*
* Fault current is inductive, lagging current, lagging reactive power. Fault demands lagging reactive power.

* Whenever fault occurs, the voltage of other phase decreases due to armature reaction (demagnetization - low magnetic field).


* Fault current is max in subtransient state as minimum reactance.

③ Effect of saliency (salient pole) is neglected; the


effect of non-uniform air of salient pole is neglected.

* During s.c the voltage is effected, frequency constant (Active power not change whereas reactive).

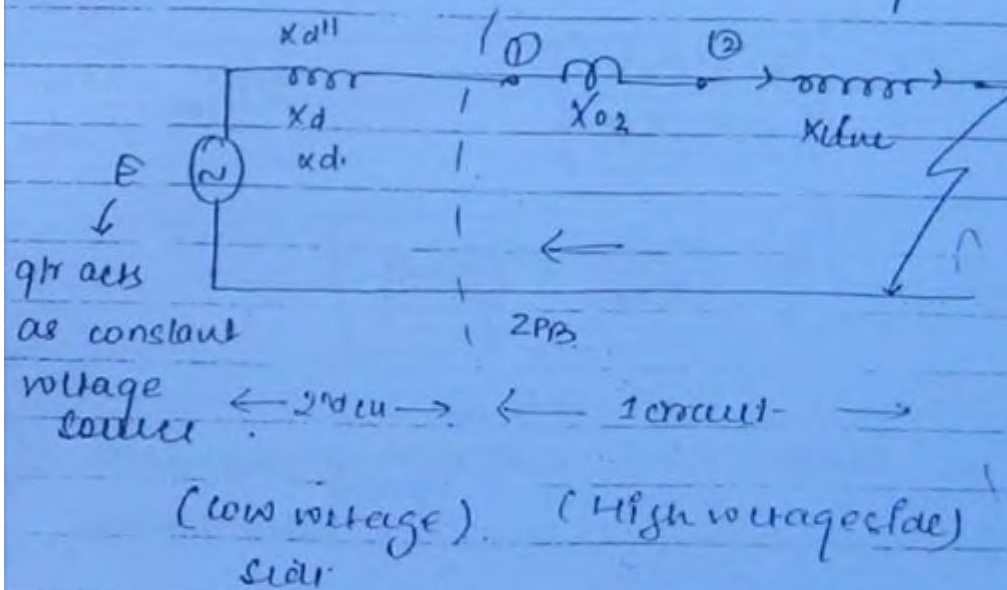* In load analysis the frequency prominently changes



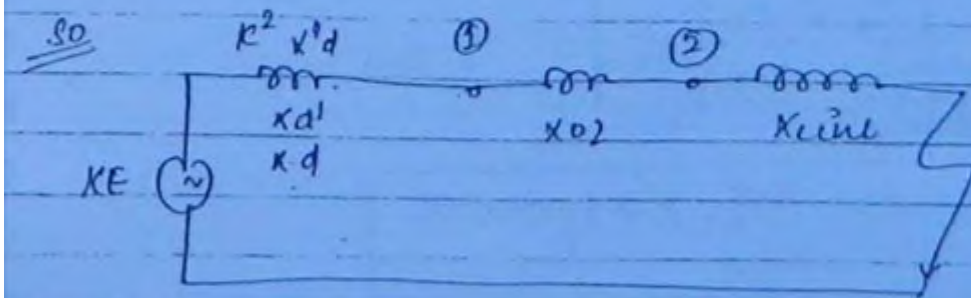→ x_{kne} can be represented as:
 x_{01} primary
 x_{02} secondary



converting q/r to high voltage side ($k \rightarrow$ turn ratio)

this method is practically impossible. so pu method is used.

- $Z_{eq}(LV) \neq Z_{eq}(HV)$
- $Z_{eq}(LV(pu)) = Z_{eq}(HV(pu))$

In pu method - x_{kne} are represented as the series reactance and discontinuity is removed as the value of impedance, current remain same at both ends LV-HV

Selection of base values: (only 4 P, V, I, Z)

(3) We select base value for power and voltage.

→ Base voltage: KV_b

Base voltage = 100KV

→ Base power: KVA_b or MVA_b

Base power = 200MW

→ Base current in (Ampere) =

$$I_b = \frac{\text{KVA}_b}{\text{KV}_b}$$

$$\frac{200 \times 10^3}{100} = 2 \times 10^3 = 2000 \text{ A}$$

$$I_b = \frac{\text{MVA}_b \times 1000}{\text{KV}_b} \text{ A}$$

acts as
conversion
factor

→ Base impedance (in Ω):

$$Z_b = \frac{\text{KV}_b^2}{\text{MVA}_b} \Omega$$

objective

$$Z_b = \frac{\text{KV}_b^2 \times 1000}{\text{KVA}} \Omega$$

conversion
factor

include

→ Base values considered when for calculation of 3 ϕ .

→ 3 ϕ power, line voltage.

$$Z_{b,1\phi} = \frac{KV_{b,1\phi}^2}{MVA_{b,1\phi}}$$

$$Z_{b,3\phi} = \frac{KV_{b,line}^2}{MVA_{b,3\phi}}$$

$$\Rightarrow \frac{(\sqrt{3} \times KV_{b,1\phi})^2}{3 \times MVA_{b,3\phi}} = \frac{KV_{b,1\phi}^2}{MVA_{b,1\phi}}$$

$$Z_{b,3\phi} = Z_{b,1\phi}$$


② whenever we change base values, pu value change not actual values.

$$Z_{pu,old} = \frac{Z_{actual}}{Z_{b,old}} = \frac{Z_{actual}}{KV_{b,old}^2 / MVA_{b,old}}$$

$$Z_{pu,res} = \frac{Z_{actual}}{Z_{b,res}} = \frac{Z_{actual}}{KV_{b,res}^2 / MVA_{b,res}}$$

$$Z_{pu,res} = Z_{pu,old} \times \left(\frac{KV_{b,old}}{KV_{b,res}} \right)^2 \times \left(\frac{MVA_{b,res}}{MVA_{b,old}} \right)$$

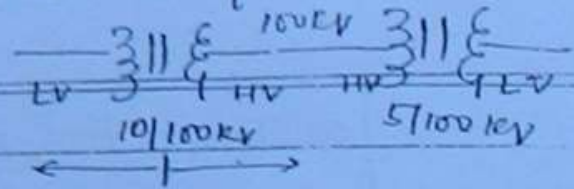→ If two π ms are connected in series no. of base values is 3
 one common, LVT_1 , $HV(T_1, T_2)$, LVT_2



Example:

Q) An equipment is having 10 pu impedance on 100 MVA, 100 kV. Its pu impedance on 10 MVA, 100 kV is —

$$Z_{pu-new} = 10 \times \left(\frac{10}{100} \right)^2 \times \left(\frac{10}{100} \right)$$


$$10 \times \frac{100}{10000} \times \frac{10}{100}$$

$$= 0.01 \text{ pu}$$

Rules of selecting base values when π ms is present in n/w:

1) In circuit containing π ms, we have to select two set of base values one for LV and another for HV side.

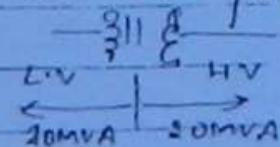
2) Common base power is selected for both sets or for entire n/w.



3) Two different base voltages must be selected for LV and HV in such a way their ratio must be equal to transformation ratio of original π ms.

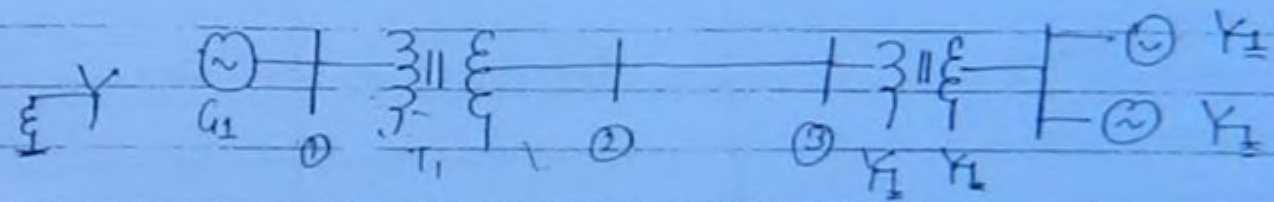Example:-

obtain the pu equivalent reactance diagram for the power s/m shown below



G1: 30 MVA, 10.5 KV, $x'' = 1.6 \text{ pu}$

G2: 15 MVA, 6.6 KV, $x''_d = 1.2 \text{ pu}$

G3: 25 MVA, 6.6 KV, $x''_d = 0.56$

T1 = 15 MVA, 33/11 KV, $x = 15.2 \Omega$
p.p.h. on HV

T2 = 15 MVA, 33/6.6 KV, $x = 16 \Omega$
on HV side

T.L = $20.5 \Omega/\text{ph}$

Initial values. (reactance)	LV side of T1	HV side of T2 and T2	LV side T2	
G1	1.6 pu on 30 MVA, 10.5 KV	—	—	
G2	—	—	1.2 pu on 15 MVA, 6.6 KV	
G3	$15.2 \times \frac{11}{33}$ $= 1.6 \text{ pu}$	15.2 pu	0.56 pu on 25 MVA 6.6 KV	
T1	—	—	—	
T2	—	16 Ω/ph	0.66 Ω/ph	0.66 Ω/ph
L	—	20.5 Ω/ph	—	

Base values =

	LV side of T_1	HV side of T_1/T_2	LV side of T_2
MVA _b	30 MVA	30 MVA	30 MVA
KV _b	11 KV	33 KV	6.2 KV
Z_b	$\frac{11^2}{30} = 4.03 \Omega$	$\frac{33^2}{30} = 36.3 \Omega$	$\frac{6.2^2}{30} = 1.28 \Omega$

formula used = $\frac{KV_b^2}{MVA_b}$

G1: 1.6 pu on 30 MVA, 10.5 KV

$$Z_{pu \text{ new}} = 1.6 \times \left(\frac{30}{30}\right) \times \left(\frac{10.5}{11}\right)^2$$

$$Z_{pu \text{ new}} = 1.46 \text{ pu}$$

$$V_{G1} = \frac{10.5}{11} = 0.96 \text{ pu}$$

Actual
Base

G2: 1.2 pu on 15 MVA, 6.6 KV

$$Z_{pu \text{ new}} = 1.2 \times \left(\frac{30}{15}\right) \times \left(\frac{6.6}{6.2}\right)^2$$

$$Z_{pu(new)} = 0.72 \text{ pu}$$

$$V_{G2} = \frac{6.6}{6.2} = 1.06 \text{ pu} \quad \boxed{V_{G2} = 1.06 \text{ pu}}$$

G3: 0.56 pu on 2.5 MVA 6.6 kV

$$Z_{pu(new)} = 0.56 \times \left(\frac{30}{2.5} \right) \times \left(\frac{6.6}{6.2} \right)^2$$

$$\boxed{Z_{pu(new)} = 0.76 \text{ pu}}$$

$$V_{G3} = \frac{6.6}{6.2} = 1.06 \text{ pu}$$

T1: 1.69 pu w.r.t LV side
base impedance on LV side of T1 = 4.03 Ω

$$X_{Tpu} = \frac{1.69 \Omega}{4.03 \Omega} = 0.41 \text{ pu}$$

15.2 Ω /ph w.r.t HV side

base impedance = 36.33 Ω ✓

$$X_{Tpu} = \frac{15.2}{36.33} = 0.41 \text{ pu}$$

$$\boxed{X_{Tpu} = 0.41 \text{ pu}}$$

T2

0.56 Ω /ph w.r.t ~~1.28~~ LV side of T2

base impedance on LV side of T2 = 1.28 Ω

$$X_{Tpu} = \frac{0.56}{1.28} = 0.434 \text{ pu}$$

16 Ω /pu w.r.t to H.V side of T2

Base value = 36.33 Ω

$$X_{T2} = \frac{16}{36.33} = 0.434 \text{ pu.}$$

Line


$$X_{T2} = 0.434 \text{ pu}$$

$X_L = 20.5$ on HV side T2 and T1

base value = 36.33 Ω


$$X_{line} = \frac{20.5}{36.33} = 0.56 \text{ pu.}$$

$$X_{line} = 0.56 \text{ pu}$$

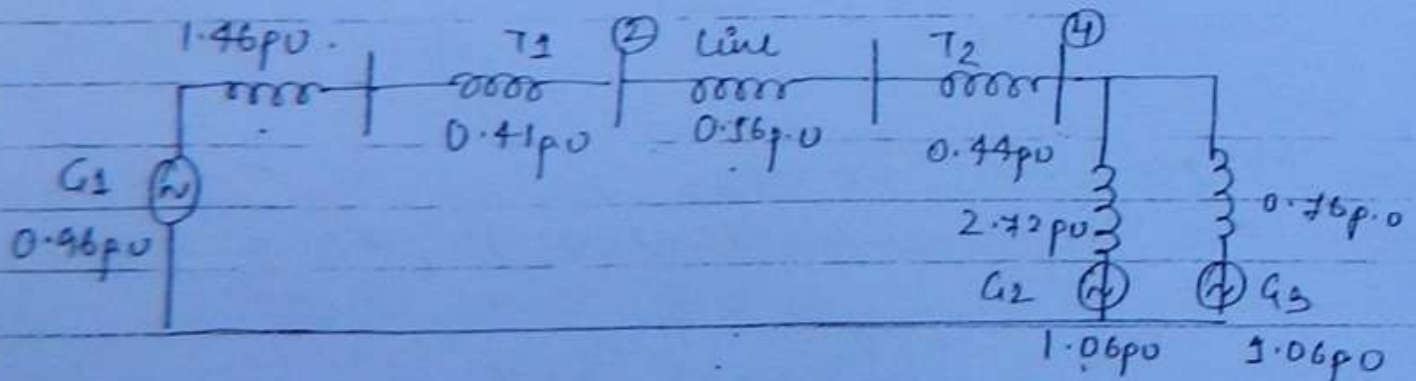

Per unit reactance diagram.

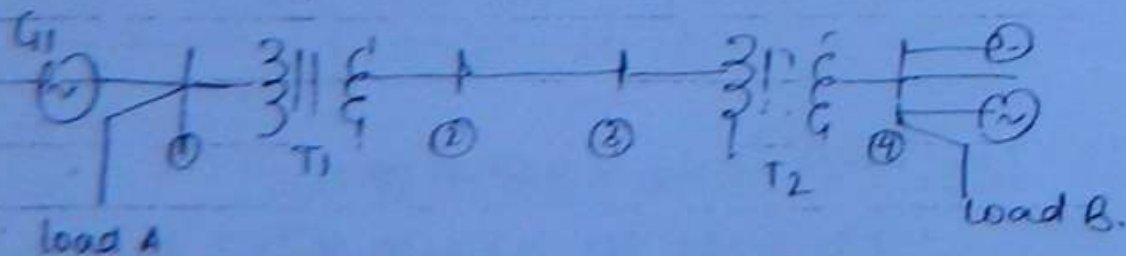b) Two loads (A) and (B) are connected to bus 1 and bus 4 respectively



Load A is 40 MW, 11 kV, 0.9 pf lag.

Load B 40 MW 66 kV, 0.5 pf lag.

represent them in reactance diagram

Solution:

$$\text{Load A} \quad V = \frac{11 \text{ kW}}{11 \text{ kV}} = 1 \text{ p.u.}$$

$$\cos \phi = 0.9 \Rightarrow \sin \phi = 0.43$$

$$P = \frac{40 \text{ MW}}{30 \text{ MVA}} = 1.33 \text{ p.u.}$$

$$P = 1.33 \text{ p.u.} \Rightarrow S = \frac{1.33}{0.9} = 1.48 \text{ p.u.}$$

$$Q = S \sin \phi = 1.48 \times 0.43 = 0.64 \text{ p.u.}$$

$$R_{\text{load A}} = V^2 / P = 1^2 / 1.33 = 0.75 \text{ p.u.}$$

$$X_{\text{load A}} = V^2 / Q = 1.56 \text{ p.u.}$$

Load B

$$V = \frac{40 \times \frac{1}{1.5}}{60} = 1.06 \text{ p.u.}$$

$$\cos \phi = 0.5$$

$$P = \frac{40}{30} = 1.33 \text{ p.u.}$$


$$S = \frac{1.33}{0.5} = 2.66 \text{ p.u.}$$

$$Q = S \sin \phi = 2.26 \text{ p.u.}$$

* load in s.c $\rightarrow$ constant impedance
load in stability $\rightarrow$ constant admittance.

$$P_{load} = \frac{V^2}{R} = \frac{1.06^2}{1.33} = 0.84 \text{ p.u.}$$
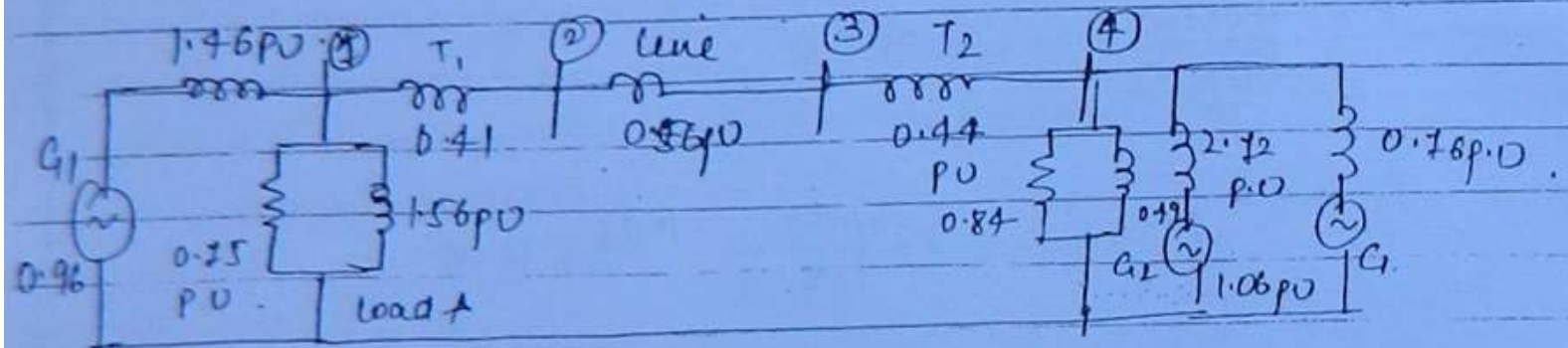
$$X_{load B} = \frac{V^2}{Q} = \frac{1.06 \text{ p.u.}}{2.28} = 0.49 \text{ p.u.}$$



$$P_{load} = \frac{V^2}{R} = \frac{1.06^2}{1.33}$$


$$X_{load B} = \frac{V^2}{Q} = \frac{1.06 \text{ p.u.}}{2.28}$$

$$\frac{1.06^2}{1.33} = 0.84 \text{ p.u.}$$

Date: 5-sept 12

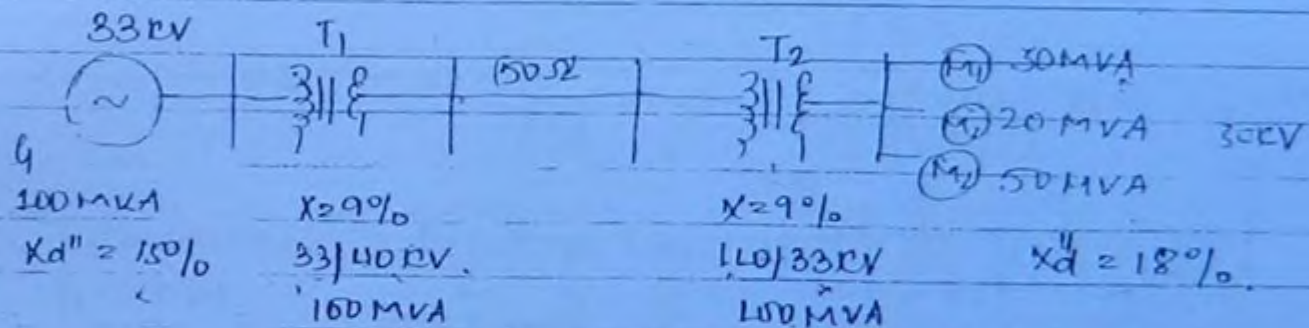Example:-

A 100 MVA, 33kV 3- ϕ g/r has sub-transient react of 15%. The g/r is connected to the m/r having rated T/P 30MVA, 20, 50 MVA. At 33kV with 18% subtransient reactance the 3- ϕ T/Ps are rated at 100 MVA, 33/110kV with leakage reactance of 9%. The line has a reactance of 50 Ω obtain pu equivalent mac. diagram.



- 1) Common base MVA: 100 MVA
 Base voltage of LV side of T1/T2 = 33kV
 " " of HV side of T1 & T2 = 110kV

- 1) $X_{G1} = 0.15 \text{ pu}$ (related value of equipment & selected base value are same)
 2) $X_{T1} = 0.09 \text{ pu}$ (" " ")
 3) $Z_b = \frac{(KV_b)^2}{MVA_b} = \frac{(110)^2}{100} = 121 \Omega$

$$Z_b = 121 \Omega$$

$$X_{line} (\text{pu}) = \frac{50}{121} = 0.41 \text{ pu}$$

$$X_{in} (\text{pu}) = 0.41 \text{ pu}$$


$$4) X_{T2} = 0.09 \text{ p.u.}$$

$$X_{m1} = X_m \left(\frac{\text{MVA}_{\text{old}}}{\text{MVA}_{\text{new}}} \right) \left(\frac{\text{KV}_{\text{base old}}}{\text{KV}_{\text{base new}}} \right)^2$$


$$= 0.18 \left(\frac{150}{50} \right) \left(\frac{30}{33} \right)^2 = 0.496 \text{ p.u.}$$

$$X_{m2} = 0.18 \left(\frac{150}{20} \right) \left(\frac{30}{33} \right)^2 = 0.74 \text{ p.u.}$$
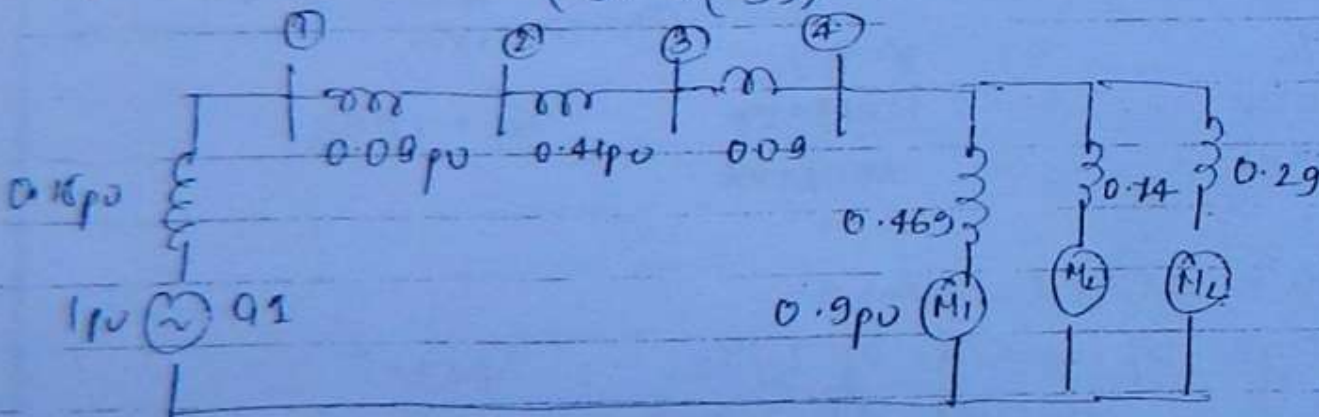
$$X_{m3} = 0.18 \left(\frac{150}{50} \right) \left(\frac{30}{33} \right)^2 = 0.24 \text{ p.u.}$$



Short circuit kVA:-

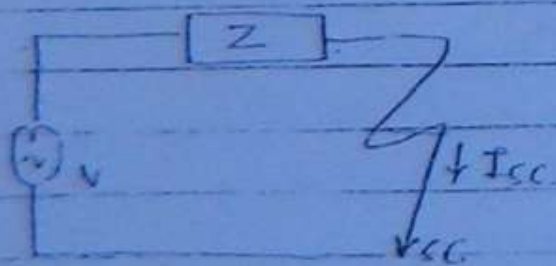

V = Rated voltage

I = Rated current

Z = internal impedance

$$I_{sc} = \frac{V}{Z} \quad \text{--- (1)}$$

$$Z_{\text{base}} = \frac{V}{I}$$

$$Z_{\text{pu}} = \frac{Z}{Z_{\text{base}}} = \frac{Z}{\frac{V}{I}}$$

Note: Ratio of rated current to short ckt current of equipment given p.u impedance

$$Z_{p0} = \frac{I}{V/2} = \frac{I}{I_{sc}}$$

$$\% Z = \frac{I}{I_{sc}} \times 100$$

$$I_{sc} = \frac{I \times 100}{\% Z}$$

$$V I_s = \frac{V I \times 100}{\% Z}$$

$$\text{Short ckt kVA} = \frac{\text{Rated or base kVA} \times 100}{\% Z}$$

Procedure of short circuit calculation:

- 1) Convert the given single line diagram of power s/m. N/w into p.v equivalent impedance diagram.
- 2) Identify the fault terminal. Across the fault terminals reduce the n/w into thevenin equivalent ckt.
- 3) Using the %age thevenin equivalent impedance short ckt kVA can be calculated using the following formulae.

$$\text{Short ckt kVA} = \frac{\text{Common base kVA} \times 100}{Z_{th} \%}$$

Example:-

A, 2 generating station having S.C capacities of 1200 MVA, 800 MVA resp. & operating at 11 kV or linked by an interconnected cable having a reactance of 0.5Ω /phase. Determine short ckt capacities of each station. (How much power flows when SC occurs)

A	
(A)	Cable
1200 MVA	
B	0.5Ω
(B)	phase
800 MVA	

Let the rated base MVA = 1200

$\therefore$ for station A, the %X is

$$1200 = 1200 \times \frac{100}{\%X}$$

$$\Rightarrow \%X_A = 100$$

Station B %age reactance is

$$800 = 1200 \times \frac{100}{\%X_B}$$

$$\%X_B = 150\%$$



$$Z_{base} = \frac{KV_p^2}{MVA_b} = \frac{(11)^2}{1200} = 0.1008 \Omega$$

$$X_{cable} = \frac{0.5}{0.1008} = 4.96 \text{ p.u.}$$

$$\%X_{cable} = 496\%$$

Now we can calculate short ckt capacities of each station when fault occurs on the terminal of station (A)

and sectⁿ (B-ii').

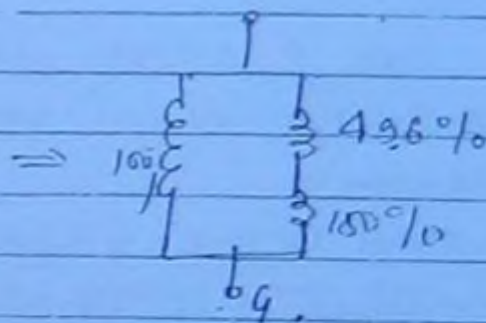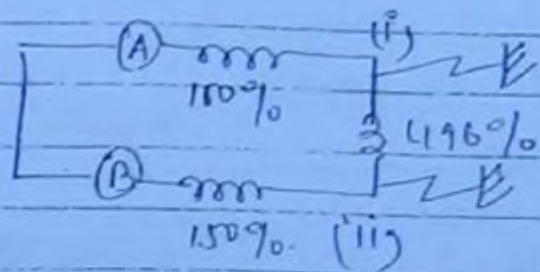


$$\%Z_{th} = 86.59\%$$

$$\text{Short circuit MVA of statⁿ A} = \frac{1200 \text{ MVA} \times 100}{86.59} = 1385 \text{ MVA}$$

When fault occurs on terminal of statⁿ B
Short ckt MVA of stat B, $X_{th} = 119.84\%$
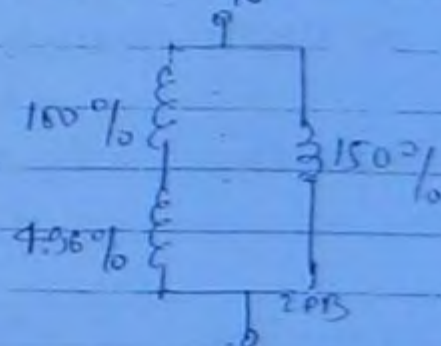
$$\text{Short circuit MVA} = \frac{1200 \times 100}{119.84} = 1001 \text{ MVA}$$




→ If we want to keep the ckt breaker at P & Q shown, then they must have breaking capacities of 1385 & 1001 MVA resp.

Quesⁿ
If we have ckt breaker of lesser capacity then how can it be effectively used?

Answer
1) To limit the short ckt current, resistance is not used due to continuous power loss.

2) Series capacitors are not used due to breakdown of dielectric during short ckt (At SC it has high voltage $I_{sc} X_c$ across & act as punctured dielectric)

5% X_{sc}

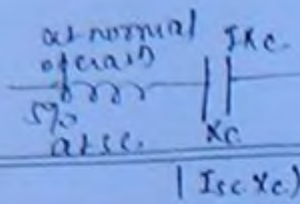

5% X_{sc}
5% X_{sc}
1

3) Series reactors are widely used but they are designed with no core material to avoid saturation problem.

(As the current starts to rise, ϕ also rises but after certain time, even increment of SC current, ϕ becomes saturated thus the value of L keeps on falling with rising I_{sc} & thus behaves as a short ckt path - this is becoz air core is used as ϕ in airgap is never saturated).

→ Purpose of using series reactor - to limit SC current

Purpose of using shunt reactors - to avoid ferranti effect

Series capacitors - to $\uparrow$ steady state power limit
(As when we have inductance then power delivered is less)

shunt capacitor - $\rightarrow$ to improve P.F

* Feeder reactors are very commonly used compared to generator & bus bar reactors.

Example:-

100 kVA equipment is having 5% reactance, To limit the short ckt kVA to 500 kVA the value of % Reactance used for series reactors is -


$$500 \geq 100 \times \frac{100}{5\% + X_{sc}\%}$$

$$5\% + X_{se} = 20$$

$$\%X_{se} = 15\%$$

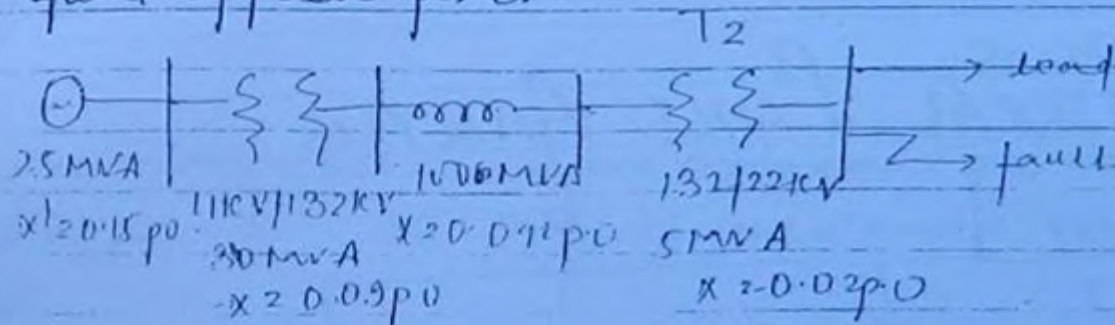Example:-

A symmetrical 3 ϕ short ckt occur on the 22kV busbar as shown in the fig. Calculate fault current and fault apparent power.



Let the common base MVA = 100 MVA


$$X_{G1} = 0.15 \times \left(\frac{100}{25}\right) \left(\frac{11}{11}\right)^2 = 0.6 \text{ pu}$$

$$X_{T1} = (0.09) \times \left(\frac{100}{30}\right) = 0.3 \text{ pu}$$

$$X_{uni} = 0.092 \text{ pu}$$

$$X_{T2} = 0.02 \times \frac{100}{5} = 0.4 \text{ pu}$$

Base current on LV side of T2 is

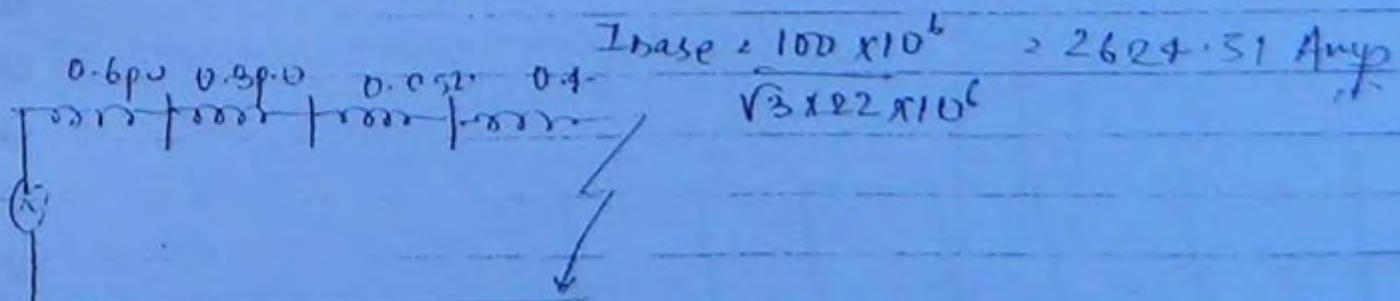

2 p.u.

$$I_f = 1 \angle 0^\circ$$

$$= V_{fu}$$


$$= j(0.6 + 0.3 + 0.092 + 0.4) \text{ total pu X}$$

$$I_f(\text{actual}) = I_f(\text{p.u.}) \times I_f(\text{base})$$

$$I_f(\text{actual}) = 0.718 \times 26424.3 = 1884.24 \text{ Amp}$$

$$\begin{aligned} \text{Fault MVA} &= 0.718 \text{ p.u.} \\ &= 0.718 \times 160 \text{ MVA} \\ &= 11.8 \text{ MVA} \end{aligned}$$

UNSYMMETRICAL FAULT ANALYSIS

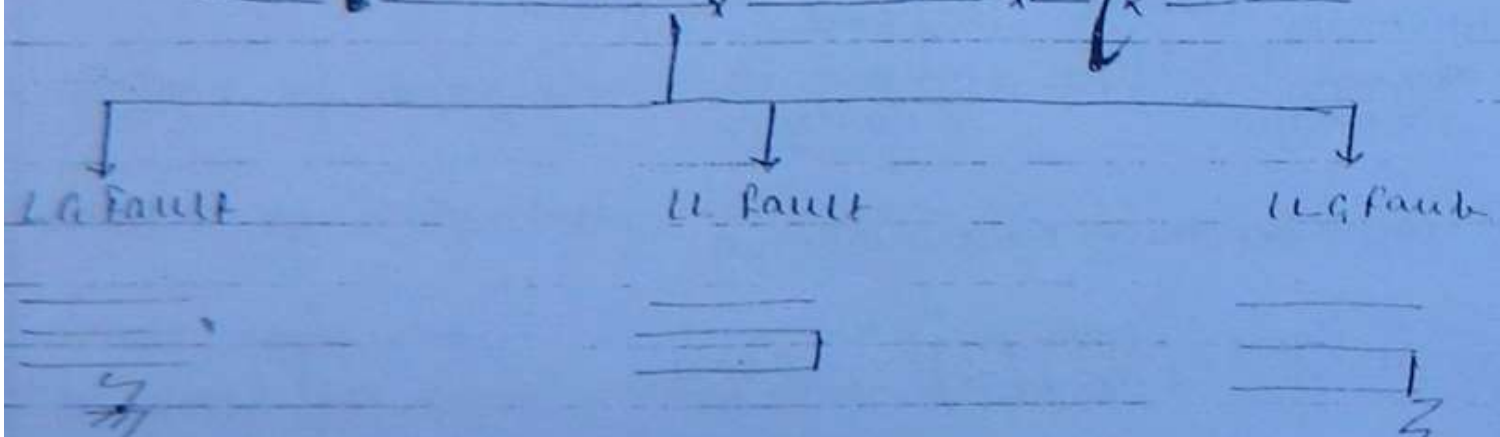

2. In unsymmetrical fault all the 3 ϕ are at different conditions


$\therefore$ By working on 1- ϕ base, we can't claim that we have complete 3 ϕ analysis

$$\begin{bmatrix} I_x \\ I_y \\ I_z \end{bmatrix} = \begin{bmatrix} \\ \\ \end{bmatrix} + \begin{bmatrix} \\ \\ \end{bmatrix} + \begin{bmatrix} \\ \\ \end{bmatrix}$$


$$\begin{matrix} I_R \\ I_Y \\ I_B \end{matrix} = \begin{bmatrix} I_{R1} \\ I_{Y1} \\ I_{B1} \end{bmatrix} + \begin{bmatrix} I_{R2} \\ I_{Y2} \\ I_{B2} \end{bmatrix} + \begin{bmatrix} I_{R0} \\ I_{Y0} \\ I_{B0} \end{bmatrix}$$

$\downarrow$ $\downarrow$ $\downarrow$
 +ve sequence -ve seq. zero sequence


Sequence Components:

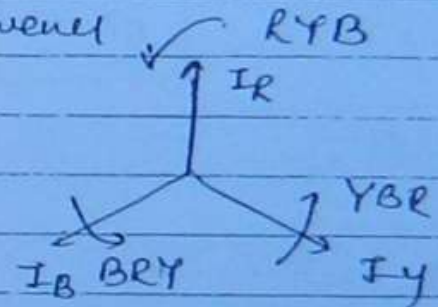

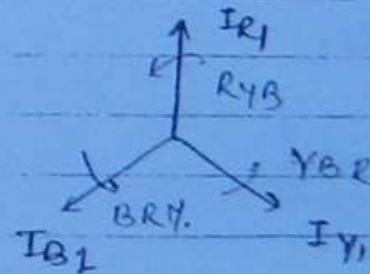+ve sequence — these component are having exactly same as the original unbalanced vectors.




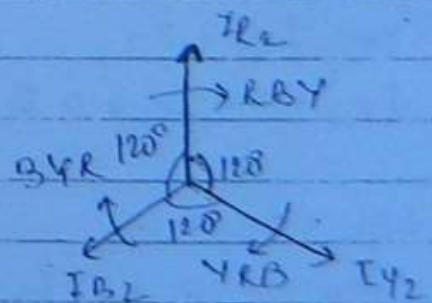-ve sequence: these component have a sequence exactly opposite to that of original unbalance vector.



Zero Sequence —

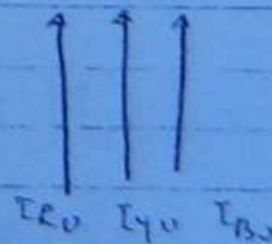these components have no sequence. (equal magnitude)



→ If we want to convert B, Y component
component then we have 'a' operator


$$\boxed{\begin{aligned} a &= 1 \angle 120^\circ \\ a^2 &= 1 \angle 240^\circ \end{aligned}}$$

$$I_{R1} = I_{R1} \angle 0^\circ$$

$$I_{Y1} = I_{R1} \angle 240^\circ \\ a^2 I_{R1}$$

$$I_{B1} = I_{R1} \angle 120^\circ \\ a I_{R1}$$

$$\boxed{I_{R0} = I_{Y0} = I_{B0}}$$

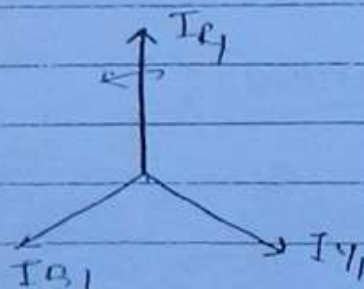

$$\boxed{\begin{aligned} I_{R2} &= I_{R2} \angle 0^\circ \\ I_{Y2} &= I_{R2} \angle 120^\circ \\ &\quad a I_{R2} \\ I_{B2} &= I_{R2} \angle 240^\circ \\ &\quad a^2 I_{R2} \end{aligned}}$$

$$I_R = I_{R0} + I_{R1} + I_{R2}$$

$$I_Y = I_{Y0} + I_{Y1} + I_{Y2} \\ I_{R0} + a^2 I_{R1} + a I_{R2}$$

$$I_B = I_{B0} + I_{B1} + I_{B2} \\ I_{R0} + a I_{R1} + a^2 I_{R2}$$

$$\begin{bmatrix} I_{R1} \\ I_Y \\ I_B \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix}$$

$$\boxed{\begin{aligned} [I]_{RYB} &= [A] [I]_{012} \\ [V]_{RYB} &= [A] [V]_{012} \end{aligned}}$$

Relation of operator 'a' $\rightarrow$

(a) $\rightarrow$ also known as transformation

$$\rightarrow a = 1 \angle 120^\circ = 1 (\cos 120 + j \sin 120) \\ = -0.5 + j0.866$$

$$\rightarrow a^2 = 1 \angle 240^\circ = 1 (\cos 240 + j \sin 240) \\ = -0.5 - j0.866$$

$$\rightarrow a^3 = 1 \angle 360^\circ = 1$$

$$\rightarrow a^4 = a^3 \cdot a = a$$

$$\rightarrow a^5 = a^3 a^2 = a^2$$

$$\rightarrow 1 + a + a^2 = 0$$

$$\rightarrow 1 - a = 1 - (-0.5 - j0.866) = \frac{3}{2} + j\frac{\sqrt{3}}{2} = \sqrt{3} \left(\frac{\sqrt{3}}{2} + j\frac{1}{2} \right) \\ \sqrt{3} \angle 30^\circ$$

$$\rightarrow 1 - a = \sqrt{3} \angle -30^\circ$$


$$\rightarrow [I]_{RYB} = [A] [I]_{012}$$

$$\rightarrow [I]_{012} = [A^{-1}] [I_{RYB}]$$

$$\text{where } [A]^{-1} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$$

* The original N/w are mutually fixed.

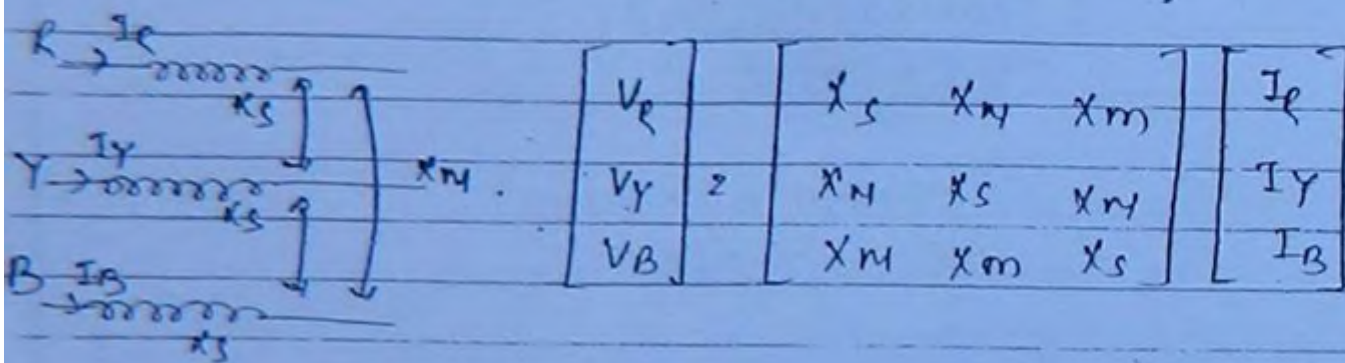* The three sequence N/w +ve, -ve, zero sequence N/w's are mutually disjoint



$$[V]_{RYB} = [X]_{RYB} [I]_{RYB}$$

$$[A][V]_{012} = [X]_{RYB}[A][I]_{012}$$

$$[V]_{012} = [A]^T [X]_{RYB} [A] [I]_{012}$$

$$[X]_{012} = \begin{bmatrix} X_s + 2X_m & 0 & 0 \\ 0 & X_s - X_m & 0 \\ 0 & 0 & X_s - X_m \end{bmatrix}$$

The off diagonal elements are zero in the above matrix, we can conclude that the +ve, -ve, zero sequence N/w's are mutually disjoint.

Example:-

A transmission line has self reactance of $50.6 \Omega/\text{phase}$ & mutual reactance of 90.1Ω b/w any 2 phase. Find +ve, -ve & zero sequence reactance of the transmission line.

$$X_0 = X_s + 2X_m$$

$$= j0.6 + 2(j0.1)$$

$$= j0.8 \Omega$$

$$X_1 = X_s - X_m$$

$$= j0.6 - j0.1$$

$$= j0.5 \Omega$$

$$X_2 = X_s - X_m$$

$$= j0.6 - j0.1$$


$$= j0.5 \Omega$$

→ for static devices phase sequence is not imp.

Example:

On a 3 ϕ balanced s/m, the current in each phase is 10 A rms. The phase sequence is RYB. Find the sequence current. Find the sequence components.

Soln:

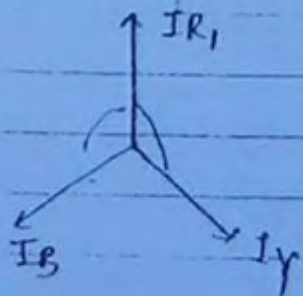

$$I_R = 10 \angle 0^\circ$$

$$I_Y = 10 \angle 240^\circ = a^2 10$$

$$I_B = 10 \angle 120^\circ = a 10$$

$$[I]_{RYB} = [A][I]_{012} = [I]_{012} = [A^{-1}][I]_{RYB}$$

$$\begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 10 \\ a^2 10 \\ a 10 \end{bmatrix}$$

$$I_{R0} = \frac{1}{3}(10 + a^2 10 + a 10) = 0$$

$$I_{R1} = \frac{1}{3}(10 + a^3 10 + a^3 10) = 10$$

$$I_{R2} = \frac{1}{3}(10 + a^4 10 + a^2 10) = 0$$

→ By this we can say that in a balanced s/m the only current in the N/C is the sequence current.

Example:-

The fuse in Y & B are removed. Find seq components

$$I_{A0} = I_R = 10 \angle 0^\circ$$

$$I_Y = I_B = 0$$

$$\begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$

$$I_{R1} = I_{R2} = I_{R0} = 10/3 \text{ A}$$

SEQUENCE IMPEDANCES:

Generator:-

$$X_{G1} \approx X_{G2}$$

the seq reactance (the seq reactance)

[strictly speaking X_{G2} is slightly less than X_{G1}]

(calculated)

$$X_{a1} = \frac{X_d'' + X_{a1}''}{2}, \frac{X_d' + X_{a1}'}{2}, \frac{X_d + X_{a1}}{2}$$

$$X_{a1} = X_d'', X_d', X_d$$

(cylindrical)
or


$$X_{G0} \ll X_{a1}$$

For static devices like (T/F & Transmission line)

$$X_1 = X_2$$


$$X_0 \gg X_1$$


Sequence N/W:-

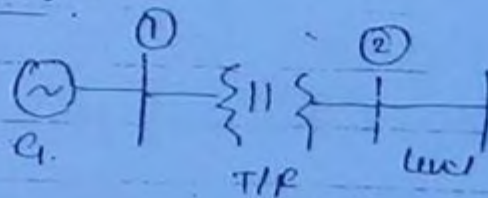

Generator Representation:-

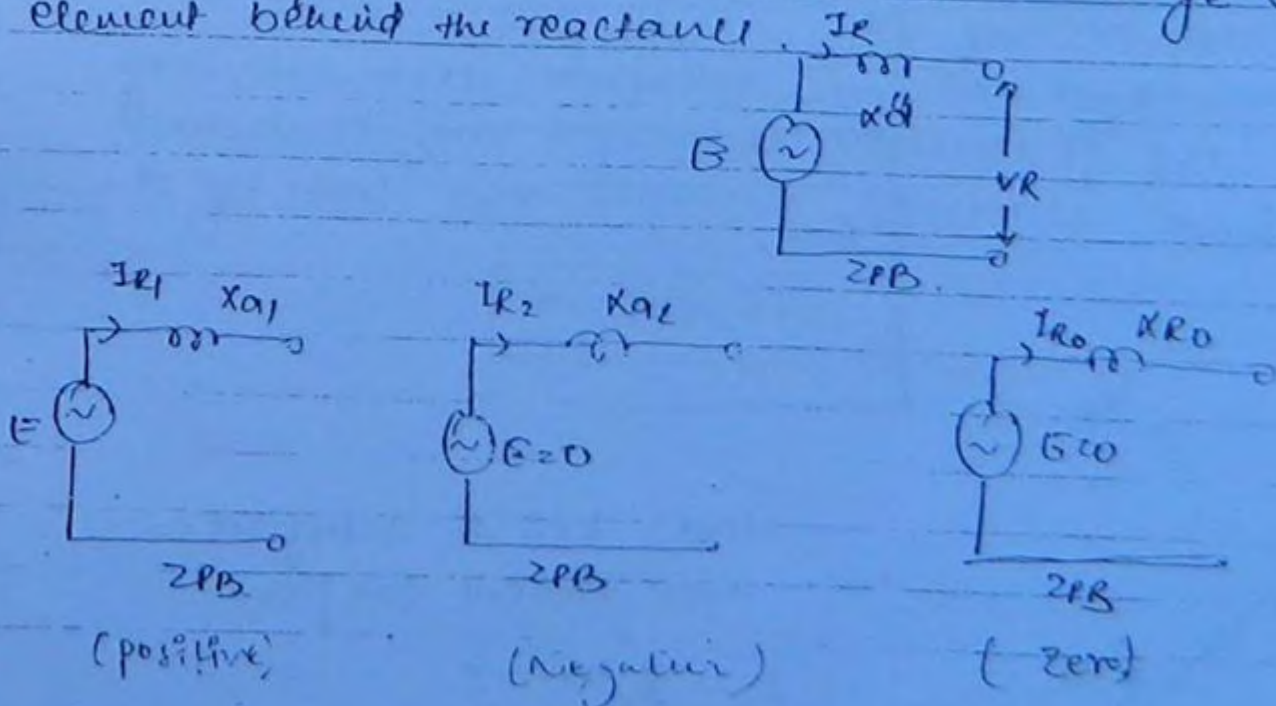In original N/W with symmetrical fault analysis Gen. is used as const voltage element behind the reactance.




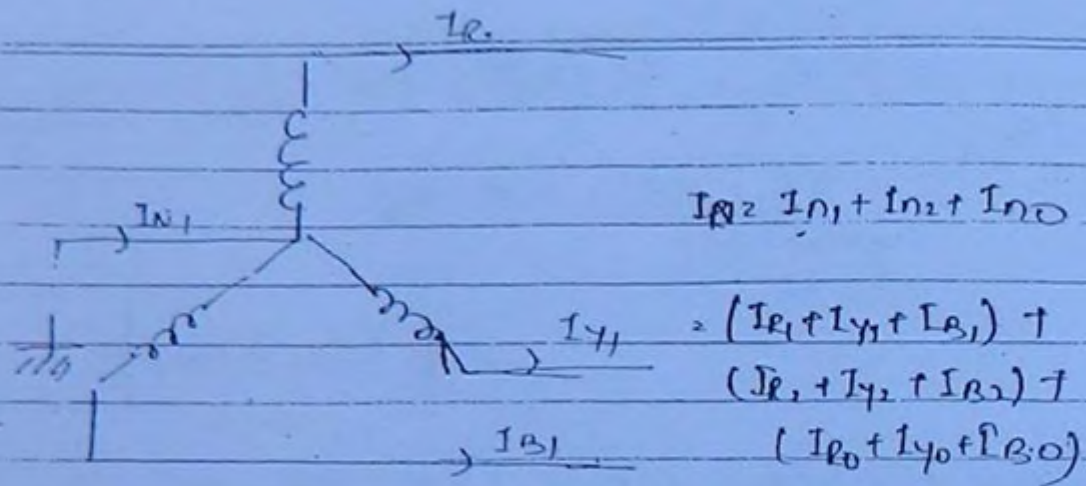

I_{N0} is sum of outgoing current $= 0$ $I_N = 3I_{R0}$



∴ positive seq current will flow whether neutral is grounded or not

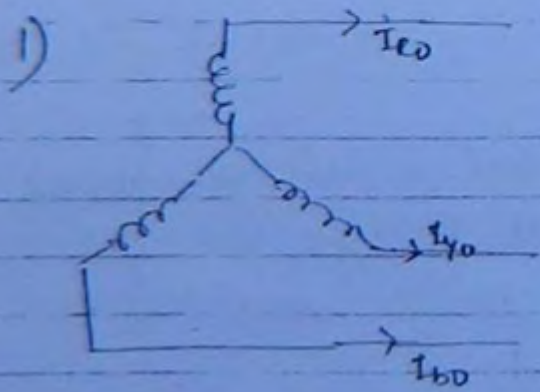→ If neutral grounded with inductor then:-





Sum of incoming current $= 0$
Sum of outgoing current $= 3I_{N0}$
KCL not satisfied.
So such current does not exist

∴ open circuit

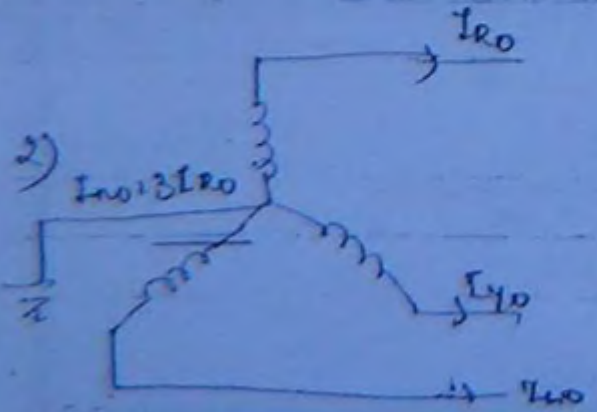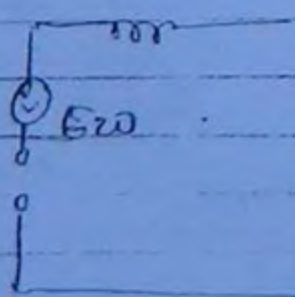

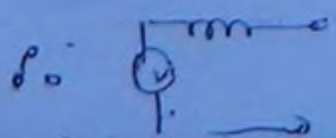Here KCL is satisfied so now current can flow



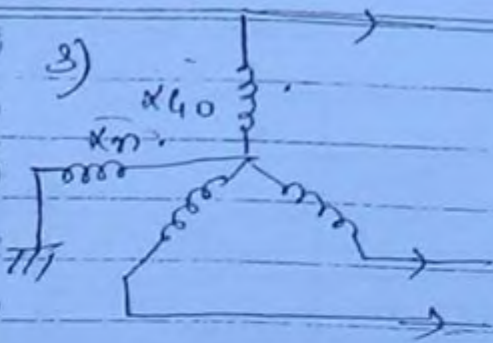

Now neutral is not ZPB
 it has drop of $3 I_{n0} X_n$
 $\therefore$ unbalanced condn.

$$V_{R1} = 3 I_{R0} X_{n0} + I_{n0} X_{G0}$$


$$X_0 = (X_{G0} + 3X_n)$$

Notes



- 1) Only positive seq n/w contain voltage source
- 2) Negative & zero seq do not contain voltage source
- 3) Condition of neutral has got no effect in the representn of gen. both in +ve & -ve seq n/w
- 4) However, conditn of neutral has got effect in the representn of gen, in the zero seq n/w
 If neutral is unloaded show open ckt. If neutral is solidly grounded show a.s.c.
 If the neutral is grounded with reactance X_n , $3X_n$ must be added to zero sequence reactance of g/p. X_{G0} to get total zero sequence reactance.

$$X_0 = 3X_{G0} + 3X_n$$

Transformer Representatⁿ

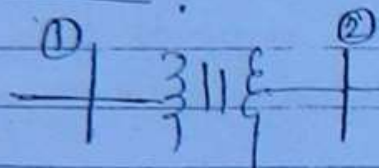


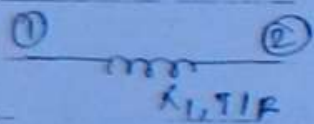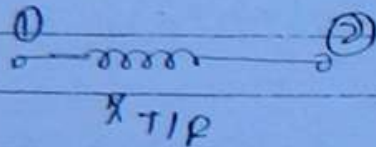→ So original n/w T/F is shown as series reactance.




ZPB

positive
Seq.

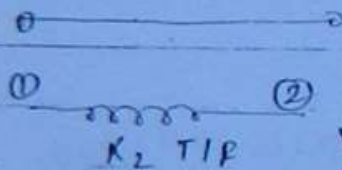

ZPB



Negative
Seq.

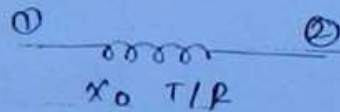



ZPB

Zero
Seq.

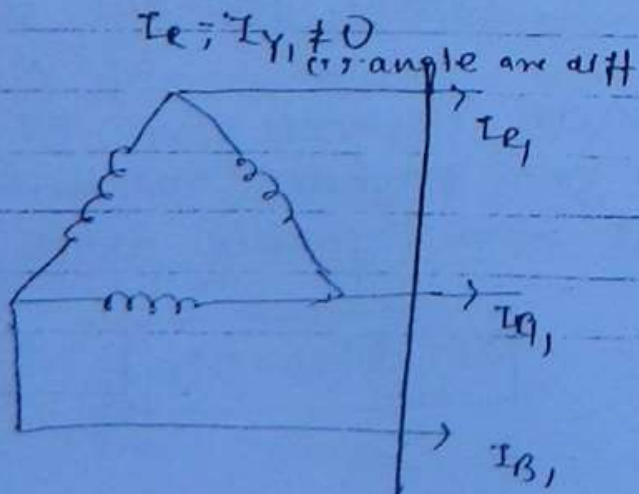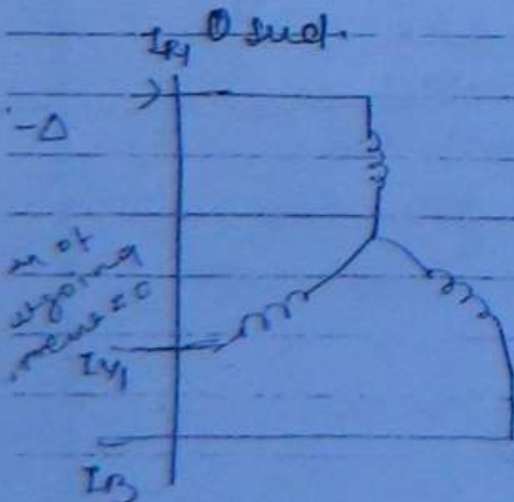→ lower X_{new} primary & secondary. can be connected in both star & delta.



∴ type of
windg has
no relation
of T/F

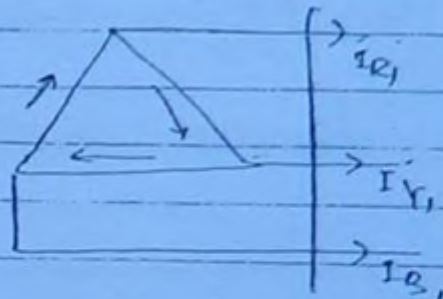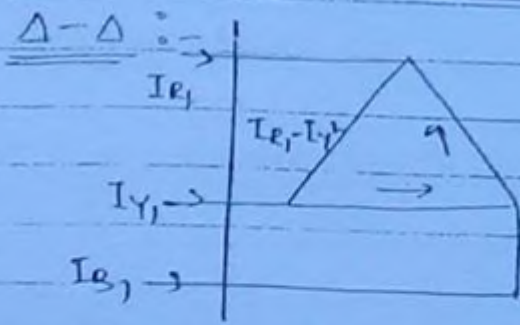

Conclusion:



x_{mes} has no effect
of type of n/w
whether γ or Δ
no effect due to
neutral ground

$I_{R1} - I_{Y1} \neq 0$

$\therefore$ Mag is same but phase angle $= 120^\circ$

Zero Sequence:


1) $\gamma-\Delta$

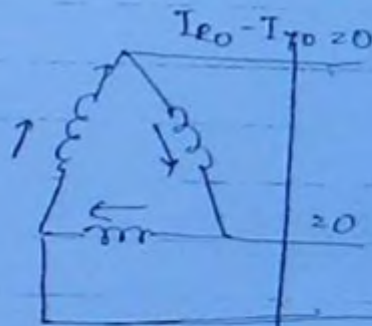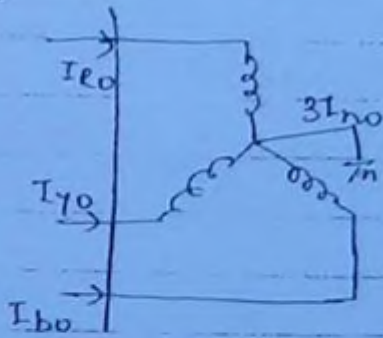

KCL is not
satisfied

$\therefore$ in coming $= 3I_R$
Outgoing $= 0$



$\therefore$ O.C

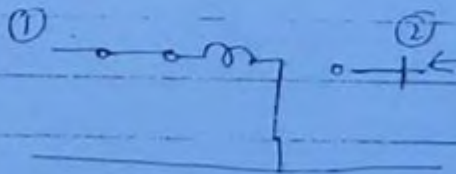

$\rightarrow$ If star point is grounded
then KCL is satisfied

S.C


2) $\gamma-\gamma$

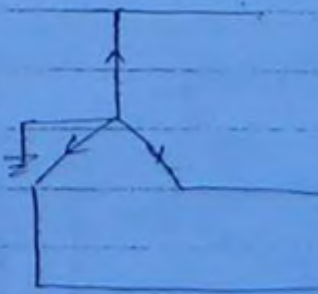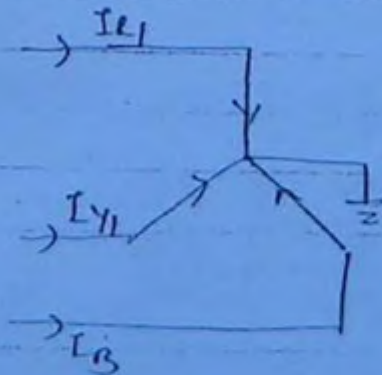


→ If secondary is ungrounded.



→ If it is grounded.

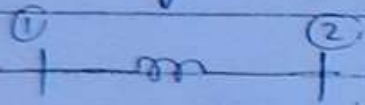

SWITCH DIAGRAM:

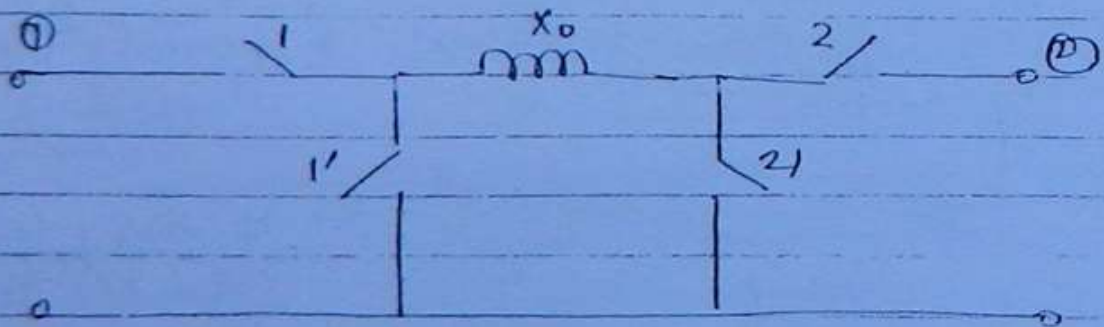

*

1, 1' → Primary


2, 2' → Secondary

1, 2 → Series switches



1', 2' → Shunt switches

Representatn of Transmission line -

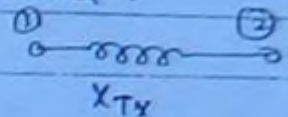on symmetrical fault represented as series reactance.





① the sequence

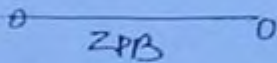
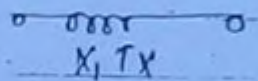


→ No conditⁿ for T.L

② -ve sequence

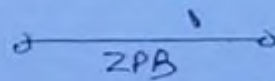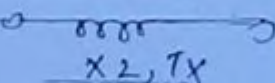


③ Zero sequence

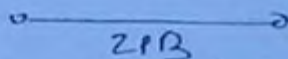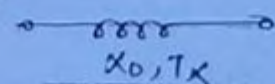

* Without verifying any conditⁿ a T.L can be simply represented as series reactance element in all 3-sequence n/w

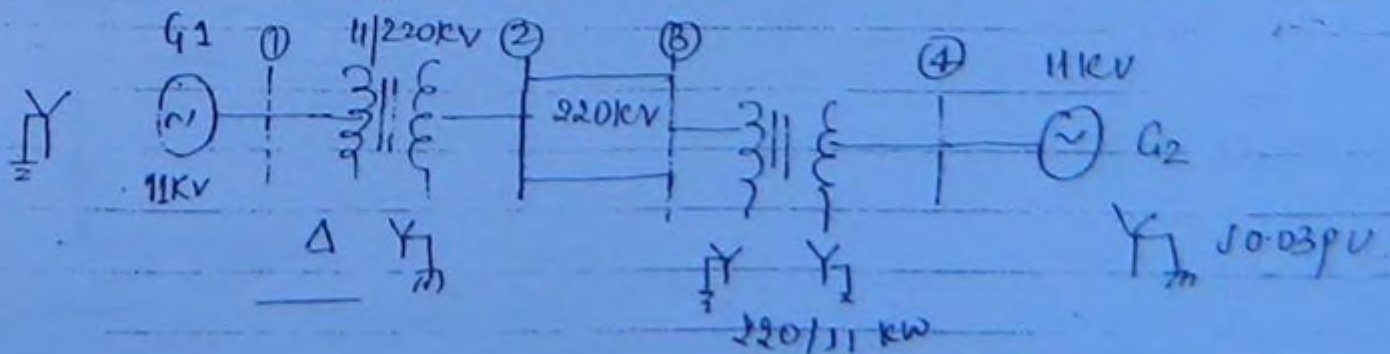Problem:-

Obtain the 3-sequence n/w for the n/w shown in figure



$$\rightarrow G_1 \rightarrow X_1 = X_2 = j0.25 ; X_0 = j0.05 \text{ pu.}$$

$$G_2 \rightarrow X_1 = X_2 = j0.2 ; X_0 = j0.05 \text{ pu.}$$


$$T_1 \rightarrow X_1 = X_2 = X_0 = j0.06 \text{ pu.}$$

$$T_2 \rightarrow X_1 = X_2 = X_0 = j0.07 \text{ pu}$$

$$L_1, L_2 \rightarrow X_1 = X_2 = X_0 = j0.3.$$


Common base MVA = 100.

Solution:

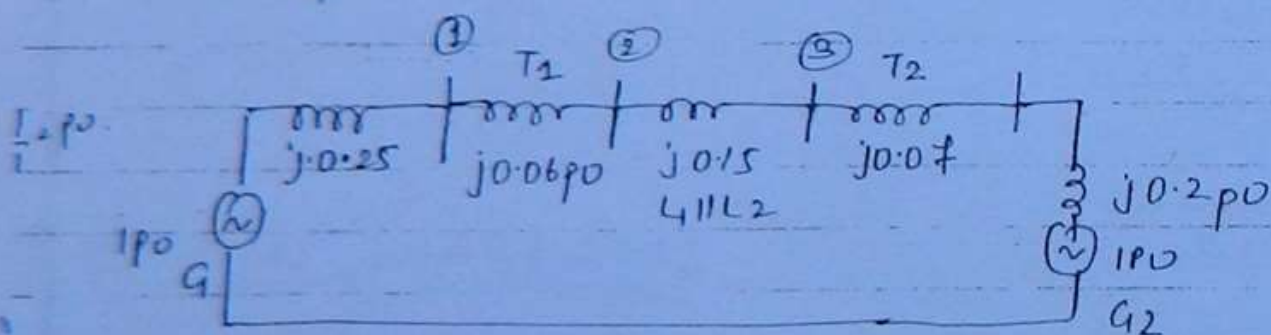


↳ Positive sequence N/W.

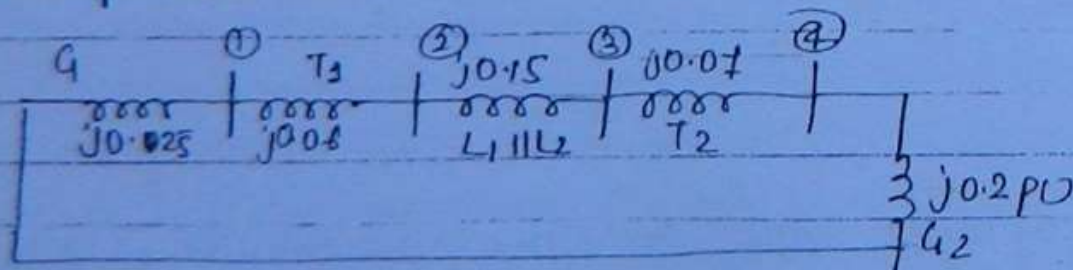⇒ Negative sequence N/W: (without voltage source rest same)



⇒ Zero Sequence N/W:

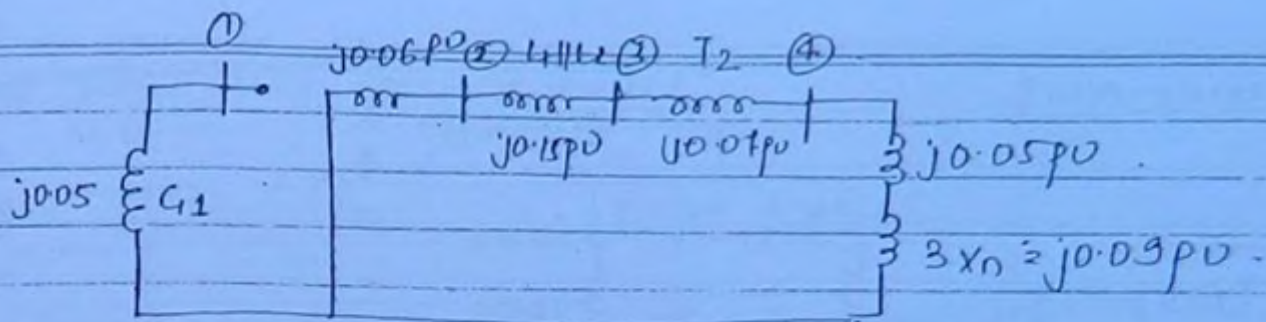

2



Part B

Let the fault is occurred on bus (3), reduce the 3-sequence n/w into thevenin equivalent n/w.


As the voltage on both side is same so circulating current is zero, so drop is also zero, so the same voltage 1 pu appears across bus (3) (parallel).

Thevenin's equivalent
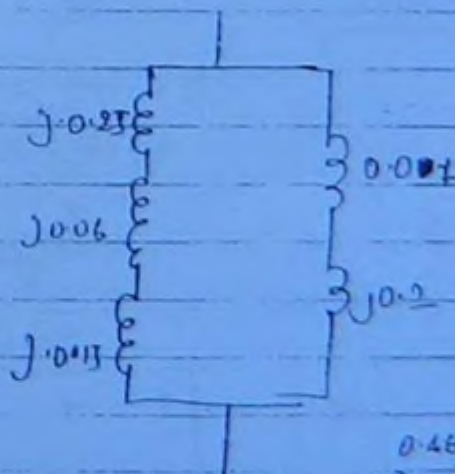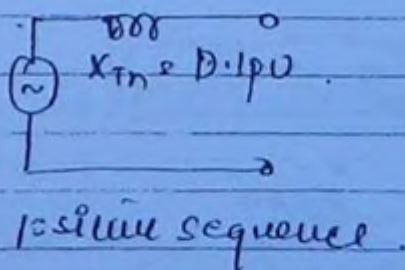
$$V_m = 1 \text{ pu} ; X_{Tn} = j0.17 \text{ pu}$$





-ve sequence n/w same & no voltage

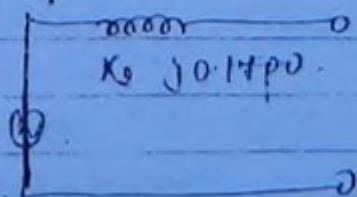




Zero sequence n/w flow 4m (Q2)

→ Zero sequence n/w?

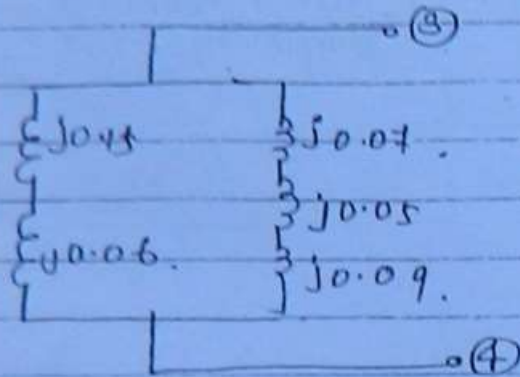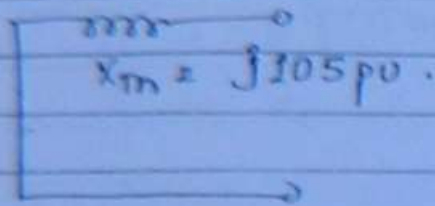

4 Voltage Sequence:-

0.21C

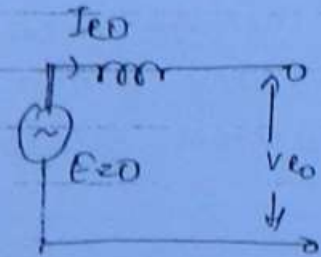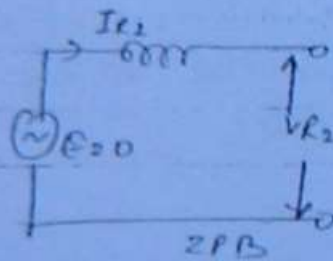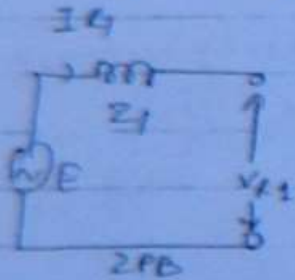

$$V_{L1} = E - I_{L1} Z_1$$

$$V_{L2} = E - I_{L2} Z_2$$

$$V_{L0} = E - I_{L0} Z_0$$

$$V_{L2} = -I_{L2} Z_2$$

$$V_{L0} = -I_{L0} Z_0$$

* Positive S.

* Negative

* Zero

$$\begin{bmatrix} V_L \\ V_Y \\ V_B \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_{L0} \\ V_{L1} \\ V_{L2} \end{bmatrix}$$

→ Power c/s not connected to c/m is distributed c/m

Single line Ground Fault:

R $\frac{1}{3} I_f = I_f$ $\downarrow$ Z_f

Before fault:-

$$\begin{matrix} Y \\ B \end{matrix} \quad \boxed{I_R = I_B = I_Y = 0}$$

During fault:

$$\boxed{I_R = I_f}$$

$$\boxed{I_Y = I_B = 0}$$

$$\begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_f \\ 0 \\ 0 \end{bmatrix}$$

$$\boxed{I_{R0} = \frac{1}{3} I_f, I_{R1} = I_{R2}}$$

$$\therefore \boxed{I_{R1} = I_{R2} = I_{R0} = I_f/3 = I_{R0}/3} \rightarrow \text{①}$$

→ All sequence current are equal & LG fault.

$$V_R = V_f = I_f Z_f = I_R Z_f = 3 I_{R1} Z_f$$

$$V_{R1} + V_{R2} + V_{R0} = 3 I_{R1} Z_f$$

substituting value of V

$$\rightarrow (E - I_{R1} Z_1) - I_{R2} Z_2 - I_{R0} Z_0 = 3 I_{R1} Z_f$$

Current are equal.

$$\rightarrow E - I_{R1} Z_1 - I_{R1} Z_2 - I_{R1} Z_0 = 3 I_{R1} Z_f$$


$$I_e = \frac{E}{Z_1 + Z_2 + Z_0 + 3Z_f} = I_{e2} = I_{e0} \quad \text{--- (2)}$$

$$I_{fLG} = I_e = 3I_{R1}$$

$$\therefore I_{fLG} = \frac{3E}{Z_1 + Z_2 + Z_0 + 3Z_f}$$

Objective:-

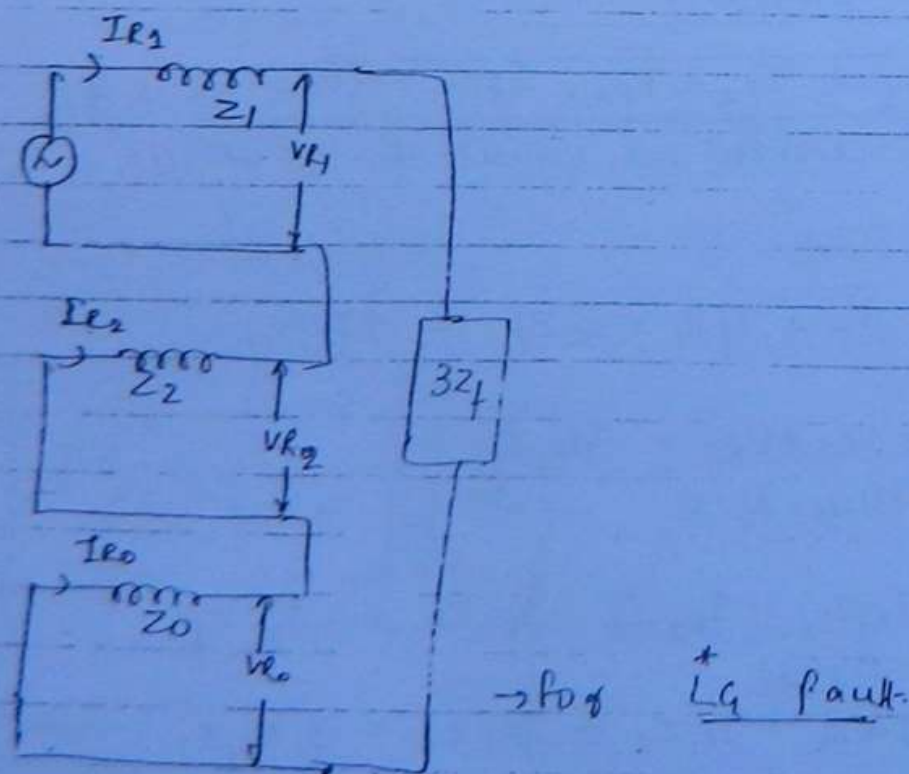→ Particular fault for all sequence current equal → LG fault.



→ Zero sequence is possible with grounding only

§ Comments


for LG fault :-

→ All sequence n/w are connected in series

→ All sequence currents are equal

$$\rightarrow I_{fLG} = 3I_{R1} = 3I_{R2} = 3I_{R0} = \frac{3E}{Z_1 + Z_2 + Z_0 + 3Z_f}$$

Line to line fault :-

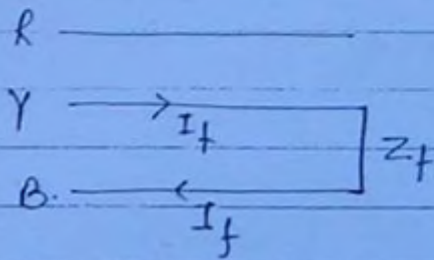


Before fault


$$I_R = I_Y = I_B = 0$$

During fault :-

$$I_f = I_Y = -I_B$$

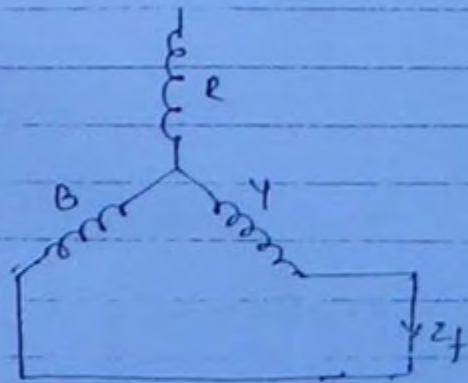

(Current circulates as shown)

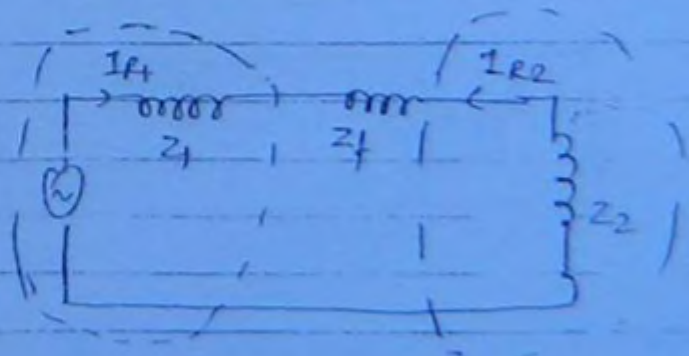

→ Fault in which fault current is $\sqrt{3} I_{R1}$ or $\sqrt{3} I_{R2}$ → LL Fault.

$$I_{R1} = -I_{R2} \quad \& \quad I_{R0} = 0$$

Two sequences are connected in series opposition

Magnitude :-

$$I_{R1} = -I_{R2} = \frac{E}{Z_1 + Z_2 + Z_f}$$

Calculating I_f

$$\begin{aligned} I_{fLL} &= I_f = I_{R0} + a^2 I_{R1} + a I_{R2} \\ &= (a^2 - a) I_{R1} \end{aligned}$$

$$\begin{aligned} \therefore (a^2 - a) &= (-0.5 - j0.866 + 0.5 - j0.866) \\ &= -j1.732 = -j\sqrt{3} \end{aligned}$$

$$I_{fLL} = \frac{-j\sqrt{3}E}{Z_1 + Z_2 + Z_f}$$

$$|I_{fLL}|^2 = \frac{3E^2}{Z_1^2 + Z_2^2 + Z_f^2}$$

Comments:

for line to line fault:-


→ Positive and negative sequence n/w are connected in series opposition.

→ $I_{R1} = -I_{R2}$ and $I_R = 0$

→ Magnitude of fault current is

$$I_{fLL} = \sqrt{3} I_d R_1 = \sqrt{3} I_d R_2 = \frac{\sqrt{3} E}{Z_1 + Z_2 + Z_f}$$

Double line ground fault:

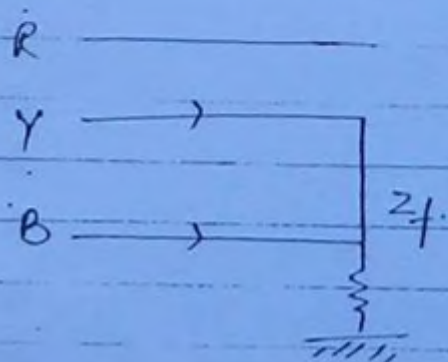

Before fault


$$I_R = I_B = I_Y = 0$$

during fault

$$I_f = I_Y + I_B$$

$$V_f = V_Y = V_B = I_f Z_f$$

Derivation:-

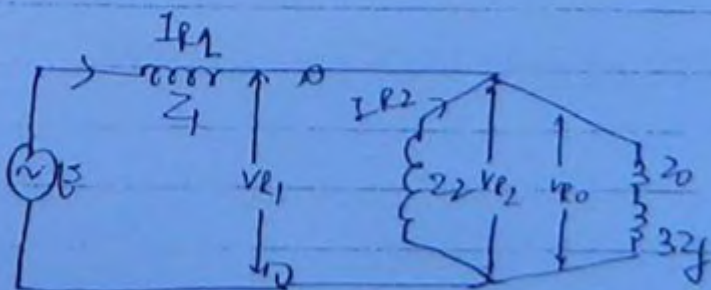

All sequences are in parallel. so

$$\rightarrow \boxed{V_{R1} = V_{R2} = V_{R0}}$$

$$\boxed{I_{R1} = -(I_{R2} + I_{R0})} \rightarrow \text{objective}$$

Magnitude:

$$\boxed{I_{R1} = \frac{E}{Z_1 + (Z_2 \parallel (Z_0 + 3Z_f))}}$$

$$\& \boxed{I_{R2} = -I_{R1} \times \frac{Z_0 + 3Z_f}{Z_2 + Z_0 + 3Z_f}}$$

$$\boxed{I_{R0} = -I_{R1} \times \frac{Z_2}{Z_2 + Z_0 + 3Z_f}}$$

using sequence current find I_f and I_B .

$I_{f \neq}$

$$\boxed{I_f = I_f + I_B}$$

$I_{f \neq}$

Magnitude of double line fault is 3 times the zero fault.

$$I_{R \neq 0}$$

$$\overline{I_{R1} + I_{R2} + I_{R0} \neq 0}$$

$$I_{fug} = I_f + I_B$$

$$= (I_{R0} + a^2 I_{R1} + a I_{R2}) + (I_{R0} + a I_{R1} + a^2 I_{R2})$$

$$I_{fug} = [2I_{R0} + (a^2 + a)I_{R1} + (a^2 + a)I_{R2}]$$

$$I_{fug} = 2I_{R0} - I_{R1} - I_{R2}$$

$$\because a^2 + a = -1$$

$$2I_{R0} - (I_{R1} + I_{R2})$$

$$\boxed{I_{fug} = 3I_{R0}}$$

$$\therefore I_{R1} + I_{R2} = -I_{R0}$$

Problems:-

On a balanced 3- ϕ /4-w.

Comment:-

→ All sequence n/w are connected in parallel.


→ $V_{R1} = V_{R2} = V_{R0}$.

→ $I_{R1} = -(I_{R2} + I_{R0})$

Problem:-

The current in each phase of a balanced 3 ϕ system is 10A. The phase sequence is RYB. Find the resultant sequence current.

Solution:-

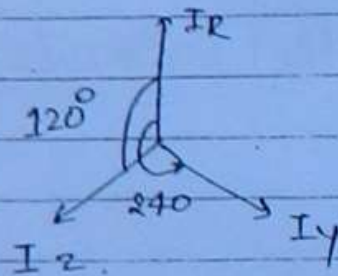

$$I_R = 10 \angle 0^\circ = 10$$

$$I_Y = 10 \angle 240^\circ = a^2 10$$

$$I_B = 10 \angle 120^\circ = a 10$$

$$\begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 10 \\ 10a^2 \\ 10a \end{bmatrix}$$

$$I_{R0} = \frac{1}{3} [10 + 10a^2 + 10a] = \frac{10}{3} \times 0 = 0A$$

$$I_{R1} = \frac{1}{3} [10 + 10a^3 + 10a^3] = \frac{1}{3} \times 30 = 10A$$

$$I_{R2} = \frac{1}{3} [10 + 10a^4 + 10a^4] = \frac{1}{3} [10 + 10a + 10a^2] = 0A$$

Problem 2°

In above c/m the fuses in Y and B phase are removed


$$I_Y = I_B = 0, \quad I_R = 10$$

$$\begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$

$$I_{R0} = I_{R1} = I_{R2} = 10/3$$

* Under balanced condition we only have 1 +ve sequence run

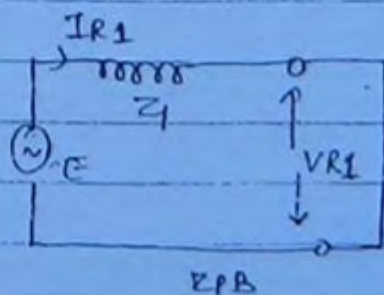3-φ fault using sequence N/w (+ve sequence):



$$\begin{bmatrix} I_R \\ I_Y \\ I_B \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 0 \\ I_{R1} \\ 0 \end{bmatrix}$$

$$\boxed{I_{f, 3\phi} = I_{R1} = E/Z_1}$$

$$I_R = I_{R1}$$

$$I_Y = a^2 I_{R1}$$

$$I_B = a I_{R1}$$

→ In phase fault the fault ^{current} impedance will not is not

not limited by impedance Z_f , hence Z_f is not considered in 3 ϕ fault.

→ Ground also do not effect the 3 ϕ fault current.
Also no difference b/w 3 ϕ fault and ground fault.

→ All the 3 ϕ voltage including the sequence voltage is zero.


Comparison:

3- ϕ fault

$$I_{f-3\phi} = \frac{E}{Z_1}; Z_f = 0$$

$$\rightarrow I_{f-LG} = \frac{3E}{Z_1 + Z_2 + Z_0}$$

Case: 1 Solidly grounded alternator:

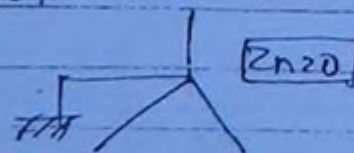

$$Z_0 = Z_{a0} + 3Z_n$$

$$= Z_{a0}$$

∴ 4 alternat
sequence
current

$$Z_2 \approx Z_1$$

$$Z_0 \gg Z_1$$

$$I_{f-3\phi} = \frac{E}{Z_1} \text{ --- (1)}$$

$$I_{f-LG} = \frac{3E}{Z_1 + (\approx Z_1) + (< Z_1)}$$


$$= \frac{3E}{2Z_1} \approx 1.5 \times \frac{E}{Z_1}$$

$$I_{fLG} > I_{f3\phi}$$

$$= 1.5 \times I_{f3\phi}$$

• For solidly grounded, alternator LG fault is more severe.

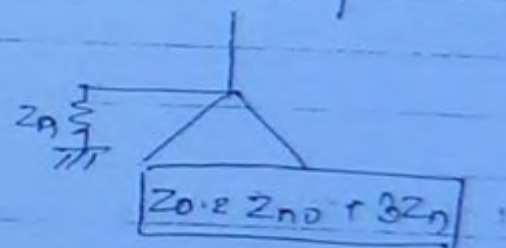Case 2°: Alternator neutral grounded with the impedance Z_n



Z_0 depends on Z_n .

$$I_{f3\phi} = \frac{E}{Z_1}$$

$$I_{fLG} = \frac{3E}{Z_1 + Z_0 + Z_n + 3Z_n}$$

Here severity of fault is decided by Z_n

$$\text{If } Z_n = \frac{1}{3}(Z_1 - Z_0)$$

$$\text{Then } I_{fLG} = \frac{3E}{Z_1 + (\approx Z_1) + Z_n + 3\left(\frac{1}{3}(Z_1 - Z_0)\right)}$$

$$\approx \frac{3E}{3Z_1} \approx I_{f3\phi}$$

*

$$I_{f3\phi} = I_{fLG} \quad \text{for } Z_n = \frac{1}{3}(Z_1 - Z_0)$$

$\text{of } Z_0 \rightarrow \frac{1}{3}(Z_1 - Z_{00}) ; I_{fLQ} > I_{f3\phi}$
 ~~$I_{fLQ} > I_{f3\phi}$~~
 $\rightarrow \frac{1}{3}(Z_1 - Z_0) \Rightarrow I_{fLQ} = I_{f3\phi}$
 $\rightarrow > \frac{1}{3}(Z_1 - Z_{00}) \Rightarrow I_{f3\phi} > I_{fLQ}$

Objective


① zero sequence current can flow from a line into a xmer bank if the winding of xmer are.

a) $\Delta - \Delta$

b) $\Delta - Y$

c) $Y - Y_1$

d) $\Delta - \Delta$

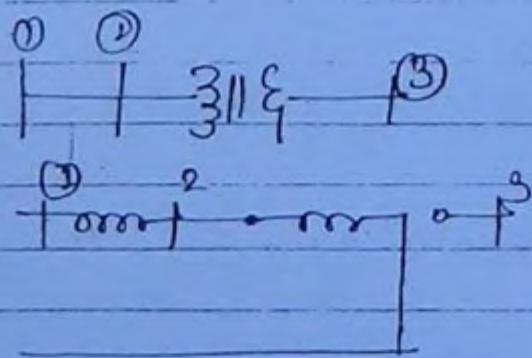


② for s/m shown in figure what is the L-G fault on the right side of xmer equivalent to

a) L-G fault on Gtr side of xmer


b) L-L fault on Gtr of xmer

c) LLG fault on Gtr side of xmer

d) 3 ϕ fault on gtr xmer

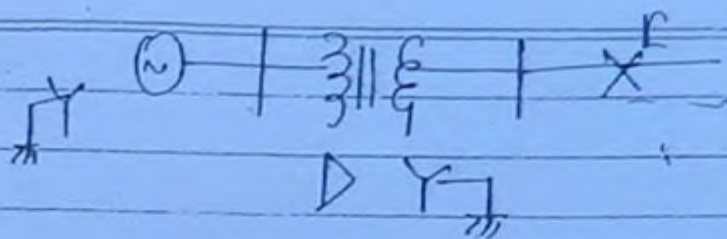

zero sequence diagram.

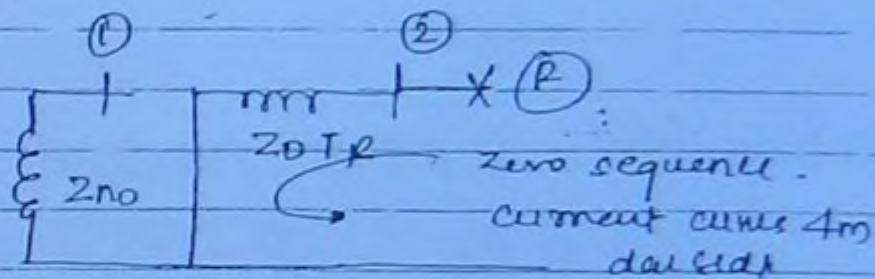

not supplying the zero sequence current so L-L fault on GTR side

③

The L-G fault and the 3 ϕ fault at the terminal of unloaded synchronous GTR is to be same. If terminal voltage is 1 pu, $Z_1 = Z_2 = Z_{12} = j0.1$ and $Z_0 = j0.05$ pu of for the alternator, then the required inductive reactance for nodal grounding is -

$$Z_n = \frac{1}{3} (Z_1 - Z_0)$$

$$\frac{1}{3} (j0.1 - j0.05)$$

$$= j0.0166$$


$$0.066$$

$$0.05$$


$$0.01$$

$$0.0166$$

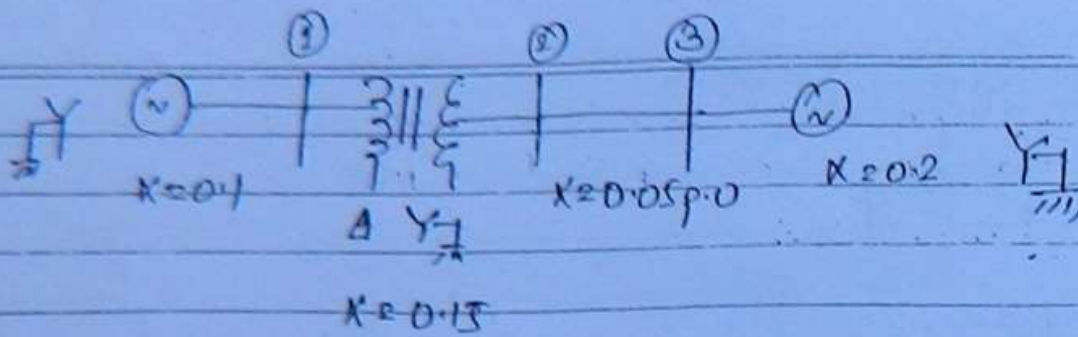④ The zero sequence reactances are indicated in n/w shown below. All the equipment have equal sequence impedances, if L-G fault occurs on bus 3 ϕ the fault current is




→ Reducing two sequence reactance :-

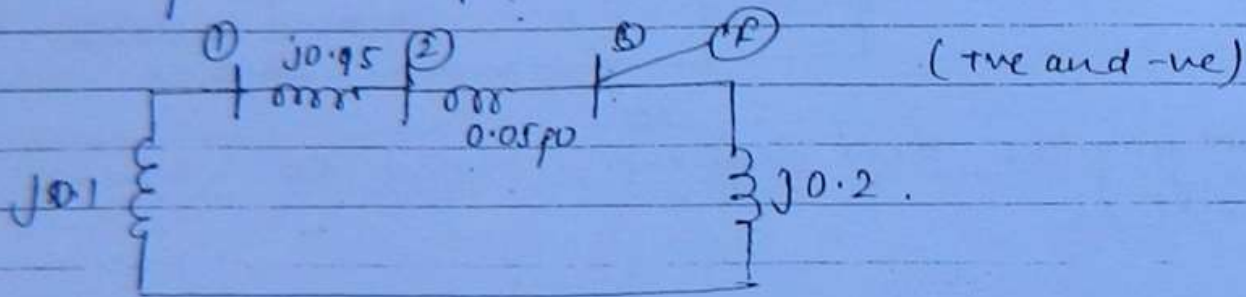

$$\Rightarrow (0.1j + j0.15 + j0.05) \parallel j0.2$$
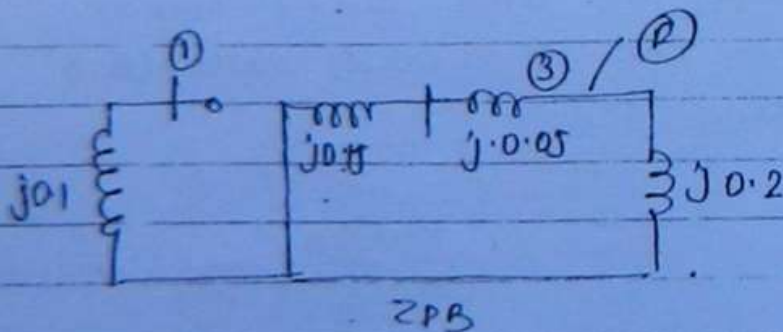
$$= Z_{1TH} = Z_{2TH} = j0.12 \text{ pu}$$



$$\Rightarrow (j0.15 + j0.05) \parallel j0.2$$

$$Z_{0TH} = j0.1 \text{ pu}$$

$$I_f = \frac{3E}{Z_1 + Z_2 + Z_0} = \frac{3 \times 1}{j0.12 + j0.12 + j0.1} = 8.823 \angle -90^\circ \text{ pu}$$

4. In an unbalanced 3- ϕ s/m the currents are measured as $I_R = 0$, $I_Y = 6 \angle 60^\circ$, $I_B = 6 \angle -120^\circ$. The corresponding sequence currents will be.

a) 0 $3 - j\sqrt{3}$ $-3 + j\sqrt{3}$

b) 0 $-3 - j\sqrt{3}$ $3 - j\sqrt{3}$

c) 0 $-9 + j3\sqrt{3}$ $9 - j3\sqrt{3}$

d) 0 $9 - j3\sqrt{3}$ $-9 + j3\sqrt{3}$

$$\begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 0 \\ 6 \angle 60^\circ \\ 6 \angle -120^\circ \end{bmatrix}$$

$$I_{R0} = \frac{1}{3} [0 + 6 \angle 0^\circ + 6 \angle -120^\circ]$$

$$I_{R1} = \frac{1}{3} [0 + a^2 6 \angle 60^\circ + a 6 \angle -120^\circ]$$

$$I_{R2} = \frac{1}{3} [0 + a 6 \angle 60^\circ + a^2 6 \angle -120^\circ]$$

5) A star connect 3 ϕ , 11KV, 25MVA alternator with its neutral grounded with 0.03 pu reactance and x_1, x_2 and zero reactances of 0.2, 0.1, 0.1 respectively. A SLG fault on one of its terminals would result a fault MVA of

$$I_{sc} = I \times \frac{100}{\%Z}$$

$$\frac{I}{I_{sc}} = \frac{Z_{pu}}{1}$$

$$I_{sc} = \frac{1}{Z_{pu}}$$

$$I_{PLG} = \frac{3E}{Z_1 + Z_2 + Z_0 + 3Z_n} = \frac{3 \times 11 \times 10^3}{0.2 + 0.1 + 0.1 + 3 \times 0.03} = j6 \text{ p.u.}$$

$$\therefore I_{PLG} = 6 \text{ p.u.}$$

$$\text{Since MVA} = 6 \text{ p.u.}$$

$$\text{Base MVA} = 25 \text{ MVA}$$

$$\text{Since MVA} = 6 \times 25 = 150 \text{ MVA}$$

25² 0.03 28.0


a) 150 MVA

b) 125 MVA

c) 100 MVA

d) 50 MVA

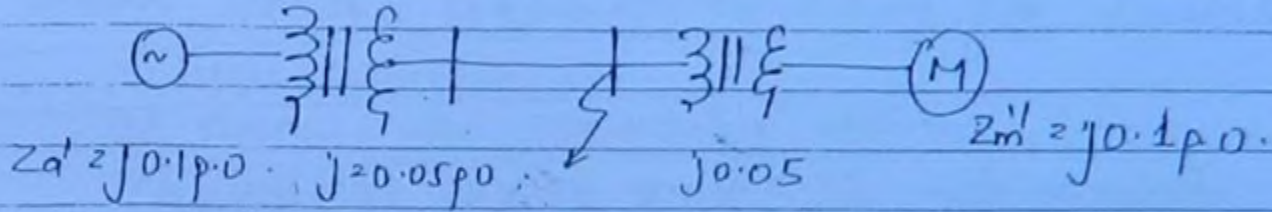6) Figure shows a single line diagram with all reactance in per unit on common base. The system is on no load. When a 3 ϕ fault occurs at F on HV side, the fault current will be —




$$\text{Hent}^\circ = \frac{I}{I_{sc}} \cdot Z_{p.o} \cdot I_{sc} - \ln \phi_u$$

$$I = 1 \mu\text{V}$$

$$\Rightarrow \frac{1}{I_{sc}} = Z_{pv}$$

Equivalent: reactance diagram.

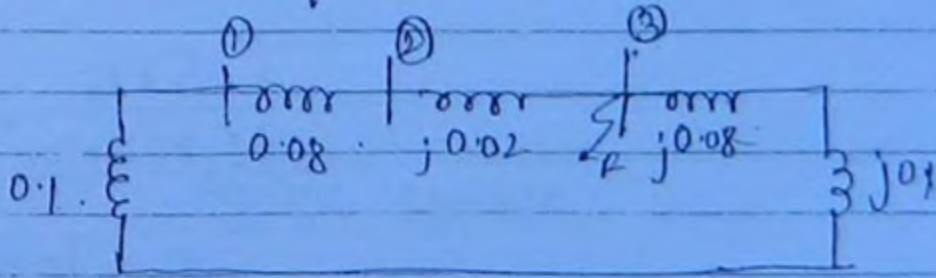

$$Z_{in} \text{ pu} = j0.122 \text{ pu}$$

$$I_a = \frac{1}{j0.122} = -j819 \text{ pu}$$

4) A 20 MVA 33 kV 3 ϕ alternator is subjected to different types of faults. $I_{f3\phi} = 319 \text{ A}$

$$I_{fL0} = 659 \text{ Amp.}$$

$$I_{fL1} = 435 \text{ Amp.}$$

determine X_1, X_2, X_0 of the glr neglect resistances.

Solution

$$I_{f2\phi} = \frac{E_1}{Z_1} = 319 = \frac{33\sqrt{3}}{Z_1} = 59.72 \Omega$$

$$I_{fL1} = \frac{\sqrt{3}E_1}{Z_1 + Z_2} = \frac{\sqrt{3} \times 33 / \sqrt{3}}{59.72 + Z_2} = 435$$

$$= 16.137 \Omega$$

$$I_{fL0} = \frac{3E_1}{Z_1 + Z_2 + Z_0 + 3} = \frac{3 \times 33 / \sqrt{3}}{59.72 + 16.137 + Z_0} = 659.$$

$$= \frac{57.15}{75.857 + Z_0} = 659$$


$$Z_0 = 10.863 \mu\Omega$$

Example:-

Two 11 kV 20 MVA, 201 Δ ϕ , Y connected glr operated in parallel. The positive, negative and zero sequence reacton of each being $j0.18$, $j0.15$, and $j0.1 p.u.$. The star point of one of the glr is isolated and that of the other is ~~also~~ earthed with 2Ω resistor. The SLG fault occurs at the terminals of one of glr, estimate.

- fault current
- current in grounding resistor
- voltage across grounding resistor (phase voltage)


Solution:-

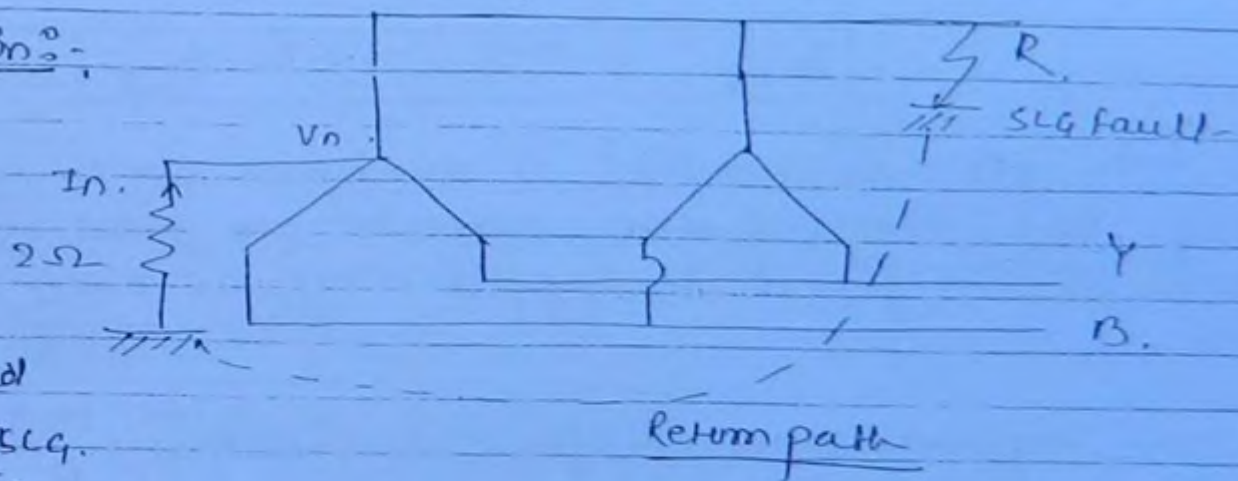


To find


- I_{fSLG}
- I_n
- V_n

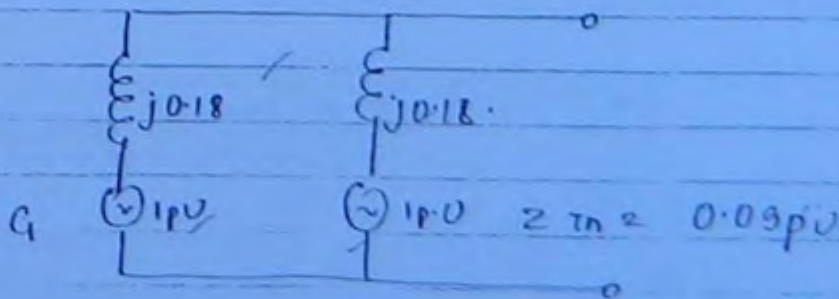~~Sequence N/W~~ Sequence N/W :- Positive Sequence.



negative sequence

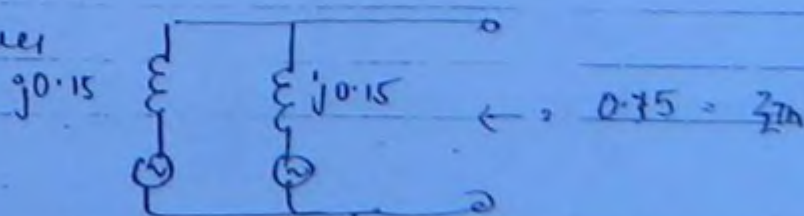

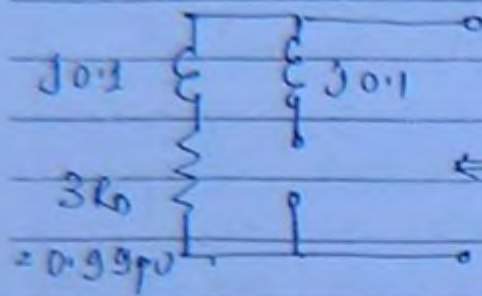

$$Z_{base} = \frac{kV_b^2}{MVA} = \frac{11^2}{20} = 6.05$$

$$Z_{0, in} = (0.99 + j0.1) \text{ pu}$$

$$R_n = \frac{.2}{6.05} = 0.033 \text{ pu}$$

$$I_{fsc} = \frac{3E}{Z_1 + Z_2 + Z_0 + 3} = \frac{3 \times 1}{j0.05 + j0.15 + [0.99 + j0.1]}$$

$$I_{fLg} = 2.92 \angle -14.38^\circ \text{ Amp}$$

Note:

a) Since gr to neutral is unloaded we cannot supply any zero sequence current. The total zero sequence to the fault is supplied by G1 only

→ only zero sequence current flow the neutral to ground.
 → for L-G fault we need return path


b) Current in grounding resistor is equal to fault current since fault & R_L act as return path for fault current

$$I_N = 2.92 \angle -14.32^\circ \text{ p.u.}$$

$$V_L = 2.92 \times 0.33 = 0.9636 \text{ p.u.}$$

$$\text{per phase voltage} = \frac{0.9636 \times 1100}{\sqrt{3}} = 6.12 \text{ KV}$$

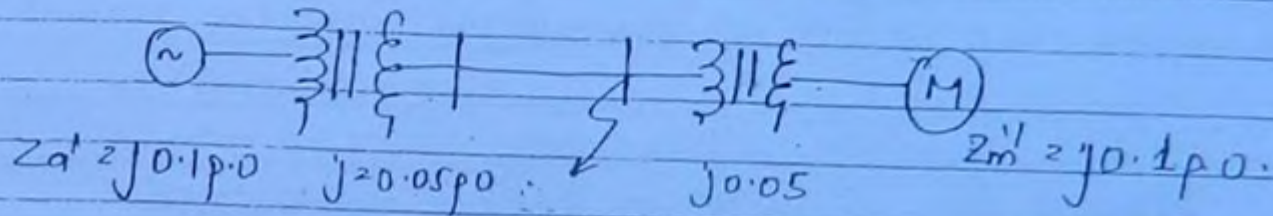- 6) Figure shows a single line diagram with all reactance in pu per unit on some base. The system is on no load. When a 3 ϕ fault occurs at 'F' on HV side, the fault current will be —




$$\text{Hent} = \frac{I}{I_{sc}} = Z_{pu} \therefore I, I_{sc} - \text{in pu}$$

$$I = 1 \text{ pu}$$

$$\Rightarrow \boxed{\frac{I}{I_{sc}} = Z_{pu}}$$

Equivalent reactance diagram:

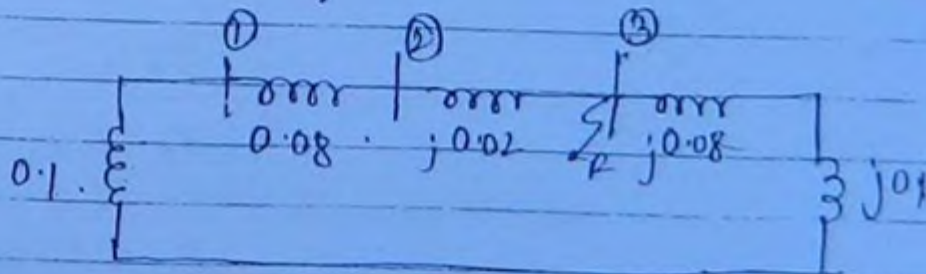

$$Z_{th \text{ pu}} = j0.122 \text{ pu}$$

$$I_{sc} = \frac{1}{j0.122} = -j8.19 \text{ pu}$$

- 7) A 20 MVA 33 kV 3 ϕ alternator is subjected to different types of faults. $I_{3\phi} = 319 \text{ A}$

$$I_{FLG} = 659 \text{ Amp.}$$

$$I_{FLI} = 435 \text{ Amp.}$$

determine X_1, X_2, X_0 of the glr neglect resistances.

Solution

$$I_{F3\phi} = \frac{E_1}{Z_1} = \frac{319}{\frac{33\sqrt{3}}{Z_1}} = 59.72 \Omega$$

$$I_{FLI} = \frac{\sqrt{3}E_1}{Z_1 + Z_2} = \frac{\sqrt{3} \times 33 / \sqrt{3}}{59.72 + Z_2} = 435$$

$$= 16.137 \Omega$$

$$I_{FLG} = \frac{3E_1}{Z_1 + Z_2 + Z_0 + Z} = \frac{3 \times 33 / \sqrt{3}}{59.72 + 16.137 + Z_0} = 659.$$

$$= \frac{57.15}{75.857 + Z_0} = 659$$

$$75.857 + Z_0$$


$$Z_0 = 10.863 \mu\Omega$$

Example:-

Two 11kV 20MVA, 201 3 ϕ , Y connected glr operated in parallel. The positive, negative and zero sequence reactance of each being $j0.18$, $j0.15$, and $j0.1p.u.$. The star point of one of the glr is isolated and that of the other is ~~also~~ earthed with 2Ω resistor. The SLG fault occurs at the terminals of one of glr, estimate.

- Fault current
- Current in grounding resistor
- Voltage across grounding resistor (phase voltage)


Solution:-

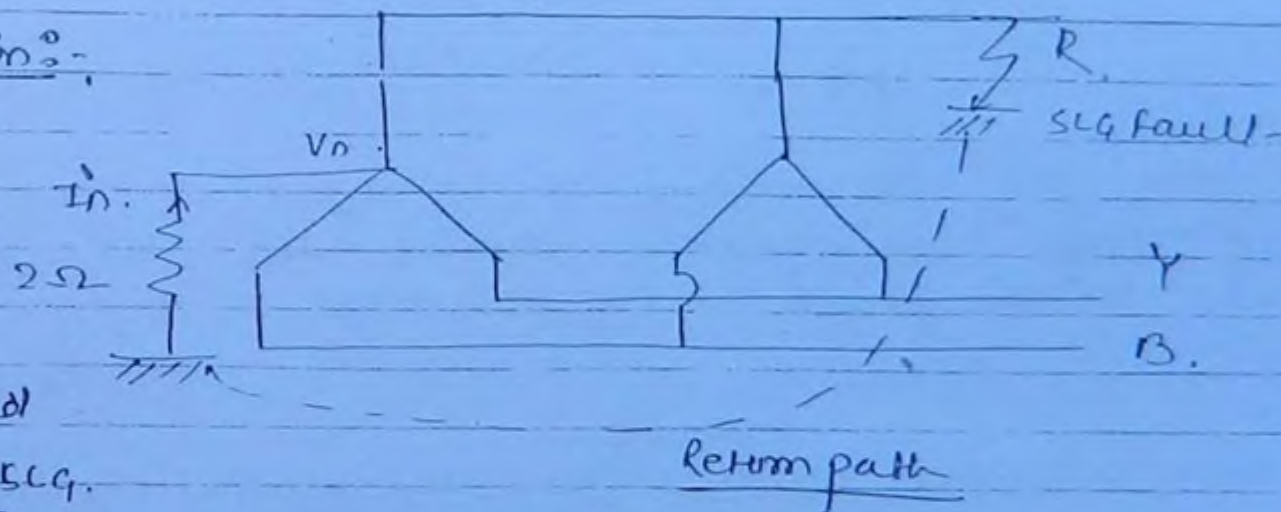


to find


- I_{FSLG}
- I_n
- V_n

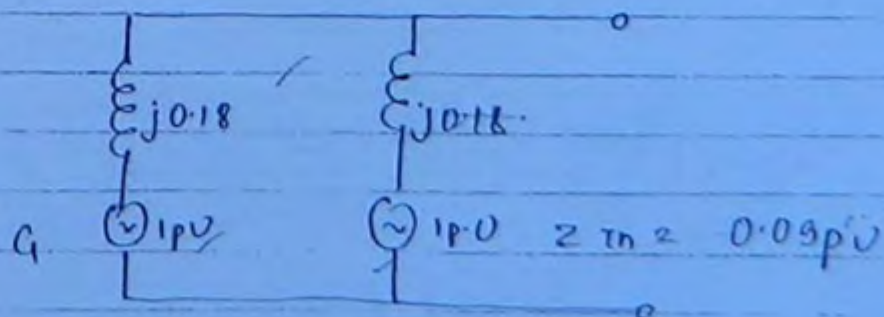~~2nd~~ Sequence N/W :- Positive Sequence.



Negative Sequence

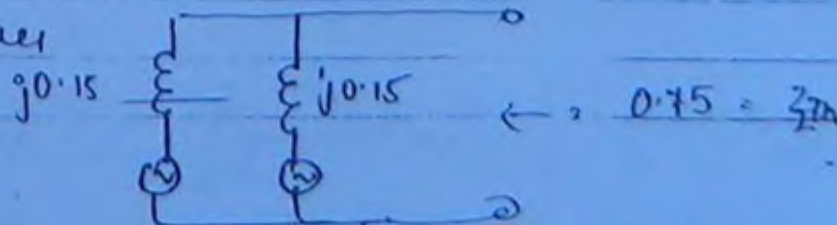

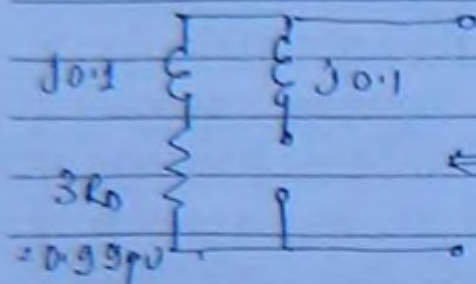

$$Z_{base} = \frac{kV_b^2}{MVA} = \frac{11^2}{20} = 6.05$$

$$Z_{0, in} = (0.99 + j0.1) p.u.$$

$$R_n = \frac{2}{6.05} = 0.33 p.u.$$

$$I_{fsc} = \frac{3E}{Z_1 + Z_2 + Z_0 + 3} = \frac{3 \times 1}{j0.05 + j0.15 + [0.99 + j0.1]}$$

$$I_{fLg} = 2.92 \angle -14.58^\circ \text{ Amp.}$$

Note:

a) Since gr to neutral is unloaded we cannot supply any zero sequence current. The total zero sequence to the fault is supplied by G1 only

→ Only zero sequence current flow from neutral to ground.
→ For L-G fault we need return path

b) Current in grounding resistor is equal to fault current since fault & R_L act as return path for fault current

$$I_N = 2.92 \angle -14.52^\circ \text{ p.u.}$$


$$V_L = 2.92 \times 0.33 = 0.9636 \text{ p.u.}$$

$$\text{Pre phase voltage} = \frac{0.9636 \times 1100}{\sqrt{3}} = 6.12 \text{ KV}$$

Problem:-

Two identical 11kV, 50MVA, 3 ϕ alternators are connected in parallel and supply a substation by a feeder. The sequence impedances are marked in figure. Calculate the potential of alternator neutral with respect to ground if a LLG fault occur on Y-B phases of substation.

Solution

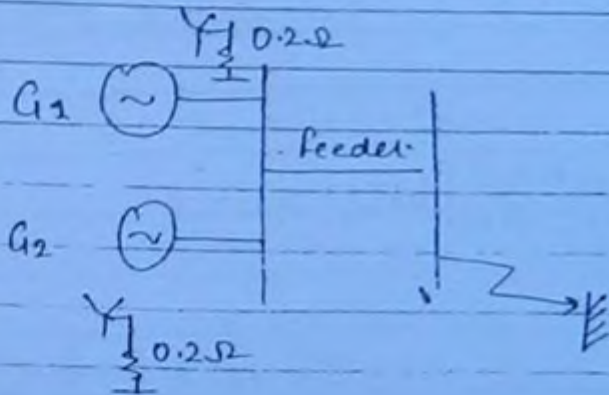

$G_1, G_2 \rightarrow 11\text{kV}, 50\text{MVA}$

$X_1 = j0.68\Omega, X_2 = 0.4$

$X_0 = 0.2\Omega$

Feeder $\rightarrow Z_1 = Z_2 = (0.4$

$Z_0 = 0.7 + j3\Omega$

~~Sequence Impedances~~ $Z_{base} = \frac{11\text{kV}^2}{50} = 2.42\Omega$

$G_1 \& G_2$

$$X_1 = j0.68 / 2.42 = j0.28 \text{ p.u.}$$

$$j0.68 / 2.42 = 0.28$$

$$X_2 = j0.4 / 2.42 = j0.16 \text{ p.u.}$$

$$X_0 = j0.2 / 2.42 = j0.08 \text{ p.u.}$$


$$R_0 = j0.2 / 2.42 = j0.08 \text{ p.u.}$$

Feeder

$$Z_1 = \frac{(0.4 + j0.7)}{2.42} = (0.165 + j0.289) \text{ p.u.}$$


$$Z_0 = (0.7 + j3) / 2.42 = (0.28 + j1.239) \text{ p.u.}$$

1st sequence

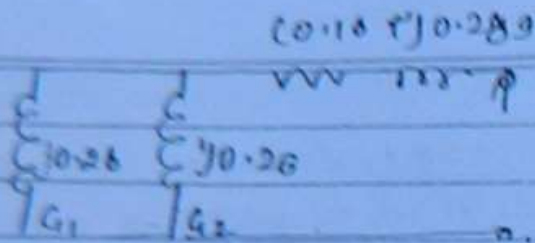


$$Z = 0.16 + j0.419 \text{ p.u.}$$

2nd sequence

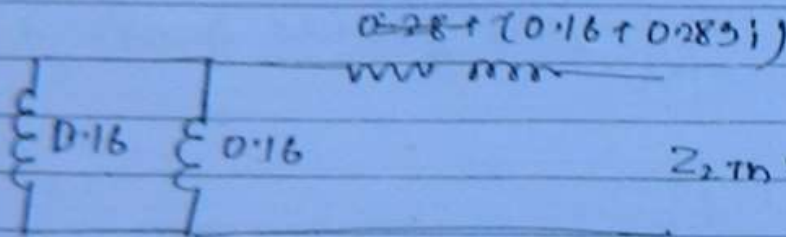

$$Z_{2n} = 0.16 + j0.369 \text{ p.u.}$$


Zero sequence

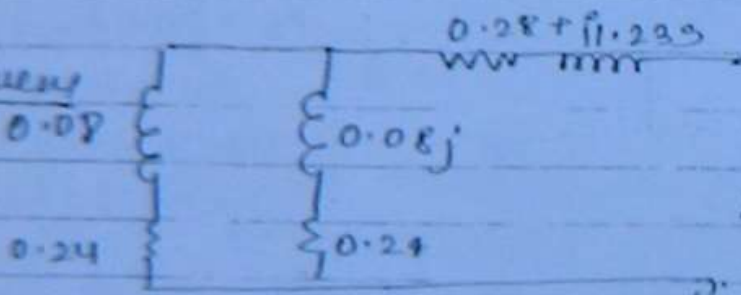

$$Z_{0n} = 0.4 + j1.279$$

∴

As 3 φ are connected in parallel!

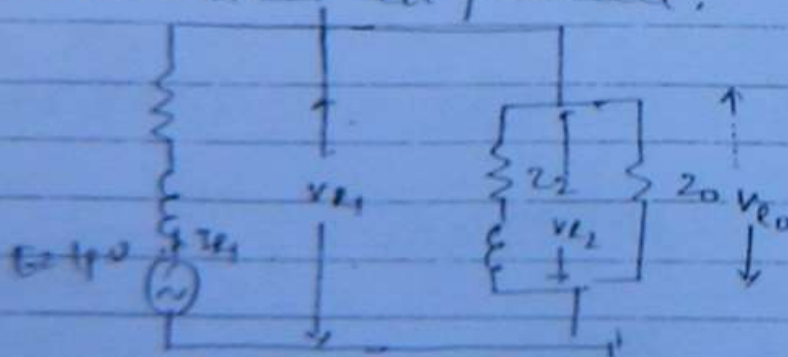

$$V_{L1} > V_{L0}$$


$$V_{L1} = E - I_{L1} Z_1$$

$$I_{L1} = \frac{1 \angle 0}{Z_1 + (Z_2 || Z_0)}$$

$$12 \angle 0^\circ \\ (0.16 + j0.419) + (0.06 + j0.365 \parallel 0.4 + j1.279)$$

Solve : $\rightarrow$

Ans $0.456 - j1.223 \text{ p.u.}$

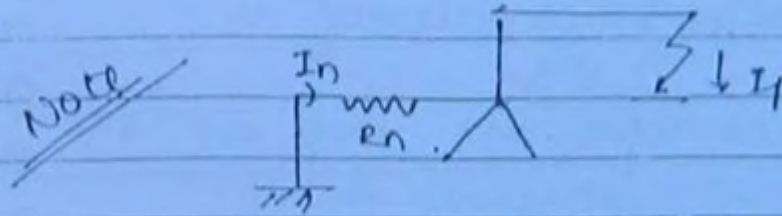

$$I_n = I_{n1} + I_{n2} + I_{n0}$$

$$I_f = I_f = 3I_{R0} \quad (\text{Zero sequence current or fault current})$$

$$V_{R0} = -I_{R0} Z_f$$

$$= 8 (0.456 - j1.223) \times (0.4 + j)$$

$$V_{R0} = 120 - (0.456 - j1.223) \times (0.16 + j0.149)$$

$$V_{R0} = (0.738 + j0.121) \quad 0.408 - j0.012$$

$$I_{R0} = \frac{(0.738 + j0.121)}{0.4 + j1.279} = \frac{(0.25 - j0.458) \text{ A}}{(0.0823 - j0.293i)}$$

Note

As there are eq^{ts} two equivalent parallel path the zero sequence current supplied by each G₁ is half of the total sequence current.

$$V_m = 3 I_{L0} R_0$$

$$3 \left(\frac{0.096 - j0.29}{2} \right) \times 0.083$$

$$(0.012 - j0.036) \text{ pu} \times \frac{1100}{\sqrt{3}}$$

Fault Analysis using Z-bus:-

→ use Z-bus algorithm to draw Z-bus matrix.

Graph Theory:- circuit $\cong$ Network.

∴- The purpose of to study Graph theory is that computer performs the n/w analysis

∴- Subject which deals with geometrical representation of object :- Topology

HINTS:-


→ N/w analysis means finding a current through and voltage across every branch of n/w

→ N/w analysis can be carried by using either loop analysis or nodal analysis.


→ The basis for loop analysis is KVL and for nodal analysis is KCL

→ The KCL and KVL do not depend upon type of element but it depends upon structure (graph or geometrical representation) of n/w

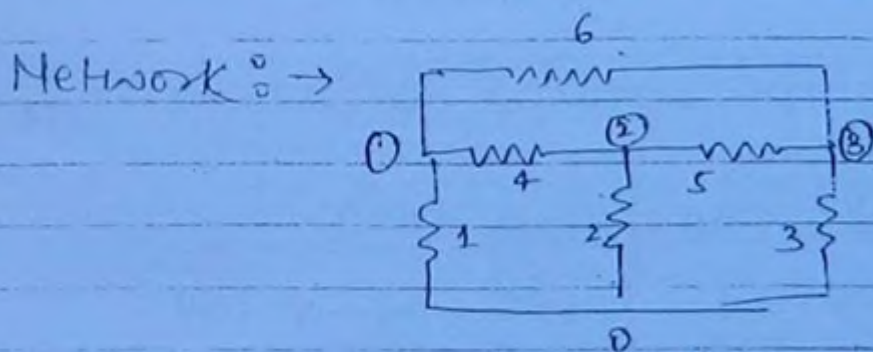→ We pass the information regarding structure of n/w to computer through incidence matrices $L+1$,



node = 4
element $e = 6$

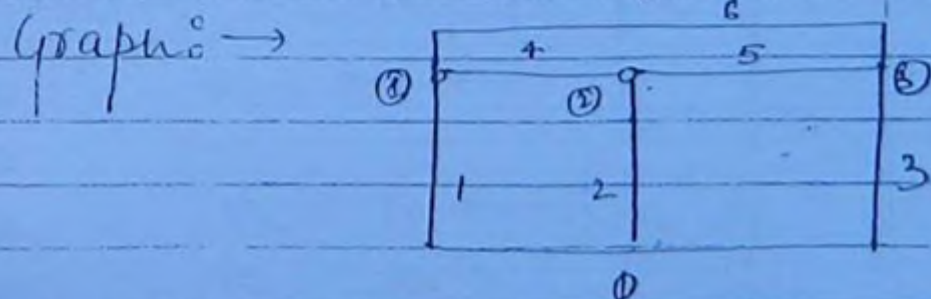


$\rightarrow$ structure remains

→ when direction is given $\rightarrow$ oriented graph


→ No overlapping $\rightarrow$ Planar Graph

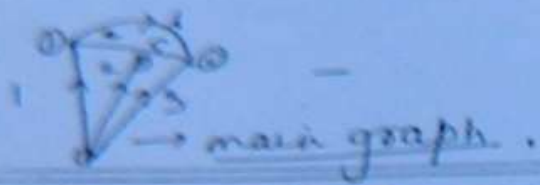* Graph theory cannot be applied on Non-Planar graph



* Sub-graph :- graph from original. 2, ① ② ③

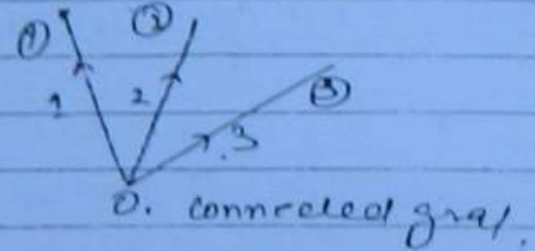* connected sub-graph :- One can go from one to another node




* minimum no of connected graph $(n-1)$.

* A well connected sub-graph without closed loops $\rightarrow$ tree.

1, 2, 3 $\rightarrow$ Twig / branch, no of twig $(n-1)$.

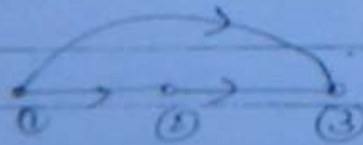* those element which are left, if form the graph then is called as Co-tree.



$$\boxed{\text{Tree} + \text{Co-tree} = \text{Graph}}$$

$$\begin{aligned} \text{links} &= E - (\text{twig}) \\ &= E - (n-1) \end{aligned}$$

$$\boxed{\text{links} = E - n + 1}$$

	①	②	③
1	-1	0	0
2	0	-1	0
3	0	0	-1
4	+1	-1	0
5	0	-1	+1
6	+1	0	-1

$$[V] = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ 1 \\ V_6 \end{bmatrix}$$

$$[U] = [A][V]$$

$$U_1 = -V_1$$

$$U_2 = -V_2$$

$$U_3 = -V_3$$

$$U_4 = V_1 - V_2$$


$$U_5 = V_3 - V_2$$

$$U_6 = V_1 - V_3$$

→ Type 2. Modification:

An element with self impedance (Z_s) is added b/w an already existing bus (K) and new bus (q).

* (new element is added to Kth bus)

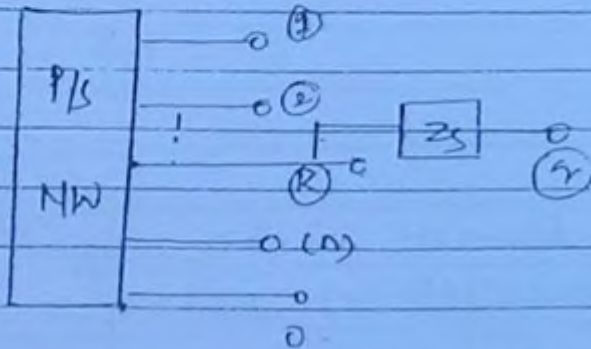


$$Z_{bus}(new) = \begin{matrix} Z_{bus}(old) & qth\ column \\ \hline Z_{1K} & Z_{1q} \\ Z_{2K} & Z_{2q} \\ \vdots & \vdots \\ Z_{K1}, Z_{K2} & Z_{Kq} \\ \vdots & \vdots \\ Z_{nK} & Z_{nq} \\ \hline Z_{q1}, Z_{q2}, \dots, Z_{qn} & Z_{qq} \end{matrix}$$

$$Z_{qq} = Z_{KK} + Z_s$$

- $Z_{Kq}(row)$ is copy for row Z_{qK}
- $Z_{1K}(column)$ is copy for Z_{1q} .

$$Z_{bus}(new) = \begin{matrix} & & & & Z_{1K} \\ & & & & Z_{2K} \\ & & & & \vdots \\ & & & & Z_{nK} \\ & & & & \hline Z_{K1}, Z_{K2}, \dots, Z_{Kn} & & & & Z_{KK} + Z_s \end{matrix}$$

Example:

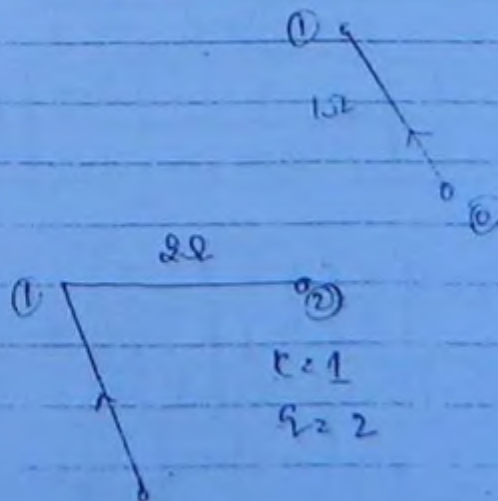


$$Z_{bus}(old) = \begin{matrix} 1 & 2 \\ \hline 1 & 1.5 \end{matrix}$$

$$Z_{bus}(new) = \begin{matrix} & 1 & 2 \\ \hline 1 & 1 & K_{12} \\ 2 & Z_{21} & Z_{22} \end{matrix}$$

	k	①	②	
$Z_{bus}^{(new)2}$	①	1	1	$\begin{bmatrix} 1 & 1 \\ 1 & 3 \end{bmatrix}$
	②	1	3	

⇒ Type 3 Modification :-

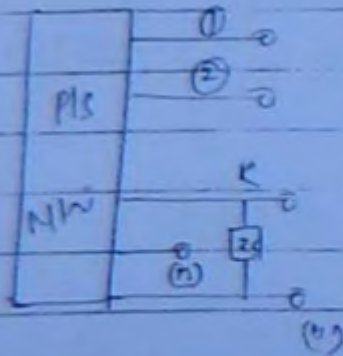
An element with self impedance is added b/w old bus (k) and reference bus (0).



$$Z_{bus}^{(new)} = Z_{bus}^{(old)} - \frac{1}{Z_{kk} + Z_s} \begin{bmatrix} Z_{k1} \\ Z_{k2} \\ \vdots \\ Z_{kn} \end{bmatrix} \begin{bmatrix} Z_{k1} & \dots & Z_{kn} \end{bmatrix}$$


(1xn)
A (n x 1)

Example

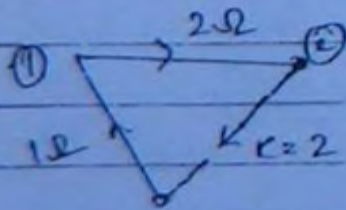

$$Z_{bus}^{res} = \begin{bmatrix} 1 & 1 \\ 1 & 3 \end{bmatrix} - \frac{1}{Z_{kk} + Z_s} \begin{bmatrix} Z_{12} \\ Z_{22} \end{bmatrix} \begin{bmatrix} Z_{21} & Z_{22} \end{bmatrix}$$

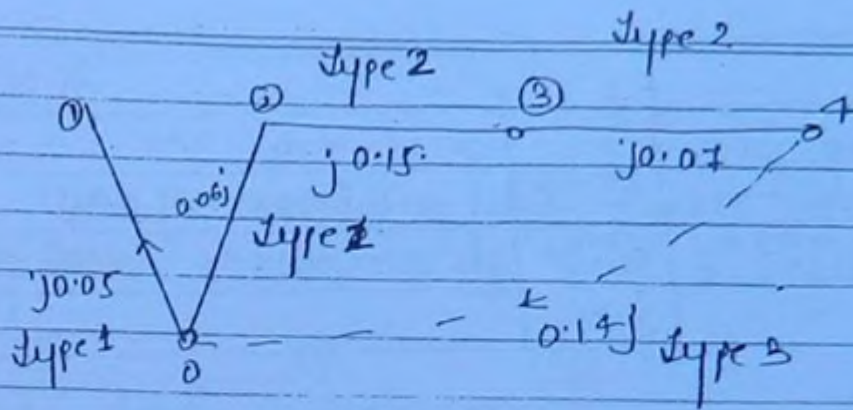
$$= \begin{bmatrix} 1 & 1 \\ 1 & 3 \end{bmatrix} - \frac{1}{3+3} \begin{bmatrix} 1 \\ 3 \end{bmatrix} \begin{bmatrix} 1 & 3 \end{bmatrix}$$



Step 1:


Z_{bus}

①	②
①	$j0.05$

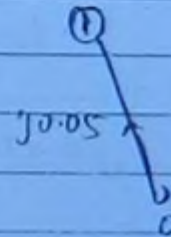


Z_{bus}

	①	②
①	$j0.05$	0
②	0	$j0.06$

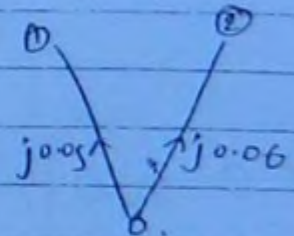

Z_{bus}


	①	②	③
1	$j0.05$	0	0
2	0	$j0.06$	$j0.06$
3	0	$j0.06$	$j0.21$

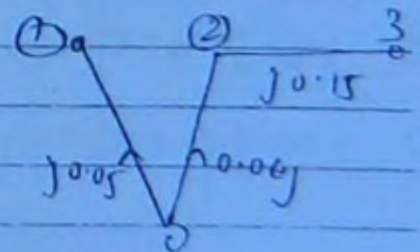

$$\begin{array}{r} 0.06 \\ 0.15 \\ \hline 0.21 \end{array}$$

Z_{bus}

	1	2	3	4
1	$j0.05$	0	0	0
2	0	$j0.06$	$j0.06$	$j0.06$
3	0	$j0.06$	$j0.21$	$j0.2$
4	0	$j0.06$	$j0.21$	$j0.28$

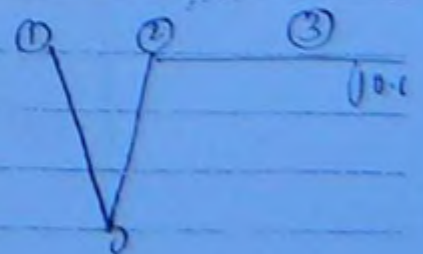

$$\begin{array}{r} 0.21 \\ 0.07 \\ \hline 0.28 \end{array}$$

$$Z_{bus \text{ old}} = \frac{1}{j0.28 + 0.14} \begin{bmatrix} 0 \\ j0.06 \\ j0.21 \\ j0.28 \end{bmatrix} \begin{bmatrix} 0 & j0.06 & j0.21 & j0.28 \end{bmatrix}$$


$$Z_{bus \text{ old}} = \frac{1}{j0.42} \begin{bmatrix} 0 & -3.6 \times 10^{-3} & -0.0126 & 0.0168 \\ 0 & -3.6 \times 10^{-3} & -0.0126 & 0.0168 \\ 0 & -0.0126 & -0.0441 & 0.0588 \\ 0 & -0.0168 & -0.0588 & 0.0784 \end{bmatrix}$$

$$\begin{bmatrix} j0.05 & 0 & 0 & 0 \\ 0 & j0.06 & j0.06 & 0.04 \\ 0 & j0.06 & j0.21 & 0.21 \\ 0 & j0.06 & j0.21 & 0.28 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & j8.57 \times 10^{-3} & 0.03 & 0.04 \\ 0 & j0.03 & j0.105 & 0.14 \\ 0 & j0.04 & j0.14 & j0.1866 \end{bmatrix}$$


$$Z_{bus \text{ new}} = \begin{bmatrix} -j0.05 & 0 & 0 & 0 \\ 0 & j0.254 & j0.03 & j0.02 \\ 0 & j0.03 & j0.105 & j0.07 \\ 0 & j0.02 & j0.07 & j0.158 \end{bmatrix}$$

IES - 1999

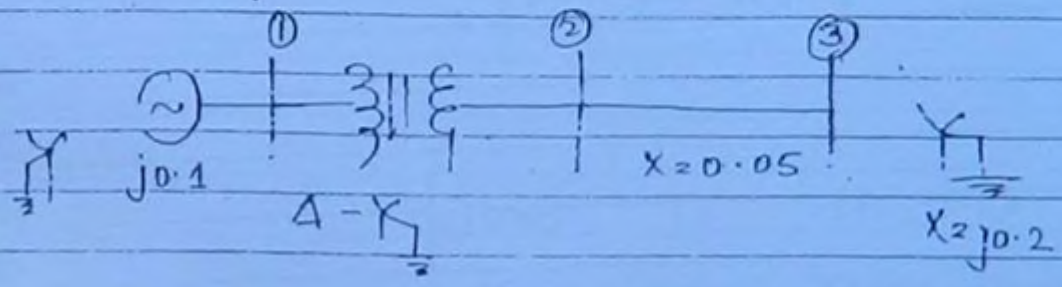
The per unit zero sequence reactances of the n/w are shown in figure. The zero sequence driving point reactance of ~~load~~^{node} 3 will be.



Zero sequence n/w.

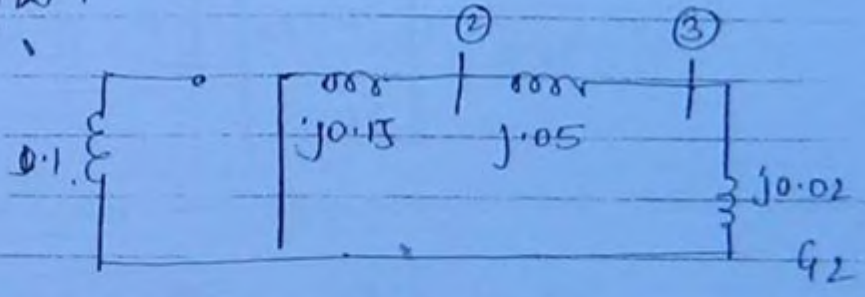

Graph

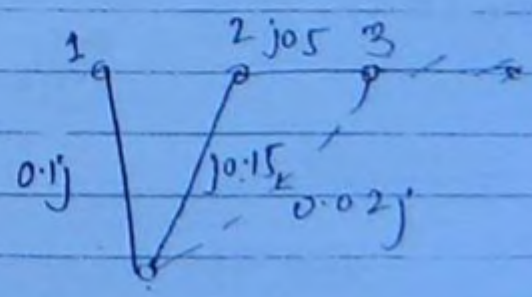

$Z_{bus} =$ ① $\begin{bmatrix} 0.1j \end{bmatrix}$

$Z_{bus} =$

	①	②
①	$0.1j$	0
②	0	$j0.15$

Z_{bus}

	1	2	3
1	$j0.1$	0	0
2	0	$j0.15$	$j0.15$
3	0	$j0.15$	$j0.2$

0.15
 $+0.5$

Z_{bus}

$$Z_{bus}(old) = \frac{1}{0.2j + j0.2} \begin{bmatrix} 0 \\ j0.15 \\ j0.2 \end{bmatrix} \begin{bmatrix} 0 & j0.15 & j0.2 \end{bmatrix}$$

$$Z_{bus}(old) = \frac{1}{0.4j} \begin{bmatrix} 0 & 0 & 0 \\ 0 & & \\ 0 & & -0.04 \end{bmatrix}$$

$$j0.2 = \frac{1}{0.04j} [-0.04]$$

$$0.2j = 0.1j$$

$$Z_{33} = 0.1j$$

CALCULATION OF FAULTS USING Z_{BUS} :-

$$Z_{1, Bus} = Z_{2, Bus} = \begin{bmatrix} j0.15 & j0.12 & j0.107 & j0.0739 \\ j0.1266 & j0.157 & j0.132 & j0.0384 \\ j0.107 & j0.132 & j0.154 & j0.114 \\ j0.079 & j0.038 & j0.114 & j0.136 \end{bmatrix}$$

$Z_0(bus)$

$$= \begin{bmatrix} j0.05 & 0 & 0 & 0 \\ 0 & j0.051 & j0.03 & j0.02 \\ 0 & j0.03 & j0.105 & j0.07 \\ 0 & j0.02 & j0.04 & j0.093 \end{bmatrix}$$

3- ϕ fault :- (Except the sequence no other components)

$$\overset{(2)}{Z_{bus}} = \overset{(1)}{Z_{bus}} = \overset{(2)}{I_{bus}} = \overset{(1)}{I_{bus}} = 0$$

Let fault occur on bus (k).

$$\boxed{I_k^{(1)} = I_f = \frac{E}{Z_{kk'}}} \text{ --- fault current.}$$

at kth bus

$$I_R = I_k^0 \angle 0^\circ$$

$$I_Y = I_k^0 \angle 240^\circ$$

$$I_B = I_k^0 \angle 120^\circ$$

* → at faulted bus k all voltage voltages are zero

$$V_k^{(0)} = V_k^{(1)} = V_k^{(2)} = 0$$

Healthy phase voltage:-

when the fault occurs at bus (k)

voltage bus (i) is

$$V_i^{(1)} = E - Z_{ik}^{(1)} \cdot I_k^{(1)}$$

for $i = 1, 2, \dots, n$

$i \neq k$

$i \rightarrow$ healthy bus

$k \rightarrow$ faulted bus

$$V_i^{(2)} = V_i^{(0)} = 0$$

Line to Ground fault:-

fault occurs at (k)

$$I_k^{(1)} = I_k^{(2)} = I_k^{(0)} = \frac{E}{Z_{kk}^{(1)} + Z_{kk}^{(2)} + Z_{kk}^{(0)}}$$

three phase current at bus (k)

$$\begin{bmatrix} I_k \\ I_V \\ I_B \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_k^{(0)} \\ I_k^{(1)} \\ I_k^{(2)} \end{bmatrix}$$

Zbus Building Algorithm:


The bus admittance matrix (Y_{bus}) can be obtained easily by taking inverse of Y_{bus} bus impedance matrix Z_{bus} can be obtained. But this method has following disadvantages:-

→ Y_{bus} is highly dimensional matrix. To find Inverse of such a big matrix is difficult.


→ N/W changes in power system takes place regularly for these changes every time we had to modify Y_{bus} and then we have to find Z_{bus} . This is quite difficult process.

→ To avoid above difficulties Z_{bus} Building algorithm is used. For a given power s/m bus impedance matrix $Z_{bus}(\text{old})$ already exist. For the N/W changes now this matrix will be updated

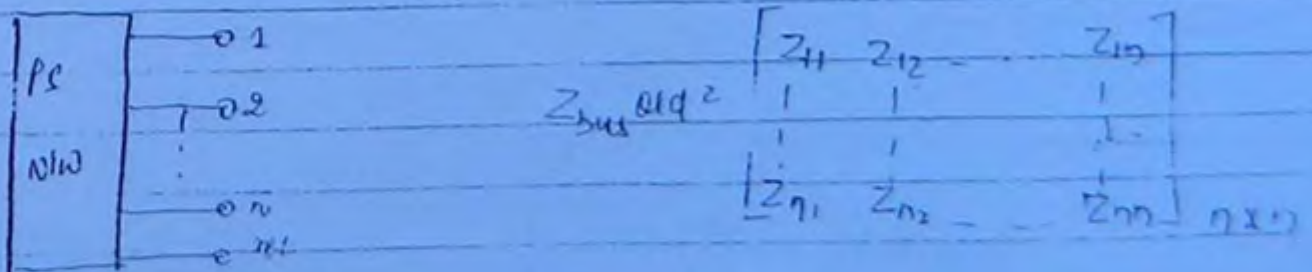→ There are four types of modification takes place in n/w.




~~TYPE MODIFICATION~~

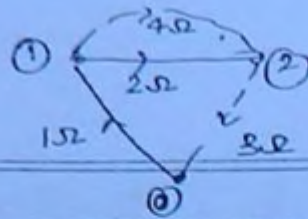

TYPE MODIFICATION :-

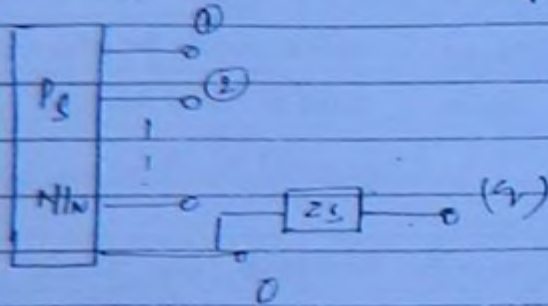An element with self impedance z_s is added b/w the reference bus and new bus 'q'



$$Z_{bus}(new) = \begin{bmatrix} Z_{bus}(old) & \begin{matrix} z_{1q} \\ z_{2q} \\ \vdots \\ z_{qn} \end{matrix} \\ \begin{matrix} z_{q1} & z_{q2} & \dots \end{matrix} & \begin{matrix} z_{qq} \end{matrix} \end{bmatrix}$$

(n+1) x (n+1)

* All elements are zero except diagonal


$$\begin{aligned} z_{1q} &= z_{q1} = 0 \\ z_{2q} &= z_{q2} = 0 \\ z_{iq} &= z_{qi} = 0 \end{aligned}$$

and $\boxed{z_{qq} = z_s}$

$$\Rightarrow Z_{bus}(new) =$$

$$\begin{bmatrix} & 0 \\ & 0 \\ & 1 \\ & \vdots \\ & 0 \\ 0 & 0 & \dots & 0 & 0 \end{bmatrix} \begin{matrix} z_s \end{matrix}$$

Example:

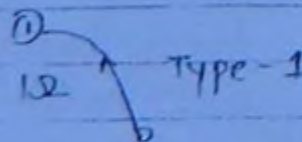

$$Z_{bus}(new) = \begin{bmatrix} 1 & 1\Omega \end{bmatrix}$$

$$I_{fLG} = I_{fK} = \frac{3E}{Z_{KK}^{(1)} + Z_{KK}^{(2)} + Z_{KK}^{(0)}}$$

when fault occur at bus (K) the healthy phase voltage V_i .

$$V_i^{(1)} = E - Z_{iK}^{(1)} I_K^{(1)}$$

$$V_i^{(2)} = -Z_{iK}^{(2)} I_K^{(2)}$$

$$V_i^{(0)} = -Z_{iK}^{(0)} I_K^{(0)}$$

at bus (I) the 3- ϕ voltage are

$$\begin{bmatrix} V_R \\ V_Y \\ V_B \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_i^{(0)} \\ V_i^{(1)} \\ V_i^{(2)} \end{bmatrix}$$

Line to line fault -

of bus (K).

fault is occur on only two phases

$$I_K^{(1)} = -I_K^{(2)} = \frac{E}{Z_{KK}^{(1)} + Z_{KK}^{(2)}}$$

$$I_{fLL} = \frac{\sqrt{3}E}{Z_{KK}^{(1)} + Z_{KK}^{(2)}}$$

Healthy bus voltage:

$$V_i^{(1)} = E - I_K^{(1)} Z_{iK}^{(1)}$$

$$V_i^{(2)} = -I_k^{(2)} Z_{ik}^{(2)}$$

$$\text{for } i = 1, 2, \dots, n \\ i \neq k.$$

The 3 ϕ voltages at bus (1)

$$\begin{bmatrix} V_R \\ V_Y \\ V_B \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 0 \\ V_i^{(1)} \\ V_i^{(2)} \end{bmatrix}$$

Numerical:

A 3 ϕ death s.c occurs at bus (2) of system find

a) Fault current

b) Line to Neutral voltage at bus (2)

1) Fault at bus (2)

$$I_f = I_2^{(1)} = \frac{E}{Z_{kk}'} = \frac{E}{Z_{22}''} = \frac{120^\circ}{j0.157} = 6.36 \angle -90^\circ$$

$$I_{bus} = \frac{100}{\sqrt{3}(220) \times 10^3} = 262.43 \text{ Ams.}$$

$$|I_f| = 6.36 \times 262.43 = 1669.9 \text{ Ams}$$

$$I_R = 1669 \angle -90^\circ$$

$$I_Y = 1669 \angle -210^\circ \text{ or } 1669 \angle 150^\circ$$

$$I_B = 1669 \angle -330^\circ \text{ or } 1669 \angle 30^\circ$$

voltages:

$$V_B^{(1)} = E - Z_{32}^{(1)} I_2^{(1)}$$

$$120^\circ - j132 \times j6.36 \angle -90^\circ$$

$$V_B^{(1)} = 0.16 \angle 0^\circ \text{ p.u.}$$

$$V_B^{(1)} = 0.16 \times \frac{220}{\sqrt{3}} = 12.7 \angle 0^\circ \text{ kV}$$

at bus (3)

$$V_R = 2037 \angle 0^\circ \text{ kV}$$

$$V_Y = 2037 \angle -120^\circ \text{ kV}$$

$$V_B = 2037 \angle 120^\circ \text{ kV}$$

Numerical:

A (SLG) fault occurs at bus (3) find the fault current

$$I_f = I_3^{(1)} = \frac{E}{Z_{33} + Z_{33}^2 + Z_{33}^{(0)}}$$

$$\frac{220}{\sqrt{3}} \times \frac{1}{j0.154 + j0.154 + j0.105}$$

$$I_f = 7.26 \angle -90^\circ \text{ p.u.}$$

* P_2
 dead SC $\rightarrow$ no current flow through other.

$$P = \frac{V^2 \cos \phi}{V^2} \rightarrow P.U. \left/ \frac{2}{\cos 0} = 1.0 \text{ (value)} \right.$$

$$I_{pLG} = 7.26 \angle 260.43^\circ$$

$$I_{pLG} = 1905.4 \angle -90^\circ$$

Consideration of Prefault load current:

Using the load condition the first step being the calculation of internal emfs of G/R and M/R. When the fault occurs the two sources at the two ends will drive the current into fault. The following numerical is shown below:-


Numerical:

A single line G/R and M/R are rated at 30 MVA, 13.2 kV and both have subtransient reactance of 20%. The line connecting them has a reactance of 10% on base of machine rating. The M/R is drawing 20 MW at 0.8 lead at terminal voltage of 12.8 kV with a symmetrical when

3 ϕ fault occurs at the M/R terminals. Find subtransient fault current.

$$\text{Base KV} = 13.2 \text{ KV}$$

$$\text{Base MVA} = 30 \text{ MVA}$$

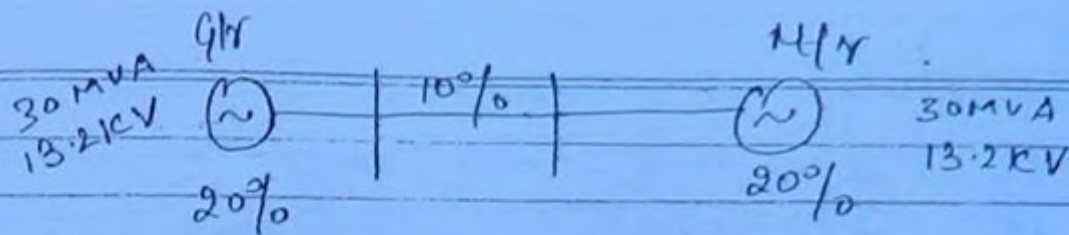

Power drawn by M/R = 20 MW at 12.8 kV, 0.8 pf

Active power = 20 MW $\Rightarrow P$

$$= \frac{20}{30} = 0.66 \text{ pu}$$

$$\text{Terminal voltage} = 12.8 \text{ kV} = \frac{12.8}{13.2} = 0.96 \text{ pu}$$

$$\cos \phi = 0.8$$


$$V_{pu} I_{pu} \cos \phi = P_{pu}$$

$$0.96 \times I_{pu} \times 0.8 = 0.66$$

$$I_{pu} = 0.86 \text{ pu}$$

$$I_{pu} = 0.86 \angle 36.86^\circ \text{ pu}$$
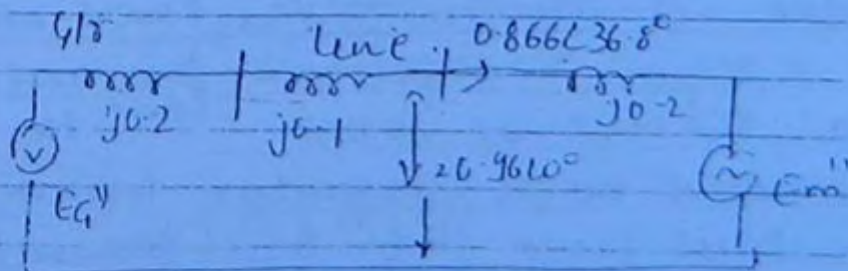
$$\text{Let } V = 0.96 \angle 0^\circ \text{ pu}$$




$$E_G'' = 0.96 \angle 0^\circ - 0.866 \angle 36.8^\circ \times 0.3 \angle 90^\circ$$

$$= 0.83 \angle 14.50^\circ$$

$$E_M'' = 0.96 \angle 0^\circ - 0.866 \angle 36.8^\circ \times 0.2 \angle 90^\circ$$

$$= 1.01 \angle -7.42^\circ$$

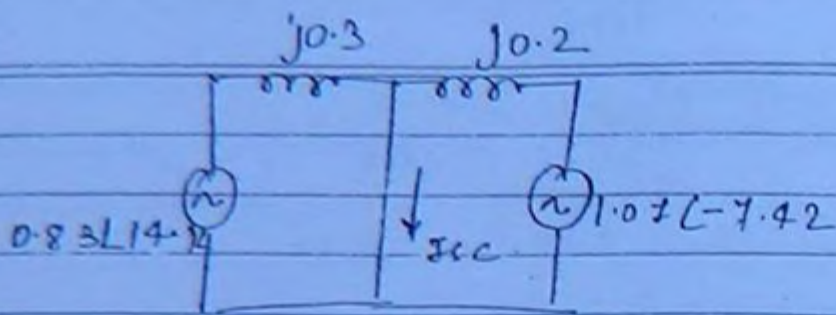

$$I_{sc} = I_{sc}^I + I_{sc}^{II}$$

$$= \left(\frac{0.83 \angle 14.54}{0.3 \angle 90^\circ} + \frac{1.07 \angle -7.4}{0.2 \angle 90^\circ} \right)$$

$$= 7.59 \angle 89.3^\circ$$

$$|I_{sc}| = \frac{7.59 \times 30 \times 10^3}{\sqrt{3} \times 13.2 \times 10^3}$$


$$= 7.59 \times 10.48$$

$$I_{sc} = 83.73 \text{ kA}$$

Numerical:

A 50 Hz alternator is rated 500 MVA, 20 kV with $x_d = 1 \text{ p.u.}$, $x_d' = 0.2 \text{ p.u.}$ It supplies a ~~pure~~ resistive load of ~~400~~ 400 MVA at 20 kV. ^{pure} The load is directly connected across generator terminal when a symmetrical fault on load terminal the initial rms current is,
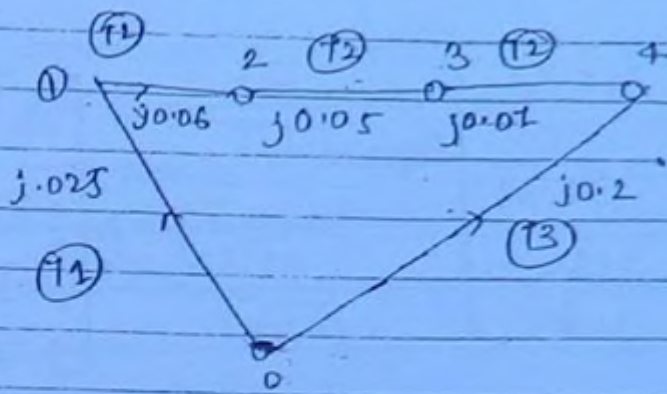
$$I_c = \frac{400 \times 10^6}{\sqrt{3} \times 20 \times 10^3} = 11547.00 \angle 0^\circ$$



Step 1

$$Z_{bus} = \begin{matrix} & (1) \\ (1) & j0.25 \end{matrix}$$

$$-1 \begin{bmatrix} j0.25 \\ j0.31 \\ j0.36 \end{bmatrix} \begin{bmatrix} j0.25 \\ j0.31 \\ j0.36 \end{bmatrix}$$

Z_{bus}

	(1)	(2)
1	$j0.25$	$j0.25$
(2)	$j0.25$	$j0.31 \quad (0.25+0.06)$

$Z_{bus} + Z_s$

$$Z_{bus, 2}$$

	(1)	(2)	(3)
(1)	$j0.25$	$j0.25$	$j0.25$
(2)	$j0.25$	$j0.31$	$j0.31$
(3)	$j0.25$	$j0.31$	$j0.36$

0.51
+ 0.5
0.36

$$Z_{bus, 2}$$


	(1)	(2)	(3)	4
(1)	$j0.25$	$j0.25$	$j0.25$	$j0.25$
(2)	$j0.25$	$j0.31$	$j0.31$	$j0.51$
(3)	$j0.25$	$j0.31$	$j0.36$	$j0.36$
4	$j0.25$	$j0.31$	$j0.36$	$j0.36 + j0.7$

$$\begin{bmatrix} j0.25 & j0.25 & j0.25 & j0.25 \\ j0.25 & j0.31 & j0.31 & j0.31 \\ j0.25 & j0.31 & j.36 & j.36 \\ j0.25 & j0.31 & j.36 & j.43 \end{bmatrix} \cdot \frac{1}{j0.43 + j0.2} \begin{bmatrix} j0.25 \\ j0.31 \\ j.36 \\ j.43 \end{bmatrix}$$

$$Z_{bus \text{ (old)}} = \frac{1}{j0.63} \begin{bmatrix} -j0.0625 & -0.0775 & -0.09 & -0.1075 \\ -0.0775 & -0.0961 & -0.1116 & -0.1333 \\ -0.09 & -0.1116 & -0.1236 & -0.1548 \\ -0.1075 & -0.1333 & -0.1548 & -0.1849 \end{bmatrix}$$

$$Z_{bus \text{ (new)}} = \begin{bmatrix} j0.15 & j0.12 & j0.107 & j0.079 \\ j0.1269 & j0.151 & j0.132 & j0.0984 \\ j0.107 & j0.132 & j0.154 & j0.114 \\ j0.076 & j0.098 & j0.114 & j0.136 \end{bmatrix}$$

Zero sequence:-

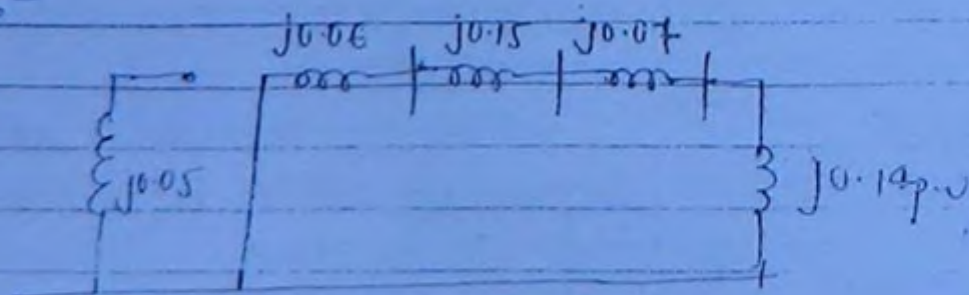


$$I_{base} = \frac{800 \times 10^6}{\sqrt{3} \times 20 \times 10^3}$$

$$14433.75 \text{ A}$$


$$I_{pu} = \frac{11547}{14433} = 0.8 \text{ p.u.}$$

Before fault:

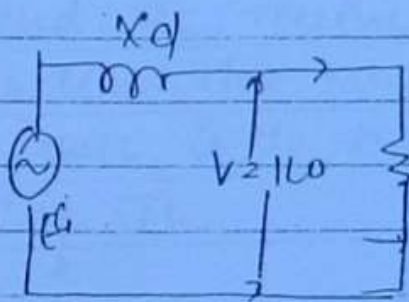


$$\text{Pre fault generate Emf} = \frac{110 + 0.8 \angle 0^\circ \times 12.90}{1.28 \angle 38.65^\circ \text{ p.u.}}$$

During short ckt

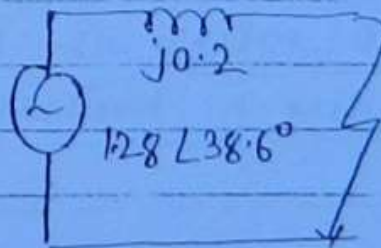

$$I_{sc}'' = \frac{1.28}{0.2} = 6.4$$
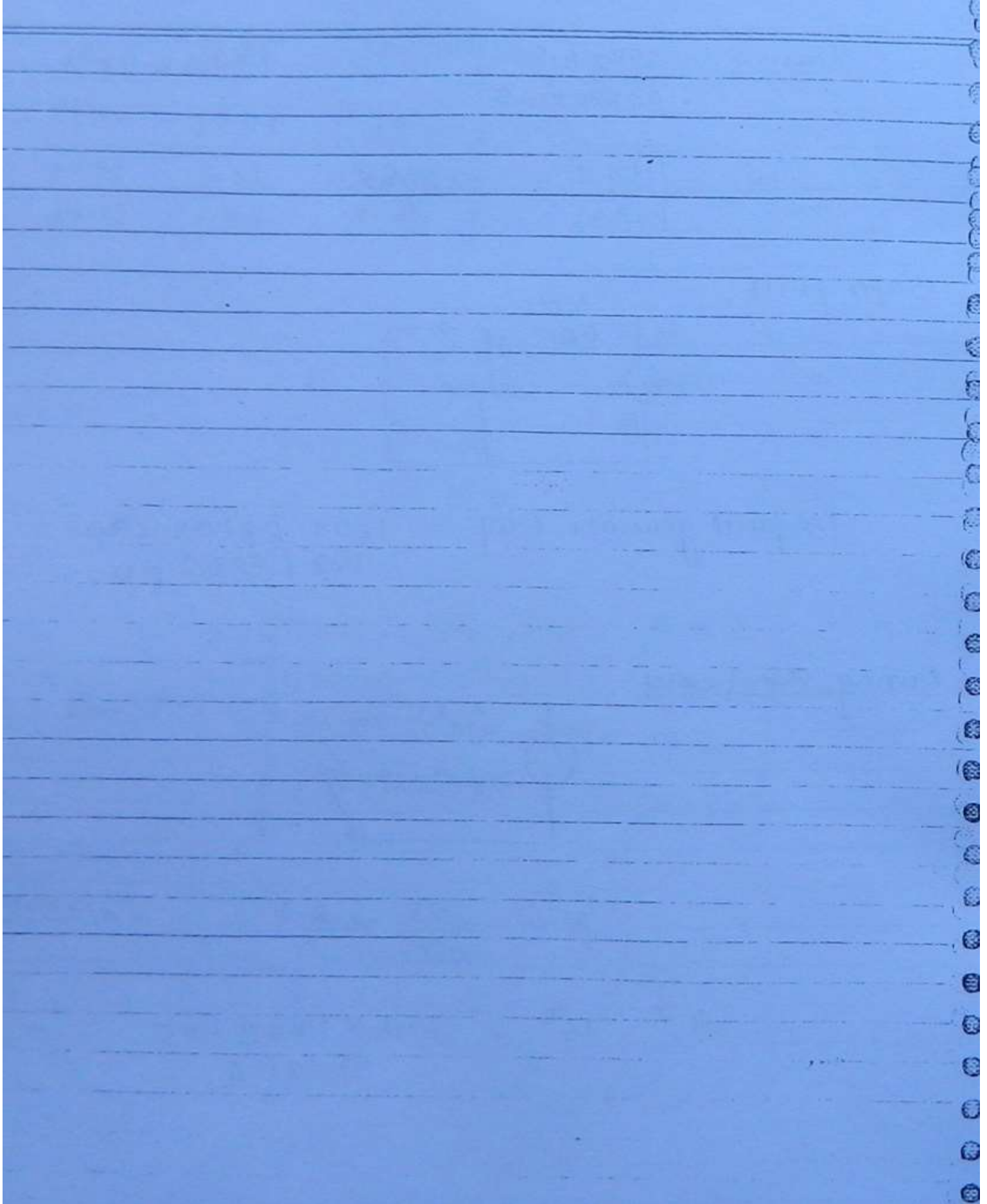
$$I_{sc}'' = 6.4 \times 14433.75 = 92.32 \text{ kA}$$



* Question:-

A 32KV single circuit 5 ϕ T.L has the ABC parameters

$$A = D = 1 \angle 0^\circ$$

$$B = 11.18 \angle 63.43^\circ$$

The T.L is to deliver 1.5 MVA at 0.85 p.f lagging at the load end. the receiving end voltage is 32KV line to line. How much active power and reactive power is to be dispatched from the sending end of T.L

Solution:-

The given data donot refer to load condenser method or source condenser method. $A = D$.

The parameter B refers to the impedance of T.L which is connected in series. therefore the given data refers to nominal π method.

$$V_R = 32 \text{KV line}$$

$$P_L = \sqrt{3} V_{LL} I_{LL} \cos \phi_L$$

$$Q_L = \sqrt{3} V_{LL} I_{LL} \sin \phi_L$$

$$V_S = AV_R + BI_R$$

$$= (1 \angle 0^\circ) \left(\frac{32000}{\sqrt{3}} \right) + (11.18 \angle 63.43^\circ) (155.2 \angle -31.7^\circ)$$

$$= 19111.4 \angle 2.34^\circ$$

$$V_{LL} = \sqrt{3} \times 19111.4 = 34.24 \text{KV}$$

$$V_A = \sqrt{3} V_{LL} I_{LL}$$

$$1.5 \times 10^6 = \sqrt{3} \times 32 \times 10^3 \times I$$

$$I_{LL} = 155.32 \text{A}$$

$$I_R = |I_R| \angle \phi_R = 155.2 \angle -31.7^\circ$$

$$AD - BC = 1$$

$$1 \times 1 - 11.8262.45 = 1$$

$$\Rightarrow \boxed{K=0}$$

$$\therefore CV_R + DI_R = I_S$$

$$\Rightarrow I_S = CV_R$$


$$I_S = 0. V_R + (120^\circ) (135.2 \angle -31.7^\circ)$$

$$135.2 \angle -31.7^\circ A$$

$$\boxed{I_S = 135.2 \angle -31.7^\circ A}$$

$$P_S = \sqrt{3} V_{LL} I_{SL} \cos \phi_S$$
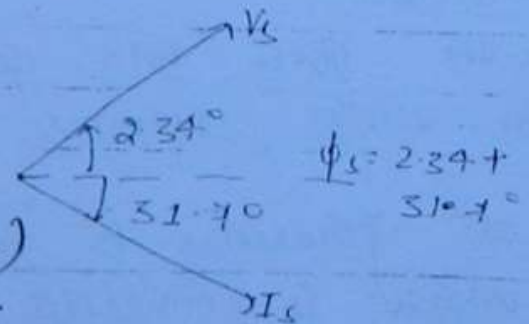
$$\sqrt{3} (34.24 \times 10^3) (135.2) (\cos 34.04^\circ)$$



$$P_S = 6.64 \text{ MW}$$

$$\text{Reactive power } Q_S = \sqrt{3} V_{LL} I_{SL} \sin \phi_S$$

$$\sqrt{3} (34.24 \times 10^3) (135.2) (\sin 34.04^\circ)$$

$$Q_S = 4.5 \text{ MVAR}$$

Power factor correction method is used to improve power factor of source

$$= \left[\begin{array}{cc|c} 1 & 1 & 1 \\ 1 & 3 & 6 \end{array} \right] \xrightarrow{[1+1]} \left[\begin{array}{cc|c} 1 & 1 & 1 \\ 2 & 4 & 7 \end{array} \right]$$


$$= \left[\begin{array}{cc|c} 1 & 1 & 1 \\ 1 & 3 & 6 \end{array} \right] \xrightarrow{2} \left[\begin{array}{cc|c} 1 & 1 & 1 \\ 0 & 2 & 5 \end{array} \right]$$

$$= \left[\begin{array}{cc|c} 1 & 1 & 1 \\ 1 & 3 & 6 \end{array} \right] \xrightarrow{1/6} \left[\begin{array}{cc|c} 1 & 1 & 1 \\ 0 & 2 & 5 \end{array} \right]$$


$$= \left[\begin{array}{cc|c} 0.83 & 0.5 & 0.5 \\ 0.5 & 0.33 & 1.5 \end{array} \right]$$

⇒ Type 4 modification :

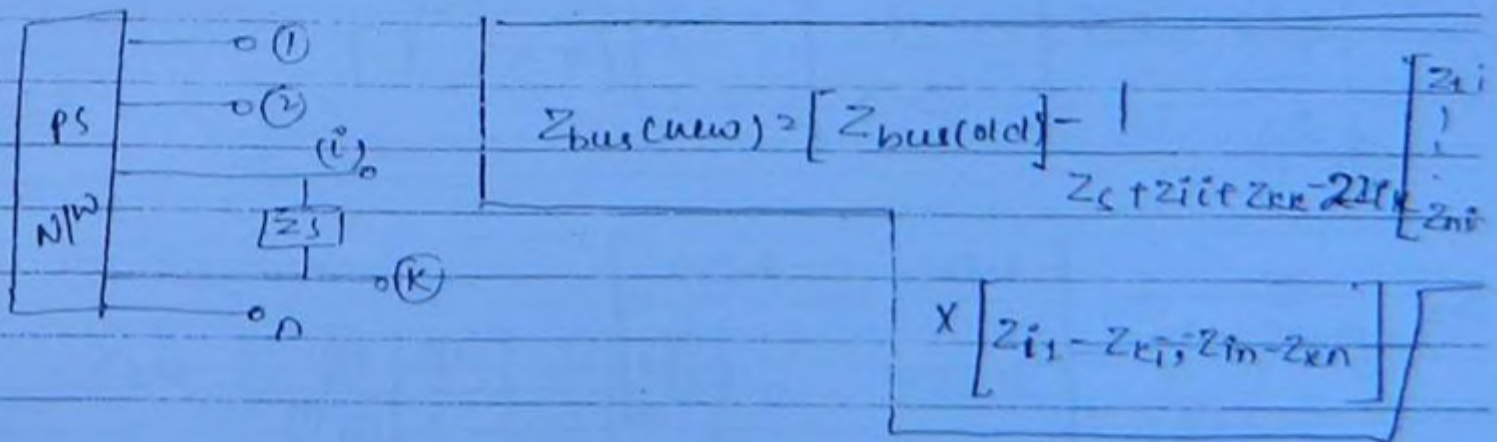An element with self impedance Z_s is added b/w old bus (i) and (k) (other than reference bus) :



Example

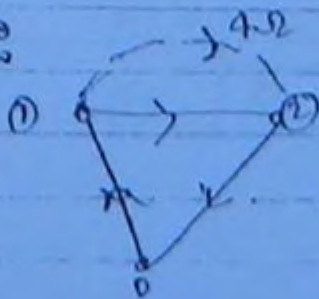

(5) 1
K=2

$$Z_{bus}(new) = \begin{bmatrix} 0.83 & 0.5 \\ 0.5 & 1.5 \end{bmatrix} - \frac{1}{4 + 0.83 + 1.5 - 2 \times 0.5} \begin{bmatrix} 0.83 & 0.5 \\ 0.5 & 1.5 \end{bmatrix}$$


$$\begin{bmatrix} Z_{11} - Z_{21} \\ Z_{21} - Z_{22} \end{bmatrix} \begin{bmatrix} Z_{11} - Z_{21} & Z_{12} - Z_{22} \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} 0.83 & 0.5 \\ 0.5 & 1.5 \end{bmatrix} - \frac{1}{4 + 0.83 + 1.5 - 2 \times 0.5} \begin{bmatrix} 0.83 - 0.5 & 0.5 - 1.5 \\ 0.5 - 1.5 & 1.5 - 0.5 \end{bmatrix} \begin{bmatrix} 0.83 & 0.5 \\ 0.5 & 1.5 \end{bmatrix}$$

$$= \begin{bmatrix} 0.83 & 0.5 \\ 0.5 & 1.5 \end{bmatrix} - 5.3 \begin{bmatrix} 0.33 & 1 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} 0.83 & 0.5 \\ 0.5 & 1.5 \end{bmatrix}$$


$$Z_{bus}(new) = \begin{bmatrix} 0.812 & 0.559 \\ 0.559 & 1.39 \end{bmatrix}$$

IES-Numerical.

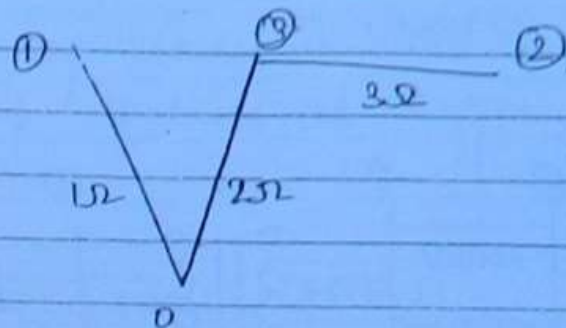

Step 1 :-


$$Z_{bus} = \begin{matrix} & \textcircled{1} \\ \textcircled{1} & \boxed{1\Omega} \end{matrix}$$

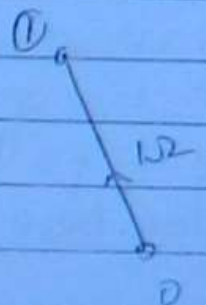

Type 1

Step 2 :-

$$Z_{bus} = \begin{matrix} & \textcircled{1} & \textcircled{3} \\ \textcircled{1} & 1\Omega & 0 \\ \textcircled{3} & 0 & 3\Omega \end{matrix}$$

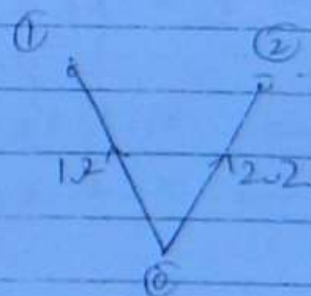


Type 1

Step 3 :-

$$K = 3$$


$$q = 2$$

$$Z_{bus} = \begin{matrix} & \textcircled{1} & \textcircled{2} & \textcircled{3} \\ \textcircled{1} & 1 & 0 & 0 \\ \textcircled{2} & 0 & 2 & 2 \\ \textcircled{3} & 0 & 2 & 5 \end{matrix}$$

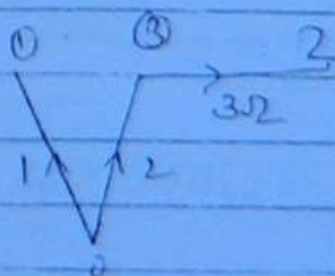

Type 2

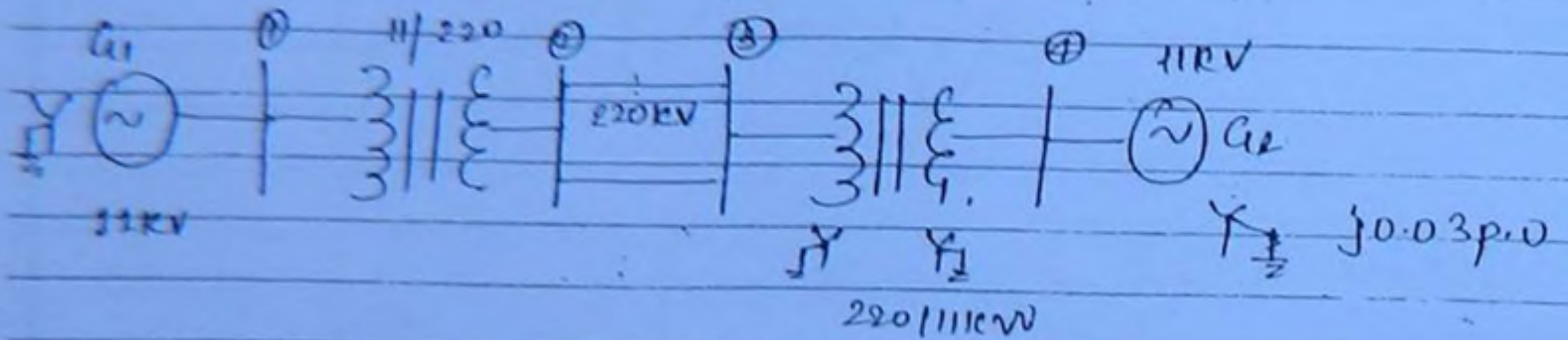Problem 2: for power s/m network shown form.
 $Z_{1 \text{ bus}}, Z_{2 \text{ bus}}, Z_{0 \text{ bus}}$.



Common base MVA = 100

$$G_1 \rightarrow X_1 = X_2 = j0.25, X_0 = j0.05 \text{ p.u.}$$

$$G_2 \rightarrow X_1 = X_2 = j0.2; X_0 = j0.05 \text{ p.u.}$$


$$T_1 \rightarrow X_1 = X_2 = X_0 = j0.06 \text{ p.u.}$$

$$T_2 \rightarrow X_1 = X_2 = X_0 = j0.07 \text{ p.u.}$$

$$L_{1,2} \rightarrow X_1 = X_2 = X_0 = j0.3$$

Solution

$\Rightarrow$ Positive Sequence n/w.


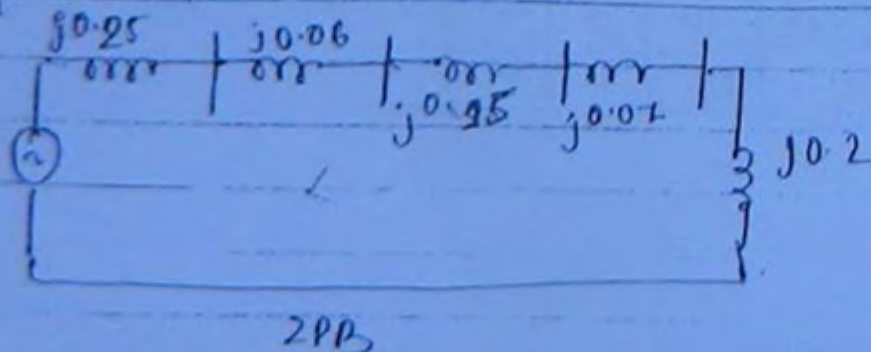


$$\frac{0.03}{2}$$

The four methods of Medium transmission line improve the p.f of line at different locatn? -

→ Long Transmission lines: (800km)

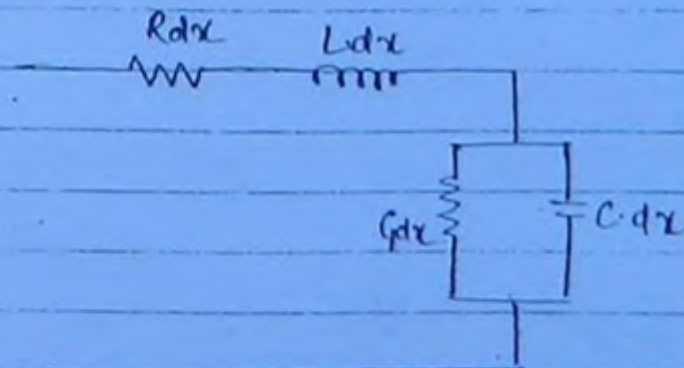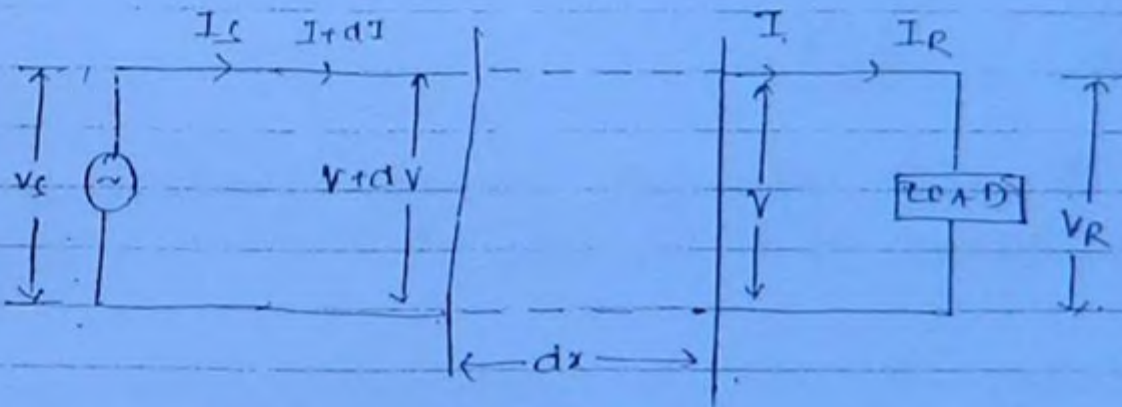On long transmission line capacitance is uniformly distributed through out the length of T.L. to determine the performance of long T.L consider a section (dx) of T.L.



$z \rightarrow$ impedance per unit length of T.L

$y \rightarrow$ shunt admittance per unit length of line.

$l \rightarrow$ total length of T.L.

$Z = z \cdot l \rightarrow$ series impedance for total length

$Y = y \cdot l \rightarrow$ shunt admittance for total length of line

Analysis of long transmission line:-

$$dv = I \cdot z dx$$

$$\frac{dv}{dx} = I \cdot z \quad \text{--- (1)}$$

$$dI = v \cdot y dx$$

$$\frac{dI}{dx} = v \cdot y \quad \text{--- (2)}$$

equation (1) and (2) represents voltage and current of the section dx of the line.

differentiating (1) wrt x

$$\frac{d^2v}{dx^2} = \frac{dI}{dx} \cdot z \quad \text{--- (3)}$$

Similarly

$$\frac{d^2I}{dx^2} = z \cdot y \cdot v \quad \text{--- (4)}$$

Equation 4 is second order differential equation.
the solution of equation (4) is

$$V = A e^{\sqrt{yz} \cdot x} + B e^{-\sqrt{yz} \cdot x} \quad \text{--- (5)}$$

A and B are unknown constants, which

⇒

$$V_L = V_R \left\{ A_1 + \frac{B_1(A_2 - A_1)}{B_1 + B_2} \right\} + \left(\frac{B_1 B_2}{B_1 + B_2} \right) I_R \quad \text{--- (C)}$$

Now,

$$I_S = I_{S1} + I_{S2}$$

$$I_S = G V_R + D_1 I_{R1} + C_2 V_R + D_2 I_{R2}$$

$$I_S = [C_1 + C_2] V_R + D_1 I_{R1} + D_2 [I_{R2} - I_{R1}]$$

$$I_S = [C_1 + C_2] V_R + [D_1 - D_2] I_{R1} + D_2 I_{R2} \quad \text{--- (D)}$$

substituting eqn (C) in (D).

$$I_S = (C_1 + C_2) V_R + D_2 I_R + (D_1 - D_2) \left\{ \frac{(A_2 - A_1) V_R + B_2 I_R}{B_1 + B_2} \right\}$$

$$I_S = \left(\frac{[C_1 + C_2] + (D_1 - D_2)(A_2 - A_1)}{B_1 + B_2} \right) V_R + \left(\frac{B_1 D_2 + B_2 D_1}{B_1 + B_2} \right) I_R$$

Question:-

A 50Hz T.L is 500km long. The parameters of the T.L are
 $R = 0.1 \Omega/\text{km}$; $X = 2 \text{ mH/km}$; $C = 0.01 \mu\text{F/km}$.

$G=0$, calculate the characteristic impedance and propagation constant of T.L

2π

$$Z_c = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \sqrt{0.1 + jx}$$

in per phase.

$$R = 0.1 \times 500 = 50 \Omega$$

$$L = 2 \times 10^{-3} \times 500 = 1 \text{ H}$$

$$C = 0.01 \times 10^{-6} \times 500 = 5 \times 10^{-6} \text{ F}$$

$$2\pi\omega f = 2 \times 3.14 \times 50$$

$\rightarrow$

$$Z_c = \sqrt{\frac{50 + j \times 2 \times \pi \times 50 \times 1}{0 + j \times 2 \times \pi \times 50 \times 5 \times 10^{-6}}} = \sqrt{\frac{Z/\phi}{Y/\phi}}$$

$$= \sqrt{\frac{514.96 \angle 80.95^\circ}{1570 \angle 90^\circ}} = 450.1 \angle -4.5^\circ$$

$$\gamma = \sqrt{ZY} = \sqrt{0.704 \angle 85.47^\circ}$$

Questⁿ:

- 2) A 66kV, 3- ϕ , 50Hz, 150km long T.L is open circuited at the receiving end, each conductor has resistance of $0.25\Omega/\text{km}$ and inductive reactance of $0.5\Omega/\text{km}$ and capacitive admittance to the neutral is $B_c = 4 \times 10^{-6} \text{ S/km}$.

- 1) Draw the nominal π equivalent ckt and indicate the value of each parameter.
- 2) Calculate the receiving end voltage if the sending end voltage is 66kV.

Solutⁿ

1) total impedance per phase $Z/\phi = R/\phi + jX/\phi$


$$= \left(\frac{0.25\Omega}{\text{km}} \times 150 + j \frac{0.5\Omega}{\text{km}} \times 150 \right)$$

$$Z/\phi = (37.5 + j75)\Omega$$

$$Y/\phi = G/\phi + jB/\phi$$

$$0 + j \frac{4 \times 10^{-6} \text{ S}}{\text{km}} \times 150$$

$$Y/\phi = j6 \times 10^{-4} \text{ S}$$

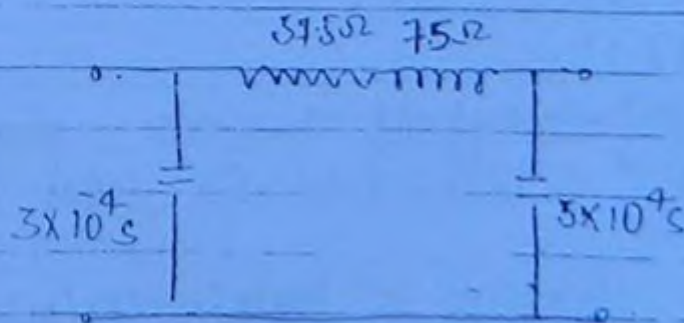

$$2) \quad I_R = 0$$

$$\Rightarrow V_S = A V_R + B I_R$$

$$V_S = A \cdot V_{RD}$$

$$V_{RD} = \frac{V_S}{A} = \frac{V_S}{1 + \frac{YZ}{2}}$$

$$V_{RD} \Rightarrow \frac{66 \times 10^3}{1 + \frac{(37.5 + j75)(j6 \times 10^{-4})}{2}}$$

$$V_{RD} = 67.5 \angle -0.66^\circ \text{ kV}$$

Questⁿ

Two identical 3- ϕ T.L are connected in parallel to supply a total load of 100 MW at 132 kV and 0.8 p.f (lag) at the receiving end. The ABCD parameters of each T.L are as follows


$$A = D = 0.98 \angle 1^\circ$$

$$B = 100 \angle 75^\circ \Omega$$

$$C = 5 \times 10^{-4} \angle 90^\circ$$

Determine the ABCD constants of combined n/w

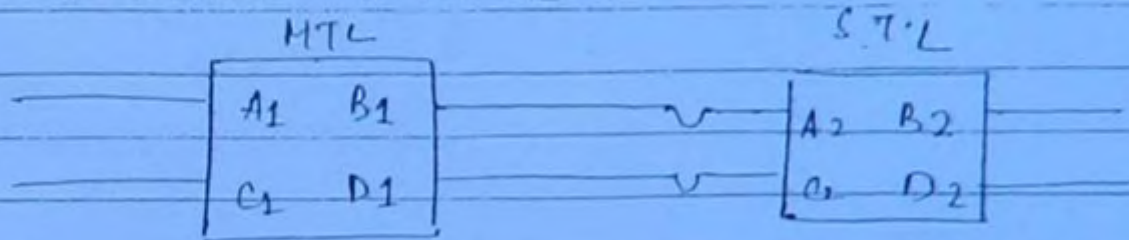6) A medium line π parameters ABCD is extended by connecting a short-line of impedance Z connected in series. The overall ABCD parameters of the series combination will be.



$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 + \frac{YZ}{2} & Z(1 + \frac{YZ}{4}) \\ Y & 1 + \frac{YZ}{2} \end{bmatrix} \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$

$$\begin{bmatrix} (1 + \frac{YZ}{2}) & Z(1 + \frac{YZ}{4}) + Z(1 + \frac{YZ}{2}) \\ Y & YZ + 1 + \frac{YZ}{2} \end{bmatrix}$$


7) A 220kV, 20km long 3 ϕ T.L has the following ABCD constant

$$A = D = 0.96 \angle 3^\circ$$

$$B = 55 \angle 65^\circ \Omega/\phi$$

$$C = 5 \times 10^{-4} \angle 80^\circ S/\phi$$

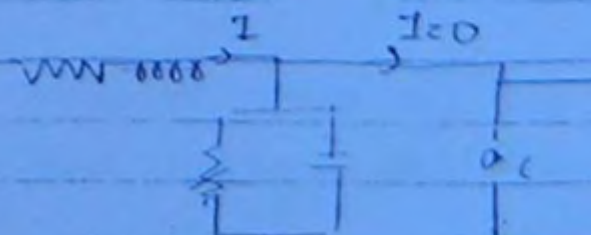The charging current per phase when a receiving end is open circuited is.



$$I_s = CV_R + DI_R$$


$$I_R = 0 \Rightarrow I_s = CV_R$$

$$5 \times 10^{-4} \times \left(\frac{220 \times 10^3}{\sqrt{3}} \right) = \frac{11}{\sqrt{3}} \text{ A.}$$

NOMINAL T AND π NETWORK FOR

LONG T.L.

condition 1: T network.

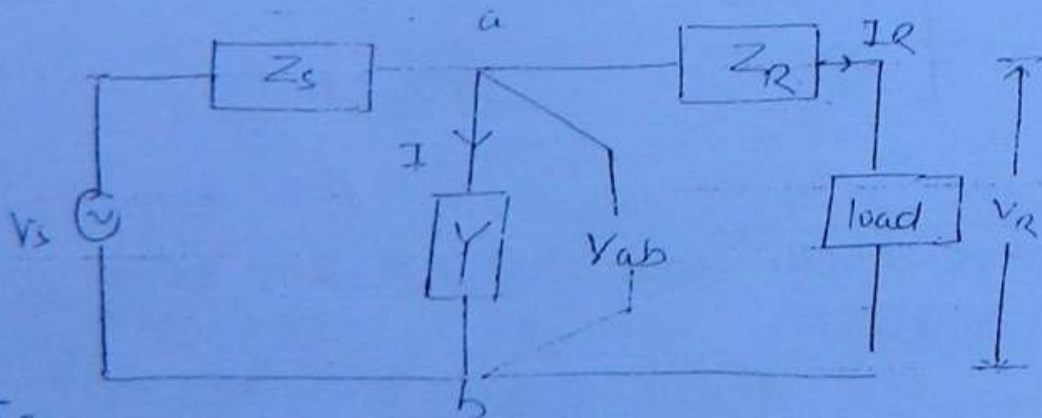

$$V_{ab} = V_R + Z_R I_R$$



$$I = Y V_{ab} = Y (V_R + Z_R I_R) = Y V_R + Y Z_R I_R$$

$$I_s = I + I_R = (Y V_R + Y Z_R I_R) + I_R$$


$$I_s = Y V_R + I_R (1 + Y Z_R) \quad \text{--- (1)}$$

$$A_0 \angle A_1 \angle A_2$$

$$D_0 \angle D_1 \angle D_2$$

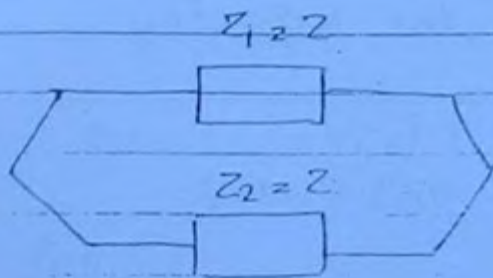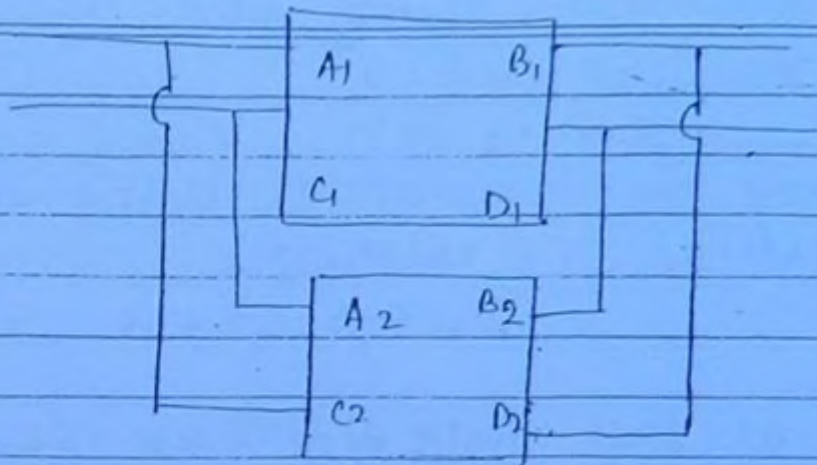
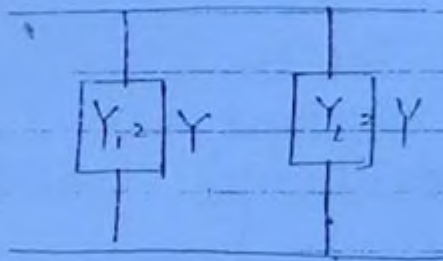
$$B_0 = \frac{Z}{2} \angle \frac{\theta}{2} = \frac{100}{2} \angle \frac{175.5^\circ}{2}$$



$$C_0 = Y_1 + Y_2 = 2Y = 2C = 2(5 \times 10^{-4} \angle 90^\circ)$$

$$10 \times 10^{-4} \angle 90^\circ$$

$$= 1.5 \times 10^{-4} \angle 90^\circ = 1.5 \times 10^{-4} \angle 90^\circ$$

$$0.98 \angle 1.2^\circ$$

$$6.1 \angle 1.2^\circ$$

Objective:

1) The surge impedance of 50km long TL is 50Ω so

for a length of 25km, the surge impedance is

→ surge impedance is independent of length

2) for long TL for a particular receiving end voltage, when the sending end voltage is calculated


it is more than the actual value when calculated by nominal π method.

As voltage drop in nominal π method is more than nominal π method.

- 2) the voltage is at both ends of T.L are 132 kV and its reactance is 40 Ω the capacity of line is.

$$\frac{33}{132 \times 132} \times 40 \Rightarrow 435.6 \text{ MW}$$

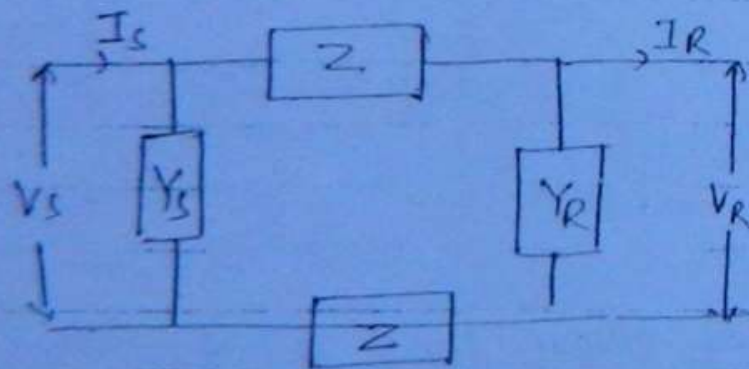- 3) the equivalent π n/w is given, if the T.L is short T.L then A, B, C, D constant are -



$$\begin{aligned} A &= 1 \\ B &= Z \\ C &= 0 \\ D &= 1 \end{aligned}$$

For any short T.L we get same value $\nearrow$

- 4) to increase the power transferred, the surge impedance must be decreases

from (1)

$$C = Y, \quad D = 1 + Y \cdot Z_R$$

$$V_s = V_R + I_s Z_s + I_R Z_R$$

$$V_s = V_R + \{ Y V_R + I_R (1 + Y Z_R) \} Z_s + I_R Z_R$$

$$V_s = (1 + Y Z_s) V_R + I_R (Z_s + Y Z_s Z_R + Z_R) \quad \text{--- (2)}$$

from (2)

$$A = 1 + Y Z_s, \quad B = Z_s + Z_R + Y Z_s Z_R$$

Condition 2: Symmetrical T-n/w

$$Z_s \rightarrow \frac{1}{2} Z_T, \quad Z_R \rightarrow \frac{1}{2} Z_T; \quad Y = Y_T$$


$$A = 1 + Y Z_s = 1 + \frac{Y_T Z_T}{2}$$

$$D = 1 + Y Z_R = 1 + \frac{Y_T Z_T}{2}$$

$$B = Z_s + Z_R + Y Z_s Z_R = \frac{1}{2} Z_T + \frac{1}{2} Z_T + Y_T \frac{Z_T}{2} \frac{Z_T}{2}$$

$$C = Y = Y_T$$

Condition 4: Nonlinear π network:-

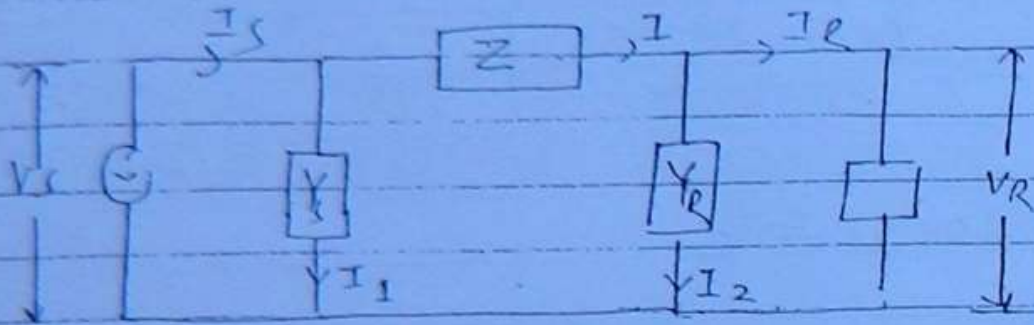

$$I_1 = Y_c V_c \quad \text{--- (1)}$$

$$I_2 = Y_R \cdot V_R \quad \text{--- (2)}$$

$$I = I_R + I_2 \quad \text{--- (3)}$$

$$I_R + Y_R \cdot V_R \quad \text{--- (5)}$$

$$I_s = I_1 + I$$

$$Y_c V_s + (I_R + V_R Y_R) \quad \text{--- (4)}$$

Now

$$V_s = V_R + IZ$$

$$V_R + (I_R + Y_R V_R) Z$$

$$V_R + I_R Z + V_R Y_R Z$$

$$V_s = V_R (1 + Z Y_R) + Z I_R \quad \text{--- (6)}$$

from eqn 5

$$\begin{cases} A = 1 + ZY_R \\ B = Z \end{cases}$$

substituting (5) $\rightarrow$ (4)

$$\begin{aligned} I_S &= Y_C \{ V_R (1 + ZY_R) + ZI_R \} + I_R + Y_R V_R \\ &= V_R (Y_C + ZY_C Y_R + Y_R) + I_R (1 + ZY_C) \end{aligned}$$

$$\therefore \begin{cases} C = Y_C + Y_C + ZY_C Y_R \\ D = 1 + ZY_C \end{cases}$$

symmetrical π -n/w:-

$$Z = Z_\pi, Y_C = \frac{Y_\pi}{2}, Y_R = \frac{Y_\pi}{2}$$

$$\begin{cases} A = 1 + Z, Y_R = 1 + Z_\pi \cdot \frac{Y_\pi}{2} \\ B = Z = Z_\pi \end{cases}$$

$$C = Y_C + Y_R + ZY_C Y_R$$


$$\frac{Y_\pi}{2} + \frac{Y_\pi}{2} + Z_\pi \frac{Y_\pi}{2} \frac{Y_\pi}{2}$$

$$C = \frac{Y_\pi + Z_\pi Y_\pi^2}{4}$$

$$D = 1 + ZY_C = 1 + Z_\pi \frac{Y_\pi}{2}$$

	T	π
A	$1 + YZ_c$	$1 + Y_e Z$
B	$Z_c Z_e + Z_c Z_e Y$	Z
C	Y	$Y_s + Y_e + Y_s Y_e Z$
D	$1 + YZ_e$	$1 + Y_s Z$

EQUIVALENT T-NETWORK OF LTL :

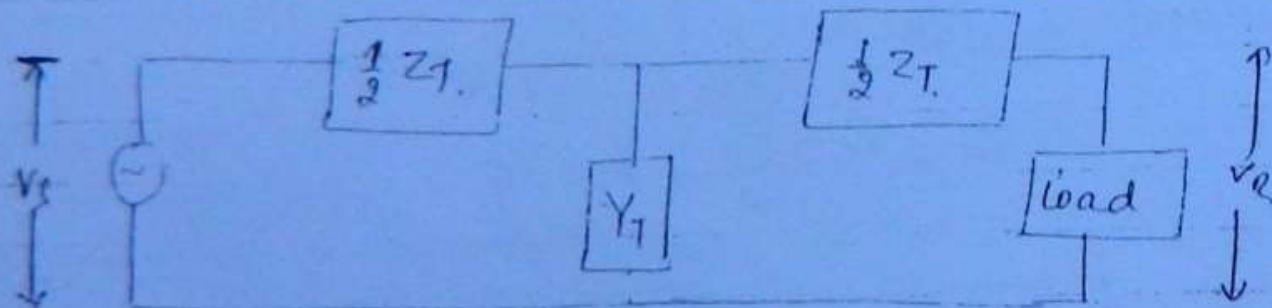

$$A = D = 1 + \frac{Y_T \cdot Z_T}{2}$$

$$(Z_T Y_T)$$

$$B = Z_T \left(1 + \frac{Y_T Z_T}{4} \right)$$

$$\frac{1}{2} Z_T = g$$

$$1 + \frac{Z_T Y_T}{2} = A$$

$$\Rightarrow \frac{Z_T Y_T}{2} = A - 1$$

$$\Rightarrow \frac{Z_T Y_T}{2} = \cosh \gamma x - 1$$

$$\frac{Z_T}{2} = \frac{\cosh \gamma x - 1}{Y_T}$$

$$\frac{Z_T}{2} = \frac{\cosh \gamma x - 1}{C} = \frac{\cosh \gamma x - 1}{\frac{1}{Z_c} \sinh \gamma x} = Z_c \frac{(\cosh \gamma x - 1)}{\sinh \gamma x}$$

$$\Rightarrow Z_c \frac{2 \sinh^2 \gamma x / 2}{2 \sinh \gamma x / 2 \cosh \gamma x / 2}$$


$$\frac{Z_T}{2} = Z_c \tanh \frac{\gamma x}{2}$$

we know that $Z_c = \sqrt{\frac{Z}{Y}} \Rightarrow \sqrt{\frac{Z \cdot Z}{Z Y}} = \frac{Z}{\sqrt{Y}}$

$$= \frac{Z \cdot x}{\gamma \cdot x} = \frac{\text{total series impedance (Z)}}{\gamma x}$$

$$\boxed{\frac{Z_T}{2} = \frac{Z}{2} \left(\frac{\tanh \gamma x / 2}{\frac{\gamma x}{2}} \right)} \quad \text{--- (1)}$$

EQUIVALENT π N/W.

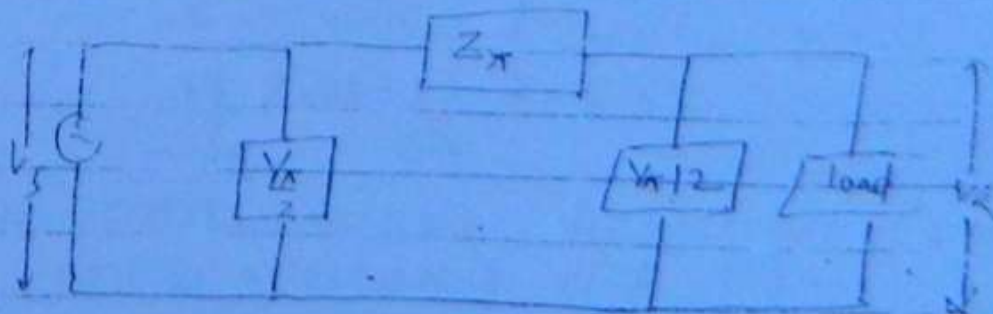

$$A = D = 1 + \frac{1}{2} Y_{\pi} Z_{\pi}$$

$$B = Z_{\pi}$$

$$C = Y_{\pi} \left\{ 1 + \frac{Y_{\pi} Z_{\pi}}{2} \right\}$$

to find :- $Z_{\pi} = ?$

$$\frac{Y_{\pi}}{2} = ?$$

$$1 + \frac{1}{2} Y_{\pi} Z_{\pi} = A$$

$$\frac{1}{2} Y_{\pi} Z_{\pi} = A - 1$$

$$\frac{Y_{\pi}}{2} = \frac{A-1}{B}$$

$$\frac{Y_{\pi}}{2} = \frac{\cosh \gamma x - 1}{Z_c \sinh \gamma x}$$

$$\frac{Y_{\pi}}{2} = \frac{1}{Z_c} \frac{2 \sinh^2 \gamma x / 2}{2 \sinh \gamma x \cosh \gamma x / 2}$$

$$\frac{Y_{\pi}}{2} = \frac{1}{Z_c} \tanh \frac{\gamma x}{2}$$

$$Z_c = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{Z \cdot Y}{Y \cdot Y}} = \frac{Y}{Y}$$


$$\cancel{Y \cdot X} \text{ by } \frac{Y \cdot X}{Y \cdot X} = \frac{Y \cdot X}{Y} = \frac{YX/2}{Y/2}$$

$$\frac{YX}{2} = \frac{1}{YX/2 / Y/2} \tanh \frac{YX}{2}$$

$$\boxed{\frac{YX}{2} = \frac{Y}{2} \left(\frac{\tanh \frac{YX}{2}}{YX/2} \right)}$$

CONCEPT OF TRAVELLING WAVES:

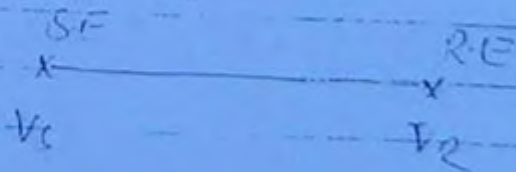• Voltage and current travels in the form of waves from sending end to the receiving end of T.L in form of waves



SE $\rightarrow$ RE is called Incident wave
 $V, I \rightarrow V = Z_c I$

• Voltage wave and current wave travels gradually from sending end to receiving end.

- The voltage wave and current wave travelling from sending end to receiving end through T.L are reflected back in T.L when $Z_L \neq Z_c$

- The voltage wave and current wave reflected back into T.L are known as reflected voltage wave V' and reflected current I'

$$I' = - \frac{V'}{Z_c} \quad (\text{---ve as reflected wave})$$

- The voltage wave and current wave travelling through the load are known as Transmitted or refracted voltage wave (V'') and current wave (I'')

$$I'' = \frac{V''}{Z_L}$$

- Reflection does not occur when Z_L equals Z_c .

$$Z_L = Z_c$$

$$\begin{aligned} V'' &= V + V' \\ I'' &= I + I' \end{aligned}$$

Travelling Waves:

Condition 1: 'R'

receiving end of T.L terminated by resistance



$$V'' = V + V'$$

$$I'' = I + I'$$

$$I = V/Z_c$$

$$I' = -V'/Z_c$$

$$I'' = V''/R$$

$$V'' \rightarrow V, \quad V' \rightarrow V$$

Expressing transmitted voltage V'' in terms of incident voltage V and transmitted current I'' in terms of incident current I .

$$\Rightarrow V''/R = \frac{+V}{Z_c} + \left(\frac{-V'}{Z_c} \right)$$

replacing V' by $(V'' - V)$

$$V''/R = \left(\frac{+V}{Z_c} \right) + \left(\frac{V'' - V}{Z_c} \right)$$

$$\frac{V''}{R} \left[\frac{1}{R} + \frac{1}{Z_c} \right] = \frac{2V}{Z_c}$$

$$V'' = V \cdot \left[\frac{2R}{R+Z_c} \right] \quad \text{--- (1)}$$

• Transmitted voltage co-efficient $T_V = \frac{V''}{V} = \frac{2R}{R+Z_c}$

Similarly from eqⁿ (2)

$$I'' R' = I Z_c \left(\frac{2R'}{R+Z_c} \right)$$

$$I'' = I \left(\frac{2Z_c}{R+Z_c} \right)$$

• Transmitted current coefficient

$$T_I = \frac{I''}{I} = \frac{2Z_c}{R+Z_c}$$

Expressing reflected voltage (V') in terms of incident voltage (V) and reflected current (I') in terms of incident current (I).

$$\frac{V''}{R} = \frac{+V}{Z_c} + \frac{(-V')}{Z_c}$$

$$\frac{V+V'}{R} = \frac{+V}{Z_c} + \frac{(-V')}{Z_c}$$

$$V \left[\frac{1}{R} - \frac{1}{Z_c} \right] = -V' \left[\frac{1}{R} + \frac{1}{Z_c} \right]$$

$$\cancel{Z_c} R \quad V \left[\frac{Z_c - R}{R \cancel{Z_c}} \right] = -V' \left[\frac{R + \cancel{Z_c}}{R \cdot \cancel{Z_c}} \right] \dots (2)$$

- reflection coefficient of voltage $\left[\rho_v = \frac{V'}{V} = \frac{R - Z_c}{R + Z_c} \right]$

similarly using eqn (2)

$$V' = V \left(\frac{R - Z_c}{R + Z_c} \right)$$

$$-I' \cancel{Z_c} = I \cancel{Z_c} \left(\frac{R - \cancel{Z_c}}{R + \cancel{Z_c}} \right)$$

- reflection coefficient of current $\left[\rho_i = \frac{I'}{I} = \frac{Z_c - R}{Z_c + R} \right]$

$\tau_v =$	$\frac{2R}{Z_c + R}$
$\tau_i =$	$\frac{2Z_c}{Z_c + R}$
$\rho_v =$	$\frac{R - Z_c}{Z_c + R}$
$\rho_i =$ (c)	$\frac{Z_c - R}{Z_c + R}$

Condition 2: Receiving end of T.L terminated by underground cable with impedance (Z_2).


$$\bullet T_V = \frac{2Z_1}{Z_c + Z_1} \rightarrow \text{replace } R \text{ by } Z_1$$

$$\bullet T_I = \frac{2Z_c}{Z_c + Z_1}$$

$$\bullet \rho_V = \frac{Z_1 - Z_c}{Z_c + Z_1}$$

$$\bullet \rho_I = \frac{Z_c - Z_1}{Z_c + Z_1}$$

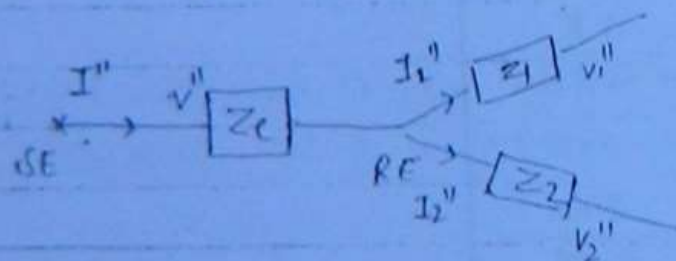Condition 3: Receiving end of T.L line forming a T junction.



+ Z_1, Z_2 connected in parallel.

$$V_1'' = V_2'' = V''$$

$$I'' = I_1'' + I_2''$$

$$\Rightarrow I'' = I + I'$$

$$\Rightarrow I_1'' + I_2'' = I + I'$$

Expressing transmitted voltage (V'') in terms of incident voltage (V), and transmitted current (I'') in terms of incident current (I):-

$$I_1'' + I_2'' = I + I'$$

$$\Rightarrow \frac{V_1''}{Z_1} + \frac{V_2''}{Z_2} = \frac{V}{Z_c} + \left(\frac{-V'}{Z_c} \right)$$

$$\Rightarrow \frac{V''}{Z_1} + \frac{V''}{Z_2} = \frac{V}{Z_c} - \frac{V'}{Z_c}$$

$$\Rightarrow V'' \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right) = \frac{V}{Z_c} - \frac{V'}{Z_c}$$

$$\Rightarrow V'' \left[\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_c} \right] = \frac{2V}{Z_c}$$

$$V'' = V \frac{(2/Z_c)}{\left[\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_c} \right]} \quad \text{--- (1)}$$

Transmitted
• reflection coefficient of voltage

$$T_V = \frac{V''}{V} = \frac{2/Z_c}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_c}}$$

now using equatⁿ (1)

$$I'' Z_1 = I \cancel{Z_c} \frac{(2/Z_c)}{\left[\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_c} \right]}$$

• Transmitted coefficient of current $\tau_1 = \frac{I_1''}{I} = \frac{2/Z_1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_c}}$

$\therefore \tau_{I_2} = \frac{I_2''}{I} = \frac{2/Z_2}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_c}}$

• Expressing reflected voltage in terms of incident voltage and reflected current in terms of incident current

$$I_1'' + I_2'' = I_0 + I'$$

$$\Rightarrow \frac{V_1''}{Z_1} + \frac{V_2''}{Z_2} = \frac{V}{Z_c} + \left(\frac{-V'}{Z_c} \right)$$

$$\frac{V''}{Z_1} + \frac{V''}{Z_2} = \frac{V}{Z_c} - \frac{V'}{Z_c}$$

$$\Rightarrow V'' \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right) = \frac{V}{Z_c} - \frac{V'}{Z_c}$$

$$\Rightarrow (V + V') \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right) = \frac{V}{Z_c} - \frac{V'}{Z_c}$$

$$\Rightarrow V \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_c} \right) = \frac{V}{Z_c} - \frac{V'}{Z_c} = \frac{V}{Z_2}$$

$$\Rightarrow V' = V \left(\frac{\frac{1}{Z_c} - \frac{1}{Z_1} - \frac{1}{Z_2}}{\left(\frac{1}{Z_c} + \frac{1}{Z_1} + \frac{1}{Z_2} \right)} \right) \quad \text{--- eqn (a)}$$

• reflected coefficient of voltage $\boxed{\rho_v = \frac{V'}{V} = \left[\frac{\frac{1}{Z_c} - \frac{1}{Z_1} - \frac{1}{Z_2}}{\frac{1}{Z_c} + \frac{1}{Z_1} + \frac{1}{Z_2}} \right]}$

Similarly: from eqn (a)

$$-I' \cdot Z_c = I \cdot Z_c \left(\frac{\frac{1}{Z_c} - \frac{1}{Z_1} - \frac{1}{Z_2}}{\left(\frac{1}{Z_c} + \frac{1}{Z_1} + \frac{1}{Z_2} \right)} \right)$$

$$\Rightarrow I' = I \left(\frac{\frac{1}{Z_1} + \frac{1}{Z_2} - \frac{1}{Z_c}}{\left(\frac{1}{Z_c} + \frac{1}{Z_1} + \frac{1}{Z_2} \right)} \right)$$

• reflected coefficient of current $\boxed{\rho_i = \frac{I'}{I} = \left[\frac{\frac{1}{Z_1} + \frac{1}{Z_2} - \frac{1}{Z_c}}{\frac{1}{Z_c} + \frac{1}{Z_1} + \frac{1}{Z_2}} \right]}$


$$\tau_v = \left(\frac{2/Z_c}{\left(\frac{1}{Z_c} + \frac{1}{Z_1} + \frac{1}{Z_2} \right)} \right)$$

$$\tau_i = \left(\frac{2/Z_1 \text{ or } 2/Z_2}{\left(\frac{1}{Z_c} + \frac{1}{Z_1} + \frac{1}{Z_2} \right)} \right)$$

$$\rho_v = \left(\frac{\frac{1}{Z_c} - \frac{1}{Z_1} - \frac{1}{Z_2}}{\left(\frac{1}{Z_c} + \frac{1}{Z_1} + \frac{1}{Z_2} \right)} \right)$$

$$\rho_i = \left(\frac{\frac{1}{Z_1} + \frac{1}{Z_2} - \frac{1}{Z_c}}{\left(\frac{1}{Z_c} + \frac{1}{Z_1} + \frac{1}{Z_2} \right)} \right)$$

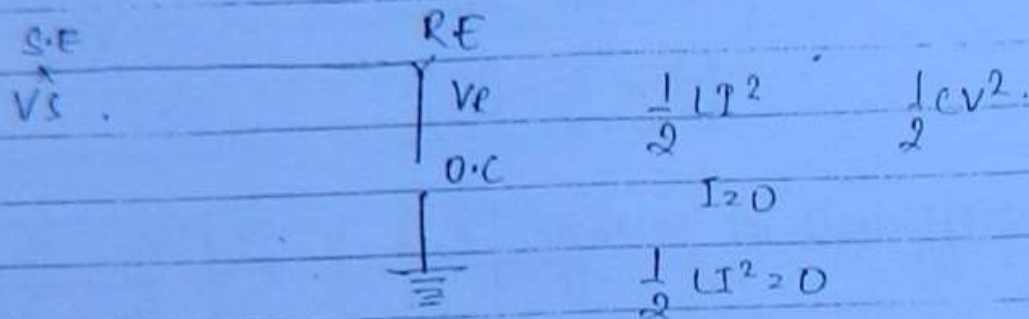Ans
Condition 4: Receiving end of T.L is open circuited.



When the receiving end of T.L is open circuited ($I = 0$).
Electromagnetic energy stored by inductor in magnetic field is equal. $\left[\frac{1}{2} LI^2 = 0 \right]$.

According to law of conservation of energy, energy cannot be destroyed but only can be converted from one form to another form. i.e. the entire electromagnetic energy is converted into electrostatic energy stored by capacitor in the electric field.

The increase in electrostatic energy increases the voltage. Let the voltage be increased by 'e' volts.

$$V \rightarrow 'e' \text{ volts.}$$

$$\text{so } \frac{1}{2} LI^2 = \frac{1}{2} Ce^2$$

$$I^2 = e^2 / LC$$


$$I^2 = e^2 / Z_c^2$$

incident current
↓
1

$$P = I^2 Z_c^2$$

$$P = I \cdot Z_c = V$$

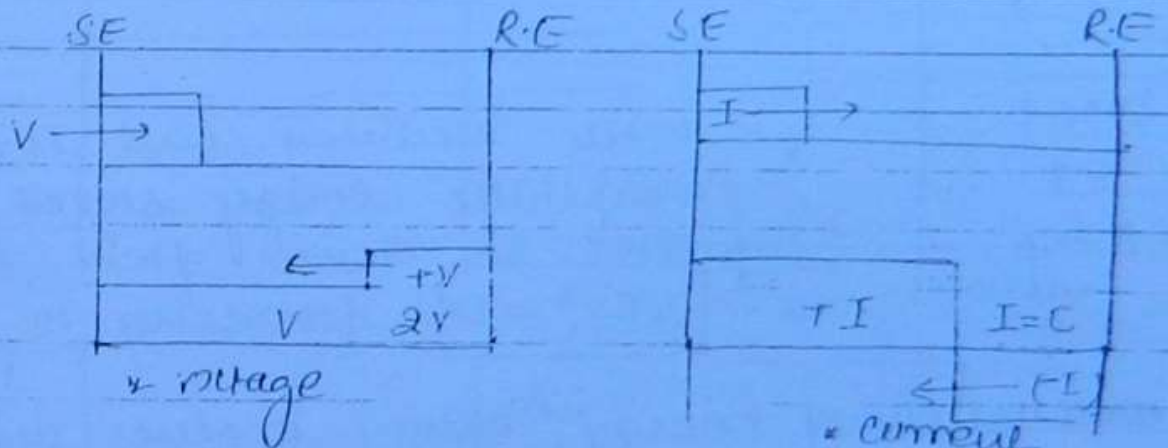when the receiving end is open circuit the voltage is increased by 'V' where V is incident or voltage at sending end.



reflection coefficient $\rho_v = +V/V = 1$

1 - - when receiving end is O.C

reflection coefficient $\rho_i = \frac{-I}{I} = -1$

$$T_v = \frac{V''}{V} = \frac{V' + V}{V} = \frac{V + V}{V} = 2$$


$$T_v = 2$$

$$T_i = \frac{0}{I} = 0$$

$$T_i = 0$$

Condition 5: Receiving end to T.L short-circuited.

SE
V_c

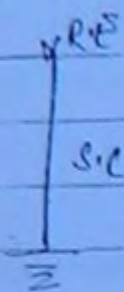

V=0

$$\frac{1}{2} LI^2, \quad \frac{1}{2} CV^2 \rightarrow 0$$

$$\frac{1}{2} LI^2$$

EME ↑

I ↑

1 Amp

when receiving end is S.C $V=0$,
electrostatic energy stored by
capacitor in electric field is equal
to $\boxed{\frac{1}{2} CV^2 = 0}$. According to law

of conservation of energy, energy is never destroy
but only is converted from one form to another
form. i.e. entire electrostatic energy is
converted into electromagnetic energy. As a
result electromagnetic energy increases and current
increase.



Let the current be increased by (1 Amp)

$$\frac{1}{2} LI^2 = \frac{1}{2} CV^2$$

$$\Rightarrow I^2 = \frac{V^2}{L/C} = \frac{V^2}{Z_c^2}$$

$$\boxed{I = \frac{V}{Z_c} = I}$$

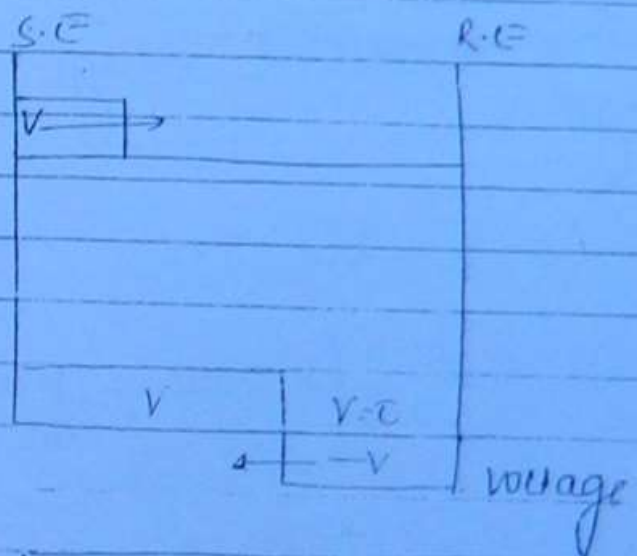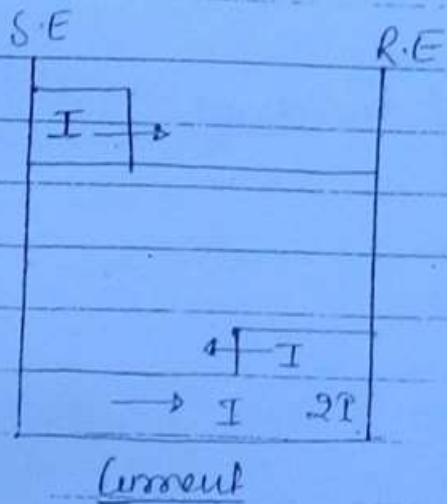The current i increases by I Amp, where I is incident current or current flowing from sending end to the receiving end of the T.L.




$$S_I = \frac{I}{I} = 1$$

$$T_I = \frac{2I}{I} = 2$$

$$S_V = \frac{-V}{V} = -1$$

$$T_V = \frac{0}{V} = 0$$

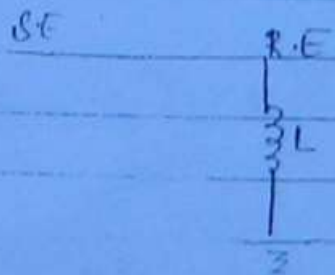Condition 6: Receiving end of T.L is terminated by inductor 'L'



$$V'' = V + V'$$

$$I'' = I + I'$$

$$I = V/Z_c \quad ; \quad I' = -V'/Z_c$$

$$I'' = \frac{1}{L} \int V''(t) dt$$

Expressing transmitted voltage in terms of incident voltage V

$$I'' = I + I'$$

$$\Rightarrow \frac{1}{L} \int V''(t) dt = \frac{V}{Z_c} + \frac{(-V')}{Z_c}$$

$$\Rightarrow \frac{1}{L} \int V''(t) dt = \frac{V}{Z_c} - \left(\frac{V'' - V}{Z_c} \right)$$

$$\Rightarrow \frac{1}{L} \int V''(t) dt \cdot = \frac{2V}{Z_c} - \frac{V''}{Z_c}$$

$$\Rightarrow \frac{1}{L} \int V''(t) dt + \frac{V''}{Z_c} = \frac{2V}{Z_c}$$

Applying Laplace Transform.

$$\frac{1}{L} \left\{ \frac{V''(s)}{s} \right\} + \frac{V''(s)}{Z_c} = \frac{2V}{sZ_c}$$

$$V''(s) \left[\frac{1}{sL} + \frac{1}{Z_c} \right] = \frac{2V}{sZ_c}$$

$$\Rightarrow V''(s) \cdot \left\{ \frac{sL + Z_c}{sL Z_c} \right\} = \frac{2V}{sZ_c}$$

$$V''(s) = \frac{2VL}{sL + Z_c}$$

dividing by L.


$$V''(s) = \frac{2V}{s + \frac{Z_c}{L}}$$

Applying inverse laplace transform.

$$\Rightarrow V''(t) = 2V \cdot e^{-Z_c/L \cdot t}$$

when T.L is terminated by inductor the incident transmitted voltage decreases exponentially due to presence of inductor.

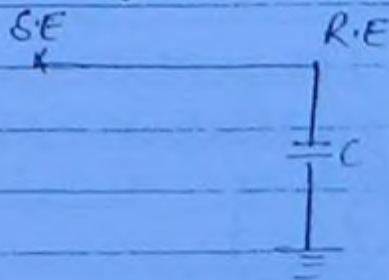condition 2: Receiving end of T.L terminated by capacitance



$$V'' = V + V'$$

$$I'' = I + I'$$

$$I = V/Z_c ; I' = -V'/Z_c$$

$$I'' = C \frac{dV''(t)}{dt}$$

$$I + I' = C \frac{dV''(t)}{dt}$$

$$\frac{V}{Z_c} = \frac{V'}{Z_c} = C \frac{dV''(t)}{dt} \Rightarrow \frac{C dV''(t)}{dt} + \frac{V''(t)}{Z_c} = \frac{2V}{Z_c}$$

applying Laplace transform

$$\frac{V(s)}{Z_c} - \frac{V'(s)}{Z_c} = \frac{C}{s}$$

$$\Rightarrow C \left\{ sV''(s) \right\} + \frac{V''(s)}{Z_c} = \frac{2V}{sZ_c}$$

$$\Rightarrow V''(s) \left\{ \frac{Cs + 1}{Z_c} \right\} = \frac{2V}{sZ_c}$$

$$\Rightarrow V''(s) \left\{ \frac{sCs + 1}{Z_c} \right\} = \frac{2V}{sZ_c}$$

$$\Rightarrow V''(s) = \frac{2V}{s(sCs + 1)}$$

dividing by CZ_c

$$V''(s) = \frac{2V/CZ_c}{s(s + \frac{1}{CZ_c})}$$

using partial fraction

$$A \cdot \frac{1}{Cs} = \frac{2V}{Cs}$$

$$A = 2V$$

$$'s': A + B = 0$$

$$B = -A = -2V$$

$$V''(s) = \frac{2V}{s} - \frac{2V}{s + \frac{1}{CZ}}$$

Applying inverse Laplace Transform:-

$$V''(t) = 2V - 2V \cdot e^{-1/CZ \cdot t}$$

$$V''(t) = 2V \left\{ 1 - e^{-1/CZ \cdot t} \right\} \text{ volt}$$

due to discharging effect.

When T.L. terminated by capacitor is decrease exponentially.

Quesⁿ:

An inductance of 800mH connect two section of T.L each having surge impedance of 350Ω. A 500

A 500kV, 2μsec rectangular surge travels along the line towards the inductance. The max^m value of transmitted wave is. $V'' = 2V e^{-Z_0/L \cdot t}$

$$V'' = 2V \cdot 500V \cdot e^{-\left(\frac{350}{800 \times 10^{-6}}\right) (2 \times 10^{-6})}$$

$$V'' = 416.86kV$$

2) A 500kV, 243cc rectangular wave surge on T.L having surge impedance of 500 Ω approaches a generating statⁿ at which the concentrated earth capacitance is 3000pF. The max^m value of the transmitted wave is

V

$$V'' = 2V \left(1 - e^{-t/\tau_c} \right)$$

$$V'' = 2 \times 500 \left[1 - e^{-\left(2 \times 10^{-6} / 350 \times 3000 \times 10^{-12} \right)} \right]$$

$$V'' = 850 \text{ kV}$$

3) A voltage surge of 60kV travelling in a line of natural impedance 500 Ω , arrives at a junction with two T.L of impedance, 650 Ω , 250 Ω . The surge voltages and current transmitted into each branch of line or ar?

$$Z_c = 500 \Omega$$

$$Z_1 = 650, \quad Z_2 = 250$$

$$V'' = V \left(\frac{2/Z_c}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_1}} \right)$$

$$V'' = 31.24 \text{ kV}$$

$$I_1'' = \frac{V_1''}{Z_1} = \frac{31.84 \times 10^3}{650} = 48.97 \text{ Amp.}$$

$$I_2'' = \frac{V_2''}{Z_2} = \frac{31.84 \times 10^3}{250} = 127.4 \text{ Amp}$$

- 4) A voltage surge of 15KV travels along a cable towards a junction with an over-head T.L. The inductance and capacitance of overhead T.L. cable are 0.3mH, 0.4uF. The inductance and capacitance of over head T.L. are 1.5mH, and 0.12uF. The increase in voltage at the junction due to surge is?

$$Z_{\text{cable}} = \sqrt{\frac{L}{C}} = \sqrt{\frac{0.3 \times 10^{-3}}{0.4 \times 10^{-6}}} = 27.38 \Omega$$

$$Z_{\text{O.H.L.}} = \sqrt{\frac{1.5 \times 10^{-3}}{0.12 \times 10^{-6}}} = 353 \Omega$$

$$V'' = \frac{2R}{Z_1 + R} \Rightarrow \frac{2Z_{\text{cable}}}{Z_1 + Z_{\text{cable}}} \text{ as surge travel through cable}$$

$$\frac{2 \times 27.38}{353 + 27.38} \cdot 15 \times 10^3 = \begin{matrix} 2048 \text{KV} \\ 2159.4 \text{V} \\ 21.84 \text{KV} \end{matrix}$$

A- 3 ϕ overhead conductors in equilateral configuration the characteristic impedance is Z_0 . What should be load impedance show that reflections do not occur in T.L.


TELEGRAPHER | WAVE EQUATION :-

$$\frac{\partial^2 e}{\partial x^2} = RGe + (RC + LG) \frac{\partial e}{\partial t} + LC \frac{\partial^2 e}{\partial t^2}$$

$$\frac{\partial^2 i}{\partial x^2} = RG i + (RC + LG) \frac{\partial i}{\partial t} + LC \frac{\partial^2 i}{\partial t^2}$$

POWER CIRCLE DIAGRAMS:

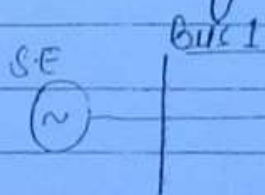
Consider the single line diagram of 3 ϕ T.L



$$V_s, I_s$$

$$S_s = P_s + jQ_s$$

$$\text{Bus 1} \rightarrow \text{SEB}$$

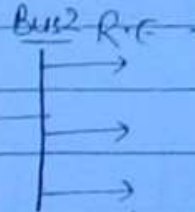

$$V_R, I_R$$

$$S_R = P_R + jQ_R$$

$$\text{Bus 2} \rightarrow \text{REB}$$

In single-line diagram bus 1 is fed by generating station and bus 2 feeds the load connected at receiving end.

Expressing I_R and I_s in terms of V_R and V_s .

$$I_s = CV_R + DI_R$$

$$I_R = \frac{I_s}{D} - \frac{CV_R}{D}$$

from the two port n/w model.

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$\Rightarrow V_s = AV_r + BI_r \quad \text{--- (1)}$$

$$I_s = CV_r + DI_r \quad \text{--- (2)}$$

$$\begin{bmatrix} V_r \\ I_r \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}^{-1} \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$

$$= \begin{bmatrix} V_r \\ I_r \end{bmatrix} = \frac{1}{AD-BC} \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$

$$\begin{bmatrix} V_r \\ I_r \end{bmatrix} = \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$

$$V_r = DV_s - BI_s \quad \text{--- (3)}$$

$$I_r = -CV_s + AI_s \quad \text{--- (4)}$$

The equation (3) and (4) gives relation b/w receiving end values and sending end values.

Step 2 $\rightarrow$ 4

$$I_r = -CV_s + A \{ CV_r + DI_r \}$$

$$I_r [1 - AD] = -CV_s + AC V_r$$

$$I_r B \phi = -\phi V_s + A \phi V_r$$

$$\left\{ P_c - \frac{|D||V_s|^2 \cos(\beta - \Delta)}{|B|} \right\}^2 + \left\{ Q_c - \frac{|D||V_s|^2 \sin(\beta - \Delta)}{|B|} \right\}^2 = \left\{ \frac{|V_s||V_r|}{|B|} \right\}^2 \quad \text{--- (15)}$$

represent the equation of circle.

$$x \rightarrow \frac{|D||V_s|^2 \cos(\beta - \Delta)}{|B|}$$


$$y \rightarrow \frac{|D||V_s|^2 \sin(\beta - \Delta)}{|B|}$$

$$\text{radius} \rightarrow \frac{|V_s||V_r|}{|B|}$$

Question:-


When the sending end voltage and receiving end voltage of T.L are constant the real power at the receiving end of the T.L is max^m for the condition

$$P_r + \frac{|A||V_r|^2 \cos(\beta - \delta)}{|B|} = \frac{|V_s||V_r| \cos(\beta - \delta)}{|B|}$$

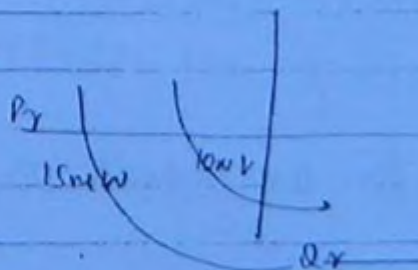

P_r is max^m when $\delta = \beta$

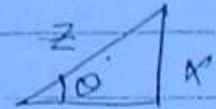2) The power circle equation of short T.L are.



For S.T.L

$$A = 1 \angle 0^\circ \quad |A| = 1 \quad \angle 20^\circ \quad |A| = 1$$

$$B = Z \quad |B| = Z \quad \beta = \theta \quad |B| = Z$$

$$C = 0$$

$$D = 1 \angle 0^\circ \quad |D| = 1 \quad \Delta = 0^\circ \quad |D| = 1$$

(A)

now equatⁿ

$$10 \rightarrow P_r + \frac{1 \cdot |V_r|^2 \cos(\theta)}{Z} = \frac{|V_r||V_s| \cos(\theta - \delta)}{Z}$$

$$11 \rightarrow Q_r + \frac{|V_r|^2 \sin \theta}{Z} = \frac{|V_r||V_s| \sin(\theta - \delta)}{Z}$$

$$13 \rightarrow P_s - \frac{1 \cdot |V_s|^2 \cos(\theta - \delta)}{Z} = - \frac{|V_r||V_s| \cos(\theta + \delta)}{Z}$$

$$14 \rightarrow Q_s - \frac{|V_s|^2 \sin \theta}{Z} = - \frac{|V_r||V_s| \sin(\theta + \delta)}{Z}$$

the power circle equatⁿ for an ideal short T.L

$$S_r = \frac{|V_r||V_s|}{|B|} \cos(\beta - \delta) - \frac{|A||V_r|^2}{|B|} \cos(\beta - \alpha) \quad \dots (9)$$

As $S_r = P_r + jQ_r$

$$P_r = \frac{|V_r||V_s|}{|B|} \cos(\beta - \delta) - \frac{|A||V_r|^2}{|B|} \cos(\beta - \alpha)$$

$$\Rightarrow P_r + \frac{|A||V_r|^2}{|B|} \cos(\beta - \alpha) = \frac{|V_s||V_r|}{|B|} \cos(\beta - \delta) \quad \dots (10)$$

Similarly:

$$Q_r = \frac{|V_r||V_s|}{|B|} \sin(\beta - \delta) - \frac{|A||V_r|^2}{|B|} \sin(\beta - \alpha)$$

$$Q_r + \frac{|A||V_r|^2}{|B|} \sin(\beta - \alpha) = \frac{|V_r||V_s|}{|B|} \sin(\beta - \delta) \quad \dots (11)$$

$$(10)^2 + (11)^2$$

$$\left\{ P_r + \frac{|A||V_r|^2}{|B|} \cos(\beta - \alpha) \right\}^2 + \left\{ Q_r + \frac{|A||V_r|^2}{|B|} \sin(\beta - \alpha) \right\}^2 = \left\{ \frac{|V_s||V_r|}{|B|} \right\}^2 \quad \dots (12)$$

Equation (12) represents the equation of circle with

x-coordinate = $-\frac{|A||V_r|^2}{|B|} \cos(\beta - \alpha)$

y-coordinate = $-\frac{|A||V_r|^2}{|B|} \sin(\beta - \alpha)$

$$\text{radius} = \frac{|V_s||V_r|}{|B|}$$

The complex power per phase at the sending end of T.L:-

$$S_s = V_s I_s^*$$

$$\Rightarrow S_s = V_s / \delta \left\{ \frac{|D||V_s|}{|B|} \angle \beta - \alpha - \delta - \frac{|V_r|}{|B|} \angle \beta \right\}$$

$$P_s + jQ_s = \frac{|D||V_s|^2}{|B|} \angle \beta - \alpha - \frac{|V_r||V_s|}{|B|} \angle \beta + \alpha$$

$$P_s = \frac{|D||V_s|^2}{|B|} \cos(\beta - \alpha) - \frac{|V_r||V_s|}{|B|} \cos(\beta + \alpha)$$

$$\cancel{P_s} + \frac{|V_r||V_s|}{|B|} \cos(\beta + \alpha) = P_s - \frac{|D||V_s|^2}{|B|} \cos(\beta - \alpha) \quad \text{--- (13)}$$

Similarly


~~Q_s~~

$$\cancel{Q_s} + \frac{|V_s||V_r|}{|B|} \sin(\beta + \alpha) = Q_s - \frac{|D||V_s|^2}{|B|} \sin(\beta - \alpha) \quad \text{--- (14)}$$

$$(13)^2 + (14)^2$$

As ideal so no losses, resistance is neglected.
 $\theta \rightarrow 90^\circ$.
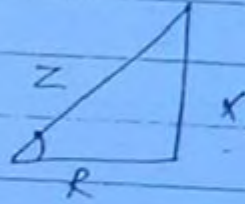
$$\tan^{-1}\left(\frac{x}{R}\right) = 90^\circ.$$



$$10 \rightarrow P_R + 0 = \frac{|V_s||V_r|\sin\delta}{Z}$$

$$11 \rightarrow Q_R + \frac{|V_r|^2}{Z} = \frac{|V_r||V_s|\cos\delta}{Z}$$

$$13 \rightarrow P_s - 0 = \frac{|V_r||V_s|\sin\delta}{Z}$$

$$14 \rightarrow Q_s - \frac{|V_s|^2}{Z} = \frac{-|V_r||V_s|\cos\delta}{Z}$$

4) For a system to operate under stable conditions load angle δ must be.

$$P_r = \frac{V_s \cdot V_r \sin\delta}{X} \quad \delta \text{ must lie b/w } 0-90^\circ.$$


5) When sending end voltage and receiving end voltage are increased by 10% the maxm active power transferred is?

$$P_{\max} = \frac{|1.1 V_s| |1.1 V_r| \sin \delta}{X}$$

$$P_{\max} = \frac{1.21 V_s V_r \sin \delta}{X}$$

CONSTANT VOLTAGE TRANSMISSION

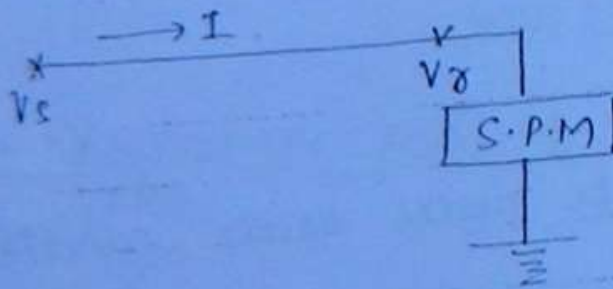- for a constant voltage transmission specially designed synchronous motors known as synchronous phase modifiers are installed at the receiving end which maintains constant voltage drop along T.L



Synchronous phase modifiers can take either lagging or leading current from the T.L by altering the excitation. Synchron

Synchronous mfr are installed in combination with gpr statn to improve the power factor at the load end of T.L

During the peak hours T.L requires lagging VAR at the receiving end.

During half peak hours T.L requires leading VAR at the receiving end to prevent the voltage drop

SPM delivers lagging VAR when excitation is increased and delivers leading VAR when excitation is decreased

Question:

1) A 200 km, 3 ϕ 50Hz T.L has following data

$$A = D = 0.938 \angle 1.2^\circ \Omega$$

$$B = 131.2 \angle -72.3^\circ \Omega$$

$$C = 0.001 \angle 90^\circ \text{ S}$$

The sending end voltage is 250 kV, determine

1) Receiving end voltage V_R when load is disconnected

2) T.L charging current

3) Maxm power that can be transmitted at the receiving end voltage of 220 kV and the corresponding load reactive power required at the receiving end.

$$V_s = AV_r + B I_r$$

when load disconnected $I_r = 0$, $V_r \rightarrow V_{R0}$

$$V_s = V_{\phi 0} / A = \frac{230 / \sqrt{3}}{0.938 \angle 1.2^\circ}$$

$$141.57 \angle -1.2^\circ \text{ KV}$$

$$\text{re } V_{CL-L} = 23 \angle 945.20 \angle -1.2^\circ \text{ KV}$$

charging current, current through capacitor when receiving end is O.C.

$$I_s = CV_R + DI_R$$

$$I_R = 0$$

$$I_{\text{charging}} = I_s = CV_R$$

$$(0.001 \angle 90^\circ) (141.57 \angle -1.2^\circ)$$

$$I_{\text{charging}} = 141.57 \angle 88.8^\circ$$

$$P_r = \frac{|V_s||V_r| \cos(\beta - \delta)}{|B|} - \frac{|A||V_r|^2 \cos(\beta - \alpha)}{|B|}$$

$$P_r \text{ is max } \beta = \delta$$

$$P_{r \text{ max}} = \frac{|V_s||V_r|}{|B|} - \frac{|A||V_r|^2 \cos(\beta - \alpha)}{|B|}$$

$$P_{rmax} = \frac{|132.79||141.57|}{131.2} - \frac{|141.57||0.938|}{131.2} \cos(72.3-1.2^\circ)$$

$$P_{rmax} = 91.2 \text{ MW.}$$

→ Reactive power: $Q_{rmax} = \beta = 0$ ✓

$$Q_r = - \frac{|A||V_r|^2 \sin(72.3-1.2^\circ)}{|B|}$$

$$Q_r = -9.$$

Disadvantage:-

→ On connecting SPM, the short-circuit current of s/m. is increased.

Question!:-

A 3- ϕ TL has resistance per phase of 5Ω and inductive reactance of $15\Omega/\text{phase}$. Determine the load, which line which the line will be supplying at 132 kV at 0.8 p.f lagging. The sending voltage is 140 kV. If a SPM is connected in parallel with load to improve the power factor upto 0.95 lagging. determine the leading MVAR supplied by synchronous phase modifier. the receiving end voltage and load are constant. Assume ABCD parameters of short T.L

Solⁿ

For a short T.L

$$A = 1, \quad \alpha = 0$$

$$B = Z = \sqrt{R^2 + X^2}$$

$$= \sqrt{6^2 + 15^2} = 15.81 \Omega$$

$$\beta = \tan^{-1}\left(\frac{X}{R}\right) = \tan^{-1}\left(\frac{15}{6}\right) = 71.6^\circ$$

step 1: receiving end circuit diagram

$$\text{radius} = \frac{|V_S| |V_R|}{|B|} = \frac{132 \times 140}{15.81} = 1168.8 \text{ MVA}$$

Horizontal Coordinate

$$= \frac{|A| |V_R|^2 \cos(\beta - \alpha)}{B}$$

$$= \frac{1 \times 132^2 \cos(71.6 - 0)}{15.81}$$

$$= -347.8 \text{ MW}$$

Vertical coordinate

$$= \frac{|A| |V_R|^2 \sin(\beta - \alpha)}{B}$$

$$= -1045.6 \text{ MVAR}$$

∴ Step 2: select power scale.


$$1 \text{ cm} = 200 \text{ MW} = 200 \text{ MVA} = 200 \text{ MVAR}$$

$$\text{radius} = \frac{1168.8}{200} = 5.85 \text{ cm}$$

$$\text{Horizontal co-ordinate} = \frac{-547.8}{200} = -1.74 \text{ cm}$$

$$\text{vertical co-ordinate} = \frac{-1045.6}{200} = -5.25 \text{ cm}$$

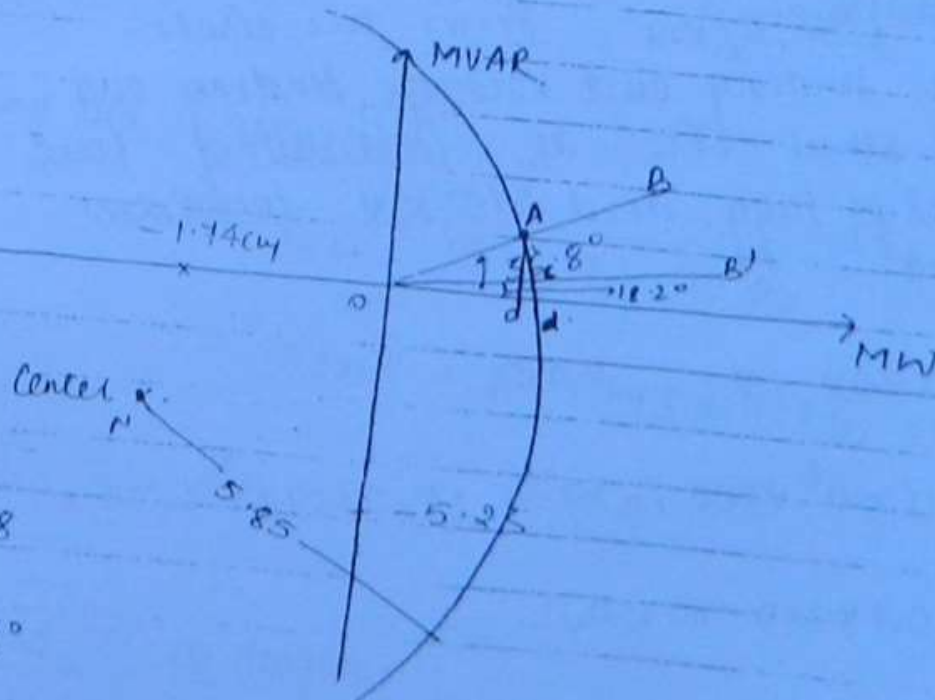∴ Step 3: Constructⁿ of circle diagram at receiving end.



$$\cos \phi_R = 0.8$$

$$\phi_R = 36.8^\circ$$

$$\cos \phi = 0.95$$

$$\phi = 18.2^\circ$$

To increase the p.f. from 0.8 lagging to 0.95 lagging
synchronous phase Modifiers are to be used

leading MVAR

MVAR (leading) supplied by synchronous phase modifier
is = 0.1 pu

$$= 0.1 \text{ pu}$$

$$= 0.1 \times 200$$

$$= 20 \text{ MVAR}$$

When T.L is supplying at 132 kV and 0.8 p.f. the power supplied is

$$P = 0.3 \text{ pu}$$

$$= 200 \times 0.3$$

$$60 \text{ MW}$$

Q) Draw the receiving end and sending end power circle diagram of 300 km T.L with resistance $0.4 \Omega/\text{km}$ and $Y = 5.15 \times 10^{-6} \angle 90^\circ \text{ S/km}$. From the circle diagram determine sending end voltage, sending end current and p.f. when T.L is delivering load of 192 MW at 0.8 p.f lagging and 275 kV consider nominal π method.

$$R/\phi = 0.4 \times 300 \Rightarrow 120 \Omega$$

$$Y = 5.15 \times 10^{-6} \times 300 \angle 90^\circ = 1.545 \times 10^{-3} \angle 90^\circ \text{ S}$$

$$X/\phi = 0.4 \times 300 = 120 \Omega$$

$$Z/\phi = R/\phi + jX/\phi$$

$$= 120 + j120$$

To find A, B, C, D constant using nominal π method.

$$A = \frac{1 + YZ}{2} = \frac{1 + \frac{1.543 \angle 90^\circ (24 + j120)}{2}}{2} = 0.9075 \angle$$

$$B = Z = 24 + j120 = 122.38 \angle 78.69^\circ \Omega$$

C = $\cancel{Y}$ not required

$$D = 0.9075 \angle 1.17^\circ$$

$$|A| = |D| = 0.9075$$

$$\alpha = 1.17^\circ$$

$$|B| = 122.38$$

$$\beta = 78.69^\circ$$

Receiving end current $I_R = ?$

$$MW = \sqrt{3} V_{RL} I_{RL} \cos \phi_R$$

$$192 \times 10^6 = \sqrt{3} \times 275 \times 10^3 \times I_{RL} \times 0.8$$

$$I_{RL} = I_R = 504 \text{ A}$$

Receiving end circle diagram

$$\text{Horizontal} = \frac{|A| |V_{RL}|^2}{3} \cos(\beta - \alpha)$$

$$= 0.9075 \times 275^2 \cos(78.69^\circ - 1.17^\circ)$$

vertical co-ordinate

$$= \frac{|A||V|^2 \sin(\beta - \alpha)}{|B|}$$


$$= -548 \text{ cm} \cdot \text{MVAR}$$

Power Scale:


$$1 \text{ cm} = 100 \text{ MW} = 100 \text{ MVAR}$$

$$= \pm 1.21 \text{ cm}$$

$$= -5.48 \text{ cm}$$

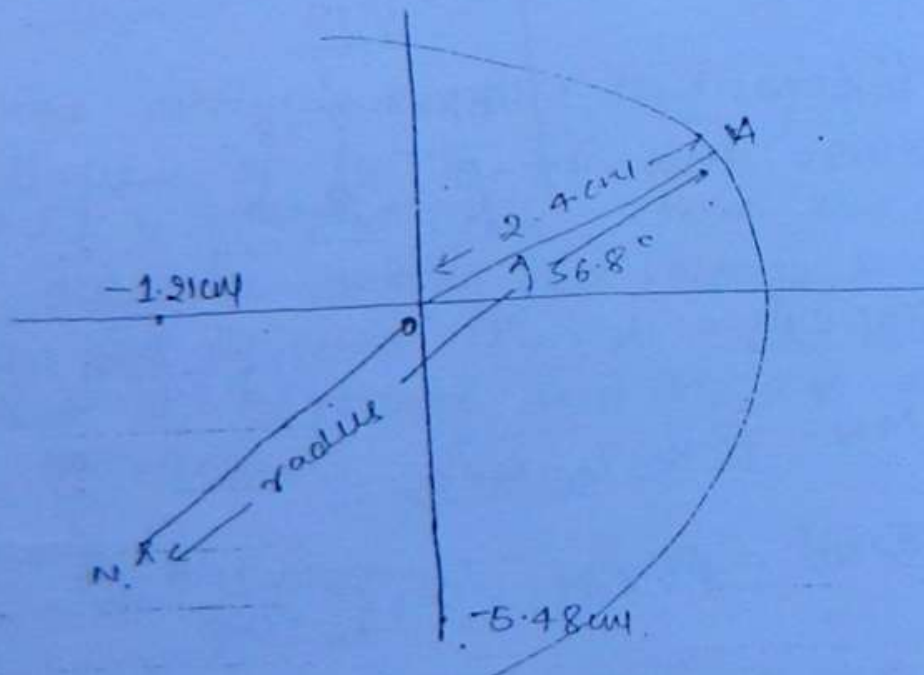

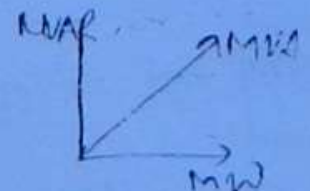Vol Angle at the receiving end at the T.L



$$V_A = \sqrt{3} \cdot V_{RL} \cdot I_{RL}$$

$$240 \text{ MVA}$$

$$\text{let } 1 \text{ cm} = 200 \text{ MVA} \Rightarrow V_A = 2.4 \text{ cm}$$

radius of the circle is equal to $NP \Rightarrow 7.6 \text{ cm}$.

$$= 7.6 \times 100 = 760 \text{ MVA}$$

The Resultant $VA \ 760 = \frac{V_s V_r}{B}$

$$760 = \frac{V_s \cdot 975}{122.38}$$

$$V_s = 838 \text{ KV}$$

2) Sending end circle diagram:-

$$\begin{aligned} \text{Horizontal} &= \frac{|D| |V_s|^2 \cos(\beta - \Delta)}{|B|} \\ &= 183 \text{ MW} \end{aligned}$$


$$\text{Vertical coordinate} = \frac{|D| |V_s|^2 \sin(\beta - \Delta)}{|B|}$$

$$827 \text{ MVAR}$$

$$\text{radius} = \frac{|V_s| |V_r|}{|B|} = 760 \text{ MVA}$$

$$100W = 100MW = 100MVAR = 100MVA$$

Constructing:

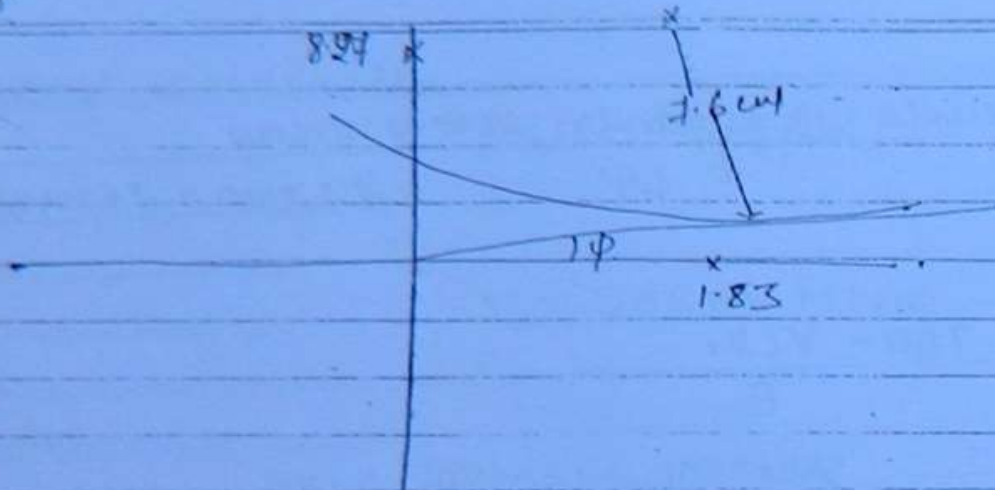

$$\phi_s(\text{graph}) = 15^\circ$$

$$\cos(\phi_s) = \cos 15^\circ = 0.966$$

→ sending end current

$$V_A = \sqrt{3} V_{SL} I_{SL} \cos \phi_s$$

$$240 \times 10^6 = \sqrt{3} \times 338 \times 10^3 \times I_{SL} \times 0.966$$

$$I_{SL} = 410 A$$

ECONOMIC ASPECT OF GENERATING STATIONS

1) Connected load:-

The sum of kW rating of all the equipments connected to a system.

2) Maximum Demand:

The highest load existing on the S/H in a given duration

3) Average load:

It is the mean of loads connected to system at different durations

4) Demand factor:

Maximum demand by connected load

It is always ≤ 1 .

5) load factor:-

Average load by max demand, always ≤ 1 .

6).

$$\text{load factor} = \frac{(\text{Energy generated for 24 hr})/24}{\text{Maximum demand}}$$

6) load duration curve:

It gives the no of house loads are existing on the system

Ques

A residential consumer has electrical equipment as follows.

10 lamps each 60 Watts

2) 2 heater, each 1000 Watts

The max^m demand is 1000 W. The consumer uses 8 lamps for 5 hr in a day and 2 heaters for 3 hr/day. Calculate

- 1) Connected load
- 2) demand factor
- 3) energy consumed per day
- 4) Avg load
- 5) load factor.

Solution.

$$(8 \times 5 \times 60) + (2 \times 1000)$$

1) Connected load

$$(10 \times 60) + (2 \times 1000)$$

$$= 2600 \text{ W}$$

$$2) \text{ demand factor} = \frac{\text{Max demand}}{\text{Connected load}}$$

$$= \frac{1000}{2600} = 0.38$$

$$3) \text{ Energy consumed per day} = (8 \times 5 \times 60) + (2 \times 1000)$$

$$= 8400 \text{ W}$$

$$= 8.4 \text{ kW}$$

$$4). \text{ Average load} = \frac{\text{Total E.G.}}{\text{No of hours}} = \frac{8400}{24} = 350 \text{ W.}$$

$$5) \text{ load factor} = \frac{\text{A.L.}}{\text{Max demand}} = \frac{350}{1000} = 0.35.$$

7) DIVERSITY FACTOR

sum of the individual max^m demand by max^m demand existing on s/m.

$$D.F = \frac{\sum (I.M.D)}{M.D \text{ of s/m}} > 1.$$

8) Coincident factor:

$$C.F = \frac{1}{\text{Diversity Factor}}$$

9) Plant capacity factor:

$$\frac{\text{Actual energy generated}}{\text{Max^m energy that can be generated}}$$

10) Reserve capacity:

$$\text{Plant capacity} - \text{Max^m demand}$$

11) Operation factor:

$$\frac{\text{No. of hours generating stat}^n \text{ is in operat}^n}{\text{Max}^n \text{ no of hours generating stat}^n \text{ can be operated}}$$

12) Utilization factor / Plant use factor:-

$$\frac{\text{Energy generated in kWh}}{\text{Plant capacity} \times \text{no of hours in operat}^n}$$

13) Firm power:

The minimum power available at any time instance.

4) Cold Reserve:

The reserve generating capacity available for service but not in operation.

5) Hot Reserve:

The reserve generating capacity which is in operatⁿ but not in service.

6) Spining Reserve: the generating capacity connected to the bus and ready to take the load is known as spinning reserve.

Question:

1) The max^m demand on G/R station is 80 MW. The plant capacity factor and Plant utilization factor are 0.5, 0.8 respectively. Determine.

- 1) Load factor
- 2) Average load
- 3) No. of units generated per day
- 4) Plant capacity
- 5) Reserve capacity


2) A G/R statⁿ operates at max^m demand of 100 MW. Load factor 0.65, plant capacity factor is equal 0.5. Plant use factor 0.75. Calculate

- 1) Average loads
- 2) No of units generated
- 3) Plant capacity
- 4) Reserve capacity
- 5) Max^m energy that can be generated by power statⁿ
- 6) No of hours the generating statⁿ operates.

CORONA



- Electrical power transmission takes place through power conductor.
- the power conductor is in the atmosphere.
- the ionisation of air surrounding the power conductor is known as corona.
- If the electric field intensity around the power conductor is greater than the dielectric strength of air then corona occurs otherwise corona does not occur.
- Corona can be eliminated by
 - 1) decreasing electric field intensity
 - 2) Increasing dielectric strength of air
 - 3)
- Due to radioactivity no. of free electrons around the power conductor results in high electric field intensity.
- For HV & EHV where the operating voltage is greater than 275 kV the free electrons travel at a higher velocity such that dielectric strength of air is neglected.

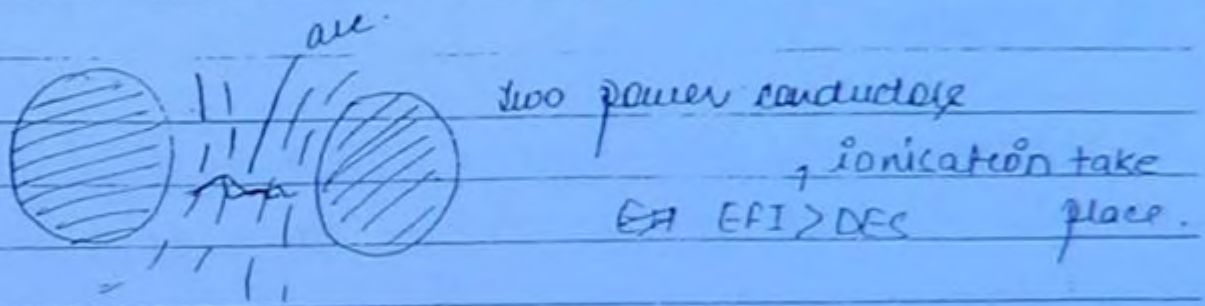→ When corona occurs due to two power conductors are is formed in the air resulting in line to line fault.



Ex

CRITICAL DISRUPTIVE VOLTAGE

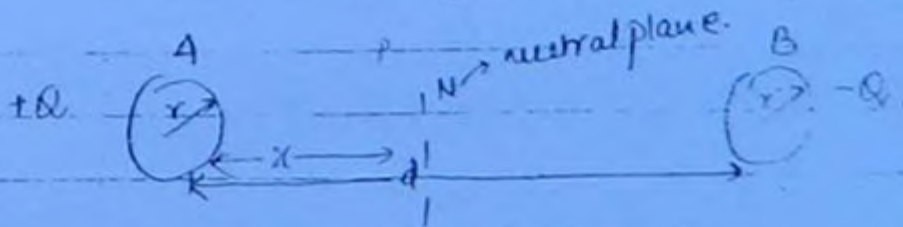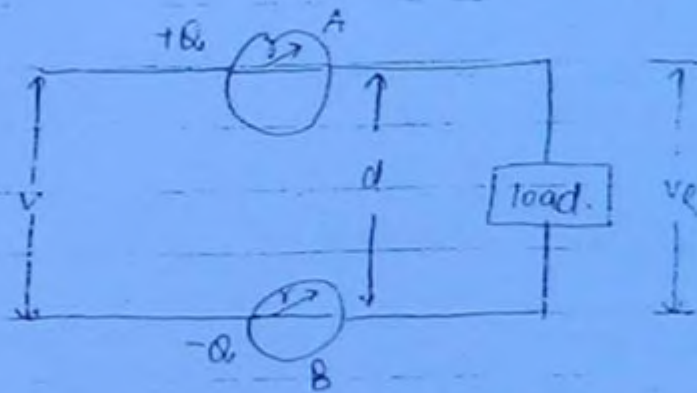

$$d \gg r$$

$$(d-r) \approx d$$

- Consider a 1- ϕ T.L
- Let ' r ' be the radius of the conductor & ' d ' be the distance between the conductors
- The distance between the conductors $(d-r) \approx d$
- Let ' Q ' be the charge per unit length of conductors
- Consider a neutral plane at middle of two conductors
- Potential of conductor 'A' w.r.t to neutral plane is $(V/2)$

Potential of conductor 'B' w.r.t neutral plane $(-V/2)$
(negative as the charge is -ve).

Consider a point 'P' at a distance 'x' from center of conductor 'A'.

To determine electric field intensity at a point 'P' consider a unit positive charge at a point 'P'.

The electric field due to conductor 'A' is repulsive.

Electric field intensity at the point 'P' due to conductor 'A'

$$E_{rA} = \frac{Q}{2\pi\epsilon_0\epsilon_r x} = \frac{Q}{2\pi\epsilon_0 x} \quad \text{--- (1)} \quad \because \epsilon_r = 1 \text{ (air)}$$

$$E_{rB} = \frac{Q}{2\pi\epsilon_0\epsilon_r (d-x)} = \frac{Q}{2\pi\epsilon_0 (d-x)} \quad \text{--- (2)}$$

Electric field intensity at the point P due to conductor 'B' is eqn (2)

Total electric field intensity b/w the two conductors

$$E_x = E_{rA} + E_{rB}$$

$$E_x = \frac{Q}{2\pi\epsilon_0} \left[\frac{1}{x} + \frac{1}{d-x} \right] \text{----- electrical field intensity}$$

- Potential difference between the two conductors.

$$V = \int_r^{d-r} E_x \cdot dx$$

$$= \int_r^{d-r} \frac{Q}{2\pi\epsilon_0} \left\{ \frac{1}{x} + \frac{1}{d-x} \right\} dx$$

$$V = \frac{Q}{2\pi\epsilon_0} \left[\left\{ \ln x \right\}_r^{d-r} - \left\{ \ln(d-x) \right\}_r^{d-r} \right]$$

$$V = \frac{Q}{2\pi\epsilon_0} \left[\ln\left(\frac{d-r}{r}\right) - \ln\left(\frac{r}{d-r}\right) \right]$$

$$V = \frac{Q}{2\pi\epsilon_0} \left\{ 2 \ln\left(\frac{d-r}{r}\right) \right\}$$

$$V = \frac{Q}{\pi\epsilon_0} \left\{ \ln\left(\frac{d-r}{r}\right) \right\}$$

potential difference

$$V = \frac{Q}{\pi\epsilon_0} \ln \frac{d}{r}$$

$$\therefore (d-r) = d$$

If when the potential difference between two conductors is grt than dielectric strength of a, the corona takes place.

The 'gradient' at a point located at a distance x from the centre of the conductor

$$E_x = \frac{Q}{2\pi\epsilon_0} \left[\frac{1}{x} + \frac{1}{d-x} \right]$$

$$= \frac{Q}{2\pi\epsilon_0} \left\{ \frac{d-x+x}{x(d-x)} \right\}$$

$$E_x = \frac{Q}{2\pi\epsilon_0} \left[\frac{d}{x(d-x)} \right]$$

Eq. 4.

substituting (3) in (4) Value $Q = \frac{\pi\epsilon_0 V}{\ln(d/r)}$

$$E_x = \frac{\pi\epsilon_0 V}{\ln(d/r)} \cdot \frac{1}{2\pi\epsilon_0} \left\{ \frac{d}{x(d-x)} \right\}$$

$$E_x = \frac{V}{2 \ln(d/r)} \left\{ \frac{d}{x(d-x)} \right\}$$

In above equation, ^{Max. value} $(V/2)$ represents the potential


of conductor A wrt neutral plane.

So,

$$E_x = \frac{V'}{\ln(d/r)} \left\{ \frac{d}{x(d-x)} \right\}$$

Here $V \rightarrow$ line voltage.
 $V' \rightarrow$ phase voltage.

$$g \propto \frac{1}{x}$$

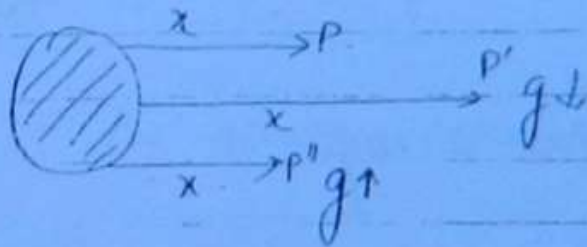

• When $x = r$ gradient is max^u.

The max^u gradient

$$g_{\max} = \frac{V'}{\ln(d/r)} \left[\frac{d}{r(d-r)} \right]$$

$$(d-r) \approx d$$

$$g_{\max} = \frac{V'}{\ln(d/r)} \left[\frac{1}{r} \right]$$

$$g_{\max} = \frac{V'}{r \ln(d/r)}$$

(critical disruptive voltage)

g_{max} is measure of critical disruptive voltage.

Definition:-

The voltage at which complete disruption of the dielectric takes place around power conductor. In general, the critical disruptive voltage is represented by

$$V' = g_{max} \cdot r \ln(d/r)$$

V' is phase voltage

Since the power conductor is in air the critical disruptive voltage

$$V' = V_d = \gamma_0 \cdot r \ln\left(\frac{d}{r}\right) \quad g_{max} \rightarrow \gamma_0 \rightarrow g_0$$

γ_0 is dielectric strength in KV/cm/peak value.

$$\gamma_0 \rightarrow 50 \text{ KV/cm/peak at NTP}$$

where $P \rightarrow$ Hg $\approx 25^\circ\text{C}$

In Numericals

$$\gamma_0 \rightarrow \frac{50}{\sqrt{2}} \text{ KV/cm/rms}$$

$$\gamma_0 \rightarrow 35.4 \text{ KV/cm/rms}$$

- At any other temp and pressure

$$\boxed{\gamma_0' = \gamma_0 \cdot \delta}$$

$\delta \rightarrow$ air density correctⁿ factor = $\frac{3.92h}{273+t}$

$h \rightarrow$ actual pressure in cm of Hg.
 $t \rightarrow$ actual temp. in $^{\circ}\text{C}$.

$\delta \ll 1$ (always) $\rightarrow$ for all other than NTP.

- for any value of temperature and pressure ($\gamma_0' < \gamma_0$).
- At any other temp and pressure.

$V_d \rightarrow$

$$\boxed{V_d = (\gamma_0 \cdot \delta) \cdot r \cdot \ln(d/r)}$$

$$\boxed{V_d = (21.1 \delta) r \ln(d/r) \text{ kV/mil.}}$$

- The critical disruptive voltage is directly related air density correctⁿ factor.
- Critical disruptive voltage depends on surface of conductor.
 'm' gives informatⁿ regarding surface of conductor.

1) $m = 1 \rightarrow$ for smooth/solid conductor

2) $m = 0.95$ to $0.98 \rightarrow$ for rough surface.
(stranded conductors)

3)


$N = 0.85$ to $0.87 \rightarrow$ cable upto 7-strands

4) $N = 0.9 \rightarrow$ cable > 7 strands.

$$V_d = (8 \times 10^6) (m) (N) (r) \ln(d/r)$$

$$V_d = (21.18) \cdot N \cdot r \ln(d/r)$$

Example:

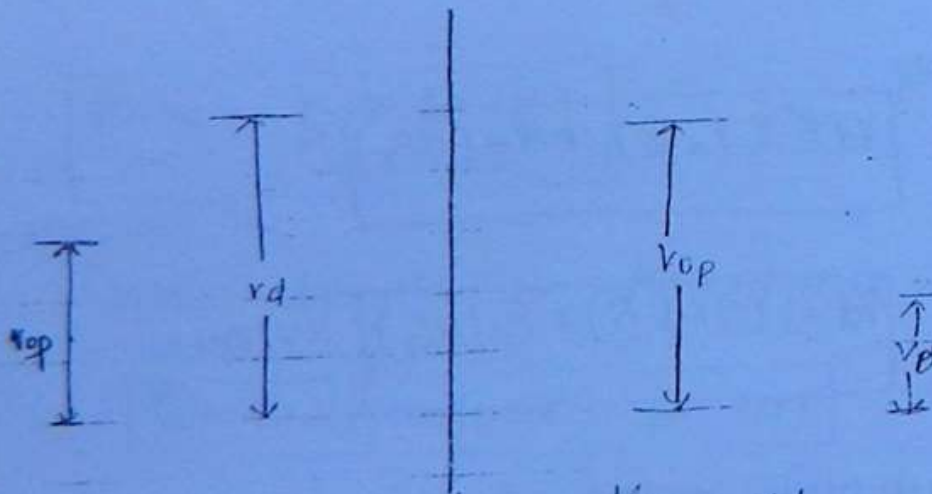

$V_{op} < V_d$
Corona does not
occur.


$V_{op} > V_d$
Corona occurs.

Electric field intensity must be more so operating
voltage must be more $> V_d$

• In terms of GMD.


$$V_d = 21.18 N \cdot \ln\left(\frac{GMD}{r}\right)$$

1) $GMD = d$ for symmetrical
N/W

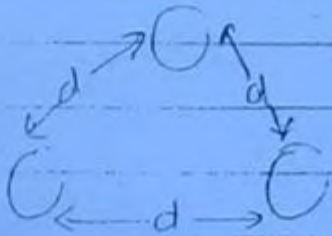

$$GMD = (x \cdot y \cdot z)^{1/3}$$

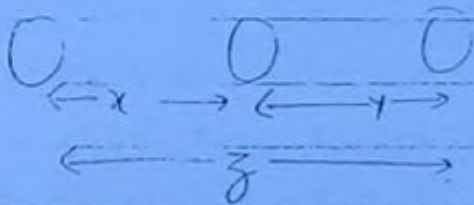2) $GMD = (x \cdot y \cdot z)^{1/3}$ unsymmetrical N/W.



OBSERVATION OF CORONA:-

- 1) Hissing noise
- 2) ozone gas
- 3) Increase in radius of conductor

VISUAL CRITICAL DISRUPTIVE VOLTAGE:-

when electric field

intensity is very high arc is formed b/w the two conductors i.e. corona is visualized.

- the electric field intensity required to visualize the corona is known as visual critical disruptive voltage.

$$V_v = \gamma_v m \cdot r \ln \left(\frac{d}{r} \right)$$

where $\gamma_v = (21.1 \delta) \left(\frac{1 + 0.5}{\sqrt{\delta r}} \right)$

- $V_v > V_d$

CORONA LOSS:-

When corona is initiated due to ionization of A, the air near surface of conductor increases the temp along the surface of conductor resulting in power loss known as Corona loss.

Corona loss

$$= 24 \times 10^{-5} \left(\frac{1 + 25}{\delta} \right) \sqrt{\frac{r}{d}} \{ (V_{ph} - V_d)^2 \} \text{ kw / km / ph}$$

* HVDC is preferred as coronal loss decreased by $\frac{1}{3}$.

FACTORS AFFECTING CORONA :-

(1) Electrical factors :-

1) Supply frequency :-

• For DC s/m $f=0$, corona loss $\propto (f+25) \propto (25)$

• For AC s/m $P_{loss} \propto (f+25)$

At normal frequency

$$P_{DC} \propto 25$$

$$P_{AC} \propto (f+25) \propto (75)$$

* *

$$P_{AC} = 3P_{DC}$$

Ques

at $f = 50\text{ Hz}$, $P_{50\text{ Hz}} = 1.2 \text{ Kw/Km/ph}$

at $f = 60\text{ Hz}$, $P_{60\text{ Hz}} = ?$

Sol

$$P_{50\text{ Hz}} \propto (f+25) \propto (50+25)$$

$$\Rightarrow 1.2 \propto (75) \quad \text{--- (1)}$$

$$P_{60\text{ Hz}} \propto (f+25) \propto (60+25)$$

$$P_{60\text{ Hz}} \propto (85) \quad \text{--- (2)}$$

$$\frac{P_{60\text{ Hz}}}{1.2} = \frac{85}{75}$$

$$P_{60Hz} = 1.36 \text{ kW/km/ph}$$


2) for 400 KV ac line $P_{loss} = 3 \text{ kW/km/phase}$

for 400 KV DC line

$$P_{DC} = ?$$

Solⁿ → for any KV $P_{DC} = \frac{1}{3} P_{AC} = 1 \text{ kW/km/ph}$

2) SUPPLY WAVEFORMS:-

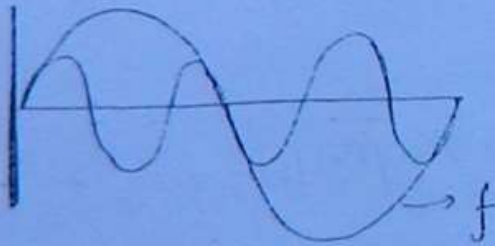

$$P_{AC} \propto (f + 25)$$

$$\bullet P_{AC} \propto (f + 25)$$

$$\bullet P_{AC} \propto (f + 3f + 25) \quad \dots \text{with 3rd harmonic}$$

$$f = 50 \text{ Hz}$$

$$1^{\circ} P_{AC} \propto (50 + 25) = 75$$


$$2^{\circ} P_{AC} \propto (50 + 150 + 125) = 225 \quad \dots \text{3rd}$$

$$3^{\circ} P_{AC} \propto (50 + 250 + 25) = 325 \quad \dots \text{5th}$$


Harmonic increases the corona loss

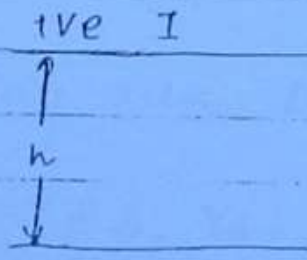3) POLARITY OF CONDUCTOR :-

- A conductor can have positive polarity and negative polarity.



Loss ↑

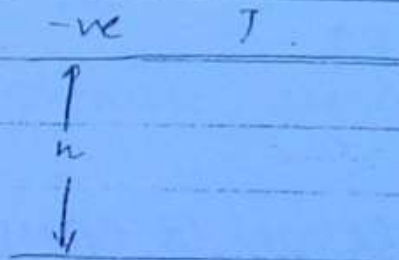

Loss ↓

- On positive polarity conductor mobility of conductor is high corona loss increases.



4) DISTANCE B/W CONDUCTORS

$$P \propto \frac{1}{\sqrt{d}}$$

$d \uparrow, P \downarrow$



$d \downarrow, P \uparrow$

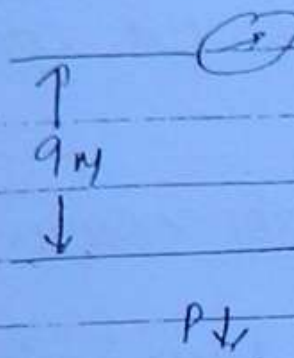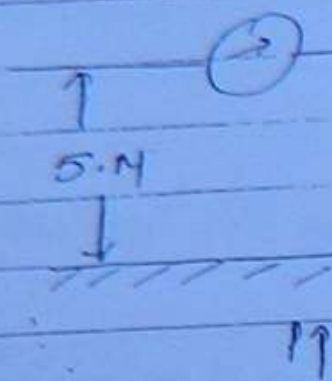- At higher distance corona loss decreases



Left ↓, so
is ionisation ↓.
as a result $P↑$

5) CONFIGURATION OF CONDUCTORS

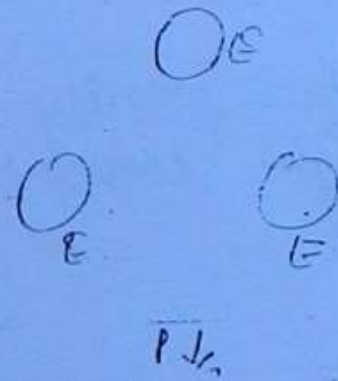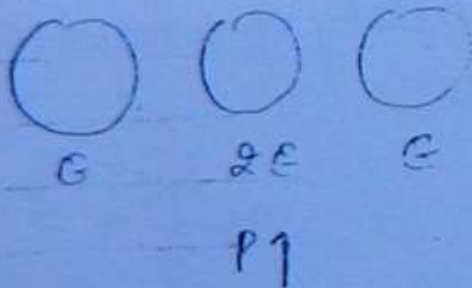

If T.L is unsymmetrically located middle conductor has high corona loss due to high electric field.
For symmetrical. n^w each conductor experience same corona loss.

(B) Atmospheric factors:


1) temperature and pressure

• As $\delta↑$ $V_d↑$, $P↓$

- Temperature and pressure $\rightarrow P \downarrow$
- deposition of ice $\rightarrow P \uparrow$

Questn 2:-

for the given 400 kV ac line.

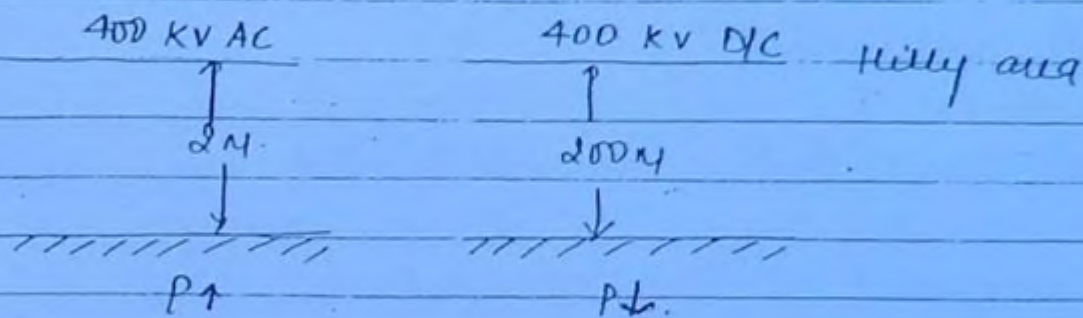

- In hilly area temp and pressure are less. ($\delta \downarrow$)
($\delta \downarrow$, $V_d \downarrow$, $P \uparrow$)

2) Deposition of ice/snow on surface of conductor.

$N \downarrow$, $V_d \downarrow$ and $P \uparrow$

C) FACTORS RELATED TO SIZE OF CONDUCTORS:-

- Corona can be decrease by selecting a conductor of small radius.
- If $\delta \downarrow$, $V_d \downarrow$, corona $\uparrow$, so while selecting radius of conductor disruptive voltage V_d and corona loss P must be considered.
- For Bundled conductors self GMD increases.

- select 'r' such that $V_d \uparrow$ and $P \downarrow$

D) PROFILE OF CONDUCTOR:-


- select d/r ratio such that $V_d \uparrow$, $P \downarrow$

DISADVANTAGE OF CORONA

- corona losses occur.
- It cause radio-interference: $\therefore$ communication line.

METHODS TO REDUCE CORONA LOSS

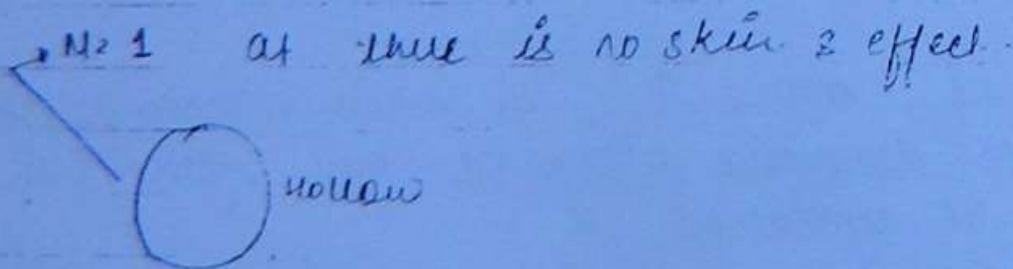- Use large size conductor.
- By use hollow conductor $\therefore$ corona loss is decreased.



- Using Bundled conductors $\therefore$ a bundled conductor

d/r ratio is more. $V_d \uparrow$, corona loss decreases.

Questⁿ

Find the corona characteristics of a 5- ϕ 220 kV T.L, 200 km. long consisting of $3 \times 100 \text{ mm}^2$ stranded conductor equally spaced. 5m apart. The air temp is 52°C and altitude is 300m corresponding to pressure of 715 mm of Hg. The frequency of s.m is 50 Hz, irregularity factor is 0.88 for the critical disruptive voltage and 0.75 for visual critical voltage.

Solⁿ

$$\bullet \frac{\pi r^2}{4} = 100$$

$$d = 5 \text{ m}$$

$$r = \sqrt{\frac{100}{\pi}} = 5.64 \text{ mm} = 5.64 \times 10^{-3} \text{ m}$$

$$\bullet \ln(d/r) = \ln\left(\frac{3000}{5.64}\right) = 6.28 = 12.58$$

$$\sqrt{r/d} = 0.043$$

$$\text{air density correctⁿ factor } \delta = \frac{3.92 \text{ h}}{273 + t}$$

$$\delta = \frac{3.92 \times 715}{273 + 32} = 9.8 \times 0.918$$

$$\begin{aligned} -V_d &= 21.1 \delta \ln(d/r) \\ &= 21.1 \times 0.918 \times 0.88 \times 5.64 \times 10^{-3} \times 6.28 \end{aligned}$$

Critical disruptive voltage.

$$= 21.1 \times 8 \times 10^{-5} \times \ln(d/r)$$
$$= 0.515 \text{ kV/m.}$$

corona loss.

$$P_{\text{loss}} = 24 \times 10^{-5} \left(\frac{1+25}{8} \right) \sqrt{\frac{r}{d}} \left\{ (V_h - V_d)^2 \right\}$$

$$= 24 \times 10^{-5} \left(\frac{75}{0.918} \right) \times 0.043 \times \left\{ \frac{220}{\sqrt{3}} - 0.604 \right\}^2$$
$$= 15.47 \text{ kV/km/ph}$$

A 3- ϕ T.L. has conductors each of radius 20mm and is arranged in form of equilateral Δ ie. Assuming the climatic conditions are good, air density factor 0.9 and irregularity factor 0.93. Find the max^m. spacing b/w the conductors if critical disruptive voltage do not exceed 250KV b/w the line. The breakdown strength is 35KV/cm (max^m)

$$V_d \rightarrow 250 \text{ kV}$$

$$m = 0.95$$

$$\delta = 0.9$$

$$r = 20 \times 10^{-3}$$

$$V_d = 21.1 \ln(d/r)$$

* critical disruptive voltage $\frac{35 \text{ cm/rms}}{\sqrt{2}}$

$$\frac{35}{\sqrt{2}} = 21.1 \times 0.9 \times 0.93 \times \ln(d/2.0) \times 70$$

$$\ln(d/r) = 1.4$$

$$d/r = e^{1.4}$$

$$d = 4.05 \times 2, \\ = 8.110 \text{ cm.}$$

$$V_d = (24.75) 11.8 \cdot r \cdot \ln(d/r) \quad \text{KV/cm.}$$

$$250/\sqrt{3} = (24.75) (0.93 \times 0.9 \times 2 \ln d/r)$$

$$d/r = 32.46$$

$$d = 32.46 \times 2$$

$$= 64.92 \text{ cm.}$$

5) find the corona characteristic of ¹¹⁰ KV T.L, 50 Hz 2- ϕ T.L, 200 km long consisting of 3 conductors 0.8 cm diameter, stranded copper conductor 2.8 m. arranged in Δ . Temp is 28°C , barometric pressure is 75 cm. $M = 0.84$ and for visual corona $M_v = 0.45$ and for general corona $M_v = 0.8$.

$$f = 50 \text{ Hz}$$

$$r = 0.4 \text{ cm}$$

$$t = 28^\circ \text{C}$$

$$l = 45 \text{ cm}$$

$$N = 0.84$$

$$N_r = 0.75$$

$$\rho = 2.8 \text{ N}$$

$$\left[\frac{r}{d} \right] \frac{0.4}{0.8} = 1.19 \text{ cm}$$

$$V_{d0} = \ln \left(\frac{d}{r} \right) = \ln \left(\frac{0.8}{0.4} \right) = 4.24$$

$$V = 21.1 \times 0.4 \times 0.84 \times \ln \left(\frac{28}{0.4} \right)$$

$$S = \frac{3.38 \times 45}{273 + 28} = 0.976$$

$$V = 21.1 \times 0.976 \times 0.4 \times 0.84 \times 4.24$$

$$= 233 \text{ KV/cm/ph}$$

critical disruptive voltage

$$21.1 \times 0.976 \times 0.75 \times 4.24$$

$$= 65.2 \text{ KV/cm/ph}$$

$$V_{d0} = 21.1 \times \left(\frac{50 + 25}{0.976} \right) \times \left(1.19 \times \sqrt{\frac{110}{\sqrt{2}}} - 29.3 \right)^2$$

$$= 25.67$$

INSULATOR


- Insulator provide insulatⁿ to the power conductor from the ground.
- Material used:

1) Porcelain (20% Si, 30% Feldspar + 50% clay) [45-17 kV]

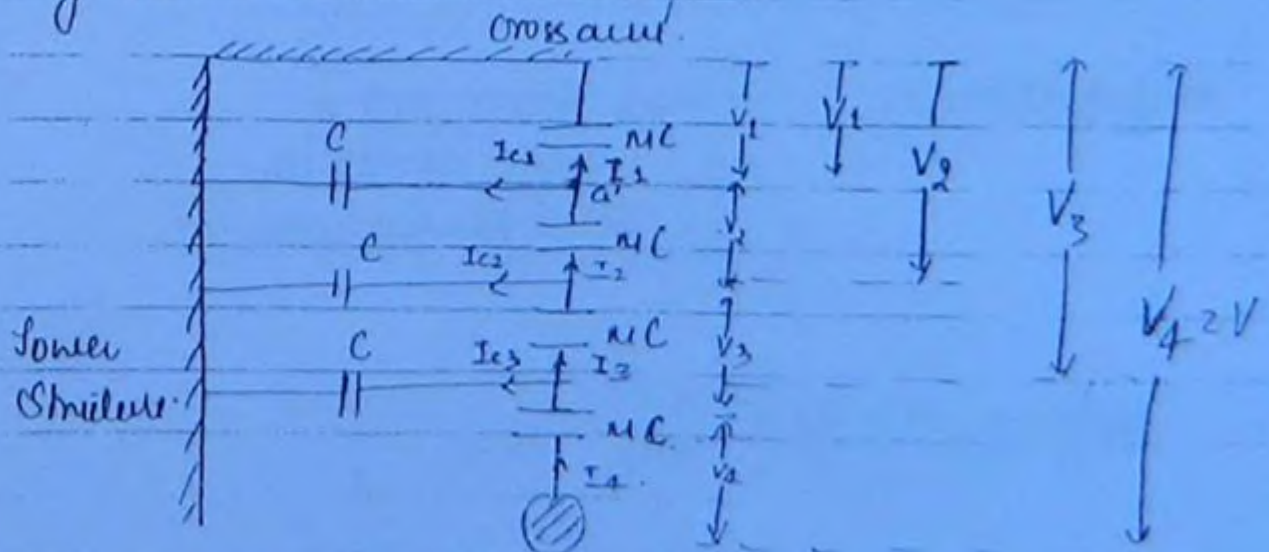2) Toughened glass [37 kV]

POTENTIAL DISTRIBUTION OVER STRING OF SUPPRESSION INSULATOR

- An insulator disc can withstand voltages upto 33 kV, the power transmission takes place at 132 kV. Therefore several insulator disc are connected in the form of string to transmit the bulk power.



- As the current is flowing from power conductor to the top insulator the disc at the bottom experience more stress. This is due to the capacitances

formed b/w the metal part of insulator and tower structure.

- The capacitance b/w metal part of the insulator and tower structure can be neglected by increasing the distance b/w the conductors. As a result the cross arm increases which increases the cost of spn.

- Therefore voltage distribution across string is not uniform due to the capacitances b/w metal part of insulator and tower structure.

- 'C' is the capacitance to the ground and, $nC \rightarrow$ mutual capacitance.

- To determine whether the distribⁿ of voltage across insulators is uniform or not. Calculate the string efficiency.

$$\text{string efficiency} = \frac{\text{voltage across string}}{n \times \frac{\text{voltage across disc}}{\text{near power conductor}}}$$

Applying KCL at 'a'

$$\sum I_{in} = \sum I_{out}$$

$$I_2 = I_1 + I_{c1}$$

$$V_2 \omega(NC) Z_2 = V_1 \omega(NC) + V_2 \omega(C)$$

$$\Rightarrow V_2 \omega \cdot NC = V_1 \omega C (N+1)$$

$$\boxed{V_2 = V_1 \left(\frac{1+N}{N} \right)} \quad \text{--- (1)}$$

• applying at 'b'.

$$I_3 = I_{C2} + I_2$$

$$V_3 \omega(NC) = (V_1 + V_2) \omega C + V_2 \omega(NC)$$

$$\boxed{V_3 = V_2 \left(\frac{N+1}{N} \right)} \quad \text{--- (2)}$$

$$V_3 N = V_2 N + V_1 + V_2$$

$$V_3 \cdot N = V_1 + V_2 (1+N)$$

$$V_3 = \frac{V_1}{N} + V_2 \left(\frac{1+N}{N} \right)$$

substituting (1)

$$V_3 = V_1 \left[\frac{1}{N} + \frac{(1+N)^2}{N^2} \right]$$

$$V_3 = V_1 \left[\frac{N + (1+N)^2}{N^2} \right]$$

$$V_3 = V_1 \left\{ \frac{N^2 + 3m + 1}{N^2} \right\} \dots \dots \dots (2)$$

apply KCL at 'c'

$$\sum I_{in} = \sum I_{out}$$

$$I_4 = I_B + I_C$$

$$V_4 \phi_{ML} = V_3 \phi_{(ML)} + (V_1 + V_2 + V_3) \phi_{\phi}$$

$$V_4 = \frac{V_1}{N} + \frac{V_2}{N} + V_3 \left(\frac{1+N}{N} \right)$$

$$V_4 = V_1 \left\{ \frac{N^2 + 3N + 1}{N^2} + \frac{3N^2 + 4N + 1}{m^3} \right\} \dots (3)$$

Let $N=5$

$$V_2 = V_1 \left(\frac{1+N}{N} \right) = V_1 \left(\frac{1+5}{5} \right) = 1.2 V_1$$

$$V_3 = \frac{V_1 \left(\frac{N^3 + 3N + 1}{N^2} \right)}{25} = \frac{V_1 \left(\frac{125 + 15 + 1}{25} \right)}{25} = \frac{41 V_1}{25} = 1.64 V_1$$

$$V_4 = 2.408 V_1$$

$$V_1 < V_2 < V_3 < V_4$$

• string efficiency = $\frac{V_1 + V_2 + V_3 + V_4}{4 \times V_4} \times 100.$

$$= \frac{V_1 + 1.2V_1 + 1.64V_1 + 2.408V_1}{4 \times 2.408V_1}$$

$$= 87.40\% \quad 54.4\%$$

Important

$$I_4 = I_3 + I_{3C}$$

$$I_n = I_{(n-1)} + I_{(n-1)C}$$

$$V_{n+1}(WMC) = V_n(WMC) + V_n(WC)$$

$$V_{n+1} = \frac{V_R + V_n}{H}$$

METHOD OF EQUALIZING THE POTENTIAL:

• 1) Selection of n :

One of the methods to equalise the potential drop across insulator disc in the string is to have higher value of n , which requires longer cross arm. thereby increasing the cost of the spur.

• 2) Capacitance grading:

In capacitance grading different insulator disc of different rating must be selected

- The disc near the cross-arm must have low capacitance or high capacitive reactance.
- The disc near the cross-arm should have minimum capacitance or max^m capacitive reactance and, as we approach to ϕ the disc near the power conductor capacitance must be maximum or capacitive reactance must be minimum.
- The ground capacitances are of equal value. and mutual capacitances are different.

$$I_{n+1} = I_n + I_{cn} \quad \dots (1)$$

$$I_{n+1} = V \cdot [\omega n C_{n+1}]$$

$$I_n = V [\omega n C_n]$$

$$I_{c3} = 3V \cdot \omega C$$

$$V_1 = V_2 = V_3 = V_g = V$$

to equate

$$V [\omega n C_{n+1}] = V [\omega n C_n] + n V \omega C$$


$$* \omega C_{n+1} = C_n + \frac{n C_n}{N}$$

DISADVANTAGES:-

- 1) different capacitances are required which require additional investment.
- 2) This method is useful except for very high voltage line.

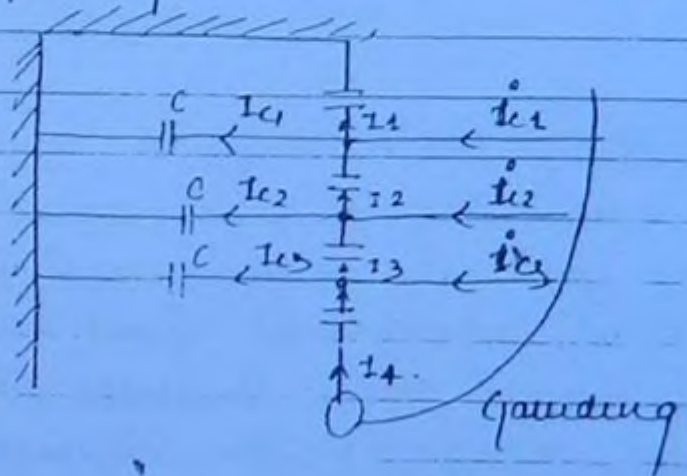iii) STATIC SHIELDING:

- In the static shielding the currents flowing in metal part of the insulator to the tower structure are cancelled by passing the same current towards the metal part of insulator.



- Equal potential across each insulator disc is obtained by means of guard ring, which operates at different potentials thereby injecting different currents.
- Guard ring can neutralize the capacitive ground currents.

$$I_{c1} = I_{t1}$$

$$I_{cn} = I_{tn}$$

- By using guard ring the capacitance of nth disc can be determined.

$$C_n = \frac{n}{K-n} \cdot C$$

- $K \rightarrow$ Total no of disc
- $n \rightarrow$ no of disc upto which guarding can be utilized.

Date?

9 Oct 2017

Question:

In transmission line consisting of 5 insulator disc the string capacitance b/w each unit and earth is $\frac{1}{6}$ times the mutual capacitance. find the voltage distribution across each insulator in the string as percentage of voltage of the conductor to the earth.

Soln


$\rightarrow N$ always grt 1

- $\frac{P_{in}}{P_{out}}$ to core capacitance = C
mutual capacitance

$$\frac{NC}{C} = 6$$

$$\therefore \boxed{N = 6}$$

$$I_5 = I_4 + I_{C4}$$

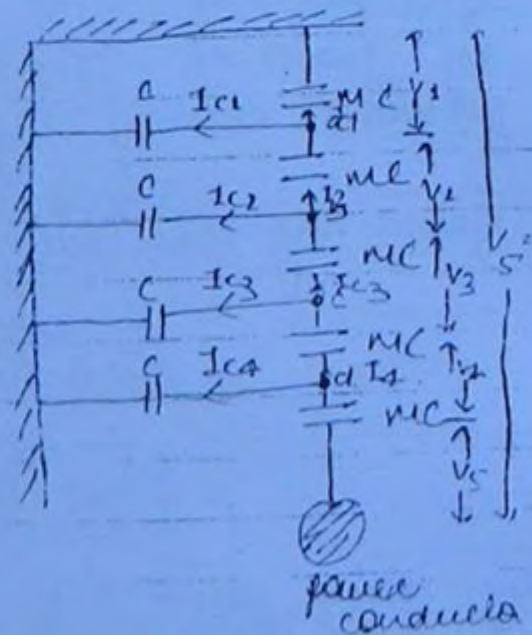

$$V_5 \times \omega n C = V_4 \omega n C + V_4 \omega C.$$

$$\therefore V_5 \cdot n = V_4 n + V_4$$

$$\boxed{V_5 = V_4 + \frac{V_4}{n}} \text{ --- (1)}$$

Imp formula

$$\text{for } n=4 \quad V_{n+1} = V_n + \frac{V_n}{n}$$

n is no of insulator from top tower in structure.

$$\bullet (n=1) \quad V_{n+1} = V_1 + \frac{V_1}{n}$$

$$V_2 = V_1 + \frac{V_1}{n}$$

$$\text{as } \boxed{V_1 = V_2}$$

$$V_2 = V_1 \left(1 + \frac{1}{n} \right)$$

$$\boxed{V_2 = V_1 \cdot \frac{7}{6}} \text{ --- (2)}$$

$$\bullet (n=2) \quad V_3 = V_2 + \frac{V_2}{n}$$

$$V_3 = V_2 + \frac{V_2 + V_2}{n}$$

$$V_3 = \frac{V_1}{n} + V_2 \left(1 + \frac{1}{n} \right)$$

substitute value of V_2 from (2)

$$V_3 = \frac{V_1}{6} + V_2 \left(\frac{7}{6} \right) \left(\frac{7}{6} \right)$$

$$\boxed{V_3 = V_1 \left(\frac{55}{54} \right)}$$

n=3

$$V_4 = V_3 + \frac{V_3}{n}$$

$$V_4 = V_3 + \frac{V_1 + V_2 + V_3}{n}$$

$$V_4 = V_3 \left(1 + \frac{1}{n} \right) + \frac{V_1 + V_2}{n}$$

$$V_4 = \frac{55 V_1}{36} + \frac{V_1}{6} + \frac{8 V_1}{6 \cdot 6}$$

$$\frac{385 V_1}{216} + \frac{V_1}{6} + \frac{4 V_1}{36}$$

$$V_4 = \frac{463 V_1}{216}$$

n=4

V

$$V_5 = V_4 + \frac{V_4}{n}$$

$$V_5 = \frac{463 V_1}{216} + \frac{V_1 + V_2 + V_3 + V_4}{n}$$

$$V_5 = \frac{463 V_1}{216} + \frac{V_1}{n} + \frac{8 V_1}{6 \cdot 6} + \frac{5 V_1}{3 \cdot 6} + \frac{463 \cdot 4 V_1}{216 \cdot 6}$$

$$\frac{V_1}{6} + \frac{4 V_1}{36} + \frac{55 V_1}{216} + \frac{9 \cdot 31 V_1}{1296}$$

$$V_5 = 811 V_1$$

voltage across string

$$V = V_1 + V_2 + V_3 + V_4 + V_5$$

$$= V_1 \left(1 + \frac{7}{6} + \frac{55}{36} + \frac{463}{216} + \frac{3.11}{216} \right)$$

$$V = V_1 \times 8.94$$

%age of V

$$\bullet V_1 = \frac{V}{8.94} \times 100 = 11.16\% V$$

$$V_2 = \frac{7}{6} \times 11.16\% \text{ of } V$$

$$\bullet V_2 = 13.03\% \text{ of } V$$

$$V_3 = \frac{55}{36} \times 11.16\% \text{ of } V$$

$$\bullet V_3 = 17.05\% \text{ of } V$$

$$\bullet V_4 = \frac{463}{216} \times 11.16\% = 25.92\% \text{ of } V$$

$$V_5 = 3.11 \times 11.16\% \text{ of } V$$

$$\bullet V_5 = 34.7\% \text{ of } V$$

String efficiency =

$$\frac{V}{n \times V_5}$$

$$\eta_{\text{string}} = \frac{V}{5 \times 34.7 V} \times 100 = 57.63\% \text{ Ans}$$

2) A string of 6 suspension insulators is to be graded to obtain uniform distribⁿ of voltage across the string if the pin to earth capacitance is equal to C and the self capacitance of the top insulator is $10C$, Find the mutual capacitance in terms of C .

xx
* insulators are to be graded so no equal value of capacitance, so do not start from top to bottom

Generalize Formula

$$C_{eq} = \frac{C_1 + nC_2}{n}$$


when grading of capacitor are asked then default value of $(N=1)$ always taken

+ Pin to earth capacitance = C

+ Capacitance of top insulator disc $C_1 = 10C$

Since capacitance across each disc is not same $(N \neq 10)$

$$\therefore C_{eq} = nC_1$$

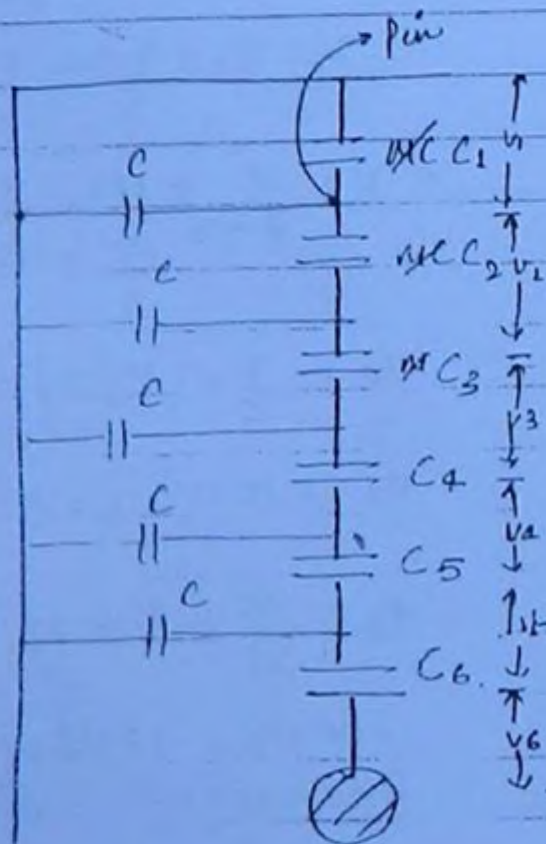

$$1) \quad n=1$$

$$C_2 = C_1 + C$$

$$\boxed{C_2 = 11C}$$

$$2) \quad n=2$$

$$C_3 = C_2 + 2C$$

$$C_3 = 11C + 2C$$

$$\boxed{C_3 = 13C}$$

$$3) \quad n=3$$

$$C_4 = C_3 + 3C$$

$$C_4 = 13C + 3C$$

$$\boxed{C_4 = 16C}$$

$$4) \quad n=4$$

$$C_5 = C_4 + 4C$$

$$16C + 4C$$

$$\boxed{C_5 = 20C}$$

$$5) \quad n=5$$

$$C_6 = C_5 + 5C$$

$$\boxed{C_6 = 25C}$$


3) A string of 4 suspension insulators is to be fitted with a guard ring / grading ring if the pin to earth capacitance is equal to C find the values of line to pin capacitances that gives uniform voltage distribution over the string.

at n^{th} juncⁿ.

$$I_{cn} = I_{cn} \text{ (as per guard ring)}$$

as voltage is uniform.
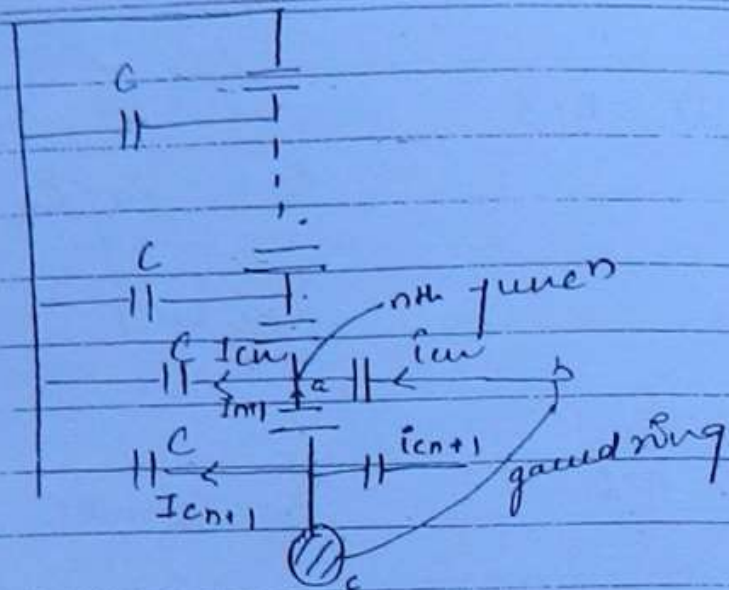
$$I_{cn} = nV \cdot \omega C \quad \text{--- (1)}$$



* voltage across ab is similar to voltage across cb as voltage across ca is known as $(K-n)V$.

so eqn (1)

$$nV \cdot \omega C = (K-n)V \cdot \omega C_n \quad \text{--- (2)}$$

* the current flowing through capacitance C_n connected b/w line and pin ca is $I_{cn} = (K-n)V \cdot \omega C_n$

where K is total no. of disc in string
 n is juncⁿ to which current I_{cn} is flowing or no. of insulator disc from top of cross arm.

$$C_n = \left(\frac{n}{K-n} \right) C$$

$$C_n = \left(\frac{6.4}{5} \right) C$$

$$C_n = \frac{6.4}{5} C$$

$$n_3 = \frac{3}{84} C = C_3$$

$$\frac{n_4 + \frac{7C}{3}}{3} = C$$

$$\frac{DS + SC + CS}{2}$$

$$n_6 = \underline{6C} = C_6$$

4) In a TL each conductor is at 20KV and is supported by a string of 5 suspension insulators. The air capacitance b/w each capacitor pin junction on tower is $1/5$ times the capacitance C of each insulator disc. A guard ring effective only over the line end insulator is fitted so that the voltage of the two units near the line end are equal. Calculate

- 1) voltage on the line end unit
- 2) the value of capacitance C_x required.


Solutⁿ

$$v_2 = v_3 \text{ (given)}$$

as.

When guard ring is connected to the insulation disc at the bottom end of the live.

$$G \cong \mathbb{Z}$$

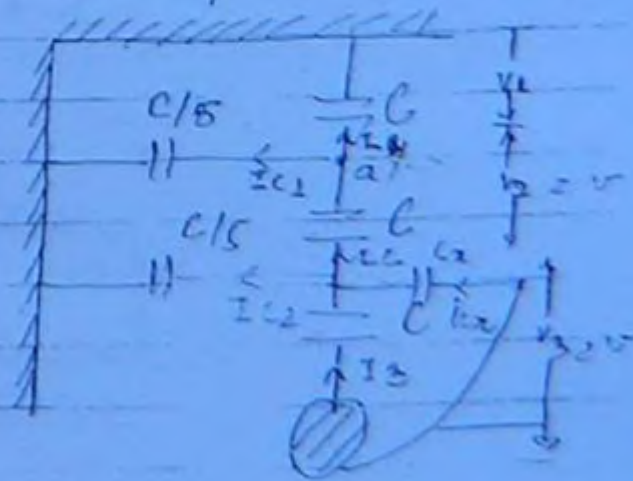

$$= \frac{(V_1 + V_2) \omega C}{5} = V \frac{\omega C x}{5}$$

$$= \frac{(V_1 + V) \omega C}{5} = V \omega C x$$

$$V_1 \cdot \frac{\omega C}{5} = V \left(Cx - \frac{C}{5} \right)$$

$$\Rightarrow \boxed{Cx = \left(\frac{V_1 + V}{V} \right) \times \frac{C}{5}} \quad \dots \textcircled{1}$$

Applying KCL at a'

$$I_1 + I_{C_2} = I_2$$

$$\Rightarrow \omega C \cdot V_2 = V_1 \cdot \omega C + V_1 \cdot \frac{C}{5}$$

$$\Rightarrow \boxed{V_2 = \frac{6}{5} V_1} \quad \dots \textcircled{2}$$

substituting on $\textcircled{1}$

$$Cx = \left(\frac{V_1}{V} + 1 \right) \times \frac{C}{5}$$

$$Cx = \left(\frac{5V_1}{5V_1} + 1 \right) \times \frac{C}{5}$$

$$Cx = \frac{11}{5} \times \frac{C}{5} =$$

$$\boxed{Cx = \frac{11}{25} C}$$

→ voltage across line end unit $V_2 = V_3 = V =$

$$V_1 + V_2 + V_3 = 20$$

$$V_1 + 2V = 20$$

$$V_1 + 2 \times 6V_1 = 20$$

$$\frac{5 + 12}{5} V_1 = 20$$

$$17/5 V_1 = 20$$

$$V_1 = \frac{100}{17}$$

$$\text{So } V = \frac{6 \times \frac{100}{17}}{5} = \frac{120}{17} \text{ kV}$$

$$V = 7.05 \text{ kV.}$$

TYPES OF INSULATOR.

1) Pin insulator: (upto 25 kV)

- A pin insulator operate upto 25 kV
- Multipin insulators operate upto 55 kV.
- vertical configuration.

2) Suspension Insulators (upto 11 kV)

- Suspension insulator operates upto 11 kV.

- No. of disc required to transmit power through a conductor at 132 kV is
horizontal configⁿ $132/11 = 12 \text{ disc.}$

→ Strain insulator: (mechanically strong).

strain insulator is mechanically strong, it is used when T.L directⁿ is changed. or when T.L is laid across a river or at the dead end of (vertical configⁿ)

→ Shackle Insulator:

shackle insulators are used for low tension lines, distribution services.

shackle insulator can be arranged either horizontally or vertically.

• Material used of insulators:

1) Synthetic Resin:


used in the region where $\times$ rainfall is more.
(14% costlier)

2) Stearlite:

used in region where snowfall is more.
(24% costlier).

GENERATING STATIONS

1) Thermal Generating Station :-

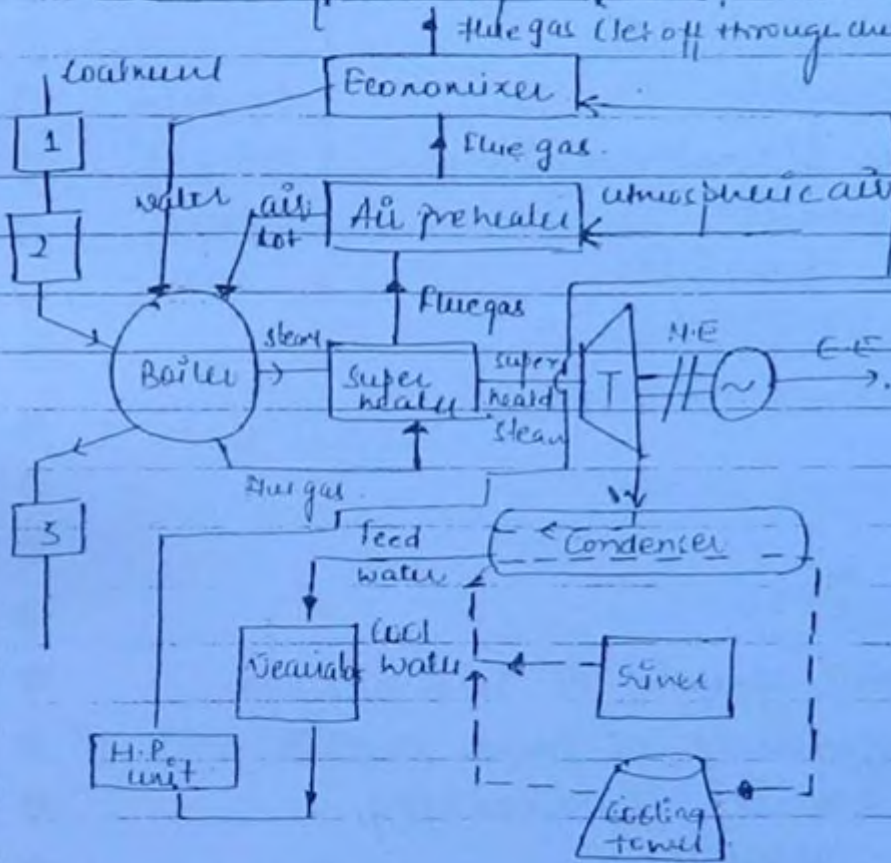


1) coal storage yard

2) coal handling yard

3) Ash storage yard

i) Coal Handling plant:

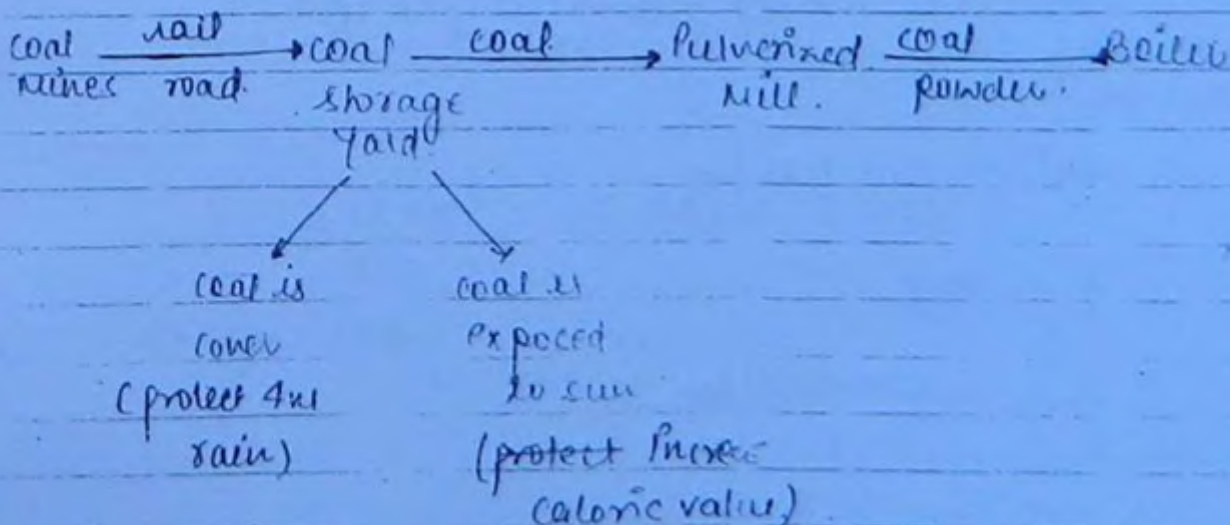

Wet coal decreases the efficiency of boiler.

Avg thermal statⁿ efficiency - 25-30%

• Types of coal used.

- | | |
|-----------------------------|---|
| 1) Peat | ↓
According
order of
Caloric
value. |
| 2) Lignite | |
| 3) Bituminous | |
| 4) Semi-Bituminous (Indian) | |
| 5) Anthracite | |
| 6) Super-Anthracite | |

• Coal in powdered form is STEAM COAL.

Question 1

A thermal power statⁿ spends Rs 10.6 lakh/yr for utilization of coal. the efficiency of power statⁿ is 30%. the calorific value of coal is 5000 kcal/kg. the cost of coal is Rs 50/ton. Calculate

- 1) Quantity of coal consumed per year
- 2) the heat input / heat of combustion
- 3) Heat output
- 4) electrical energy generated per year.
- 5) Avg load on p/g/r statⁿ.

Solⁿ

$$\text{cost} = 10.6 \text{ lakh/yr}$$

$$\eta = 30\%$$

$$\text{C.V} = 5000 \text{ kcal/kg}$$

$$\text{cost / ton} = \text{Rs } 50 / \text{ton}$$

1) Coal consumed per year?

$$= \frac{\text{cost of coal / yr}}{\text{cost of coal / ton}}$$

$$= \frac{10.6 \times 10^5}{508}$$

$$= 21200 \text{ tone/year. As}$$

2) Heat input

$$= 5000 \times 21200 \times 1000$$

$$= 1.06 \times 10^{10} \text{ kcal/year.}$$

3) Heat output

$$= 0.50 \times 1.06 \times 10^{10}$$

$$= 5.18 \times 10^9 \text{ kcal/year.}$$

4) electrical energy generated per year. (kWh)

$$\Rightarrow \text{heat o/p} = 5.18 \times 10^9 \text{ kcal/yr}$$

$$1 \text{ kWh} = 860 \text{ kcal}$$


$$= \frac{5.18 \times 10^9}{860} = 5.69 \times 10^6 \text{ kWh}$$

5) Average load.

$$= \frac{\text{Energy gen/year}}{\text{no. of hours/year}}$$

$$= \frac{5.69 \times 10^6}{365 \times 24} = 5122 \text{ kW}$$

$$0.42 \text{ MW}$$

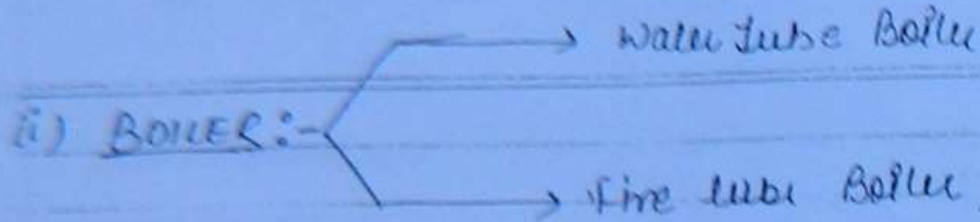

• Water tube Boiler

• ~~hot water~~ hot gases
 inside tube ← water
 hot gases

• Explosion does not occur

• 17 kg/cm^2 (Pressure)

• 100°C

• Fire tube Boiler

• water
 hot gases (inside tube)
 water

• Explosion occurs when
 temp of hot gases
 exceeds specific temp


• 85 kg/cm^2 (Pressure)

• 600°C

(ii) SUPER HEATER:

In the super heater the temperature of steam is increase by ~~increasing~~ absorbing heat of fire gases.

• Radiant Super heater

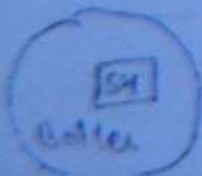

• Convection Super heater




- more efficient

- less efficient


(V) AIR PREHEATER:

In air preheater the atmospheric air absorbs the heat of flue gases and hot air is sent to the boiler for effective combustion.

Temperature

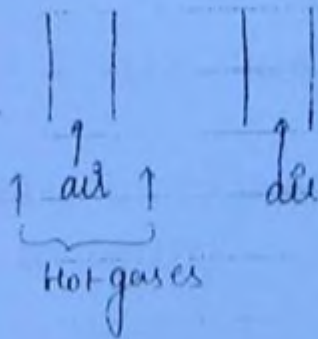

Regenerative

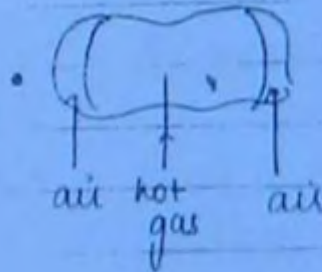

- more efficient

- less efficient

- explosion does not occur

- explosion may occur when temp. hot gases increases

Ques 10:

A thermal power plant having capacity 100 MW utilizes coal of 6400 Kcal/kg. The efficiency of boiler is 50%. efficiency of turbine g/r is 30%. calculate the no. of unit g/r per hour at rated op.

2) overall efficiency 3) Heat output in Kcal.

4) Heat input.

5) Coal utilized for generatⁿ.

Solutⁿ:

$$\text{capacity} = 100 \text{ MW}$$

$$\begin{aligned} \text{power output} &= 100 \text{ MW} \\ &= 100 \times 10^3 \text{ kW} \end{aligned}$$

$$1) \text{ Unit generated/hour} = \frac{\text{KWh}}{\text{h}} = \text{KW} = 100 \times 10^3 \text{ KW}$$

2) Overall efficiency.

$$\eta = \eta_r \times \eta_b$$

$$0.3 \times 0.9$$

$$= 0.27$$

$$\eta_{\text{total}} = 27\%$$

3) Heat output in Kcal.

$$1 \text{ kWh} = 860 \text{ Kcal.}$$

$$100 \times 10^3 \rightarrow 100 \times 10^3 \times 860$$

$$= 86 \times 10^6 \text{ Kcal/hr.}$$

• The heat output is the Kcal. of the coal burnt during combustion for hour = $86 \times 10^6 \text{ Kcal.}$

$$4) \text{ Heat Input} = \frac{86 \cdot 10^6}{0.3} = 2.86 \times 10^6 \text{ Kcal/hr}$$

5) coal utilized for generation = $\frac{2.8 \times 10^6 \text{ Kcal/hr}}{6400}$

= 437.5 Kcal/hr

V) TURBINE:

- In turbine work is done by expansion of the steam.
- Turbine converts superheated steam into mechanical energy.

IMPULSE TURBINE

- Steam is expanded completely
- Pressure on moving plates is constant

REACTION TURBINE

- Steam is expanded partially
- Pressure on moving plates is at constant



VI) CONDENSER:-

- Exhaust steam is converted into feed water
- Condenser is the equipment operating at the lowest pressure.

SURFACE

Exhaust steam

JET

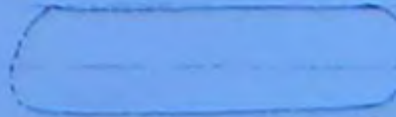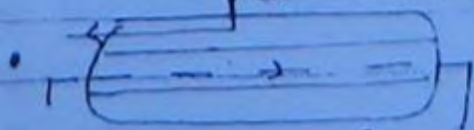

- cool water flow through tube and exhaust steam passes outside the tube.

- less efficiency


- Cool water and exhaust steam come in contact with each other

- more efficient

ii) ECONOMISER:-

Converts feed water into water at higher temp by extracting the heat from flue gases.

iii) CHIMNEY:-

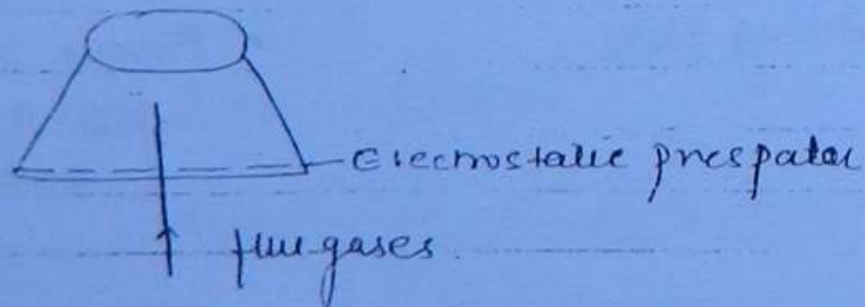

Electro-static precipitator removes the dust particles by operating at 50 KV

Induced draft fan forces the flue gases from the bottom surface to top surface

Quesⁿ

A thermal power station has efficiency 21%. 0.45 kg of coal is utilized to generate 1 kWh of energy calculate

to 1) Heat o/p

2) Calorific value of coal

3) Heat of combustion

Ans

$$\eta = 21\%$$

$$\text{Coal} = 0.45 \text{ kg}$$

$$\text{Energy generated} = 1 \text{ kWh}$$

1) Heat o/p

$$1 \text{ kWh} = 860 \text{ Kcal}$$

$$\text{Heat output} = 860 \text{ Kcal}$$

2) Calorific value of coal

$$1 \text{ kWh} \begin{cases} \rightarrow 860 \text{ Kcal} \\ \rightarrow 0.45 \end{cases}$$

$$= \frac{860 \text{ Kcal}}{0.45 \text{ kg}} = 1.91 \times 10^3 \text{ Kcal/kg}$$

3) Heat I/p

$$= \frac{860}{0.21}$$

$$= 4.1 \times 10^3 \text{ Kcal}$$

Q) A thermal power station utilizes 10.7 kg of coal to generate electrical energy of 1 kWh. The calorific value of coal is 4421 kcal/kg. The efficiency of turbine generator set is 95% and g/p is 96%. Determine the thermal efficiency.

Soln

$$1 \text{ kWh} \rightarrow 860 \text{ kcal}$$

$$\begin{aligned} \text{Heat input CV} &= 4421 \text{ CV} \times \text{Coal} \\ &= 4421 \times 10.7 \text{ kg} \\ &= 5194.7 \text{ kcal} \end{aligned}$$

$$\% \eta_{\text{th}} = \frac{860}{5194.7 \times 0.95 \times 0.96}$$

$$\eta_{\text{th}} = 0.18$$

$$\eta_{\text{th}} = 18\%$$

~~HYDROELECTRIC~~

HYDRO-ELECTRIC GENERATING STATIONS

• they are classified as below.

- 1) Generating capacity :
- a) Micro HEPs (0-5)
 - b) Small " (5-100)
 - c) Medium " (100-1000)
 - d) large " (>1000 MW)

2) Based on Head of Water :

- a) Low head. HEPs (0-70) ^{Free} Ex Propeller
- b) Medium HEPs (70-500) Kaplan
- c) High HEPs (>500) Pelton

3) Based on nature of load :

- a) Base load
- b) Peak load
- c) Pump storage plant

4) Based on Quantity of water available :

- a) Run-off river plant w/ pondage
- b) Run-off river plant w/out pondage
- c) Reservoir plant

5) Based on construction :

- a) Run off river plant w/ pondage
- b) Run off river plant w/out pondage
- c) Reservoir plant
- d) Diversion plant
- e) High head diversion canal

POWER EQUATION: Bernoulli's equation

$$P = \frac{0.736 Qwh}{75} \text{ KW}$$

$Q \rightarrow$ water discharge = m^3/sec

$w \rightarrow$ density of water
 $= 1000 \text{ kg/m}^3$

$h \rightarrow$ head of water.

$$P = \frac{736 Q \cdot w}{75} \text{ K.W}$$

$$P = 9.81 Qh \text{ KW}$$

Depending on η of generating statⁿ power transmitted to the grid or off power.

$$P_{tr} = 9.81 Qh \times \eta$$

Question:

A hydroelectric power statⁿ is supplied water from the main reservoir at a rate of $50 \text{ m}^3/\text{sec}$. The head of water $h = 50 \text{ m}$. Power developed by turbine-g/r set with $75\% \eta$ is

$$P_{tr} = 9.81 \times 50 \times 50 \times 0.75$$

$$P_{tr} = 18.4 \text{ MW}$$

Hydrological

HYDROGEN CYCLE :-

- 1) Precipitation
- 2) Evaporation
- 3) Stream flow or Runoff (m^3/sec)

$$\text{Runoff} = \text{Precipitation} - \text{Evaporation}$$

Precipitation: the volume of water available (m^3) or water discharged from the river to HE generating station.

Evaporation: the volume of water evaporated during its normal flow is evaporation.

Run-off: the volume of water available at HE q/r station is known as run off.

units:

day-sec-meter $\rightarrow m^3/sec$ in day
month-sec meter $\rightarrow m^3/sec$ in month
year-sec meter $\rightarrow m^3/sec$ in year.

- $24 \times 60 \times 60 = 86400 m^3/day$
- $30 \times 24 \times 60 \times 60 = 2.6 \times 10^6 m^3/month$
- $365 \times 24 \times 60 \times 60$

Questⁿ

A hydroelectric generating statⁿ is operating at water head of 30m. A reservoir area is 200 km^2 . The average rainfall is 420 cm/year . 50% of water is lost due to evaporatⁿ. The efficiency of turbine is 80% : efficiency of generator is 85% . The power generated is .

$$\text{Avg rainfall} = 420 \text{ cm/year}$$

$$\text{Volume of water stored in reservoir/year} =$$

$$\text{Avg rainfall} \times 200 \times 10^6$$

$$= 0.420 \times 200 \times (10^3)^2 \text{ m}^3/\text{year}$$

$$= 840 \times 10^6 \text{ m}^3/\text{year}$$

$$\text{Available water for stat} = 0.5 \times 840 \times 10^6$$

$$= 420 \times 10^6 \text{ m}^3/\text{year}$$

$$\text{Volume of water discharge/sec} = 13.21 \text{ m}^3/\text{sec}$$

$$P_g = 9.81 \times 13.21 \times 30 \times (0.8) \times (0.85)$$

$$9.3 \text{ MW}$$

Ques A hydro-electric p/lr station has the following data

- 1) operating head $\rightarrow 30\text{ m}$.
- 2) reservoir area $\rightarrow 400\text{ km}^2$
- 3) Avg rain/year $\rightarrow 125\text{ cm/year}$
- 4) yield factor $= 75\%$ (available)
- 5) $\eta_{tr} = 85\%$
- 6) $\eta_{pump\&tick} = 90\%$
- 7) $\eta_{avr} = 95\%$

the power generated is ?

$$P_{tr} = 12.5 \times 400 \times 10^6 \times 10^{-6} \\ = 5 \times 10^8 \text{ m}^3/\text{year}$$

$$\text{Available water} = \frac{5 \times 10^8}{365 \times 24 \times 60 \times 60}$$

$$Q = 11.89 \text{ m}^3/\text{sec}$$

$$P_g = 11.89 \times 30 \times 9.81 \times 0.75 \times 0.85 \times 0.90 \times 0.95 \\ =$$

can be obtained the voltage and current equation.

from eqn (1)

$$\frac{1}{Z} \frac{dV}{dx} = I$$

$$\Rightarrow I = \frac{1}{Z} \left[\frac{d}{dx} \left\{ A e^{\sqrt{Y/Z} \cdot x} + B e^{-\sqrt{Y/Z} \cdot x} \right\} \right]$$

$$I = \frac{1}{Z} \left[\sqrt{Y/Z} \cdot A e^{\sqrt{Y/Z} \cdot x} - \sqrt{Y/Z} e^{-\sqrt{Y/Z} \cdot x} \right]$$

$$I = \sqrt{\frac{Y}{Z}} \left[A e^{\sqrt{Y/Z} \cdot x} - B e^{-\sqrt{Y/Z} \cdot x} \right]$$

$$I = \frac{1}{\sqrt{Z/Y}} \left[A e^{\sqrt{Y/Z} \cdot x} - B e^{-\sqrt{Y/Z} \cdot x} \right] \quad \text{--- (2)}$$

Applying initial condition.

$V = V_R$, $I = I_R$ when $x = 0$.

Now from equation (2) we get

$$I_R = \left[\frac{1}{\sqrt{Z/Y}} \left\{ A e^0 - B e^0 \right\} \right]$$

$$I_R = \frac{1}{\sqrt{Z/Y}} [A - B] \quad \text{--- (3)}$$

Similarly:

$$V_R = A \cdot e^{\sqrt{\gamma z} \cdot 0} + B e^{-\sqrt{\gamma z} \cdot 0}$$

$$\Rightarrow V_R = A + B \quad - (8)$$

$\gamma = \sqrt{\gamma z}$ → no unit = known as propagation constant (γ)

$\gamma = (\alpha + j\beta)$ $\alpha \rightarrow$ attenuation constant
 $\beta \rightarrow$ phase constant

$\sqrt{\frac{Z_0}{Y_0}} \sqrt{\frac{Y_0}{Z_0}} \rightarrow$ characteristic impedance Z_0

$$A + B = V_R$$

$$V A - B = Z_0 I_R$$

$$2A = V_R + Z_0 I_R$$

$$A = \frac{V_R + Z_0 I_R}{2}$$

$$B = \frac{V_R - Z_0 I_R}{2}$$

substituting value of A, B.

$$V_z = \overbrace{\left(\frac{V_R + Z_c I_R}{2} \right) e^{\gamma x}}^{\text{incident wave}} + \overbrace{\left(\frac{V_R - Z_c I_R}{2} \right) e^{-\gamma x}}^{\text{reflected wave}} \quad \text{--- (9)}$$

$$= V_R \left(\frac{e^{\gamma x} + e^{-\gamma x}}{2} \right) + I_R Z_c \left(\frac{e^{\gamma x} - e^{-\gamma x}}{2} \right)$$

$$\boxed{V = V_R \cosh \gamma x + I_R Z_c \sinh \gamma x} \quad \text{--- 10}$$

Similarly,

$$I = \frac{1}{Z_c} \left\{ \left(\frac{V_R + Z_c I_R}{2} \right) e^{\gamma x} - \left(\frac{V_R - Z_c I_R}{2} \right) e^{-\gamma x} \right\}$$

$$\boxed{I = \frac{1}{Z_c} \left[V_R \left\{ \frac{e^{\gamma x} - e^{-\gamma x}}{2} \right\} + Z_c I_R \left\{ \frac{e^{\gamma x} + e^{-\gamma x}}{2} \right\} \right]} \quad \text{--- (11)}$$

$$\boxed{I = \frac{1}{Z_c} \{ \sinh \gamma x \} V_R + I_R \{ \cosh \gamma x \}} \quad \text{--- (12)}$$

When $x = l$, $V = V_L$ $I = I_L$

$$\boxed{V_L = V_R \cosh \gamma l + I_R Z_c \sinh \gamma l} \quad \text{--- (13)}$$

$$\boxed{I_L = \frac{V_R}{Z_c} \sinh \gamma l + I_R \cosh \gamma l} \quad \text{--- (14)}$$

$$A = \cosh \gamma l = D \quad \text{--- } B = Z_c \sinh \gamma l ; C = \frac{1}{Z_c} \sinh \gamma l$$

Main points :-

- # Equation (9) is combination of incident voltage wave and reflected voltage wave.
- # Incident voltage V_i wave decreases from sending end to receiving end.
- # Reflected voltage wave increases from sending end to receiving end.
- # From equation (11) current wave is combination of incident current and reflected current wave.
- # Incident current wave decreases from sending end to receiving end. so
- # Reflected current wave increases from sending end to receiving end.

- Receiving end
- Reflected voltage
- Reflected current
- Reduced.

ABCD Constants :-

1.) Power series

$$\cosh \gamma l = \left\{ 1 + \frac{(\gamma l)^2}{2!} + \frac{(\gamma l)^4}{4!} + \dots \right\}$$

$$\gamma l = \sqrt{YZ} \cdot l = \sqrt{(\gamma l)(\gamma l)} = \sqrt{YZ}$$

$$\cosh \gamma l = \left\{ 1 + \frac{(\sqrt{YZ})^2}{2!} + \frac{(\sqrt{YZ})^4}{4!} + \dots \right\}$$

$$= 1 + \frac{YZ}{2} + \frac{(YZ)^2}{24} + \dots$$

$$\cosh \gamma l \approx \frac{1 + YZ}{2}$$

$$\therefore \boxed{A = D = \cosh \gamma l = \frac{1 + YZ}{2}}$$

$$\sinh \gamma l = \left\{ \gamma l + \frac{(\gamma l)^3}{3!} + \dots \right\}$$

$$\left\{ \sqrt{YZ} + \frac{(\sqrt{YZ})^3}{6} + \dots \right\}$$

$$\sqrt{YZ} \left\{ 1 + \frac{YZ}{6} + \dots \right\}$$

$$B = Z_C \sinh \gamma l = \sqrt{\frac{Z}{Y}} \sqrt{YZ} \left\{ 1 + \frac{YZ}{6} \right\} = \boxed{B = Z \left\{ 1 + \frac{YZ}{6} \right\}}$$

$$C = \frac{1}{Z_C} \sinh \gamma l = \sqrt{\frac{Y}{Z}} \sqrt{YZ} \left\{ 1 + \frac{YZ}{6} \right\} = \boxed{C = Y \left\{ 1 + \frac{YZ}{6} \right\}}$$

$$\begin{aligned} A &= \cosh \gamma l = D \\ B &= Z_c \sinh \gamma l \\ C &= \frac{1}{Z_c} \sinh \gamma l \end{aligned}$$

③ Complex exponential:

$$\cosh \gamma l = \cosh(\alpha - j\beta)l = \cosh(\alpha l + j\beta l)$$

$$= \left\{ \frac{e^{(\alpha l + j\beta l)} + e^{-(\alpha l + j\beta l)}}{2} \right\}$$

$$= \frac{1}{2} \left\{ e^{\alpha l} e^{j\beta l} + e^{-\alpha l} e^{-j\beta l} \right\}$$

$$\cosh \gamma l = \frac{1}{2} \left[e^{\alpha l} [\beta l + e^{-\alpha l} L - \beta l] \right]$$

$$\sinh \gamma l = \sinh(\alpha l + j\beta l)$$

$$= \frac{1}{2} \left\{ e^{(\alpha + j\beta)L} - e^{-(\alpha + j\beta)L} \right\}$$

$$\sinh \gamma L = \frac{1}{2} \left\{ e^{\gamma L} - e^{-\gamma L} \right\}$$

	S.T.L	M.T.L		L.T.L
		T	Π	
A	1	$1 + \frac{YZ}{2}$	$1 + \frac{YZ}{2}$	$1 + \frac{YZ}{2}$
B	Z	$Z \left(1 + \frac{YZ}{4} \right)$	Z	$Z \left(1 + \frac{YZ}{6} \right)$
C	0	Y	$Y \left(1 + \frac{YZ}{4} \right)$	$Y \left(1 + \frac{YZ}{6} \right)$
D	1	$1 + \frac{YZ}{2}$	$1 + \frac{YZ}{2}$	$1 + \frac{YZ}{2}$

SURGE IMPEDENCE :-

the impedance of lossless transmission line is known as surge impedance.
for a lossless T.L $Z_c = Z_s$

$$Z_c = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \rightarrow \text{characteristic impedance}$$

$$R=0; G=0$$

$$Z_s = \sqrt{\frac{j\omega L}{j\omega C}} = \sqrt{\frac{L}{C}}$$

$$Z_s = \sqrt{\frac{L}{C}}$$

characteristic impedance of overhead line is 400 Ω
• underground cable is 40 Ω

Flat line OR INFINITE LINE

A lossless transmission line terminated with its characteristic impedance it is known as flat line or infinite line. the phase angle of characteristic impedance of T.L is 0° to 15°

• Surge impedance loading / characteristic impedance load

CIL and S.I.L refers to MW, MVA, ~~W~~MVAR of load connected at the receiving end of T.L, when the T.L do not have losses. SIL

$$\boxed{SIL = \frac{V_s V_R}{Z_c}}$$

If the T.L have losses

$$\boxed{CIL = \frac{V_s V_R}{Z_c}}$$

in terms of ABCD constant

$$\boxed{SIL/CIL = \frac{V_s V_R}{B}}$$

Relation b/w characteristic impedance, open-circuit impedance, short circuit impedance

$$V_s = AV_R + BI_R$$

$$I_s = CV_R + DI_R$$

Receiving end is O.C

$$I_R = 0$$

$$\Rightarrow V_c = A \cdot V_{R0} \Rightarrow A = V_c / V_{R0}$$

$$I_s = C \cdot V_{R0} \Rightarrow C = I_s / V_{R0}$$

$$\boxed{A/C = V_c / I_s} \quad \text{--- (1)}$$

Receiving end is S.C. $V_R = 0$.

$$V_c = B I_R \Rightarrow B = V_c / I_R$$

and $D = I_s / I_R$.

$$\boxed{B/D = \frac{V_c}{I_s}} \quad \text{--- (2)}$$

multiplying eqⁿ (1) and (2)

$$\frac{V_c}{I_s} = \sqrt{\frac{A \cdot B}{C \cdot D}} \quad A = D$$

$$\boxed{\frac{V_c}{I_s} = \sqrt{\frac{B}{C}}}$$

$$\begin{array}{ccc}
 S.E & & R.E \\
 X & \xrightarrow{Z_C} & X \\
 \frac{V_S}{I_S} = Z_C & & \frac{V_R}{I_R} = Z_C
 \end{array}$$

$$Z_C = \sqrt{\frac{B}{C}} = \sqrt{\frac{Z_{SC}}{Y_{OC}}}$$

$$Z_C = \sqrt{Z_{SC} Z_{OC}}$$

Question 3.

1) the surge impedance loading of 400KV T.L is

$$\frac{V_S \times V_R}{B} = \frac{V_S \cdot V_R}{Z_C} = \frac{400 \times 400}{400}$$

$$Z_C = 400 \text{ MW}$$

2) Surge impedance loading of a 220KV of T.L is

$$\frac{220 \times 220}{400} = 121 \text{ MW}$$

A T.L can be loaded more than surge impedance loading or less than surge impedance loading

Condition 1:-

$$\text{Loading} > S.I.L$$

1) Current increases.

2) load impedance (Z_L) $< Z_c$.

3) As $\frac{1}{2}LI^2 > \frac{1}{2}CV^2$, so the power factor is
lagging

4) $V_R < V_s$

Condition 2:-

$$\text{Loading} < S.I.L$$

1) Current decrease.


2) load impedance (Z_L) $> Z_c$

3) As $\frac{1}{2}LI^2 < \frac{1}{2}CV^2$, so the power factor is
leading

4) $V_R > V_s$.



Sw general TL is loaded more than surge impedance loading. Surge impedance also called Natural impedance.

CONDITION FOR ZERO REGULATION OF T.L.:-

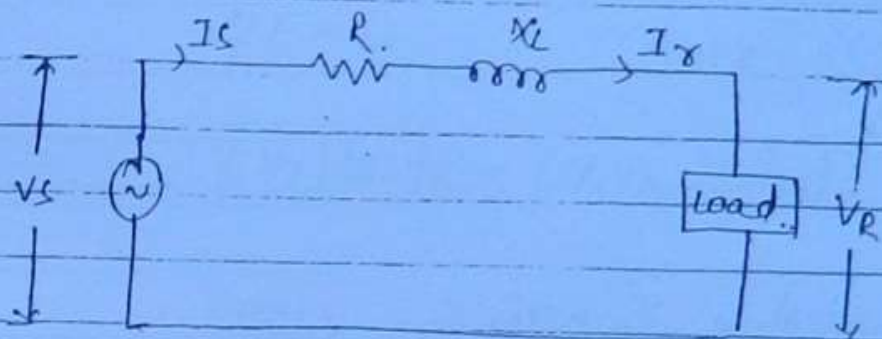

$V_s \sim \phi$

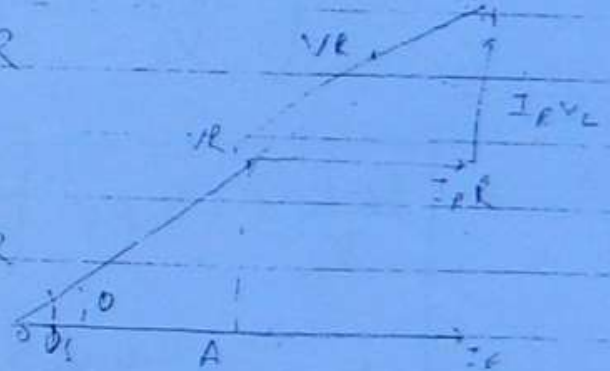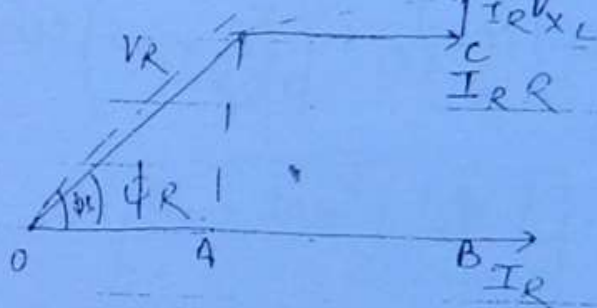consider R.F. current I_R as reference vector.



$$V_s^2 = OD^2 = OB^2 + BD^2$$

$$V_s^2 = (OA + AB)^2 + (BC + CD)^2$$

$$OB = V_s \cos \phi_s = OA + AB \\ = V_R \cos \phi_R + I_R R \quad \text{--- (1)}$$

$$BD = V_s \sin \phi_s = BC + CD \\ = V_R \sin \phi_R + I_R X_L \quad \text{--- (2)}$$

$$(1)^2 + (2)^2$$

$$V_s^2 = V_R^2 + I_R^2 (R^2 + X_L^2)$$

$$V_c - V_R \cong I_R R \cos \phi_R + I_R X \sin \phi_R$$

$$\%E = \frac{V_c - V_R}{V_R} \times 100$$

$$\frac{I_R R \cos \phi_R + I_R X \sin \phi_R}{V_R} \times 100$$

$$= \left(\frac{I_R \cdot R}{V_R} \times 100 \right) \cos \phi_R + \left(\frac{I_R}{V_R} \times 100 \right) \sin \phi_R$$

$$\frac{I_R R}{V_R} = V_R \text{ p.u.}$$

$$\frac{I_R \cdot R}{V_R} \times 100 = \% V_R$$

$$\%E = (\% V_R) \cos \phi_R + (\% V_R) \sin \phi_R$$

L --- for lagging p.f.

$$\%E = (\% V_R) \cos \phi_R - (\% V_R) \sin \phi_R$$

I --- leading p.f.

• For zero voltage regulation power factor must be leading

$$\%E = 0$$

$$(\%V_R) \cos \phi_R - (\%V_X) \sin \phi_R = 0$$

$$\%V_R \cos \phi_R = \%V_X \sin \phi_R$$

$$R \cos \phi_R = X \sin \phi_R$$


$$\tan \phi_R = R/X$$

$$\boxed{\phi_R = \tan^{-1} (R/X)}$$

When phases are given between R and X .

$$\cot \theta = R/X$$
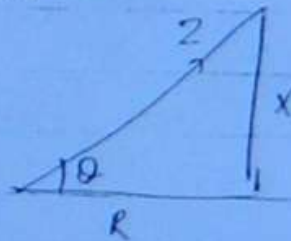
$$\therefore \tan \phi_R = \frac{R}{X} = \cot \theta$$



$$Z = R + jX$$

$$\tan \phi_R = \tan (\pi/2 - \theta)$$

$$\boxed{\phi_R = \pi/2 - \theta}$$

4. Phase angle of load at which regulatⁿ is maximum

For lagging p.f, percentage regulatⁿ is max^m.

$$\%E = (\%V_R) \cos \phi_R + (\%V_X) \sin \phi_R$$

$$\frac{d(\%E)}{d\phi_R} = (\%V_R)(-\sin \phi_R) + (\%V_X) \cos \phi_R$$

$$\frac{d(\%E)}{d\phi_R} = 0 \Rightarrow (\%V_R)(-\sin \phi_R) + (\%V_X) \cos \phi_R = 0$$

$$\Rightarrow \left(\frac{I_R \cdot R}{V_R} \times 100 \right) \sin \phi_R = \left(\frac{I_R}{V_R} \times 100 \right) \cos \phi_R$$

$$R \sin \phi_R = X \cos \phi_R$$

$$\boxed{\tan \phi_R = X/R} \quad \text{regulatⁿ is max^m}$$

From the phase Δie $\tan \theta = X/R$

$$\tan \theta_R = X/R = \tan \theta$$

$$\boxed{\phi_R = \theta}$$

X is less than R .

for max^m ratio: $\uparrow X/R$

	Zero Regulation	Max ^m Regulation
$\tan \phi_R$	R/X	X/R
ϕ_R	$\frac{\pi - \theta}{2}$	θ

When both zero

Zero Regulation = Max^m Regulation

when pf is 0.707 (lagging or leading)

as

$$\tan \phi_R = R/X \quad (=) \quad \tan \phi_R = X/R$$


$$\theta \quad [X = R]$$

$$\phi_R = \tan^{-1}(1) = 45^\circ$$

$$\cos \phi_R = \cos(45) = 0.707$$

percentage regulation of T.L (practically) around 6-7%.

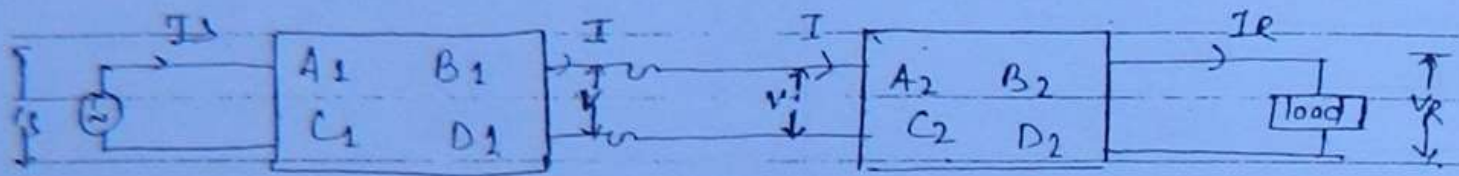T.L CONNECTED IN SERIES OR CASCADE OR TANDUMS



$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V \\ I \end{bmatrix} \quad \begin{bmatrix} V \\ I \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A_1 A_2 + B_1 C_2 & A_1 B_2 + B_1 D_2 \\ A_2 C_1 + D_1 C_2 & C_1 B_2 + D_1 D_2 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

for identical T.L

$$A_1 = A_2 = A$$

$$B_1 = B_2 = B$$

$$C_1 = C_2 = C$$

$$D_1 = D_2 = D$$

Thm for.

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A^2 + BC & AB + BD \\ AC + DC & BC + D^2 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$


$$A \longrightarrow A_1 A_2 + B_1 C_2 = A^2 + BC$$

$$B \longrightarrow A_1 B_2 + B_1 D_2 = AB + BD$$

$$C \longrightarrow A_2 C_1 + D_1 C_2 = AC + DC$$

$$D \longrightarrow B_2 C_1 + D_1 D_2 = BC + D^2$$

T.L CONNECTED IN PARALLEL

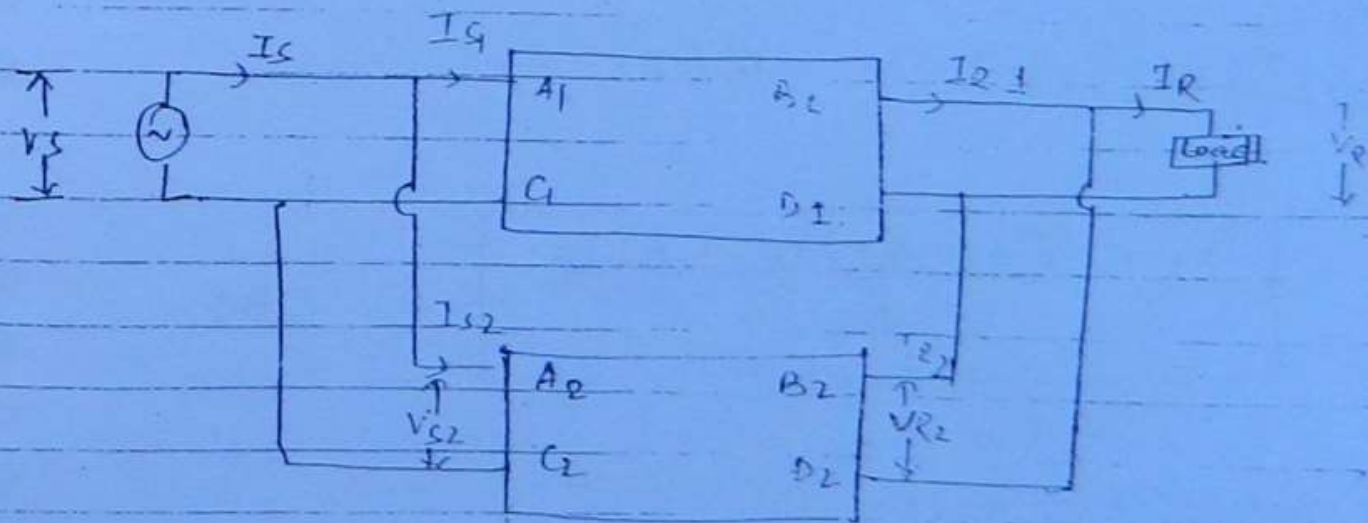

$$I_s = I_{s1} + I_{s2}$$

$$I_R = I_{21} + I_{22}$$

POWER SYSTEM-1

$$V_s = V_{s1} = V_{s2}$$

$$V_{R1} = V_R = V_{R2}$$

$$V_{s1} = V_{s1} = A_1 V_{R1} + B_1 I_{R1} = A_1 V_R + B_1 I_{R1} \quad \text{--- (1)}$$

$$V_{s2} = V_{s2} = A_2 V_{R2} + B_2 I_{R2} = A_2 V_R + B_2 I_{R2} \quad \text{--- (2)}$$

$$I_{s1} = C_1 V_{R1} + D_1 I_{R1} = C_1 V_R + D_1 I_{R1} \quad \text{--- (3)}$$

$$I_{s2} = C_2 V_{R2} + D_2 I_{R2} = C_2 V_R + D_2 I_{R2} \quad \text{--- (4)}$$

equating eqn (1) and (2)

$$A_1 V_R + B_1 I_{R1} = A_2 V_R + B_2 I_{R2}$$

$$\Rightarrow B_1 I_{R1} - B_2 I_{R2} = V_R (A_2 - A_1)$$

$$I_{R1} = \frac{(A_2 - A_1) V_R + B_2 I_{R2}}{B_1 + B_2} \quad \text{--- (5)}$$

substituting eqn (5) in (1)

$$V_{s1} = A_1 V_R + B_1 \left\{ \frac{(A_2 - A_1) V_R + B_2 I_{R2}}{B_1 + B_2} \right\}$$

288

288

1

-: HAND WRITTEN NOTES:-
OF
ELECTRICAL ENGINEERING

-: SUBJECT:-

POWER SYSTEM ^{Part II} _{IV}

1

• Components of HEPs:-

1. Reservoir: Reservoir stores water during rainy season and utilizes the stored water during summer season.

2. Dam: Provides the necessary head of water for generation.

3. Trashrack: Trashrack prevents the flow of tree leaves or any other material to reach the turbine of generating station. Trashrack is made of steel bars.

4. Spillway: During rainy season when the water reaching dam is very high the excess water may over the dam. This results the damage to the dam. Spillway is provided at the upper layer of the dam where the excess water flows through it.

5. Gates: The water stored in the reservoir is supplied to the generating station by opening the gates. Gates can be arranged in four different configurations.

1. Radial
2. Axial
3. Horizontal
4. Vertical.

6. Intake

When the spillway fails to operate the excess water can be sent to the turbine through the intake. Intake is provided with gates operating on principle of gravity.

1. Forebay:

It is the additional reservoir provided to ensure that the water stored in the main reservoir does not flow over the dam.

3. Surge tank:

Surge tank is located near the turbine of HES. When the load demand decreases, generation decreases, quantity of water to be supplied to the generating station must decrease before signal reaches operator the quantity of water discharged is high. In order to supply less water to turbine, the excess water is stored in surge tank. When the load demand increases or decreases the volume of water supplied to the generating station increases or decreases the water channel has to withstand the sudden variations in the load. This is known as water hammer.

1. Penstock:

The water channel through which the water is flowing from dam to generating station is known as penstock.

for low discharges penstock is made of 'STEEL'. for high discharges penstock is made of "reinforced concrete".

Question:

A hydroelectric power station is supplied water from a reservoir having storage capacity 50 km^2 across a dam. where the head of water is maintained at 50 m . the efficiency of turbine-glr set 60% calculate the rate of fall of water when hydro-electric power station is generating power at $30,000 \text{ kW}$.

Solution

$$A = 50 \text{ km}^2$$

$$h = 50 \text{ m}$$

$$\eta_{\text{turb}} = 60\%$$

$$P_t = 30,000 \text{ kW}$$

$$\text{Rate of fall of water } \text{m/sec} = \frac{Q (\text{m}^3/\text{sec})}{A (\text{m}^2)}$$

• Electrical power generated

$$P_t = 9.81 \times Q \times 50 \times 0.6$$

$$Q = \frac{30,000}{9.81 \times 50 \times 0.6} = 101.93 \text{ m}^3/\text{sec}$$

$$\therefore \text{Rate of fall} = \frac{101.93}{50 \times (10^3)^2} = 2.038 \times 10^{-6} \text{ m/sec}$$

2) The quantity of water stored across the reservoir is $3 \times 10^7 \text{ m}^3$.
 the head of the water $h = 150 \text{ m}$. If overall $\eta_{\text{gr}} = 70\%$ calculate
 the energy generated.

Soln

$$V = 3 \times 10^7 \text{ m}^3$$

$$h = 150 \text{ m}$$

$$\eta = 70\%$$

$$Q = \text{m}^3/\text{sec} \quad P_t \rightarrow \text{KW}$$

$$Q = \text{m}^3 \quad P_t \rightarrow \text{KW Sec}$$

$$P_t = 9.81 \times Q \times h \times \eta$$

$$P_e = 9.81 \times 3 \times 10^7 \times 150 \times 0.70 \quad \text{KW Sec}$$

• electrical power output in KW Sec = $3.089 \times 10^{10} \text{ KW Sec}$

$$\text{electrical power o/p in KWh} = \frac{3.089 \times 10^{10}}{3600}$$

$$P_e = 8.58 \times 10^6 \text{ KWh}$$

CLASSIFICATION OF TURBINE

1) Based on discharge of water:

1. High discharge
2. Medium discharge
3. Low discharge

• 2. Based on pressure of water:

a) Impulse: Pelton,

b) Reaction: Francis, Kaplan:

• 3. Based on direction of water flow:

a) Axial

b) Radial

c) Diagonal: → Denax → used in pump storage plant

d) Tangential

Denax turbine pumps water in diagonal direction and used in pumped storage plant.

• 4. Based on output power:

a) Low: 0-150000 Hp

b) Medium: 150000 - 350,000 Hp

c) High: > 350,000 Hp.

• 5. Based on specific speed:

$$(N \rightarrow \frac{1 \text{ m}^3}{\text{sec}}, P)$$

the speed at which turbine

rotates to develop 1 MW, when water is discharged at 1 m with the head of water maintain at 1 m.

$$\text{Specific speed } N_s = \frac{N \cdot P^{1/2}}{h^{5/4}}$$

$P \rightarrow$ power output in HP

$h \rightarrow$ head of water

$N \rightarrow$ actual speed in rpm.

Question:

A HEPs has average water discharge in a year as given below.

MONTH	DISCHARGE (m^3/sec)
Jan	200
Feb	400
March	600
April	2400
May	1800
June	1800
July	1600
Aug	1200
Sept	2000
Oct	1200
Nov	800
Dec	400

Calculate the average water flow and power generated when head of water is 50m and η of glr statⁿ being 90%
Draw the Hydrograph, flow duration curve and mass

curve for given data. Estimate the total storage capacity of the reservoir

Solution.

1) $Q = \frac{\text{water discharged}}{\text{no. of months in year}} = \frac{1380}{12} = 1150 \text{ m}^3/\text{sec}.$


2) for electrical power generated

$$P_t = 9.81 \times 1150 \times 0.9 \times 50$$

$$P_t = 507.6 \times 10^3 \text{ KW}$$

$$P_t = 507.6 \text{ MW}.$$

3) Hydrograph:

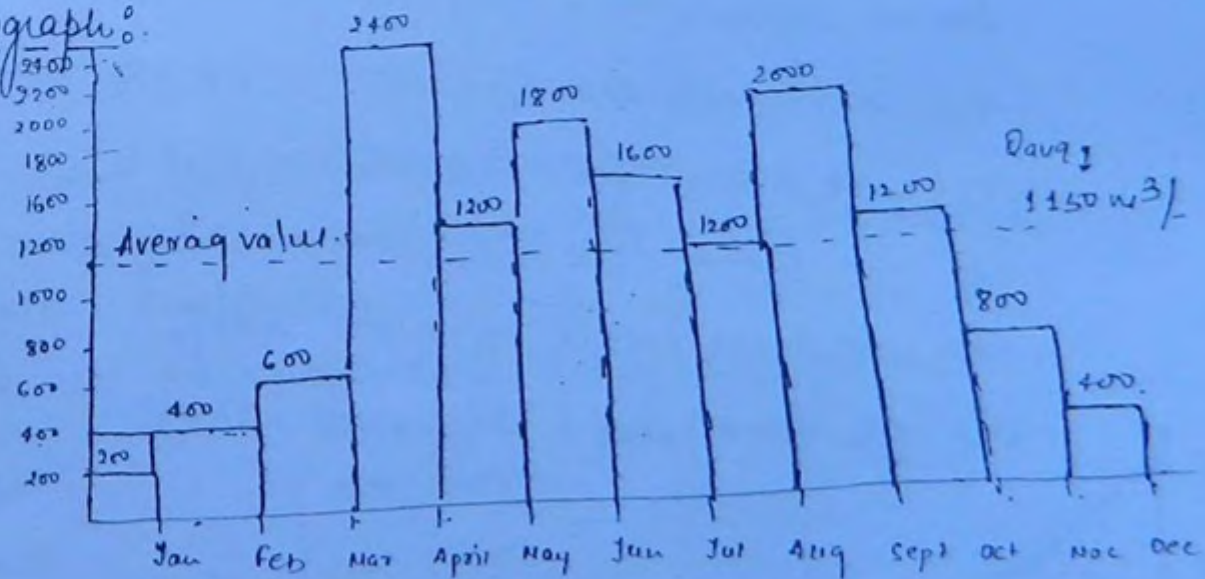

• From the hydrograph we can determine

- 1) the duration of max^m discharge.
- 2) the duration of min^m discharge.
- 3) Average discharge.

5). Flow duration curve: It gives the relation b/w the discharge in m^3/sec represented along Y-axis and percentage of time represented along X-axis.

• Jan $\rightarrow 200 m^3/sec = \frac{12}{12} \times 100 = 100\%$ (10)

• Feb $\rightarrow 400 m^3/sec = \frac{18}{12} \times 100 = 150\%$ 31.6%

• March $\rightarrow 600 m^3/sec = \frac{9}{12} \times 100 = 75\%$

• April $\rightarrow 2400 m^3/sec = \frac{1}{12} \times 100 = 8.33\%$

• May $\rightarrow 1200 m^3/sec = \frac{7}{12} \times 100 = 58.3\%$

• June $\rightarrow 1800 m^3/sec = \frac{3}{12} \times 100 = 25\%$

• Jul $\rightarrow 1600 m^3/sec = \frac{4}{12} \times 100 = 33.3\%$


• Aug $\rightarrow 1200 m^3/sec = \frac{7}{12} \times 100 = 58.3\%$

• Sept $\rightarrow 900 m^3/sec = \frac{2}{12} \times 100 = 16.67$

• Oct $\rightarrow 1200 m^3/sec = \frac{7}{12} \times 100 = 58.3\%$

• Nov $\rightarrow 800 m^3/sec = \frac{9}{12} \times 100 = 75\%$

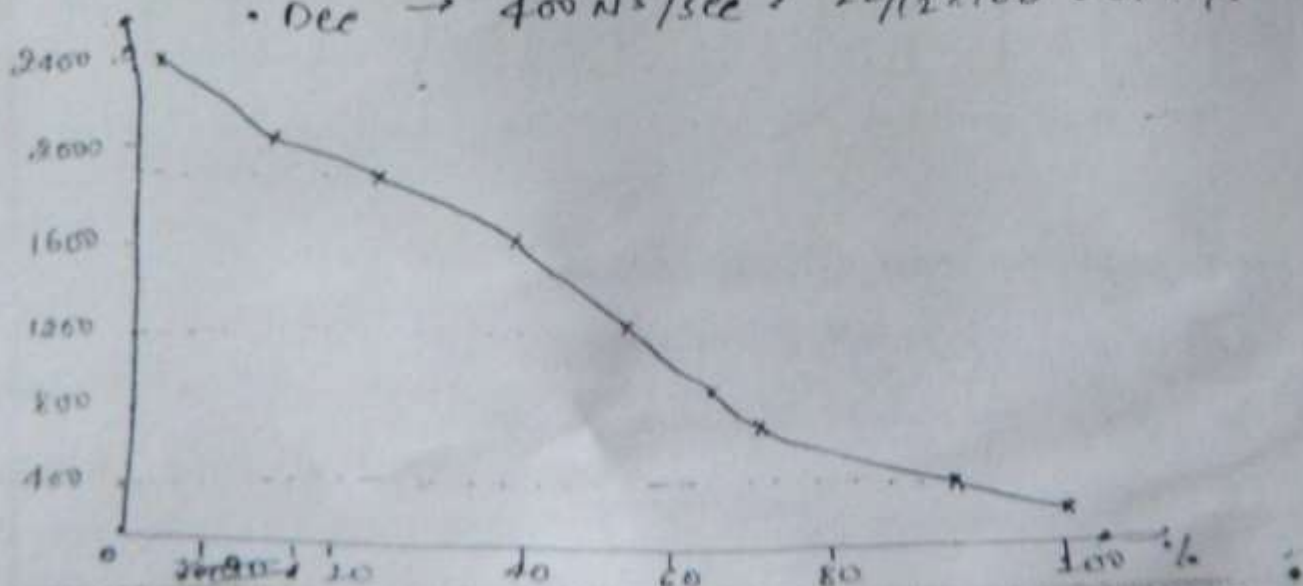• Dec $\rightarrow 400 m^3/sec = \frac{11}{12} \times 100 = 91.6\%$



4) total storage capacity:

- no store when water available $> 1250 \text{ m}^3/\text{sec}$.
- water is stored in the reservoir when quantity of water available is gr8 than quantity water sent to generating statⁿ.


total storage capacity

$$\begin{aligned} &= (2400 - 1150) + (1200 - 1150) \\ &= 1250 + 50 + 650 + 450 + 50 + 250 + 50 \\ &= 3350 \text{ m}^3/\text{sec} \\ &= \frac{3350 \times 24 \times 60 \times 60 \times 50}{1000} \\ &= 8.7 \times 10^8 \text{ m}^3/\text{month} \end{aligned}$$

5) MASS CURVE:

- find cumulative discharge.
- Mass curve gives the relation b/w cumulative discharge and time.. Cumulative discharge is obtained by adding all discharges upto end of that month



Jan - 200	Sept 11400
Feb = 600	Oct - 12600
March $\rightarrow$ 1200	Nov 13400
April $\rightarrow$ 3600	Dec 13800
May $\rightarrow$ 4800	
June $\rightarrow$ 6600	
July $\rightarrow$ 8200	
Aug $\rightarrow$ 9400	

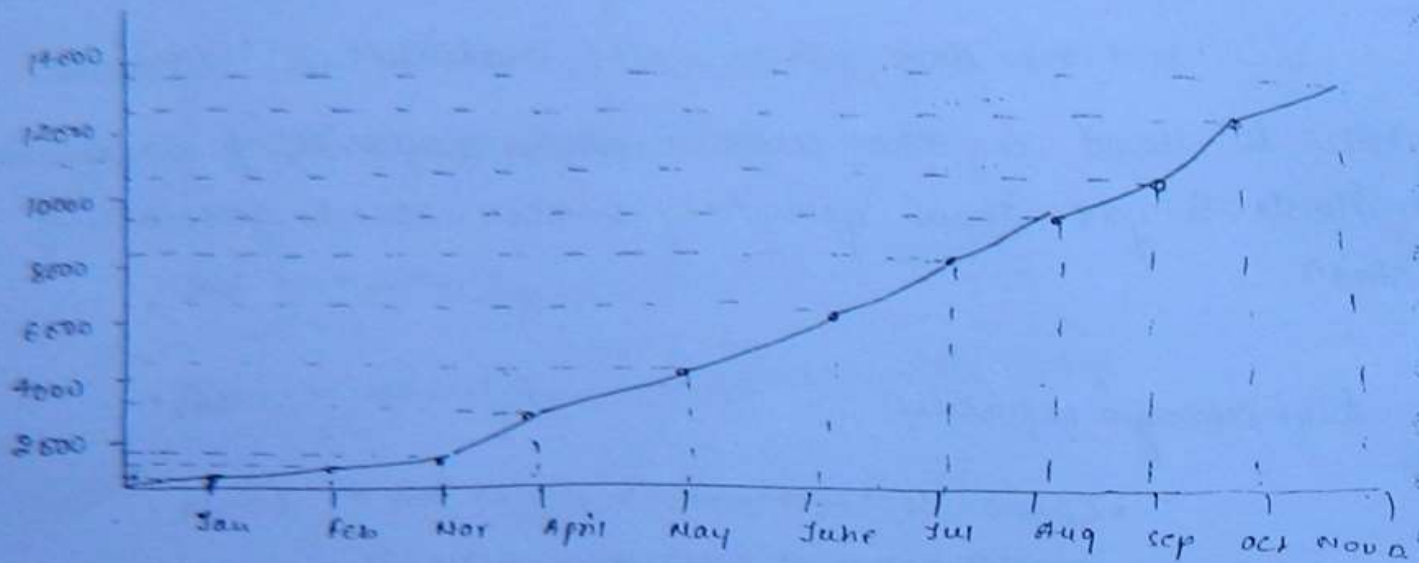

NUCLEAR GENERATING STATION

Nuclear Fission:

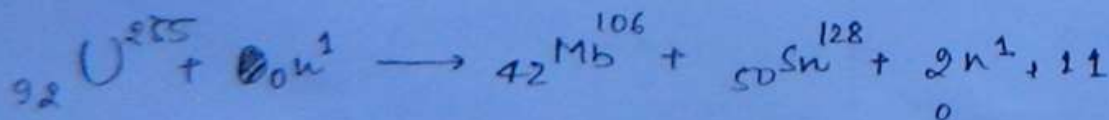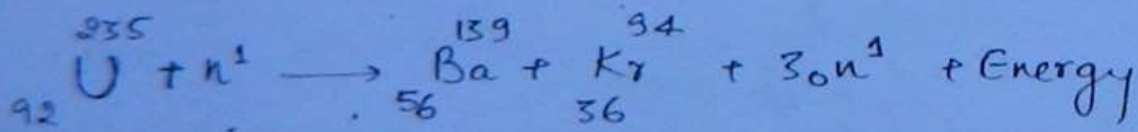When neutron collides with uranium isotope enormous amount of energy is released.




Critical Mass:

The minimum amount of mass required for nuclear chain reaction to continue is known as critical mass. for an uranium isotope.


the critical mass require 10kg. the energy generated by 1kg of Uranium is ~~250~~ 3500kg of coal.

- the process of chain reaction can be increased by following.


1. Conversion

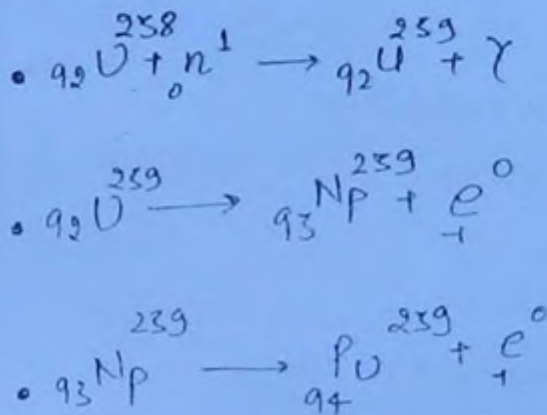

2. Breeding

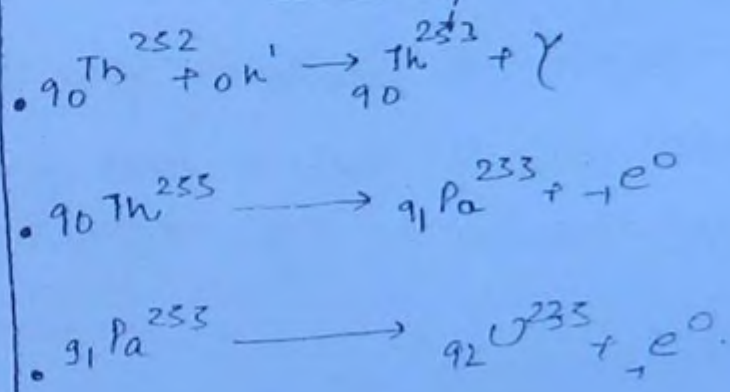

- Layout of Nuclear Power station:

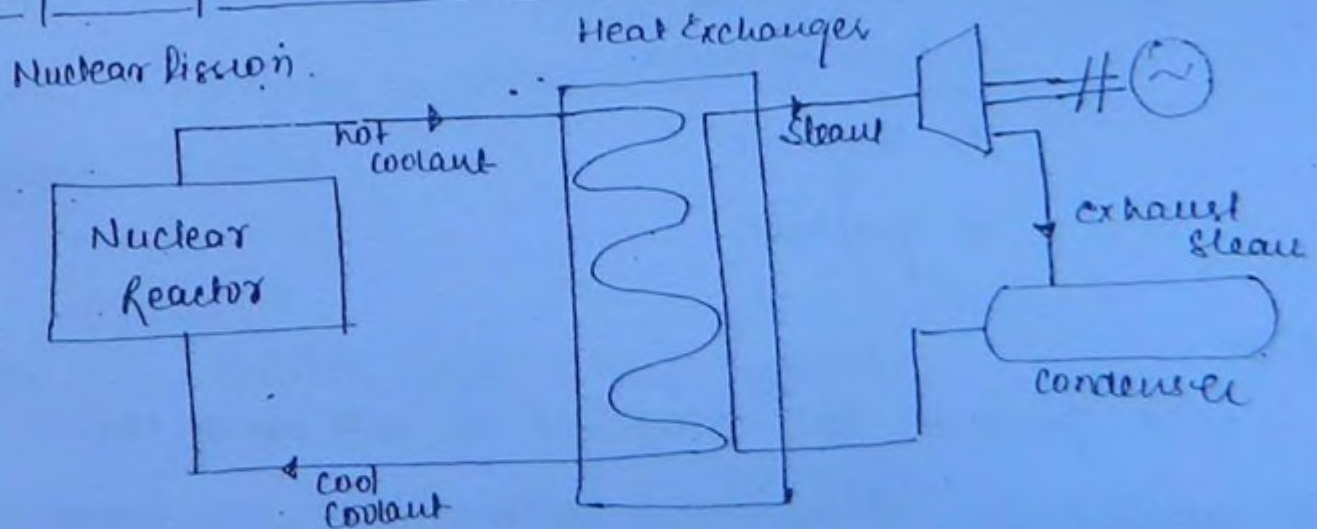

- on nuclear reactor heat transfer takes place during nuclear reaction and heat b/w heat generator & water from the condenser is converted into steam by absorbing heat of coolant.

COMPONENTS OF NUCLEAR POWER STATION

1. Reactor Core:

- In the reactor core nuclear fission take place and the energy is released
- Reactor core consist of fuel rods in the form of thin plates made of stainless steel for low capacity reactor and Zircalium for high capacity reactors.

2. Moderator:

- Moderator slows down the neutrons before they collide with uranium isotope
- Types of Moderators are.
 - a) Heavy water
 - b) Beryllium
 - c) Graphite

3. Reflector:

- It prevents the neutrons to come out of the reactor core.
- Reflector surrounds the reactor core.

4. Control Rod:

- Control rod ensures the safety of nuclear reactor

- During earthquakes control rod trips the nuclear-reactor and ensure safe operation.
- Material $\rightarrow$ high grade gbs graphite

5. Coolant:

- Coolant is used as heat transfer
- the cool water from condenser is converted into steam by absorbing the heat from the hot coolant

6. Multiplication factor (K):

$$K = \frac{\text{no. neutron released}}{\text{Neutron absorbed.}}$$

- 'K' determines the performance of nuclear reactor
- when no of neutrons released during fission is greater than no. of neutron absorbed. ($K > 1$).
- Always $1 < K < \infty$

LOAD FREQUENCY CONTROL

- To control the power output of alternators several generating stations are connected into a grid
- Grid connected s/m ensure frequency to be constant.
- Alternators connected in the form of group maintains


constant frequency.

- When load demand increases, power generation must be increased, alternator must generate more electrical power, turbine has to supply more mechanical energy to the alternator, the steam supply to turbine must increase, and SPEED GARNER must identify the increase in the load demand.

Design of speed Governor :

• Its components are:

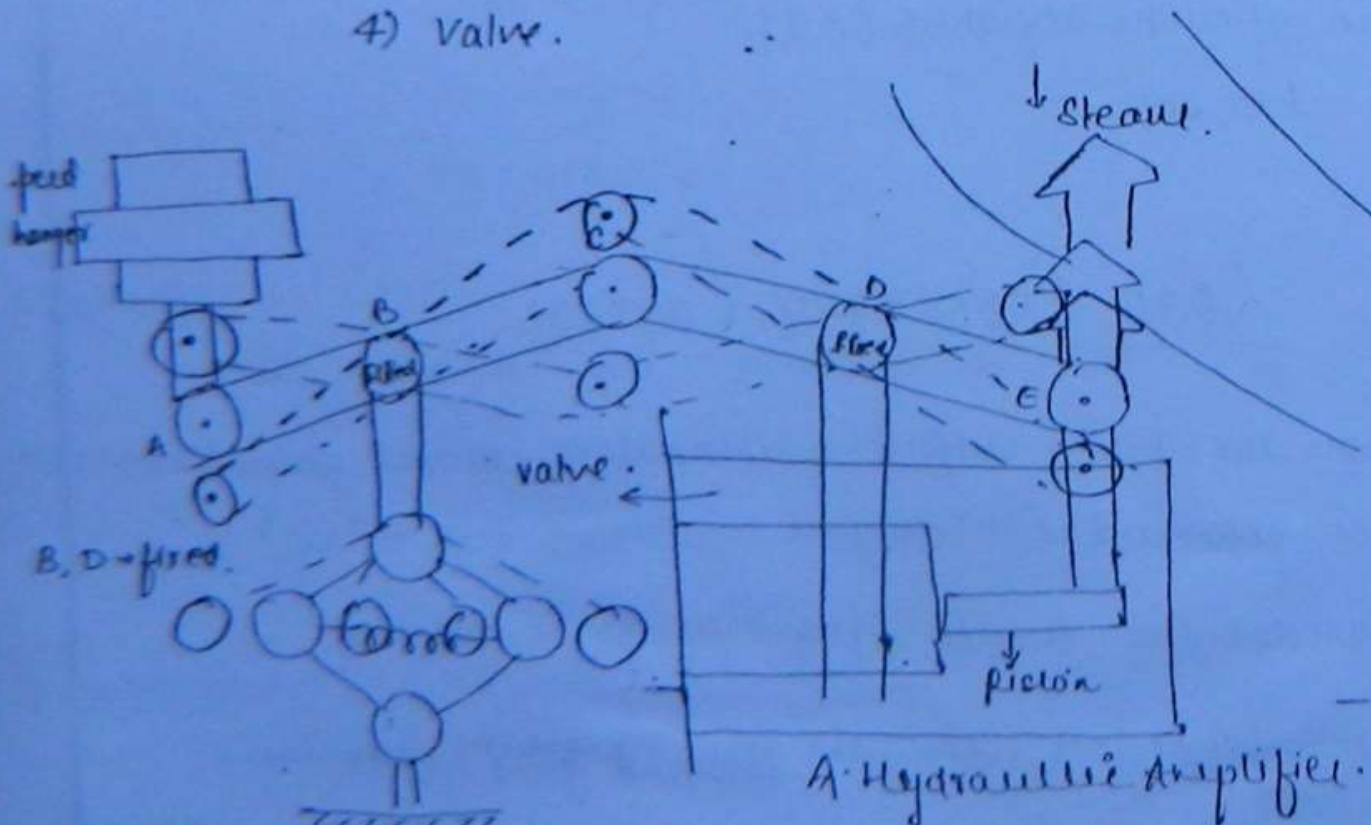- 1) speed changer
- 2) Hydraulic Amplifier
- 3) Linkage Mechanism
- 4) Valve.



• Condition 1: Increase in load demand

- # Generation must increase
- # speed of turbine must increase
- # speed changer is pulled in downward direction
- # Point A moves in downward direction depends on speed governor signal.
- # Point 'C' moves in upward direction
- # Point 'E' moves in downward direction
- # the inlet to the steam is increased.
- # Mechanical energy at the I/P alternator increase
- # Electrical energy generated by alternator increases

• Condition 2: Decrease in load demand

- # Generation must decrease
- # speed of turbine must decrease
- # speed changer is pulled in upward direction depending on signal of speed governor
- # Point A moves upward depending on speed governor signal
- # Point 'C' moves in downward direction
- # Point 'E' moves in upward direction
- # the inlet to steam is decreased
- # Mechanical energy at the I/P alternator decreases

decreases

Electrical energy generated by alternator decreases

• The load frequency control depends on:

1. Movement of fly ball governor and there after the speed changer

• Hydraulic amplifier determines actual steam input to the turbine

DESIGN EQUATIONS:

• Point 'A' and 'C' moves in opposite direction

• Let ΔP_c be the command signal given by the speed governor to the speed changer

A ↓ downward direction

speedchanger ↓ "

← governor → (expansion)

$$y_A \propto \Delta P_c$$

$$y_A = K_c \Delta P_c$$

• The extent to which point 'C' moves in

upward direction is equal to extent to point 'A' move in downward directⁿ.

$$y_c \propto (-y_A)$$

$$y_c \propto (-K_c \cdot \Delta P_c)$$

$$\boxed{y_c = -K_1 K_c \Delta P_c} \dots \dots \dots (1)$$

- Assume that volume of oil sent to hydraulic amplifier is increased. Therefore point E moves in downward directⁿ resulting in movement of point C in upward directⁿ.

$$y_c \propto (-y_E) \quad C \uparrow \text{ when } E \downarrow$$

$$\propto (\Delta f) \quad \rightarrow \text{as steam inlet } \uparrow \text{ generat}^n \uparrow \text{ frequency } \uparrow$$

$$\boxed{y_c = K_2 \Delta f} \dots \dots \dots (2)$$

- the movement of point 'A' is related w.r.t to frequency,

$$\boxed{y_c = -K_1 K_2 \Delta P_c + K_2 \Delta f} \dots \dots \dots (3)$$

$$y_d =$$

- point 'D' is located at the middle of the second section. the movement of point D is affected by the position 'C' and 'E'

$$\Delta y_c = -K_1 K_c \Delta y_A + K_2 \Delta f \quad \text{--- (3)}$$

$$\Delta y_D = K_3 \Delta y_c + K_4 \Delta y_e \quad \text{--- (4)}$$

$$\Delta y_e =$$

The volume of oil in hydraulic amplifier determine the movement point 'E'. For ' Δy_e ' to be positive, oil is taken from the hydraulic cylinder.

Depending on the position of point 'D' - Δy_e is determined.

$$\Delta y_e \propto - \int (\Delta y_D) dt$$

since oil is stored in cylinder the integral is applied.

$$\boxed{\Delta y_e = -K_5 \int (\Delta y_D) dt} \quad \text{--- (5)}$$

applying Laplace transform to the equations (3), (4), (5)

$$\Delta y_c(s) = -K_1 K_c \Delta y_A(s) + K_2 \Delta f(s) \quad \text{--- (6)}$$

$$\Delta y_D(s) = K_3 \Delta y_c(s) + K_4 \Delta y_e(s) \quad \text{--- (7)}$$

$$\Delta y_e(s) = -\frac{K_5}{s} \Delta y_D(s) \quad \text{--- (8)}$$

substituting eqn (7) in (8)

from the equation (7) and (8)

$$\Delta Y_D(s) = K_3 \Delta Y_C(s) + K_4 \left\{ -\frac{K_5}{s} \Delta Y_D(s) \right\}$$

8 → 7

$$\Delta Y_D(s) + \frac{K_4 K_5}{s} \Delta Y_D(s) = K_3 \Delta Y_C(s)$$

$$= \Delta Y_D(s) \left\{ 1 + \frac{K_4 K_5}{s} \right\} = K_3 \Delta Y_C(s)$$

$$\Rightarrow \Delta Y_C(s) = \Delta Y_D(s) \left\{ \frac{1}{K_3} + \frac{K_4 K_5}{s K_3} \right\} \dots \dots (9)$$

9 → 6

$$\Delta Y_D(s) \left\{ \frac{1}{K_3} + \frac{K_4 K_5}{s K_3} \right\} = -K_1 K_C \Delta P_D(s) + K_2 \Delta F(s) \dots \dots (10)$$

equation 10 represents the change in position in terms of frequency

from eqn 8 we have:

$$\Delta Y_E(s) = -\frac{K_5}{s} \Delta Y_D(s) = -\frac{s}{K_5} \Delta Y_E(s) \dots \dots (11)$$

11 → 10

$$= -\frac{s}{K_5} \Delta Y_E(s) \left\{ \frac{1}{K_3} + \frac{K_4 K_5}{s K_3} \right\} = -K_1 K_C \Delta P_D(s) + K_2 \Delta F(s)$$

$$= -\Delta Y_E(s) \left\{ \frac{s}{K_3 K_5} + \frac{K_4}{K_3} \right\} = -K_1 K_C \Delta P_D(s) + K_2 \Delta F(s)$$

$$= \Delta Y_E(s) \left\{ \frac{s + K_4 K_5}{K_3 K_5} \right\} = K_1 K_C \Delta P_D(s) - K_2 \Delta F(s)$$

$$\Rightarrow \Delta Y_E(s) = \left(\frac{K_3 K_5}{s + K_4 K_5} \right) (K_1 K_2 \Delta P_D(s)) - \left(\frac{K_3 K_5}{s + K_4 K_5} \right) K_2 \Delta F(s)$$

Adding $K_4 K_5$

$$\Rightarrow \Delta Y(s) = \left[\frac{\frac{K_3 K_5}{K_4 K_5}}{1 + \frac{s}{K_4 K_5}} \right] (K_1 K_c \Delta P_c(s)) - \left[\frac{\frac{K_3 K_5}{K_4 K_5}}{1 + \frac{s}{K_4 K_5}} \right] (\Delta R(s))$$

$$\Delta Y(s) = \left[\frac{\frac{K_1 K_c K_3}{K_4}}{1 + \frac{s}{K_4 K_5}} \right] (\Delta P_c(s)) - \left[\frac{\frac{K_2 K_3}{K_4}}{1 + \frac{s}{K_4 K_5}} \right] \Delta R(s)$$

$$\Rightarrow \Delta Y(s) = \left[\frac{\frac{K_1 K_c K_3}{K_4} \Delta P_c(s) - \frac{K_2 K_3 \Delta R(s)}{K_4}}{1 + \frac{s}{K_4 K_5}} \right]$$

$$\Rightarrow \left(\frac{K_1 K_c K_3}{K_4} \right) \left\{ \frac{\Delta P_c(s) - \left(\frac{K_2 K_3}{K_4} \right) \left(\frac{K_4}{K_1 K_c K_3} \right) \Delta R(s)}{1 + \frac{s}{K_4 K_5}} \right\}$$

$$G(s) \Rightarrow \frac{\left(\frac{K_1 K_c K_3}{K_4} \right)}{\left(1 + \frac{s}{K_4 K_5} \right)} \left\{ \Delta P_c(s) - \frac{1}{K_1 K_c / K_2} \Delta R(s) \right\}$$


• gain constant speed governor ω/μ

$$K_{sg} = \frac{K_1 K_c K_5}{K_4}$$

$$T_{sg} = \frac{1}{K_4 K_5}$$

• Regulation $\neq$ of speed governor $\&$ $R = \frac{K_1 K_c}{K_2}$
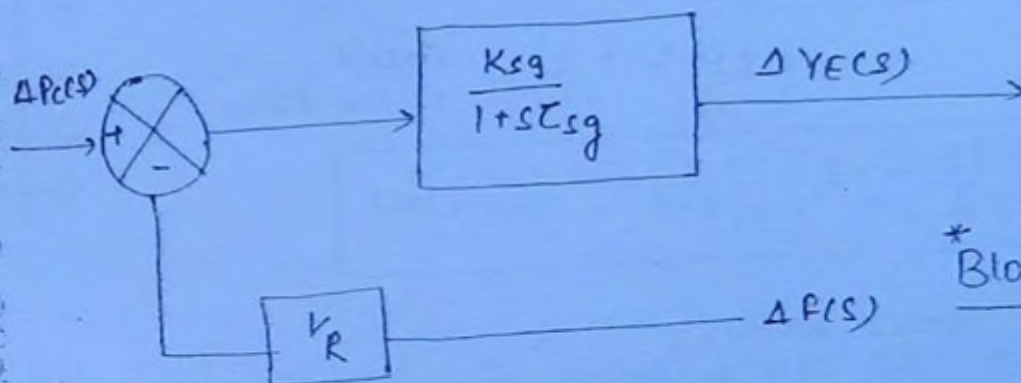
$$\Delta Y_E(s) = \left\{ \Delta P_c(s) - \frac{1}{R} \Delta F(s) \right\} \frac{K_{sg}}{1 + sT_{sg}}$$



* Block Diagram

$$\frac{\Delta Y_E(s)}{\Delta P_c(s) - \frac{1}{R} \Delta F(s)} = \frac{K_{sg}}{1 + sT_{sg}}$$


• DESIGN OF TURBINE?

1. INPUT:- change in position 'E', $\Delta Y_E(s)$

2. OUTPUT:- Change in power developed by turbine ΔP_t

$$\frac{\Delta P_t}{\Delta Y_E(s)} = \frac{K_t}{1 + sT_t}$$

• Block diagram:

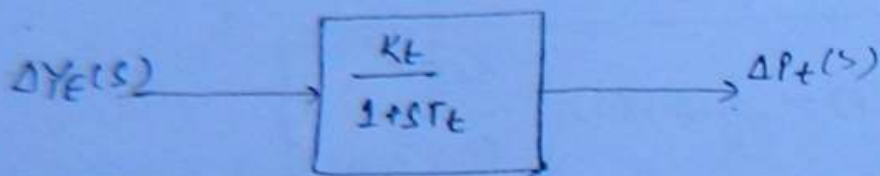

$\Delta Y_E(s)$ = input to the turbine as well as output of speed governor.

Dated
11 Oct 2020

DESIGN OF ALTERNATOR.

• the design of alternator deals with:-

1) Kinetic Energy stored by rotor of alternator

At the operating frequency $f_0 = 50\text{Hz}$, the K.E stored by alternator

$$W_{KE0} \propto f_0^2 \quad \dots \dots \dots (1)$$

let Δf be the change in frequency

$$\therefore f_{\text{new}} = (f_0 + \Delta f)$$

$$W_{KE(\text{new})} \propto f_{\text{new}}^2$$

$$\Rightarrow W_{KE(\text{new})} \propto (f_0 + \Delta f)^2 \quad \dots \dots \dots (2)$$

The K.E stored by the alternator due to change in frequency is $W_{KE(\text{new})}$.

from the equatⁿ (1) and (2)

$$\begin{aligned} \left(\frac{2}{1}\right) \rightarrow \frac{W_{KE(new)}}{W_{KE0}} &= \frac{(f_0 + \Delta f)^2}{f_0^2} \\ &= \frac{f_0^2 + \Delta f^2 + 2f_0\Delta f}{f_0^2} \\ &= \frac{f_0^2}{f_0^2} + \underbrace{\frac{\Delta f^2}{f_0^2}}_{\text{neglected as } (2/50)^2 = \text{very small}} + \frac{2f_0\Delta f}{f_0^2} \\ &= \left(1 + 2\frac{\Delta f}{f_0}\right) \end{aligned}$$

$$\boxed{W_{KE(new)} = W_{KE0} \left(1 + 2\frac{\Delta f}{f_0}\right)} \quad \text{--- (3)}$$

According to dynamics relating w/c the K.E stored by alternator

$$\begin{aligned} W_{KE0} &= H \times P_{rated} \quad \text{--- (4)} \\ &= H \times P_r, \text{ inertia constant} \end{aligned}$$

4 → 3

$$W_{KE(new)} = (H \times P_r) \left[1 + 2\frac{\Delta f}{f_0}\right]$$

$$\boxed{W_{KE(new)} = H P_r + \frac{2H P_r \Delta f}{f_0}} \quad \text{--- (5)}$$

By differentiating the above equatⁿ the electrical power developed by alternator is obtained:

$$\frac{d(W_{KE(new)})}{dt} = \frac{2H P_r}{f_0} \cdot \frac{d(\Delta f)}{dt} \quad \text{--- (6)}$$

The change in the load demand wrt change in the frequency is represented as:

The change in load demand due to all factors $\rightarrow \Delta P_D$

The change in frequency due all factor $\rightarrow \Delta f$.

Since the load demand changes not only due to frequency, the total change in load demand.

$$= \left(\frac{\partial P_D}{\partial f} \right) \Delta f.$$

$$= (B) \Delta f \dots \textcircled{7} \text{ unit W/Hz}$$

According to the power balance equation

$$\Delta P_G - \Delta P_D = \frac{2HP_r}{f_0} \frac{d(\Delta f)}{dt} + B \Delta f.$$

By considering rated capacity of alternator ' P_r ' as the reference/base value the power balance equation can be expressed in terms p.u

$$\Rightarrow \frac{\Delta P_G}{P_r} - \frac{\Delta P_D}{P_r} = \frac{\frac{2HP_r}{f_0}}{P_r} \frac{d(\Delta f)}{dt} + B_{p.u} \Delta f$$

$$\Rightarrow \Delta P_{G,p.u} - \Delta P_{D,p.u} = \frac{2H}{f_0} \frac{d(\Delta f)}{f_0 dt} + B_{p.u} \Delta f \dots \textcircled{8}$$

* In numerical B is given as $B_{p.u} \text{ MW/Hz}$.

Applying Laplace transform:

$$\Delta P_{G,pu}(s) - \Delta P_{D,pu}(s) = \frac{2H}{f_0} [s \Delta F(s)] + B_{pu} \Delta F(s)$$

$$\Rightarrow \Delta P_{G,pu}(s) - \Delta P_{D,pu}(s) = \Delta F(s) \left[\frac{s \cdot 2H}{f_0} + B_{pu} \right]$$

$$\Rightarrow \Delta F(s) = \frac{1}{\left[\frac{s \cdot 2H}{f_0} + B_{pu} \right]} \left\{ \Delta P_{G,pu}(s) - \Delta P_{D,pu}(s) \right\} \dots \dots (10)$$

Divide by B_{pu}

$$\Delta F(s) = \frac{1/B_{pu}}{\left[\frac{s \cdot 2H}{f_0 B_{pu}} + 1 \right]} \left[\Delta P_{G,pu}(s) - \Delta P_{D,pu}(s) \right] \dots \dots (11)$$

• gain constant of alternator $\rightarrow \frac{1}{B_{pu}}$

• Time constant of alternator/power sys $\rightarrow \frac{2H}{f_0 B_{pu}}$


**

$$\Delta F(s) = \frac{K_{ps}}{(1 + sT_{ps})} \left\{ \Delta P_{G,pu}(s) - \Delta P_{D,pu}(s) \right\}$$


Transfer function of alternator is:

$$\frac{\Delta F(s)}{\Delta P_{G,pu}(s) - \Delta P_{D,pu}(s)} = \frac{K_{ps}}{1 + sT_{ps}}$$

* Block Diagram:

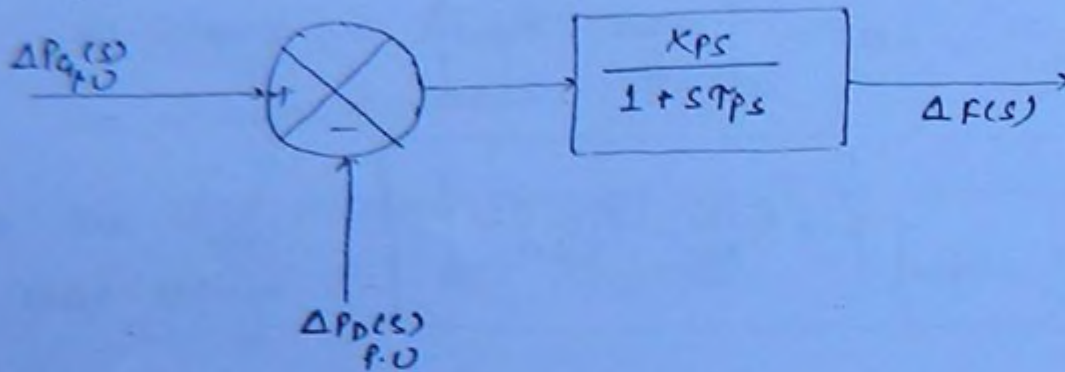

BLOCK DIAGRAM OF ISOLATED POWER SYSTEM:

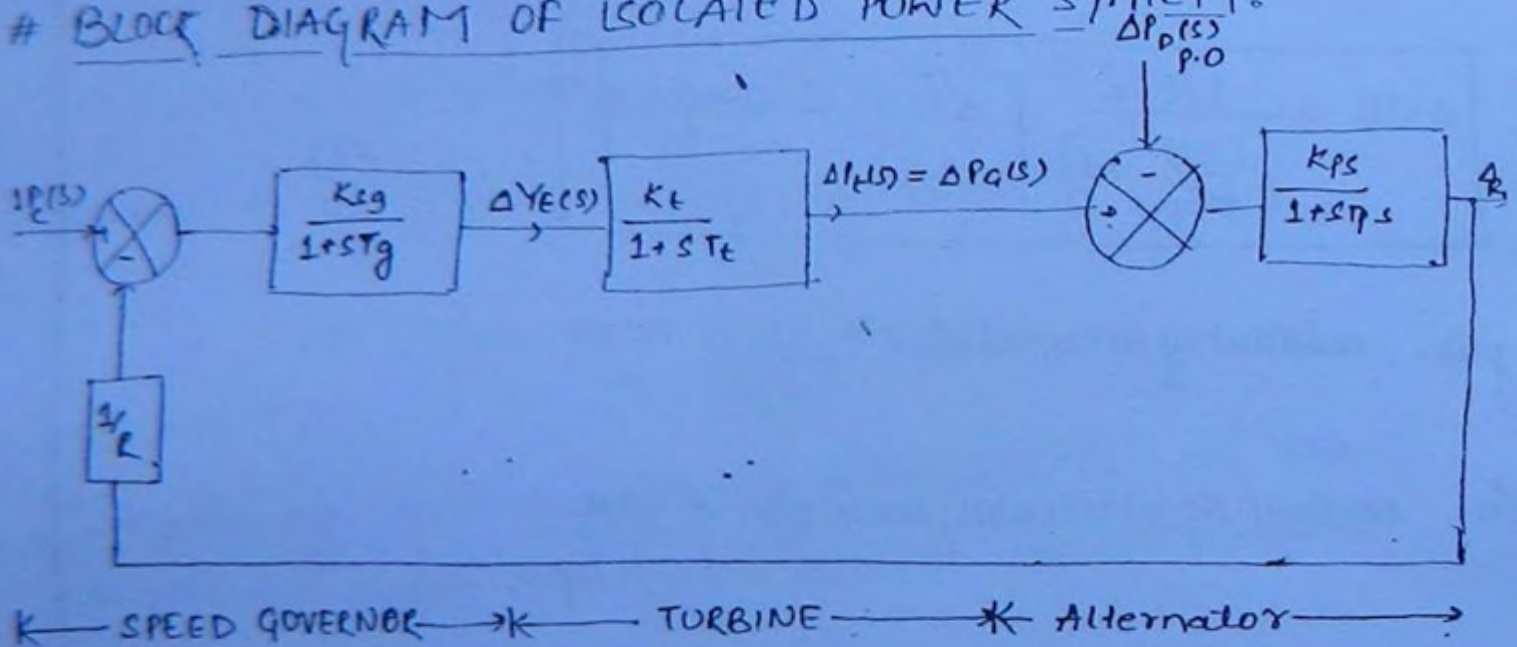

Question:

Determine the load-frequency control loop parameters of a control area with following data.

- 1) Total rated capacity 2000 MW
- 2) Normal operating load 1000 MW
- 3) Inertia constant $H = 5$

Regulation $R = 2.4 \text{ Hz/MW}$

change in load demand w.r.t frequency is 16.67 MW/Hz

Soln

$$B \approx \frac{\partial P_D}{\partial f} = 16.67 \text{ MW/Hz}$$

$$B_{pu} = \frac{B}{P_r} = \frac{16.67}{2500} = 8.335 \times 10^{-5} \text{ pu MW/Hz}$$

$$K_{ps} = \frac{1}{B_{pu}} = 120 \text{ Hz/MW}$$

$$T_{ps} = \frac{2H}{f_0 B_{pu}} = \frac{2 \times 15}{8.335 \times 10^{-5}} = 24 \text{ sec}$$

• default values of time constant when not given in numericals:


$T_{sg} = 0.4 \text{ sec}$
 $T_t = 0.5 \text{ sec}$
 $T_{ps} = 20 \text{ sec}$

STEADY STATE ANALYSIS..

Steady-state analysis deals with determining ' Δf ' due to ΔP_c and ΔP_D

• Condition 1: change in frequency of due to change in speed changer setting.

$$\Delta P_D(s) = 0$$

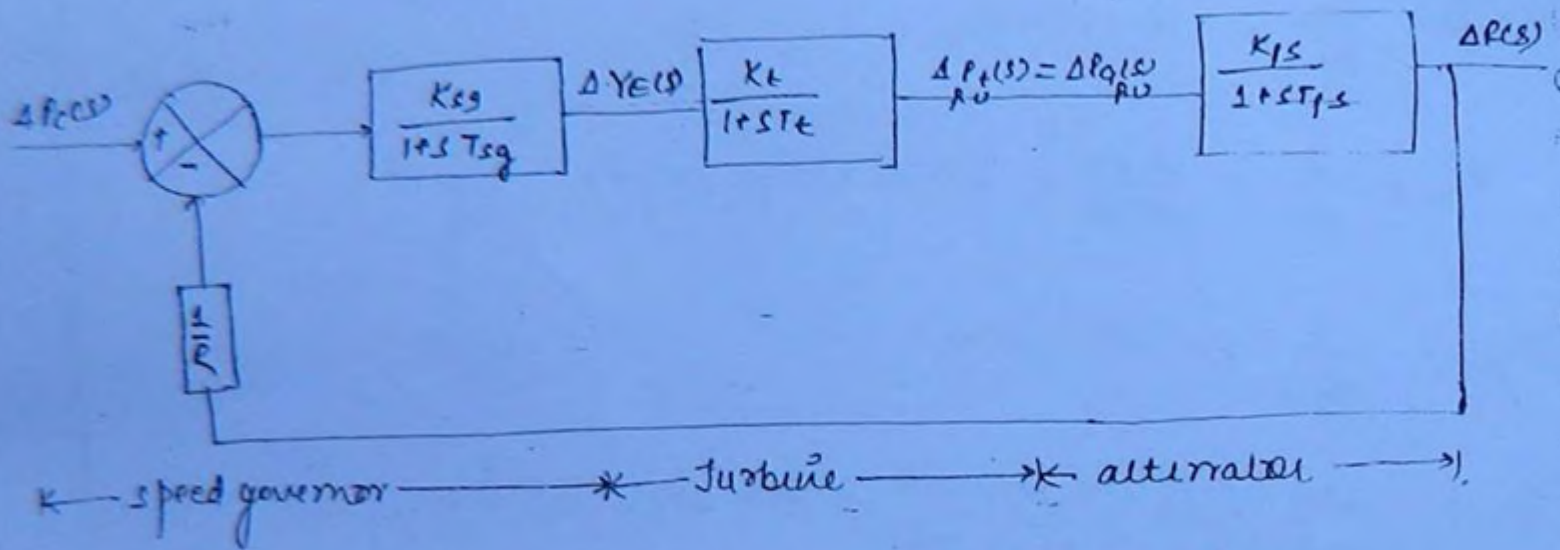

$$\left. \frac{\Delta F(s)}{\Delta P_D(s)} \right|_{\Delta P_D(s)=0} = \frac{\left(\frac{K_{sg}}{1+sT_{sg}} \right) \left(\frac{K_t}{1+sT_t} \right) \left(\frac{K_{ps}}{1+sT_{ps}} \right)}{1 + \frac{1}{R} \left[\left(\frac{K_{sg}}{1+sT_{sg}} \right) \left(\frac{K_t}{1+sT_t} \right) \left(\frac{K_{ps}}{1+sT_{ps}} \right) \right]}$$

$$\Delta F(s) = \frac{\left(\frac{K_{sg}}{1+sT_{sg}} \right) \left(\frac{K_t}{1+sT_t} \right) \left(\frac{K_{ps}}{1+sT_{ps}} \right)}{1 + \frac{1}{R} \left[\left(\frac{K_{sg}}{1+sT_{sg}} \right) \left(\frac{K_t}{1+sT_t} \right) \left(\frac{K_{ps}}{1+sT_{ps}} \right) \right]} \cdot \Delta P_D(s)$$

After taking L.C.M.:

$$\left. \Delta F(s) \right|_{\Delta P_D(s)=0} = \frac{K_{sg} \cdot K_t \cdot K_{ps}}{(1+sT_{sg})(1+sT_t)(1+sT_{ps}) + \frac{1}{R} K_{sg} K_t K_{ps}} \cdot \frac{\Delta P_D(s)}{s}$$

$$\text{error } e_{ss} = \lim_{s \rightarrow 0} s E(s)$$

the steady state change in the frequency Δf

$$\Delta f = \lim_{s \rightarrow 0} s \cdot \Delta f(s)$$

$$= \lim_{s \rightarrow 0} \left\{ \frac{K_{sg} \cdot K_t \cdot K_{ps}}{(1+sT_{sg})(1+sT_t)(1+sT_{ps}) + \frac{K_{sg} K_t + K_{ps}}{R}} \right\} \frac{\Delta P_c}{s}$$

$$= \frac{K_{sg} \cdot K_t \cdot K_{ps}}{(1+0 \cdot T_{sg})(1+0 \cdot T_t)(1+0 \cdot T_{ps}) + \frac{K_{sg} K_t + K_{ps}}{R}} \cdot \Delta P_c$$

$$= \frac{K_{sg} \cdot K_t \cdot K_{ps}}{1 + \frac{K_{sg} K_t + K_{ps}}{R}} \cdot \Delta P_c$$

consider $K_{sg} K_t = 1$

as in general
 $K_{sg} = 0.7$
 $K_t = 1.55$


$$\Delta f \Big|_{\Delta P_c \rightarrow 0} = \frac{K_{ps}}{1 + \frac{K_{ps}}{R}} \cdot \Delta P_c$$

$\div K_{ps}$

$$\Delta f \Big|_{\Delta P_c \rightarrow 0} = \frac{1}{\frac{1}{K_{ps}} + \frac{1}{R}} \cdot \Delta P_c$$


$$\Delta f \Big|_{\Delta P_c \rightarrow 0} = \frac{1}{B_{p,0} + \frac{1}{R}} \cdot \Delta P_c \quad \text{--- (1)}$$

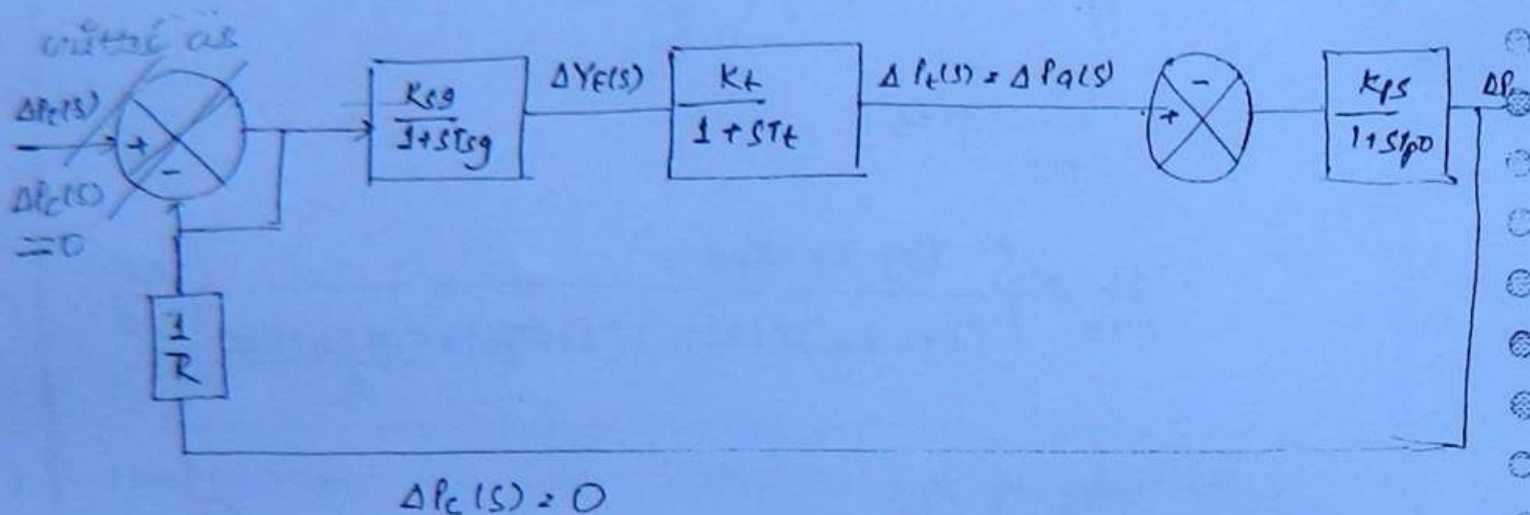- condition 2: change in frequency Δf due to ΔP_D .



- ~~speed changer sett~~

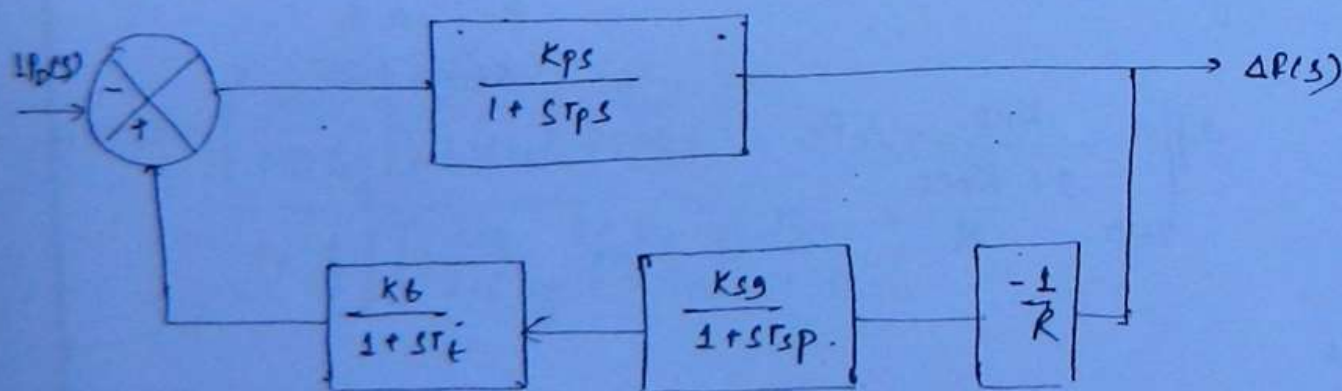- $\Delta P_c(s) = 0$ represents free governor operation (speed changer setting is constant)



$$\left. \frac{\Delta P(s)}{\Delta P_D(s)} \right|_{\Delta P_c(s) = 0}$$

$$= \frac{- \left(\frac{K_{ps}}{1 + sT_{ps}} \right)}{1 + \left\{ \left(\frac{K_{ps}}{1 + sT_{ps}} \right) \left(\frac{K_t}{1 + sT_t} \right) \left(\frac{K_{sg}}{1 + sT_{sg}} \right) \left(-\frac{1}{R} \right) \right\}}$$

Take LCM and Simplify:

$$\Delta F(s) \Big|_{\Delta P_c(s) \neq 0} = \frac{- \left(\frac{K_p s}{1 + s T_p s} \right)}{1 + \left\{ \left(\frac{K_p s}{1 + s T_p s} \right) \left(\frac{K_t}{1 + s T_t} \right) \left(\frac{K_g}{1 + s T_g} \right) \left(\frac{1}{R} \right) \right\}} \cdot \Delta P_D(s)$$

$$\Delta F(s) \Big|_{\Delta P_c(s) \neq 0} = \frac{- K_p s}{(1 + s T_p s)(1 + s T_t)(1 + s T_g) + \frac{K_p s K_g K_t}{R}} \cdot \frac{\Delta P_D}{s}$$

steady state change in frequency

$$= \lim_{s \rightarrow 0} s \cdot \left[\frac{- K_p s (1 + s T_t)(1 + s T_g)}{(1 + s T_p s)(1 + s T_t)(1 + s T_g) + \frac{K_p s K_g K_t}{R}} \right] \frac{\Delta P_D}{s}$$

$$\Delta F(s) = \frac{- K_p s}{1 + \frac{K_p s K_g K_t}{R}} \cdot \Delta P_D$$

Taking $K_g K_t = 1$

$$\Delta F(s) \Big|_{\Delta P_c(s) \neq 0} = \frac{- K_p s}{1 + \frac{K_p s}{R}} \cdot \Delta P_D$$

$\div K_p$

$$\Delta F(s) \Big|_{\Delta P_c(s) \neq 0} = \frac{-1}{B_f \cdot s + \frac{1}{R}} \cdot \Delta P_D$$

$$\therefore \frac{1}{K_p} = B_f \cdot 0$$

$$\text{Total } \Delta f_{s.s} = \Delta f_{s.s} \Big|_{\Delta P_D(s) = 0} + \Delta f_{s.s} \Big|_{\Delta P_C(s) = 0}$$

$$= \frac{\Delta P_C}{B_{pu} + \frac{1}{R}} - \frac{\Delta P_D}{B_{pu} + \frac{1}{R}}$$

$$\Delta f_{s.s} = (\Delta P_C - \Delta P_D) \left(\frac{1}{B_{pu} + \frac{1}{R}} \right) \text{ --- Steady state frequency change.}$$

Question:

Consider the Block diagram of load frequency control.
the following approximation is made regarding the analysis

$$(1 + sT_{sg})(1 + sT_t) = 1 + (T_{sg} + T_t)s = 1 + sT_{eq}$$

Determine $\Delta f(t)$ when $\Delta P_D = 0.01$
etc

Solution:

the given data corresponds to free governor operation
when $\Delta P_C(s) = 0$

$$\frac{\Delta P_D(s)}{\Delta P_C(s)} = \frac{-\left(\frac{K_P s}{1 + sT_P s}\right)}{1 + \left(\frac{K_P s}{1 + sT_P s}\right)\left(\frac{K_{sg}}{1 + sT_{sg}}\right)\left(\frac{K_t}{1 + sT_t}\right)\frac{1}{R}}$$

⇒ taking default value.

$$1 + (T_{sg} + T_t) s = 1 + (0.4 + 0.5) s = 1 + 0.9 s$$

$$\Delta F(s) = \frac{- \left[\frac{K_{ps}}{1 + s T_{ps}} \right]}{1 + \left(\frac{K_{ps}}{1 + s T_{ps}} \right) \left(\frac{K_{sg}}{1 + s T_{sg}} \right) \left(\frac{K_t}{1 + s T_t} \right)} \cdot \frac{1}{R}$$

$$\Delta F(s) = \frac{- \left(\frac{100}{1 + 20s} \right)}{1 + \left(\frac{100}{1 + 20s} \right) \left(\frac{1}{1 + 0.9s} \right) \left(\frac{1}{3} \right)} \cdot \frac{0.01}{s}$$

Since

$$K_{ps} = \frac{1}{B_{p.v}} = \frac{1}{0.01} \text{ (default value)} = 100$$

$$R = 3 \text{ (default)}$$

$$K_{sg} K_t = 1 \text{ (default)}$$

$$T_{ps} = 20 \text{ (default)}$$

$$\Delta F(s) = \frac{- 100 (1 + 0.9s)}{(1 + 20s)(1 + 0.9s) + \frac{100}{3}} \cdot \frac{0.01}{s}$$

$$\Rightarrow \frac{- 100 - 90s}{1 + 20.9s + 18s^2 + \frac{100}{3}} \cdot \frac{0.01}{s}$$

$$\Delta f(s) = \frac{-(1+0.9s)}{s(18s^2+20.9s+\frac{10}{3})}$$

$$\Rightarrow \Delta f = \lim_{s \rightarrow 0} s f(s)$$

$$= \frac{-1(1+0.9s)}{18s^2+20.9s+\frac{10}{3}}$$

$$= \frac{-1}{103/3}$$

$$\Delta f = \frac{-3}{103} = -0.0289 \text{ Hz}$$

$$\boxed{\Delta f = 0.0289 \text{ Hz}}$$

DYNAMIC RESPONSE

Dynamic response of a s/m is obtained for the step changes in the load demand.

• Dynamic response deals with following assumption:

1) Free governor operation ($\Delta f_c(s) = 0$)



2) $K_{cg}K_t = 1$

3) $T_{sg} \approx 0$, $T_t \approx 0$

So,

$$\left(\frac{K_{eg}}{1+sT_{eg}} \right) \left(\frac{K_t}{1+sT_t} \right) = \frac{1}{(1+s \cdot 0)(1+s \cdot 0)} = 1$$

$\Delta P_o(s)$

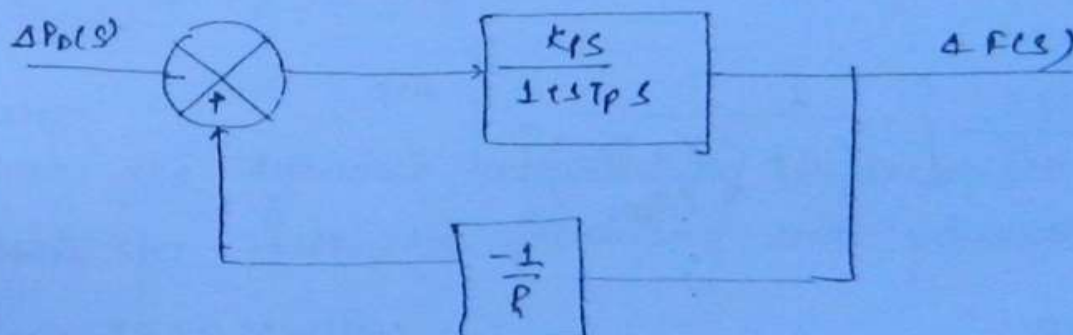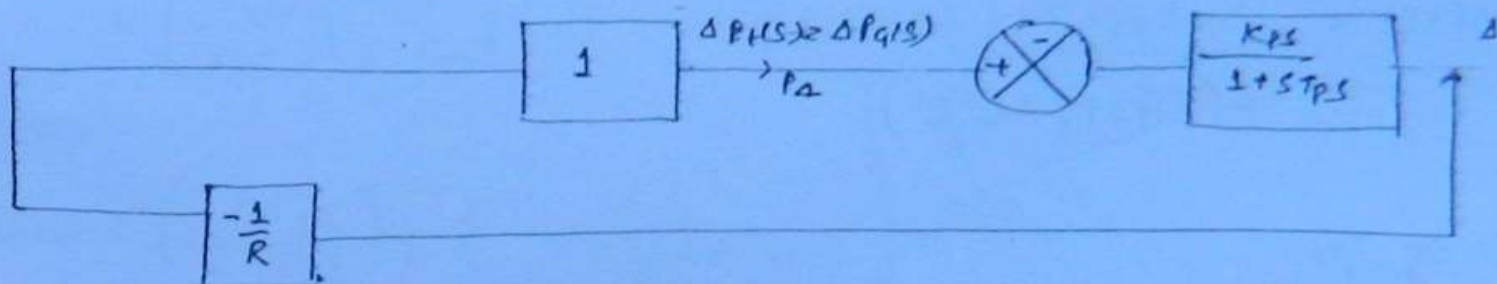

$$\Delta F(s) = \frac{- \left(\frac{Kps}{1+sTps} \right) \cdot \Delta P_D(s)}{1 - \left\{ \left(\frac{Kps}{1+sTps} \right) \left(\frac{-1}{R} \right) \right\}}$$

$$\Delta F(s) = \frac{- \left[\frac{Kps}{1+sTps} \right] \cdot \frac{\Delta P_D}{s}}{\left[1 + \left\{ \frac{s \left(\frac{Kps}{1+sTps} \right) \left(\frac{1}{R} \right) \right\} \right]}$$

$$= \frac{-K_{PS}}{\left[sT_{PS} + \left(1 + \frac{K_{PS}}{R} \right) \right]} \cdot \frac{\Delta P_D}{s}$$

$$\Delta F(s) = \frac{-K_{PS}}{s \left(sT_{PS} + \left(1 + \frac{K_{PS}}{R} \right) \right)} \Delta P_D$$

Divide by T_{PS}

$$\Delta F(s) = \frac{-K_{PS}/T_{PS}}{s \left(s + \left\{ \frac{1}{T_{PS}} + \frac{K_{PS}}{T_{PS} \cdot R} \right\} \right)} \Delta P_D$$

$$\Delta F(s) = \frac{-K_{PS}/T_{PS}}{1} \left\{ \frac{1}{s \left[s + \left(\frac{R + K_{PS}}{RT_{PS}} \right) \right]} \right\} \Delta P_D$$

Applying partial fraction:

$$\frac{1}{s \left[s + \left(\frac{R + K_{PS}}{RT_{PS}} \right) \right]} = \frac{A}{s} + \frac{B}{s + \left[\frac{R + K_{PS}}{RT_{PS}} \right]}$$

$$1 = A \cdot \left(\frac{R + K_{PS}}{RT_{PS}} \right)$$

$$\therefore A + B = 0$$

$$\Rightarrow A = \frac{RT_{PS}}{R + K_{PS}}$$

$$B = -A = \frac{-RT_{PS}}{R + K_{PS}}$$

$$\Delta f(s) = \left(-\frac{K_{ps}}{T_{ps}} \right) \left[\frac{R_{tps}/R + K_{ps}}{s} - \frac{R_{tps}/R + K_{ps}}{s + \left(\frac{R + K_{ps}}{R_{tps}} \right)} \right] \Delta P_D$$

$$= \left(-\frac{K_{ps}}{T_{ps}} \right) \left(\frac{R_{tps}}{R + K_{ps}} \right) \left\{ \frac{1}{s} - \frac{1}{s + \left(\frac{R + K_{ps}}{R_{tps}} \right)} \right\} \Delta P_D$$

$$\Delta f(s) = \left(-\frac{R K_{ps}}{R + K_{ps}} \right) \left\{ \frac{1}{s} - \frac{1}{s + \left(\frac{R + K_{ps}}{R_{tps}} \right)} \right\} \Delta P_D$$

Taking inverse Laplace:

$$\Delta f(t) = \left(-\frac{R K_{ps}}{R + K_{ps}} \right) \left\{ 1 - e^{-\left(\frac{R + K_{ps}}{R_{tps}} \right) t} \right\} \Delta P_D$$

Question:

Obtain the dynamic response of uncontrolled isolated power s/w with the following loop parameters. Regulation $R = 2\%$

- $K_{ps} = 75 \text{ pu MW/Hz}$

- $T_{ps} = 20 \text{ sec}$

- $\Delta P_D = 0.02 \text{ pu}$

$$= -\left(\frac{2 \times 75}{2 + 75} \right) \left\{ 1 - e^{-\left(\frac{2 + 75}{2 \times 20} \right) t} \right\} 0.02$$

$$= -1.94 \left\{ 1 - e^{-1.94 t} \right\} 0.02$$

$$\Delta f(t) = 0.038 (1 - e^{-3.88 t})$$

Dynamic response is represented in 4th Quadrant

dynamic response is always exponential increasing in the fourth quadrant.

• Dynamic response always gives $\Delta f \neq 0$

• The change in frequency Δf can be made equal to 0 by means of $\propto$ proportional and integral controller.

INTEGRAL CONTROLLER:-


• Integral controller is represented in the feedback path


• Let K_i be the gain constant of integral controller

Negative sign indicates that for positive frequency error the speed changer should move in downward direction

• $\Delta f = 0$ can be made by replacing speed governor with integral controller. i.e. FREE GOVERNOR OPERATION.

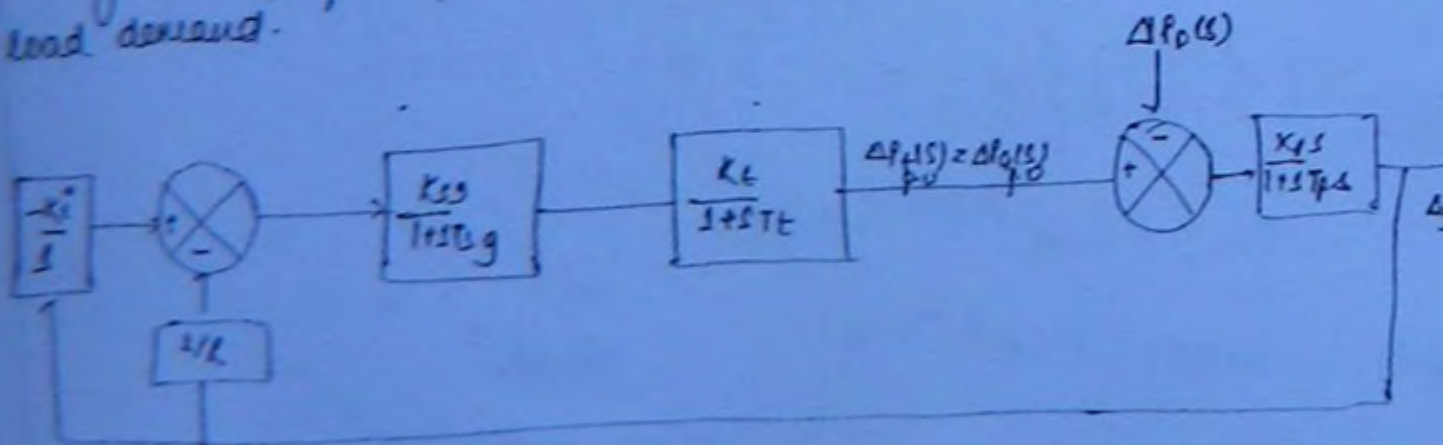• Change in frequency is determined for the changes in the load demand.



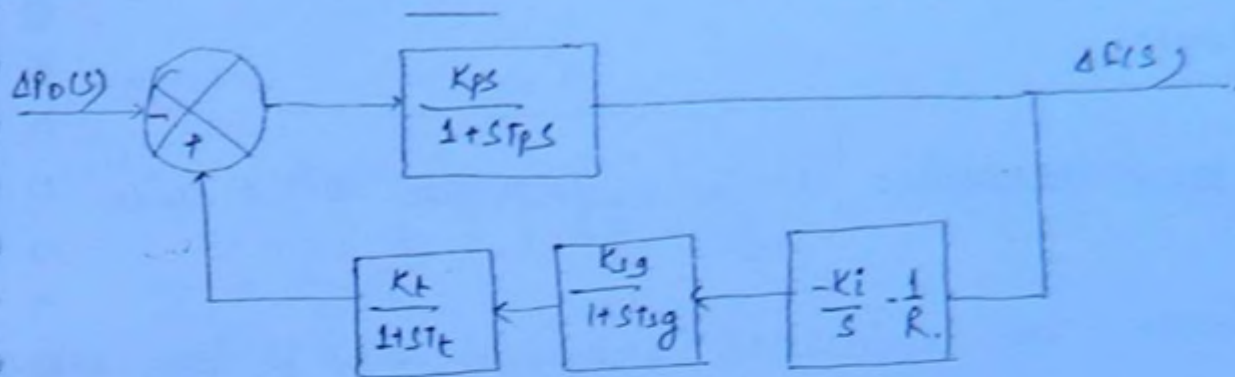

$$\frac{\Delta F(s)}{\Delta P_D(s)} = \frac{-\left(\frac{K_{ps}}{1 + sT_{ps}}\right)}{1 - \left(\frac{K_{ps}}{1 + sT_{ps}}\right)\left(\frac{K_t}{1 + sT_t}\right)\left(\frac{K_{sg}}{1 + sT_{sg}}\right)\left(-\frac{K_i}{s} - \frac{1}{R}\right)}$$

$$\Delta F(s) = \frac{-\left(\frac{K_{ps}}{1 + sT_{ps}}\right) \cdot \frac{\Delta P_D(s)}{s}}{1 + \left(\frac{K_{ps}}{1 + sT_{ps}}\right)\left(\frac{K_t}{1 + sT_t}\right)\left(\frac{K_{sg}}{1 + sT_{sg}}\right)\left(\frac{+K_i}{s} + \frac{1}{R}\right)}$$

$$\Delta F_{s.s} = \lim_{s \rightarrow 0} s \cdot \Delta F(s)$$

$$\Delta F(s) = \cancel{s} \cdot \frac{-\left(\frac{K_{ps}}{1 + sT_{ps}}\right) \cdot \frac{\Delta P_D(s)}{\cancel{s}}}{1 + \left(\frac{K_{ps}}{1 + sT_{ps}}\right)\left(\frac{K_t}{1 + sT_t}\right)\left(\frac{K_{sg}}{1 + sT_{sg}}\right)\left(\frac{+K_i}{s} + \frac{1}{R}\right)}$$

$$= \frac{-(K_{ps})(1 + sT_{sg})(1 + sT_t)}{(1 + sT_{ps})(1 + sT_{sg}) + K_{ps}K_{sg}K_t\left(\frac{K_i}{s} + \frac{1}{R}\right)} \cdot \Delta P_D$$

$$\boxed{\Delta f_{s.s} = \frac{1}{\infty} = 0}$$

Dynamic Response:

• Dynamic response determines change in frequency w.r.t time.

• Assumption:

1) $K_g K_t = 1$

2) $T_g = T_t \equiv 0$

3)

So,

$$\Delta F(s) = \frac{-(K_p s)(1+sT_g)(1+sT_t)}{(1+sT_p s)(1+sT_g s)(1+sT_t) + K_p s K_g K_t \left(\frac{K_i}{s} + \frac{1}{R}\right)} \cdot \Delta \frac{P_D}{s}$$

$\Rightarrow$

$$= \frac{-K_p s (1+s \cdot 0)(1+s \cdot 0)}{(1+sT_p s)(1+s \cdot 0)(1+s \cdot 0) + 1 \cdot K_p s \left(\frac{K_i}{s} + \frac{1}{R}\right)} \cdot \Delta \frac{P_D}{s}$$

$$= \frac{-K_p s}{\left[(1+sT_p s) + K_p s \left(\frac{K_i}{s} + \frac{1}{R}\right) \right]} \cdot \frac{\Delta P_D}{s}$$

$$\Delta F(s) = \frac{-K_p s}{(s + s^2 T_p s + K_p s K_i + s \frac{K_p s}{R})}$$

$$\Delta F(s) = \frac{-K_p s}{[s^2 T_p s + s \left(\frac{1 + K_p s}{R}\right) + K_p s K_i]} \Delta P_D$$

$$\Delta f(s) = \frac{-K_{ps}/T_{ps}}{\left[s^2 + s \left(\frac{1}{T_{ps}} + \frac{K_{ps}}{R T_{ps}} \right) + \frac{K_{ps} K_i}{T_{ps}} \right]} \Delta P_D \quad \text{--- (4)}$$

• The roots of quadratic equation determines the nature of the Integral controller.

CRITICAL GAIN: ($K_{icritical}$)

Roots of above equation (4).

$$\frac{- \left(\frac{1}{T_{ps}} + \frac{K_{ps}}{R T_{ps}} \right) \pm \sqrt{\left(\frac{1}{T_{ps}} + \frac{K_{ps}}{R T_{ps}} \right)^2 - 4 \cdot 1 \cdot \left(\frac{K_{ps} K_i}{T_{ps}} \right)}}{2 \cdot 1}$$

equating to 0.

$$\left(\frac{1}{T_{ps}} + \frac{K_{ps}}{R T_{ps}} \right)^2 - 4 \cdot \left(\frac{K_{ps} K_i}{T_{ps}} \right) = 0$$

$$K_{ic} = \frac{T_{ps}}{4 K_{ps}} \left(\frac{1}{T_{ps}} + \frac{K_{ps}}{R T_{ps}} \right)^2$$

$$= \frac{T_{ps}}{4 K_{ps}} \left[\frac{1}{T_{ps}^2} + \left(\frac{K_{ps}}{R T_{ps}} \right)^2 + \frac{2 K_{ps}}{R T_{ps}^2} \right]$$

$$= \frac{T_{ps}}{4 K_{ps}} \cdot \frac{K_{ps}^2}{T_{ps}^2} \left[\frac{1}{K_{ps}^2} + \frac{1}{R^2} + \frac{2}{R K_{ps}} \right]$$

$$4 K_{ic} = \frac{K_{ps}}{T_{ps}} \left(\frac{1}{K_{ps}} + \frac{1}{R} \right)^2$$

$$K_{ic} = \frac{K_{ps}}{4T_{ps}} \left[\frac{1}{K_{ps}} + \frac{1}{R} \right]^2 \dots \text{Critical Gain.}$$

3rd term of inertia constant:

$$K_{ic} = \frac{1/B_{po}}{\frac{2 \times 2H}{B_{fo}}} \left[B_{po} + \frac{1}{R} \right]$$

$$\therefore T_{ps} = \frac{2H}{B_{fo}}$$

$$K_{ic} = \frac{1}{8H/B_{fo}} \left[B_{po} + \frac{1}{R} \right]$$

$$\underline{\text{Inf}} \quad K_{ic} = \frac{f_o}{8H} \left(B_{po} + \frac{1}{R} \right)^2$$

Question

For an isolated integral controlled power sys. find the value of critical gain the system parameters are given as follows

Total Capacity = 1000 MW

Load demand = 600 MW

Inertia constant $H = 5 \text{ sec}$

Regulation $R = 4\%$

The nominal operating frequency is 50 Hz

the sys load increases by 1% if sys frequency increases by 1%

Solution:

$$B = \frac{\partial D}{\partial f}$$

$$P_D = 600 \text{ MW}$$

$$f = 50 \text{ Hz}$$

$$\frac{\partial D}{\partial f} \text{ load demand } \rightarrow \frac{1\% \text{ of } 600}{1\% \text{ of } 50} = 12 \text{ MW/Hz}$$

$$B_{p.u} = \frac{12}{1000} = 0.012 \text{ p.u./MW/Hz}$$

$$K_{ic} = \frac{\frac{10}{50}}{8 \times 5} \left(\frac{0.012}{2} + \frac{1}{2} \right)^2$$

$$K_{ic} = \frac{10}{8} (0.012 + 0.5)^2$$

$$K_{ic} = 0.085$$

$$K_{ic} = 0.32768$$

PERFORMANCE OF TRANSMISSION LINE

the performance of overhead T.L can be obtained by

- 1) Efficiency
- 2) Regulation

Efficiency:-

$$\frac{\text{Power O/P}}{\text{Power I/P}} \times 100$$

$$= \frac{\text{Power O/P}}{\text{Power O/P} + \text{Power losses}} \times 100$$

$$= \frac{\text{Power I/P} - \text{Power losses}}{\text{Power I/P}}$$

∴ the power losses are the active power losses

$$1\phi = I^2 R$$

$$3\phi = 3I^2 R$$


I = phase current

R = Resistance / phase.

• Regulation - for rotating M/C speed regulation is obtained.

for static M/C or stationary M/C voltage regulation

is measured.

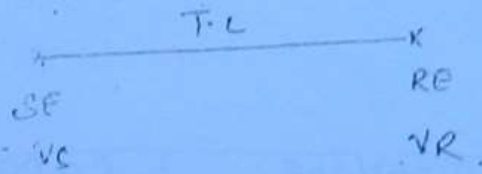

$$\% E = \frac{V_S - V_R}{V_R} \times 100$$

• Condition :-

When the receiving end is open circuited
current $I=0$, voltage drop across $T.L = 0$ $\therefore$

$$V_S = V_R$$

∴

$$\% E = \frac{V_{R0} - V_R}{V_R} \times 100$$

The change in receiving end voltage from no-load to full load expressed w.r.t receiving end voltage at full load is V_R .

For a better T.L $\% \eta$ must be high & $\% E$ must be ON.

CLASSIFICATION OF TL

TL are classified based on -


1) length.

- ii) operating voltage
- iii) effect of capacitance

	Length	operating voltage	capacitance
Short T.L	(0-80) km	(0-20) kV	Neglected
Medium T.L	(80-200) km	(20-100) kV	Lumped or Concentrated
Long T.L	(>200 km)	> 100 kV	uniformly distributed

• SHORT TRANSMISSION LINE :-

• Equivalent
ckt

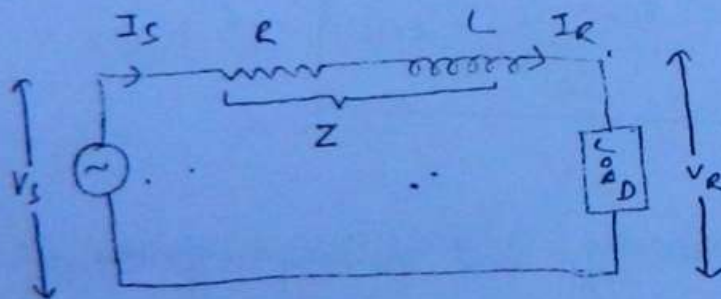

• Mathematical relations :-

- $I_s = I_R = I$ (say)

- Resistive voltage drop = IR


- Reactive voltage drop = $jX_L(I)$

- Total voltage drop = $I(R + jX_L)$

- Sending end voltage $V_s = V_R + I_R + j I_X L$
 $= V_R + I \underbrace{(R + j X_L)}$
 $V_s = V_R + I Z$

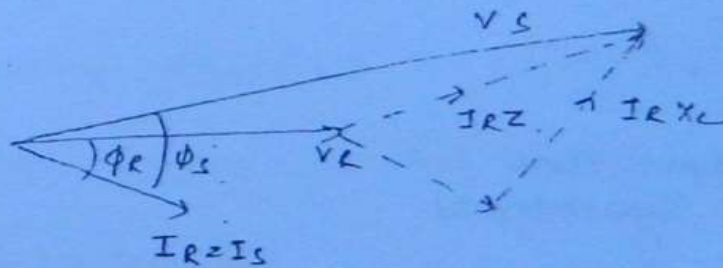5) Vector diagram -

- Consider Receiving end voltage ' V_R ' as the reference vector.
- Assume that the load is R-L load $\therefore I_R$ lags V_R by an angle ϕ_R where ϕ_R lies b/w 0 to 90° .



- Imp
- $\phi_s > \phi_R$
 - $\cos \phi_s < \cos \phi_R$

4) 2-port network parameters:

$$V_s = A V_R + B I_R \quad \text{--- (i)}$$

$$I_s = C V_R + D I_R \quad \text{--- (ii)}$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix} \quad -$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

B → Impedance
C → Admittance

$$A = D = 1$$

$$B = Z$$

$$C = 0$$

alter →

$$\begin{aligned} V_s &= V_R + Z I_R \\ &= 1 \cdot V_R + Z \cdot I_R \end{aligned}$$

$$\therefore A = 1, B = Z$$

$$\begin{aligned} I_s &= I_R \\ &= 0 \cdot V_R + 1 \cdot I_R \end{aligned}$$

$$\therefore C = 0, D = 1$$

$A = D$ ∵ Short line line symmetrical.

Short line is Reciprocal because

$$AD - BC = 1$$

$$1 \times 1 - 0 \times Z = 1$$

$$1 = 1$$

Questⁿ

A - 1- ϕ T.L is transmitting 1.1 MW power to factory at 11 kV $\cos \phi = 0.8$ PF lagging. It has total resistance of 2.5Ω & reactance of 3.0Ω

Determine:

1) Voltage at the sending end

2) Sending end P.F

3) %age regulation

4) %age efficiency

unless specified by default take all data as receiving end data.

$$P_R = 1.1 \text{ MW}$$

$$V_R = 11 \text{ kV}$$

$$\cos \phi_R = 0.8 \text{ lag}$$

$$R/\text{phase} = 2 \Omega$$

$$X/\text{phase} = 3 \Omega$$

$$P_R = I_R V_R \cos \phi_R$$

$$I_R = \frac{1.1 \times 10^6}{0.8 \times 11 \times 10^3}$$

$$I_R = 125 \text{ A}$$

$$I_R = |I_R| \angle \phi_R$$

$$I_R = 125 \angle -36.8^\circ$$

$$V_S = V_R + I_R Z$$


$$= 11 \times 10^3 + 125 \angle -36.8^\circ \times (2 + j3)$$

$$= 11000 \angle 0^\circ + (125 \angle -36.8^\circ)(3.6 \angle 56.3^\circ)$$

$$= 11.42 \angle 0.75^\circ \text{ kV}$$

$$Z/\text{phase} = 2 + j3 \\ = 3.6 \angle 56.3^\circ$$
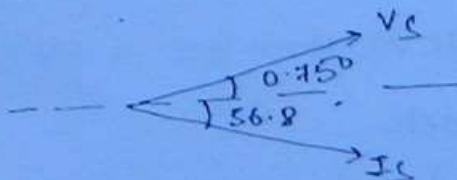
$$\text{ii) } \cos \phi_S = \cos \angle V_S \cdot I_S$$



$$\phi_S = 36.8 + 0.75$$

$$= 37.55$$

$$\cos \phi_S = \cos(37.55)$$

$$\cos \phi_S = 0.79 \text{ lag}$$

$$\eta = \frac{\text{Power o/p}}{\text{Power o/p + losses}} \times 100$$

$$= \frac{1.1 \times 10^6}{1.1 \times 10^6 + I^2 R} = \frac{1.1 \times 10^6}{1.1 \times 10^6 + (125)^2 \times 2}$$

$$\eta = 91.24\%$$

$$\% E = \frac{V_s - V_R}{V_R} \times 100$$

$$= \frac{11420 - 11000}{11000} \times 100$$

$$= 3.86\%$$

9) asked A, B, C, D

$$A = 1$$

$$B = Z = 3.6$$

$$C = 0$$

$$D = 1$$

Quest?

An overhead 3- ϕ T.L deliver 5MW at 22KV at 0.8 lagging. the resistance & reactance of each conductor are 4Ω & 6Ω . Determine

- 1) Sending end voltage
- 2) % Regulation
- 3) % age η

Solution

$$P_R = 5 \text{ MW}$$

$$V_R = 22 \text{ kV}$$

$$\cos \phi_R = 0.8 \text{ lag}$$

→ in 1- ϕ

$$P_R = V_R I_R \cos \phi_R$$

→ in 3- ϕ

$$P_R = 3 V_{Rm} I_{Rm} \cos \phi_R$$

$$= \sqrt{3} V_{RL} I_{RL} \cos \phi_R$$

until & unless specified all the value given is line value only

$$P_R = \sqrt{3} V_{RL} I_{RL} \cos \phi_R$$

$$I_{RL} = \frac{5 \times 10^6}{22 \times 10^3 \times 0.8} = 164 \text{ A}$$

$$V_{Rm} \rightarrow V_L / \sqrt{3}$$

$$I_R = 164 \angle -\cos^{-1} 0.8$$
$$= 164 \angle -36.8^\circ \text{ A}$$

$$V_{Rm} \rightarrow V_L / \sqrt{3}$$

$$Z = 4 + j6 \Omega$$
$$= 7.21 \angle 56.31^\circ$$

$$V_S = \frac{22000 \angle 0^\circ + (164 \angle -36.8^\circ)(7.21 \angle 56.31^\circ)}{\sqrt{3}}$$

$$V_S = 13.817 \angle 1.63^\circ \text{ kV}$$

$$V_{SL} = \sqrt{3} V_S$$

$$= 23.94 \text{ kV}$$

$$\% E = \frac{V_S - V_R}{V_R} \times 100$$

$$= \frac{25940 - 22000}{22000} \times 100 = 8.82\%$$

$$\% \eta = \frac{\text{o/p}}{\text{o/p} + \text{losses}}$$

$$\begin{aligned} \text{losses} &= 3 \cdot I^2 R \\ &= 3 \times (164)^2 \times 4 \\ &= 322.75 \text{ kW} \end{aligned}$$

$$\% \eta = \frac{5 \times 10^6}{5 \times 10^6 + 322.75 \times 10^3}$$

$$\% \eta = 95.9\%$$


MEDIUM TRANSMISSION LINE

A medium T.L can be represented in 4 - method.

- 1) Load condenser method
- 2) Source condenser method
- 3) Nominal - P method
- 4) Nominal - π method

LOAD CONDENSER METHOD


Equivalent Ckt:-

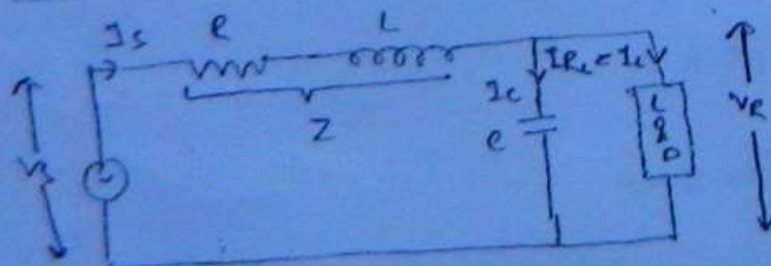

2) Mathematical Relation

- $I_s = I_R + I_C$
- Resistive voltage drop $= I_s R$
- Reactive voltage drop $= I_s (jX_L)$
- Total voltage drop $= I_s R + I_s (jX_L)$
 $= I_s (R + jX_L)$
 $= I_s \cdot Z$
- $V_s = V_R + I_s R + I_s (jX_L)$
 $V_s = V_R + I_s Z$
- voltage across capacitor (V_C) $= V_e$

3) Vector diagram:

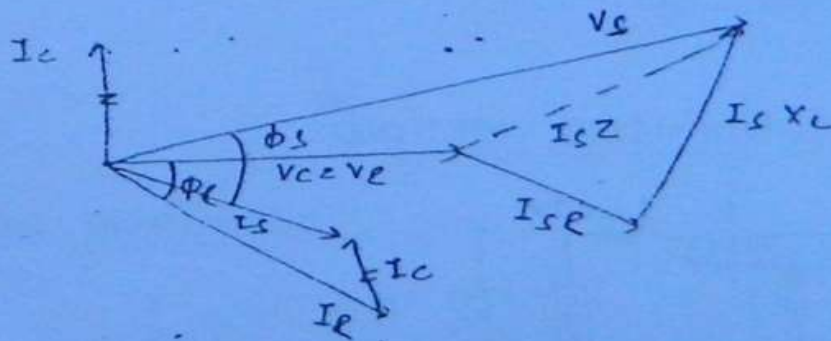

- For RL load I_R lags V_R by an angle ϕ_e

2) 2-port Network Parameters:-

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$= \begin{bmatrix} 1+YZ & Z \\ Y & 1 \end{bmatrix} \begin{bmatrix} V_L \\ I_L \end{bmatrix}$$

$$A = 1+YZ$$

$$B = Z$$

$$C = Y$$


$$D = 1$$

- $A \neq D \therefore$ Not symmetrical
- $AD - BC = (1+YZ) \cdot 1 - Z \cdot Y = 1$

$\therefore$ It is reciprocal

Load condenser method is not symmetrical
 $\therefore$ capacitor is not symmetrical in the equivalent circuit

2) SOURCE CONDENSER METHOD

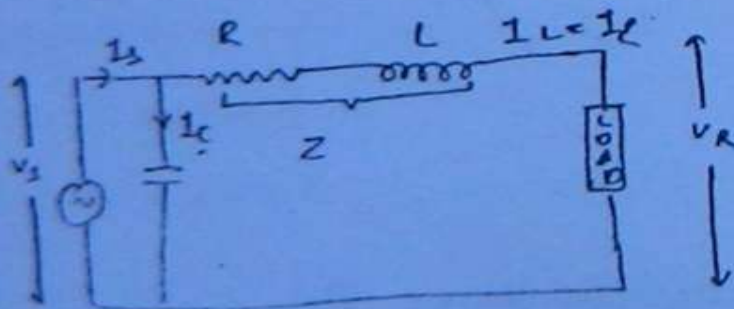

$$I_s = I_L + I_c$$

2) Mathematical Relation:-


- Mathematical $I_s = I_L + I_c$
- Resistive voltage drop $I_L R$

- Reactive voltage drop $= I_R(jX_L)$

- Total voltage drop $= I_R R + I_R(jX_L)$
 $= I_R(R + jX_L)$
 $= I_e Z$

- Sending end voltage $V_s = V_e + I_R R + I_R(jX_L)$
 $V_s = V_e + I_e Z$

Vector diagram

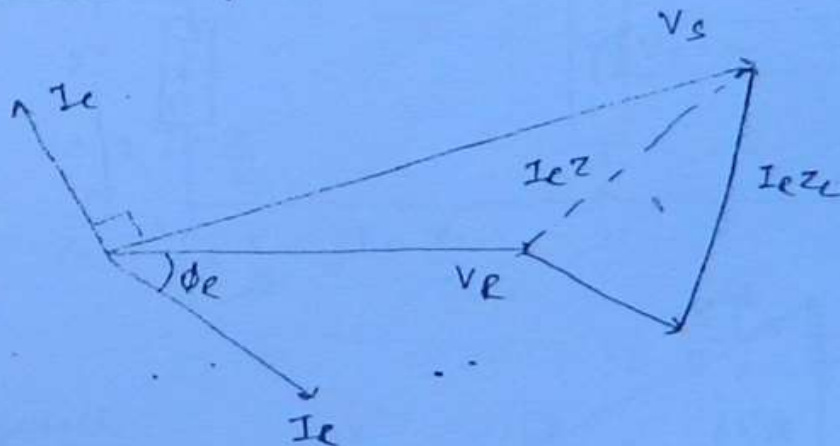

2-port N/W parameters. ✓

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_e \\ I_e \end{bmatrix}$$

→ see from the sending end, the branch that comes first fill those values in 1st matrix.

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & Z \\ Y & 1 + YZ \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$A = 1$$

$$B = Z$$

$$C = Y \quad D = 1 + YZ$$

$$A \neq D$$


So not symmetrical

$$AD - BC = 1$$


∴ Reciprocal

5) NOMINAL T-METHOD / MIDDLE CONDENSOR METHOD:

Equivalentckt:

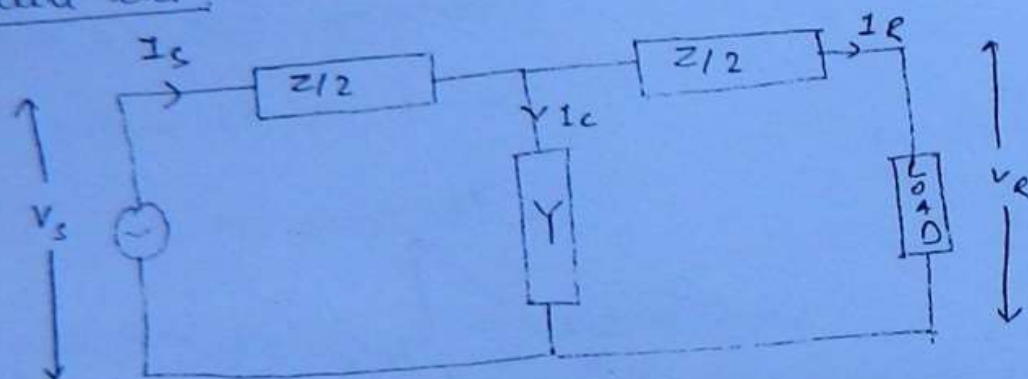
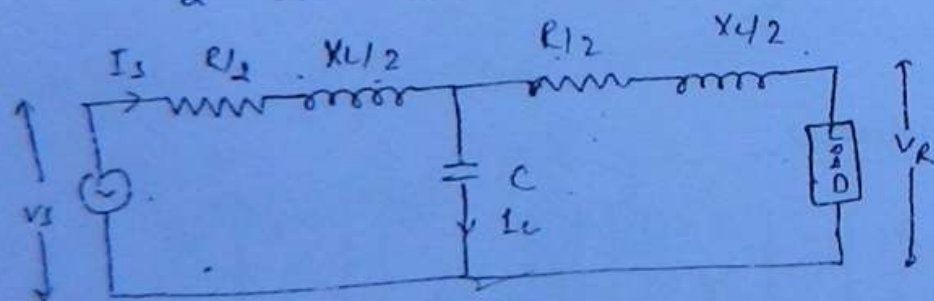
$$\frac{Z}{2} = \frac{R}{2} + j \frac{X_L}{2}$$



$$I_s = I_R + I_c$$

$$\text{Resistive voltage drop} = I_s \cdot \frac{R}{2} + I_R \cdot \frac{R}{2}$$

$$R/2 (I_s + I_R)$$

$$\text{Total reactive drop} = I_s \left(j \frac{X_L}{2} \right) + I_R \left(j \frac{X_L}{2} \right)$$

$$= j \frac{X_L}{2} (I_s + I_e)$$

$$\bullet \text{ total voltage drop} = \left(\frac{R}{2} + j \frac{X_L}{2} \right) I_s + I_e \left(\frac{R}{2} + j \frac{X_L}{2} \right)$$

$$= I_s \cdot \frac{Z}{2} + I_e \cdot \frac{Z}{2}$$

$$\bullet V_c = V_R + I_e \cdot \frac{Z}{2}$$

$$= V_R + I_e \left(\frac{R}{2} + j \frac{X_L}{2} \right)$$


$$V_c = V_R + I_e \cdot \frac{R}{2} + j I_e \frac{X_L}{2}$$

$$V_R = V_c$$

$$\bullet V_s = V_c + I_s \frac{Z}{2}$$

$$= V_c + I_s \cdot \frac{R}{2} + j I_s \cdot \frac{X_L}{2}$$


vector diagram

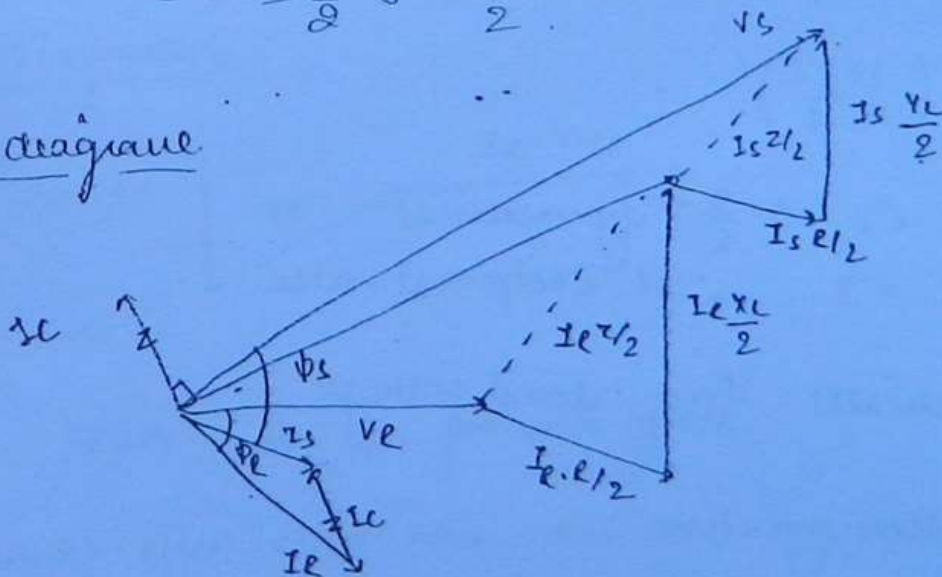

2-port N/w parameters

$$\begin{bmatrix} V_c \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & Z/2 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} 1 & Z/2 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$

$$I_s = I_c$$

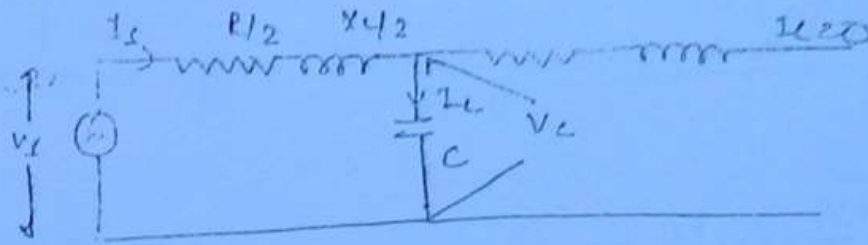

- Total resistive drop $= I_c \cdot R/2$


- Total reactive drop $= I_c \cdot j \frac{X_L}{2}$

- $V_c = V_L$

- Sending end voltage $V_s = V_c + I_c \frac{R}{2} + I_c j \frac{X_L}{2}$

$$\text{OR } V_s = V_R + I_c \frac{R}{2} + I_c j \frac{X_L}{2}$$

Vector diagram

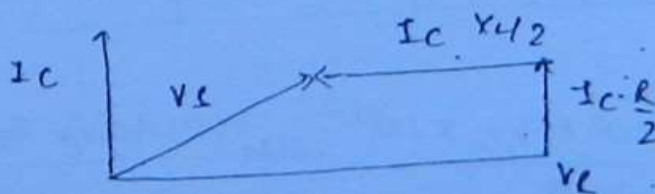

$V_R > V_L$ is the ferranti effect.

- Ferranti effect occurs when the receiving end of T.L is operating under no-load condition or very light load condition

$$\text{OR } V_{R0} > V_L$$

$$V_{R0} = \text{Voltage across Capacitor} \\ = I_C \cdot (-jX_C)$$

$$\therefore I_C = \frac{V_S}{R_{L0} + j\frac{X_L}{2} - jX_C}$$

$$= \frac{V_S}{\frac{R}{2} + j\frac{\omega L}{2} - j\frac{1}{\omega C}}$$

Imp

$$V_{R0} = \left(\frac{V_S}{\frac{R}{2} + j\frac{\omega L}{2} - j\frac{1}{\omega C}} \right) \left(-j\frac{1}{\omega C} \right)$$

Example

the % age rise in the voltage at the receiving end of a TL of length 200 km operating at 50 Hz is

$$\text{Increase in voltage} = \frac{\omega^2 L^2 V_R \times 10^{-10}}{18} \text{ volts}$$

$$\% \text{ age } \uparrow \text{ in voltage} = \frac{\omega^2 L^2 V_R \times 10^{-10}}{18} \times 100$$

$$= \frac{\omega^2 L^2 V_R \times 10^{-10} \times 100}{18}$$



$$= \frac{(2\pi \times 50)^2 \times (200)^2 \times 10^8}{18}$$

$$= 2.18\%$$

- * Ferranti effect is more severe in long T.L when compared with medium T.L
- * Ferranti effect is negligible in short T.L

4) NOMINAL- π METHOD / SPLIT CONDENSER METHOD

1) Equivalent ckt -

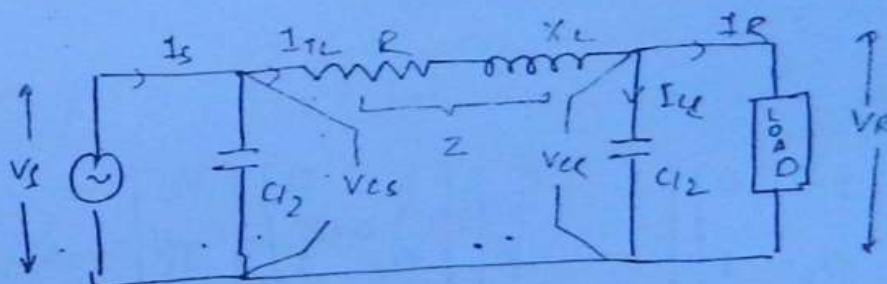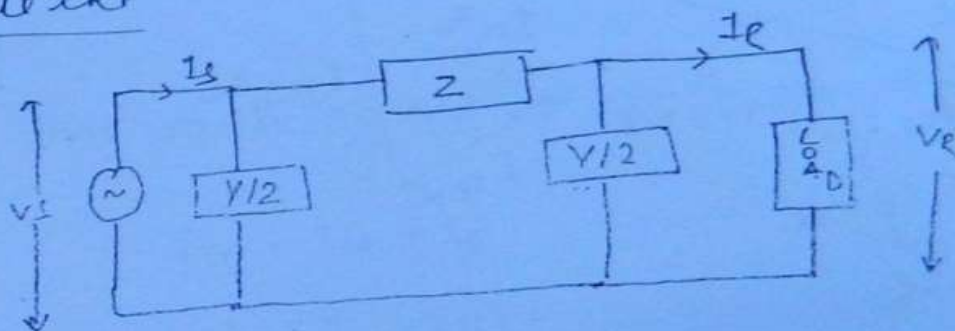


Mathematical Relations:

- $I_{TL} = I_r + I_C$; $I_s = I_C + I_{TL}$
- $V_{CR} = V_r$
- $V_{CC} = V_s$
- Total resistive drop = $I_{TL} R$
- Total reactive drop = $I_{TL} j X_L$
- Total voltage drop = $I_{TL} (R + j X_L)$

• Sending end voltage (V_s) = $V_r + I_{TL}R + I_{TL}jX_L$

Vector diagrams:-

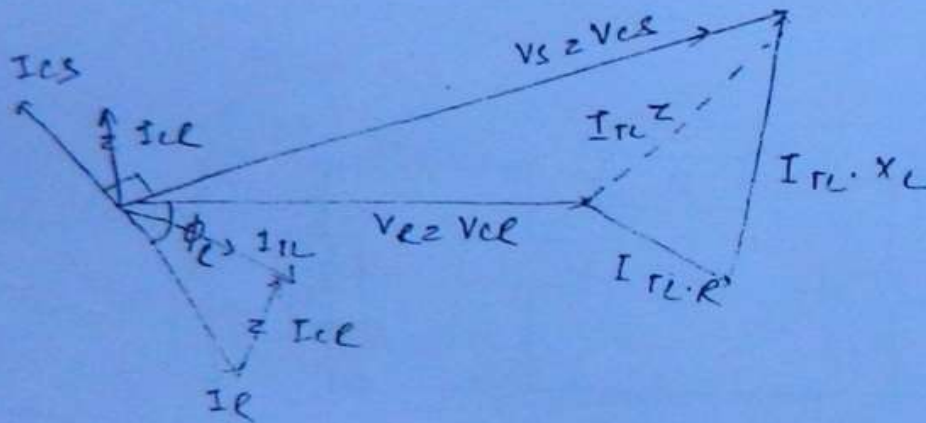

3 port N/w parameters —

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y/2 & 1 \end{bmatrix} \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y/2 & 1 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 + \frac{ZY}{2} & Z \\ \frac{Y}{2} + (\frac{ZY}{2} + 1)\frac{Y}{2} & 1 + \frac{ZY}{2} \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

$$A = 1 + \frac{ZY}{2} \quad A = D$$

$$B = Z$$

$$C = \frac{Y}{2} + \frac{ZY^2}{4} + \frac{Y}{2}$$

$$z = Y + \frac{ZY^2}{4}$$

$$C = Y \left(1 + \frac{ZY}{4} \right)$$

- $A = D$ ∴ it is symmetrical.
 $AD = BC = 1$ also so reciprocal! also

condition -

Assume that receiving end of T.L is open circuited

$$I_{TL} = I_{CR} + I_R$$

$$= I_{CR} + 0$$

$$I_{TL} = I_{CR}$$

$$V_{RO} = V_{CR} = I_{CR} \left(-j \frac{X_C}{2} \right)$$

⏟
 α this is wrong

$$V_{RO} = I_{CR} (-j X_{C1/2})$$

where $X_{C1} = \frac{2}{\omega C}$
 $\therefore \frac{2}{\omega C}$

$$I_{CR} = \frac{V_S}{R + jX_L - jX_{C1/2}}$$

$$V_{L0} = \left(\frac{V_s}{R + jX_L - jX_{C1/2}} \right) (-jX_{C1/2})$$

$$V_{L0} = \left(\frac{V_s}{R + j\omega L - j\frac{2}{\omega C}} \right) \left(-j\frac{2}{\omega C} \right)$$

NOTE:

- Load condenser method is used to improve the P.F of the load.
- Source condenser method is used to improve the P.F of the source.
- Nominal π -method is used to improved the P.F of both source & load.
- Nominal T-method is used to improve the P.F to T.L.

Quesⁿ

A 220KV T.L represented as π -method has the following parameters

$$A = 0.925^\circ$$

$$B = 80 \angle 65^\circ \Omega$$

The sending end voltage is maintained at 220KV
 Is $\uparrow$ in voltage at the receiving end & the
 line losses on no-load condⁿ are?

$$V_s = 220 \text{ KV}$$

$$V_s = AV_R + BI_e$$

No-load so $I_e = 0$

$$V_s = AV_{R0}$$

$$\therefore V_{R0} = \frac{V_s}{A} = \frac{220}{0.9} = 244.4 \text{ kV}$$

$$\uparrow \text{ in voltage} = (244.4 - 220) \text{ kVolts} \\ = 24.4 \text{ kV}$$

line losses $= 0$ ($\because$ the system is under no load)

Questⁿ

A 3- ϕ T.L, 120 km long, 50 Hz delivers a connected load of 30 MVA, 110 kV & 0.8 p.f lagging. The resistance is $10 \Omega/\text{phase}$ & reactance is $40 \Omega/\text{phase}$. & Capacitive susceptance is $6 \times 10^{-4} \text{ S}$. Find the voltage regulation by nominal π method.

From the capacitive susceptance

$$I_{CR} = V_R / (j X_{C1/2}) = V_R (j B_{C1/2})$$

$$= \left(\frac{110000}{\sqrt{3}} \right) (j 6 \times 10^{-4})$$

$$= (0 + j 11\sqrt{3}) \text{ A}$$

$$11\sqrt{3} \angle 90^\circ \text{ A}$$

$$I_{TL} = I_L + I_{Lr}$$

$$= (157.46 \angle -36.8) + (11\sqrt{3} \angle 90^\circ)$$

$$I_{TL} = 146.8 \angle -30.9^\circ \text{ A}$$

$$\text{voltage drop across } T_L = I_{TL} (R + jX_L)$$

$$= (146.8 \angle -30.9^\circ) (10 + j40)$$

$$= 6052.49 \angle 45.12^\circ \text{ V}$$

$$\text{Sending end voltage } V_s = V_R + \text{voltage drop}$$

$$= \frac{11000}{\sqrt{3}} + (6052.49 \angle 45.12^\circ)$$

$$= 67990.74 \angle 3.6^\circ \text{ V}$$

$$V_{SL} = \sqrt{3} \times V_s / \text{phase}$$

$$= \sqrt{3} \times 67990.74$$

$$= 117.6 \text{ kV}$$

$$\% \text{e} = \frac{V_s - V_R}{V_R} \times 100$$

$$= \frac{117.6 - 110}{110} \times 100$$

$$= 6.9\%$$

Example

A 3- ϕ feeder having a resistance of 5Ω & reactance of 10Ω supplies a load of 2MW, at 0.85 p.f lagging. The receiving end voltage is maintained at 11kV by means of static condenser taking 2.1 MVAR from the line. Calculate sending end voltage, sending end p.f, regulation & efficiency of feeder.

- The given data corresponds to load condenser method.

$$W = \sqrt{3} \cdot V_{RL} \cdot I_{RL} \cos \phi_R$$

$$2 \times 10^6 = \sqrt{3} \times 11 \times 10^3 \times I_{RL} \times 0.85$$

$$I_{RL} = 123.5 \text{ A}$$

$$I_R = 123.5 \angle -31.78^\circ \text{ A}$$

$$I_C = ?$$

Capacitive current

$$\text{VAR} = \sqrt{3} V_{RL} I_C \sin \phi$$

$$2.1 \times 10^6 = \sqrt{3} \times 11 \times 10^3 \times I_C \sin 90^\circ$$

$$I_C = 110.22 \text{ A}$$

$$I_C = 110.22 \angle +90^\circ \text{ A}$$


$$I_S = I_R + I_C$$

$$= 123.5 \angle -31.78^\circ + (110.22 \angle 90^\circ)$$

TYPES OF CONDUCTORS :-


1. Solid conductor
2. Stranded conductor
3. Composite conductor ($\leq 220\text{KV}$)
4. Bundled conductor ($> 275\text{KV}$)

SOLID CONDUCTOR

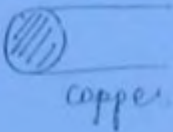

- A solid conductor consists of single strand
- High electrical conductivity
- Due to solid mesh, strength is $\uparrow$
- Transportation is difficult
- Stringing of solid conductor is very difficult

STRANDED CONDUCTOR

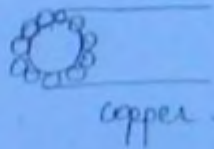

- Stranded conductor consists of 2 or more strands arranged such that the required mesh strength is obtained & are connected in parallel to $\uparrow$ the current carrying capacity.
- High electrical conductivity
- The required mesh strength can be obtained by selecting no. of strands
- Transportation is easier
- Stringing of stranded conductor is easy

• for a solid conductor
in ac s/w skin effect
is more

for a stranded conductor
in ac s/w skin effect
is less

SAG AND TENSION.

1. parabolic method $< 300 \text{ km}$
2. catenary method $> 300 \text{ km}$.
3. Effect of external factors on calculation of Sag & Tension
4. calculation of sag and tension when Transmission towers are located at different height from ground level.
5. calculation of basic terms involved with Sag & Tension

CALCULATION OF SAG AND TENSION BY PARABOLIC METHOD.


- Parabolic method. is used to determine sag and tension for spans upto 300 m and sag without exceeding 5% of the span length.
- CATENARY: A line conductor of uniform cross-section and material perfectly flexible but stretches inelastic b/w the two supports, hanging freely

~~and its~~ influence of its own weight takes the form of curve known as catenary.

SPAN: The horizontal distance b/w the adjacent supports is known as span.

SAG: For the vertical distance between the conductor at the midpoint and the tie line joining two adjacent level supports is known as sag.

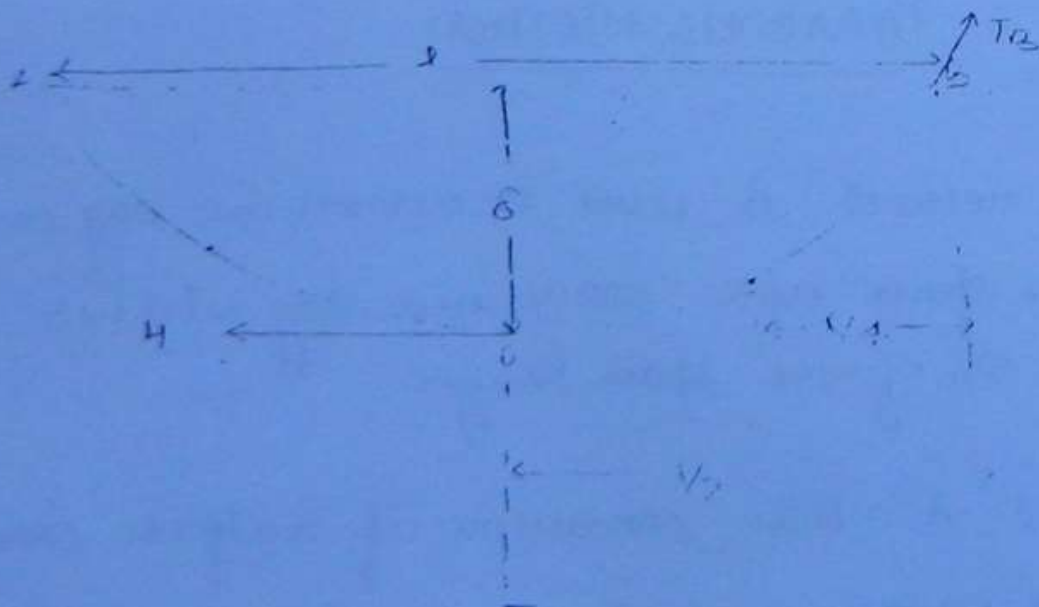• Sag is measured along the resultant load on the conductor.



• Consider a T.L. 'AOB' freely suspended.

between the supports A and B. the lowest point is consider O.

- let 'l' be span length
 $w \rightarrow$ weight/unit length of the conductor
 $\delta \rightarrow$ T.L line sag.
 $H \rightarrow$ Horizontal tension in T.L at the point of max^m sag.
 $T_B \rightarrow$ tension at the support B, due to T.L.

• consider the equilibrium of the portion 'OB' of the conductor. the forces acting are:-

- 1) Horizontal tension 'H' at point O.
- 2) the weight of portion OB acting vertically downwards through the center of gravity at a distance 'l/4' from the point 'B'.
- 3) Tension T_B at the support B.

• obtaining the ^{ve} moment at the point B

$$H \cdot \delta = w \times OB \times l/4$$

$$H \cdot \delta = \omega \cdot \frac{l}{2} \cdot \frac{1}{4}$$

$$\Rightarrow \boxed{H = \frac{\omega l^2}{8\delta}}$$

and

$$\boxed{\delta = \frac{\omega l^2}{8H}}$$

horizontal tension,


sag.

- the sag in a freely suspended conductor is directly proportional to weight/unit length of the conductor, square of span length and inversely proportional to horizontal tension (H).

CATENARY METHOD

- Catenary method is applicable when the length of span is greater than 300m and sag is more than 5% of the span length.
- In catenary method, a part of section OB is considered.
- Consider a point 'P' on the curve such that

$$OP = x_m$$

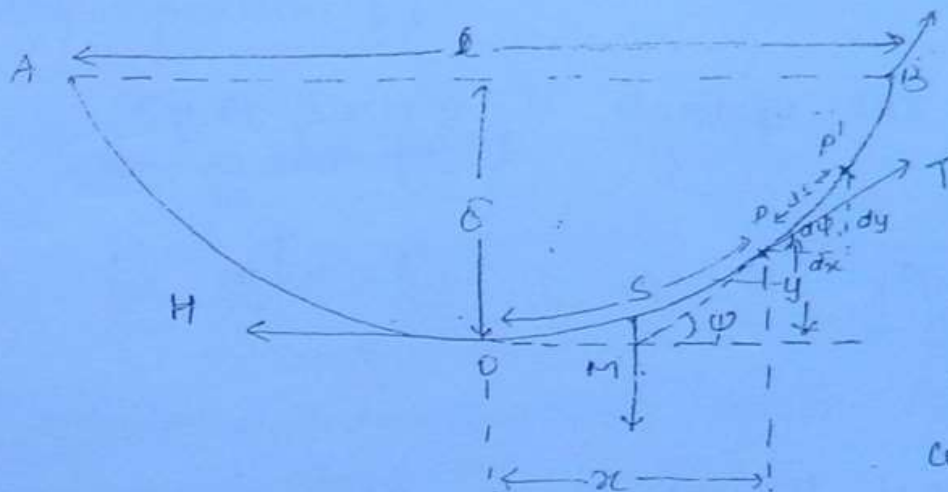

$$\cos \phi = H/T$$

$$\sin \phi = w.s./T$$

- the three forces acting on point 'P' on the curve are:

1) Horizontal tension 'H' at lowest point

2) weight of section OP. acting through its center of gravity i.e. $w.OP = w.s.$

3) tension 'T' acting at point 'P' along the tangent to the curve at point 'P'

- finding the intersection point of the three forces and the intersection point is 'M'.

so


$$H = T \cos \phi$$

$$ws = T \sin \phi$$

$$\tan \phi = \frac{ws}{H}$$


- Let (x, y) be the coordinates of point P.
- considering the triangle involving (x, y) .

$$s^2 = x^2 + y^2$$

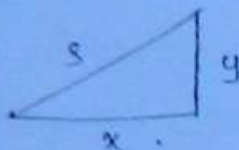

- Extend the point P upto point P' on the T.L. such that $PP' = dL$.

$$ds^2 = dx^2 + dy^2$$

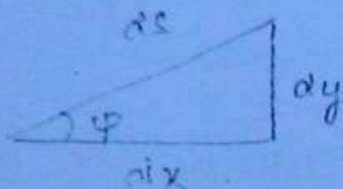

divide by dx^2

$$\left(\frac{ds}{dx}\right)^2 = 1 + \left(\frac{dy}{dx}\right)^2$$

$$\therefore \frac{dy}{dx} = \text{slope of T.L.} = \frac{\omega \cdot c}{H} = \tan \phi$$

$$\Rightarrow \left(\frac{ds}{dx}\right)^2 = 1 + \left(\frac{\omega \cdot c}{H}\right)^2$$

$$\frac{ds}{dx} = \sqrt{1 + \left(\frac{\omega \cdot c}{H}\right)^2}$$

$$\frac{dx}{ds} = \frac{1}{\sqrt{1 + (\omega \cdot c / H)^2}}$$

$$\Rightarrow dx = \frac{ds}{\sqrt{1 + (\omega \cdot c / H)^2}} \quad \text{--- (1)}$$

Integrating equation (1)

$$x = -\frac{H}{\omega} \sinh^{-1}\left(\frac{\omega s}{H}\right)$$

$$\boxed{x = \frac{H}{\omega} \sinh^{-1}\left(\frac{\omega s}{H}\right) + C_1} \quad \text{--- (2)}$$

$C_1 \rightarrow$ constant of integration which is evaluated from the condition at point 0

At point 0

$$x = 0 ; s = 0$$

so. eqn (2)

$$0 = 0 + C_1$$

$$\boxed{C_1 = 0}$$

so equation (2) will be

$$\boxed{x = \frac{H}{\omega} \sinh^{-1}\left(\frac{\omega s}{H}\right)} \quad \text{--- (3)}$$

rearranging we get

$$\boxed{\frac{H}{\omega} \left(\sinh \frac{x\omega}{H} \right) = s} \quad \text{--- (4)}$$

$$\frac{dy}{dx} = \tan \phi = \frac{\omega s}{H}$$

$$dy = \frac{\omega s}{H} \cdot dx$$

so

$$dy = \sinh\left(\frac{wx}{H}\right) dx \quad \therefore \frac{ws}{H} = \sinh\left(\frac{wx}{H}\right)$$

on integrating above equation we have.

$$y = \frac{H}{w} \cosh\left(\frac{wx}{H}\right) + C_2 \quad \dots \dots (5)$$

now at $x=0$, $y=0$.

$$\text{so } C_2 = -H/w.$$

so

$$y = \frac{H}{w} \cosh\left(\frac{wx}{H}\right) - \frac{H}{w} \quad \dots \dots (6)$$

$\therefore$ vertical distance / catenary eqn.

- Equation '6' is known as EQUATION OF CATENARY
- Representing the parameter in terms of the tension 'T'.

using eqn

$$T \cos \phi = ws H$$

$$T \sin \phi = wx.$$

on squaring and adding we get

$$(T \cos \phi)^2 + (T \sin \phi)^2 = H^2 + wx^2$$

$$\boxed{T = \sqrt{T^2 + (ws)^2}} \quad \text{--- Tangential tension (2)}$$

- The above equation represents the tension acting tangentially at a point 'p' in terms of Horizontal tension and weight of the conductor for the section OP.

- Dividing the above equation with H or substitute (ws/H) .

$$T = \sqrt{H^2 + H^2 \left[\sinh\left(\frac{wx}{H}\right) \right]^2}$$

$$T = H \sqrt{1 + \sinh^2 \frac{wx}{H}}$$

$$\boxed{T = H \cosh \frac{wx}{H}} \quad \text{--- (3)}$$

EVALUATION OF SAG(S) LENGTH OF CONDUCTOR(L) AND TENSION(T). AT SUPPORT B.

- At support B:-

$$x = l/2$$

$$s = L/2$$

$$y = \delta$$

the above relation are satisfied at the support
B i.e. transmission tower located at the point
B:

now equation 6:

$$y = \frac{H}{w} \cosh\left(\frac{wx}{H}\right) - \frac{H}{w}$$

$$\delta = \frac{H}{w} \cosh\left(\frac{wl}{2H}\right) - \frac{H}{w} \quad x=1/2$$

$$\boxed{\delta = \frac{H}{w} \left[\cosh\left(\frac{wl}{2H}\right) - 1 \right]} \quad \dots \dots (9)$$

now equation 8:

$$T = H \cosh\left(\frac{wx}{H}\right)$$

$$\boxed{T = H \cosh\left(\frac{wl}{2H}\right)} \quad \dots \dots (10)$$

equation 4:

$$\frac{H}{w} \sinh\left(\frac{wx}{H}\right) = z$$

$$\frac{H}{w} \sinh\left(\frac{wl}{2H}\right) = L/2$$

$$\boxed{L = \frac{2H}{w} \sinh\left(\frac{wl}{2H}\right)} \quad \dots \dots (11)$$

Approximate Results: By expansion series

- from eqn (9). on expanding cosh we get

$$\delta = \left(\frac{H}{\omega}\right) \left[\cosh\left(\frac{\omega l}{2H}\right) - 1 \right]$$

$$\delta = \left(\frac{H}{\omega}\right) \left[1 - \left(\frac{\omega l}{2H}\right)^2 \frac{1}{2!} + \left(\frac{\omega l}{2H}\right)^4 \frac{1}{4!} - \dots \right]$$

$$\delta = \frac{H}{\omega} \cdot \frac{\omega^2 l^2}{2H^2} \cdot \frac{1}{2}$$

neglecting higher terms

$$\boxed{\delta = \frac{\omega l^2}{8H}} \quad \dots \quad (13)$$

- from equation (10)

$$T = H \cosh \frac{\omega l}{2H}$$

$$T = H \left[1 + \left(\frac{\omega l}{2H}\right)^2 \frac{1}{2!} + \dots \right]$$

$$T = H + \frac{H \omega^2 l^2}{4H^2} \cdot \frac{1}{2}$$

$$\boxed{T = H + \frac{\omega^2 l^2}{8H}} \quad \dots \quad (14)$$

$$T = H + \omega \cdot \left(\frac{\omega l^2}{8H}\right)$$

$$\boxed{T = H + \omega \cdot \delta} \quad \dots \quad (15)$$

equation (31)

$$L = 2\left(\frac{H}{w}\right) \sinh \frac{wl}{2H}$$

$$L = 2\left(\frac{H}{w}\right) \left[\left(\frac{wl}{2H}\right) + \left(\frac{wl}{2H}\right)^2 \frac{1}{3!} + \dots \right]$$

$$L = 2\left(\frac{H}{w}\right) \left\{ \dots \right\}$$

$$L = \frac{2H}{w} \cdot \frac{wl}{2H} + \frac{2H}{w} \cdot \frac{w^2 l^3}{8H^3} \cdot \frac{1}{6}$$

$$L = l + \frac{1}{24} \frac{w^2 l^3}{H^2} \quad (16)$$

$$L = l + \frac{1}{24} \frac{w^2 l^3}{64 \delta^2}$$

$$\therefore H \delta = \frac{wl^2}{8H}$$

$$L = l + \frac{64 \delta^2}{24 \cdot l^2}$$

$$L = l + \frac{8 \delta^2}{3 l} \quad (17)$$

question:

the span b/w the two conductors/towers is 200m.

the ultimate tensile strength of conductor is 5758 kg/f

the weight of the conductor is 604 kgf/km.

the safety factor is 2. the sag is

Ans 2

$$\delta = \frac{5458 \times 250 \times 10^{-3}}{2}$$

$$\text{Horizontal tension} = \frac{\text{tensile strength}}{2} = 5458/2$$

$$\delta = \frac{604 \times (200 \times 10^{-3})^2 \times 2}{5458 \times 8}$$

$$\delta = 1.048 \text{ m}$$

LOADING ON CONDUCTORS

- There are three forces acting on conductor.

1) weight of conductor


2) Ice loading

3) wind loading.

- The weight of conductor acts vertically downwards and depends on conductor type.

- The weight of conductor/unit length is obtained from mechanical characteristic of conductor.

Ice loading

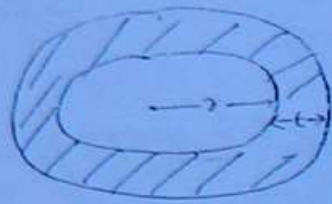

$r \rightarrow$ radius of conductor
 $t \rightarrow$ thickness of ice coating

- Due to deposition of ice on the surface of conductor the weight/unit length of conductor increases.

- Area of cross-section of conductor. $\pi r^2 = \frac{\pi D^2}{4}$ --- (1)

Area of cross-section of conductor + ice coating

$$A_{\text{con+ice}} = \frac{\pi (D+2t)^2}{4} \quad \text{--- (2)}$$

Area of cross-section of ice coating

$$= \frac{\pi}{4} [D^2 - (D+2t)^2]$$

$$= \frac{\pi}{4} [\cancel{D^2} + \cancel{D^2} + 4t^2 + 4Dt]$$

$$= \frac{\pi}{4} [\cancel{4t^2} + \cancel{4Dt}]$$

$$\boxed{A_{\text{ice}} = \pi t(t+D) \text{ m}^2} \quad \text{--- (3)}$$

- Volume of ice per unit length of conductor

$$\boxed{V = \pi t(t+D) \text{ m}^3} \quad \text{--- (4)}$$

- let ρ_i be the weight density of ice. the weight of the ice coating per unit length:

$$\omega = \underbrace{\pi t(t+0)}_{\text{volume}} \cdot \underbrace{\rho_i}_{\text{weight density}}$$

→ where $\rho_i = 9135 \text{ kgf/m}^3$
 $= 896 \text{ N/m}^3$

- Due to ice coating the weight of the conductor increase and the vertical weight increases.

3) WIND Loading:-

- Assume that conductor is covered with ice coating
- let 'r' be the radius of conductor and 't' be the thickness of ice coating

wind exerts horizontal pressure depending on velocity of wind acting $\perp$.

Area projected per unit length of ice covered conductor.

• the wind pressure acts on area $-\frac{\pi(D+2t)^2}{4}$

• $(D+2t)$ is surface exposed to wind pressure.


• force exerted due to wind perpendicular to direction of span per unit length of conductor.

$$F = (D+2t)_m \times P \text{ (N/m)}$$

$$F = (D+2t) \times P \text{ where Newton.}$$

where P is the wind pressure acting in a direction $\perp$ the direction of the span.

Resultant bending:-

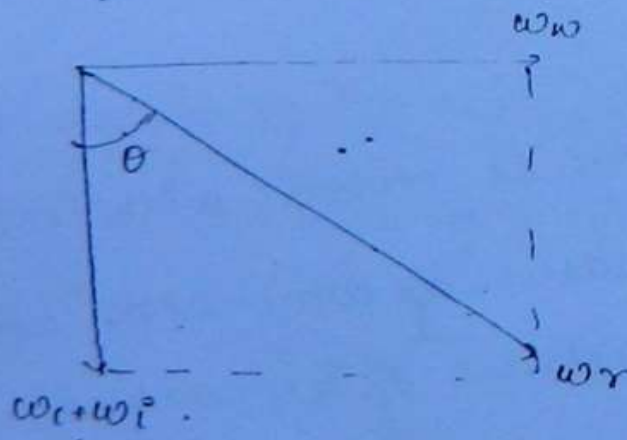

• ' θ ' represent the angle by which conductor is shifted from its original position due to wind pressure.

$$w_r = \left[(w_w)^2 + (w_c + w_i)^2 \right]^{1/2}$$

Question:-

A T.L has span of 275m between level supports. The conductor has diameter of 19.53mm, weighs 0.844kgf/m with ultimate breaking strength 4950kgf. Each conductor has radial covering of ice 9.53mm thick and is subjected to horizontal wind pressure 40kgf/m² of ice covered projected area. If the factor of safety is two. The deflected sag and vertical component of sag are.

Soln

$$l = 275 \text{ m}$$

$$D = 19.53 \text{ mm}$$

$$w = 0.844 \frac{\text{kgf}}{\text{m}}$$

• weight of ice per meter length of the conductor

$$w_i = \pi t (D + t) \rho_i$$

$$= \pi t (D + t) \times 913.5$$

$$= 3.14 \times 9.53 \times 10^{-6} (19.53 \times 10^{-6} + 9.53 \times 10^{-6}) \times 9$$

$$= 0.755 \text{ kgf}$$

$$1.54 \times 10^{-1}$$

$$w_w = (D + 2t) \times P$$

$$\Rightarrow (3.859 \times 10^{-5}) \times 40$$

$$= 1.54 \times 10^{-3} \text{ kgf/m}$$

$$= 1.54 \text{ kgf/m}$$

• weight of conductor, 0.844 kgf

resultant weight

$$w_r = [(1.54)^2 + (0.795 + 0.844)^2]^{1/2}$$

$$w_r = 2.25 \text{ kgf}.$$

• working tension $H = \frac{\text{ultimate strength}}{\text{safety factor}} = \frac{7950}{2}$
 $= 3975$

$$\delta = \frac{w_l^2}{8H}$$


→ deflected sag due to w_r $\Rightarrow \frac{2.25 \times 275^2}{8 \times 3975} = 5.35 \text{ m}$

→ vertical sag $\delta \Rightarrow \frac{(w_l + w_r) \times 275^2}{8 \times 3975} = 5.89 \text{ m}.$

CALCULATION OF SAG WHEN TRANSMISSION TOWER

ARE LOCATED AT DIFFERENT HEIGHT AN.

GROUND LEVEL.

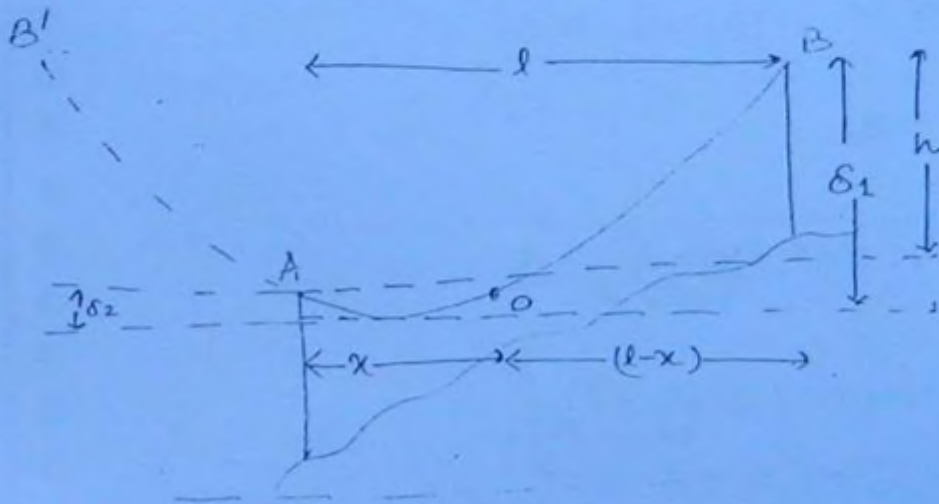

- the transmission towers are not at the same level in hilly area.

let

$l \rightarrow$ horizontal span length b/w A and B.

$h \rightarrow$ difference in level b/w two supports A B.

$x \rightarrow$ horizontal distance of support A from lowest point O.

$(l-x) \rightarrow$ horizontal distance of B from lowest point O.

- B'O B. represents the entire catenary conductor AOB is portion of catenary B'O B, the portion

OA and OB may be treated as catenaries of sag δ_2 and δ_1 .

- The vertical reaction at lower support, $w x$.
- vertical reaction at higher support $w(l-x)$.
- Tension at support A

$$T_A = H \cosh\left(\frac{wx}{H}\right) \quad \text{--- (1)}$$

$$T_B = H \cosh\left(\frac{w(l-x)}{H}\right) \quad \text{--- (2)}$$

- Sag b/w lowest point 'O' and the support 'A'

$$\delta_2 = \frac{H}{w} \left[\cosh\left(\frac{wx}{H}\right) - 1 \right] \quad \text{--- (3)}$$

- sag between lowest point and the support 'B'

$$\delta_1 = \frac{H}{w} \left[\cosh\left(\frac{w(l-x)}{H}\right) - 1 \right] \quad \text{--- (4)}$$

- In terms of tension T

$$\delta = \frac{wx^2}{2T} \quad \therefore x = l/2 \text{ and } \delta = \frac{wl^2}{8T}$$

$$\boxed{\begin{aligned}\delta_2 &= \frac{\omega(x)^2}{2T} \\ \delta_1 &= \frac{\omega(l-x)^2}{2T}\end{aligned}} \quad \text{--- (5) --- (6)}$$

now

$$\boxed{h = \delta_1 - \delta_2}$$

$$= \frac{\omega}{2T} [(l-x)^2 - x^2]$$

$$h = \frac{\omega}{2T} [l^2 + x^2 - 2lx - x^2]$$

$$h = \frac{\omega l}{2T} (l - 2x)$$

$$\Rightarrow (l - 2x) = \frac{2hT}{\omega l}$$

$$2x = l - \frac{2hT}{\omega l}$$

$$\boxed{x = \frac{l}{2} - \frac{hT}{\omega l}} \quad \text{--- (7) ---}$$

$$\text{so } (l - x) = l - \left[\frac{l}{2} - \frac{hT}{\omega l} \right]$$

$$\boxed{(l - x) = \frac{l}{2} + \frac{hT}{\omega l}} \quad \text{--- (8) ---}$$

- If $\left[\frac{h}{l} < \frac{HT}{wl} \right]$ then x is negative i.e. tower tower, A and B are located on the same side of the lowest point O.

Question:-

A TL conductor at a river crossing is supported by two towers at height 30m and 90m, above water level. The horizontal distance b/w the towers is 270m. If the tension in conductor is 1800 kgf and weight of conductor is 1 kgf/m. determine the clearance b/w conductor and the water at a point located at the center b/w the towers.


Solution:-

- Horizontal distance b/w the towers (span) $l = 270m$
- vertical distance b/w two supports

$$h = (90 - 30) = 60m$$

$$\begin{aligned}
 x &= \frac{l}{2} - \frac{hT}{wl} = \frac{270}{2} - \frac{60 \times 1800}{1 \times 270} \\
 &= \frac{270}{2} - 400 \\
 &= -265m.
 \end{aligned}$$

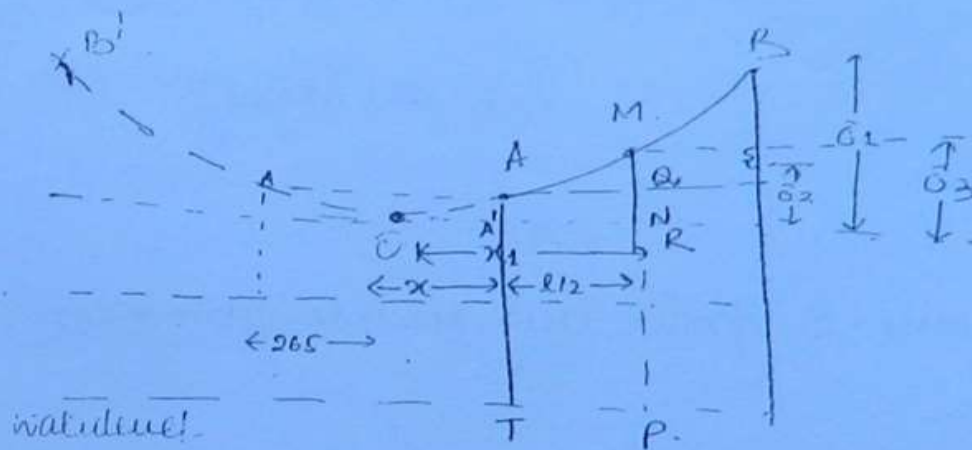negative value of x indicates that both towers are located on one side of lowest point O .



Let 'M' be the point located at the center between the two towers. The horizontal distance of M from the lowest point 'O' is equal to

$$x_1 = OA' + A'N$$

$$= x + A'N$$

$$= 265 + l/2$$

$$= 265 + \frac{270}{2}$$

(+ve sign as represented on other side)

$$x_1 = 400m$$

The height of point 'A' from the lowest point 'O'

$$\delta_2 = \frac{w x^2}{2T}$$

$$= \frac{1 \times 265^2}{2 \times 1800} = 19.50m$$

• height of point M from the lowest point O.

$$\delta_0 = \frac{w x_1^2}{2T} = \frac{1 \times 400 \times 2}{2 \times 1800}$$

$$= 44.44 \text{ m}$$

• height of point B from the lowest point O

$$\delta_1 = \frac{w (265 + 270)^2}{2T} = 19.50 \text{ m}$$

• the distance b/w the midpoint M b/w the supports at A and B to the water level.

$$MP = MQ + QP$$


$$MP = (6582)^{\frac{1}{2}} \text{ AT}$$

$$MP = 2(44.44 - 19.5) + 50$$

$$MP = 54.94 \text{ m}$$

STRINGING CHART
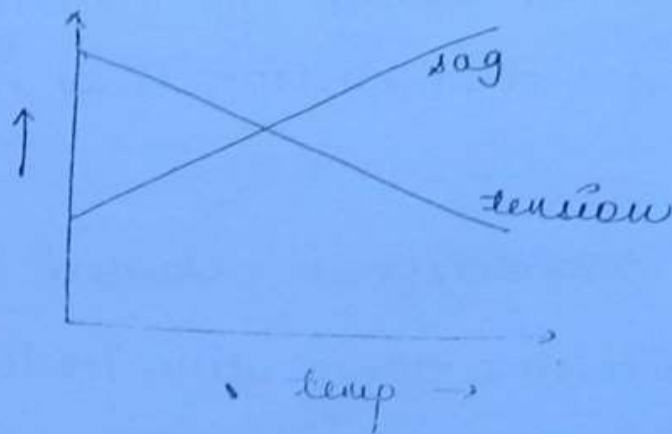
#. stringing charts gives the relation b/w tension and temp and sag and temp.



SAG TEMPLATE

• sag template is used to allocate the position and high height of the supports.

- sag template is made of transparent & celluloid or other material paper.

- sag template consist of 4 different characteristic

1) HOT template curve / HOT curve : hot curve is obtained between sag at max^m temp

- HOT curve determines the ground clearance.

2) Ground Clearance Curve:

Ground clearance curve is below the hot curve and it is drawn parallel to hot curve.

3) Support Post curve:

This curve is drawn for locating the position of supports for transmission lines.

4) Cold curve / uplift curve:

Cold curve is obtained by plotting the sag at minimum temp with ice loading and wind loading with respect to span length.

POWER CABLES

- A cable consists of 3 components:
 - 1) Conductor
 - 2) Insulator / Dielectric
 - 3) Sheath.

≡ CONDUCTOR:

- A conductor provides a path of conduction for current.

≡ DIELECTRIC:

It withstands service voltage and isolates conductor from other material.

3) SHEATH:


sheath donot allow the moisture content into the cables and prevent cables from chemical forces.

DIELECTRIC STRESS.

- when the electrostatic field is uniform, the stress of dielectric.

$$= \frac{\text{Applied voltage (V)}}{\text{thickness of dielectric}}$$

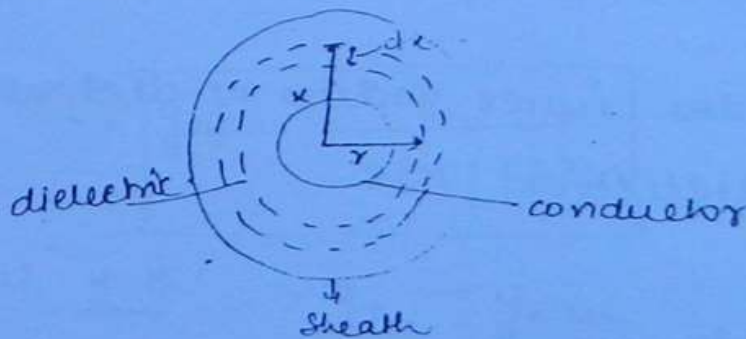- In underground cables the electro-static field is not uniform. therefore the dielectric stress at any point in a single-core cable can changes w.r.t distance x .



- $r \rightarrow$ radius conductor / inner radius of dielectric
- $R \rightarrow$ internal radius of sheath / outer radius of insulation
- $\epsilon_0 \rightarrow$ permittivity of free space

$Q \rightarrow$ charge/unit of length of conductor

$V \rightarrow$ voltage b/w the phase and neutral

- Electric flux density at the distance x from centre of conductor

$$D_x = \frac{Q}{2\pi x} \text{ C/m}^2$$

- dielectric stress

$$g_x = \frac{D_x}{\epsilon} = \frac{D_x}{\epsilon_0 \epsilon_r}$$

$$g_x = \frac{Q}{2\pi \epsilon_0 \epsilon_r x} \quad (1)$$

- Total dielectric stress is obtained by varying x from $(r \text{ to } R)$.

- Potential difference b/w the inner radius of dielectric and outer radius of dielectric

$$V = \int_{x=r}^{x=R} g_x dx$$

$$V = \int_r^R \frac{Q}{2\pi \epsilon_0 \epsilon_r x} dx$$

$$V = \frac{Q}{2\pi\epsilon_0\epsilon_r} \ln(x) \Big|_r^R$$

$$V = \frac{Q}{2\pi\epsilon_0\epsilon_r} \ln(R/r) \quad \text{--- (2)}$$

from eqn (1)

$$\frac{Q}{2\pi\epsilon_0\epsilon_r} = x \cdot g_x \quad \text{--- (3)}$$

substituting in (2)

$$V = x \cdot g_x \ln(R/r)$$

$$g_x = \frac{V}{x \ln(R/r)} \quad \text{--- (4)}$$

at $x=r$. $g_x \rightarrow g_{max}$

$$\therefore g_{max} = \frac{V}{r \ln(R/r)} \quad \text{--- (5)}$$

at $x=R$. $g_x \rightarrow g_{min}$

$$g_{min} = \frac{V}{R \ln(R/r)} \quad \text{--- (6)}$$

if now

$$\frac{g_{max}}{g_{min}} = R/r \quad \text{--- (7)}$$

Economical Size of cable.

- For g_{max} to be minimum $r \ln(R/r)$ has to be max.
- The condition for minimum g_{max} is

$$\frac{d}{dr} [r \ln(R/r)] = 0$$

$$= \frac{d}{dr} [r \{ \ln R - \ln r \}] = 0$$

$$= \frac{d}{dr} [r \ln R - r \ln r] = 0$$

$$\Rightarrow \left[\ln(R) \frac{d}{dr}(r) + r \frac{d}{dr}(\ln R) \right] - \frac{d}{dr}(r \ln r) = 0$$

$$= [\ln(R) + 0 - 1 - \ln r] = 0$$

$$\Rightarrow \ln R - 1 - \ln r = 0$$

$$\boxed{R/r = e = 2.718}$$

Ex:

A single core cable for a working voltage of 6.5 kV (b/w core and sheath) has conductor of 10 mm overall diameter, which is insulated to a thickness of

4.5mm. the maxⁿ electric stress on insulation is

Solⁿ

$$r = \frac{10\text{mm}}{2} = 5\text{mm}$$

$$R = 5\text{mm} + 4.5 = 12.5\text{mm} \\ (r + t)$$

$$g_{\text{max}} = \frac{V}{r \ln(R/r)} = \frac{6.5 \times 10^3}{5 \ln\left(\frac{12.5}{5}\right)} = 1.49 \text{ KV/mm.}$$

Quesⁿ

A single core cable is operating on a 3- ϕ phase 275KV system. the maximum dielectric stress should not exceed 15KV/mm. the overall diameter of single core cable and the most economical diameter of single core cable are.

Solⁿ

$$\text{Rms value of phase voltage} = \frac{275}{\sqrt{3}} = 158.77 \text{ KV}$$

$$g_{\text{max}} = 15 \text{ KV/mm.}$$

$$15 \text{ KV} = \frac{V}{r \ln(R/r)} = \frac{224.5}{r \ln(R/r)}$$

$$\text{Max value the phase voltage} = 158.77 \times \sqrt{3} = 275 \text{ KV}$$

$$\Rightarrow r \ln(R/r) = 0.01496$$

For most economical diameter,

$$R/r = e$$

$$\ln(R/r) = 1$$

$$r = \frac{224.5}{15} = 14.96 \text{ mm}$$

economical diameter of conductor $= 2 \times r = 29.92$

economical diameter of cables $= 2 \times R$
 $= 81.38 \text{ mm}$


GRADING OF CABLES

- the electrostatic stress in single core cable has max value at g_{max} and it decreases as we move towards sheath where electrostatic stress is minimum.
- for safe working of a cable having homogeneous dielectric, the strength of dielectric must be greater than g_{max} .
- If the dielectric of higher strength is used for cable, it is useful only near the

conductance surface where the stress is max.

- As we move away from the conductor, electrostatic stress decreases and dielectric increasingly strong therefore the cables must be graded such that the dielectric strength varies based on 'x'

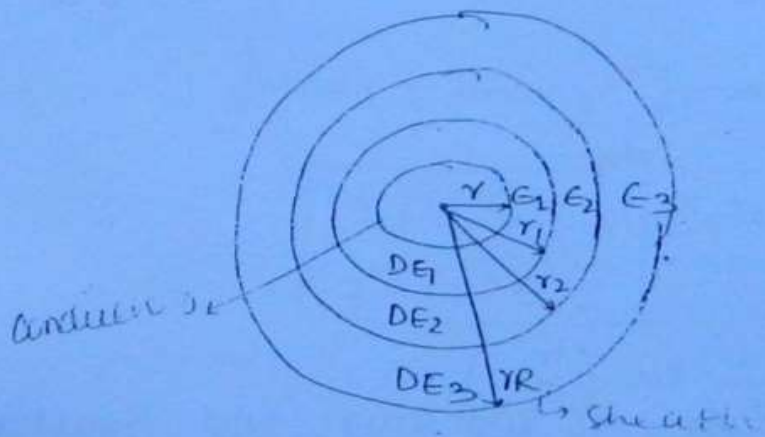1) Dielectric grading / Capacitance Grading



* potential difference across inner layer.

$$V_1 = \int_{x=r}^{x=r_1} \frac{q \cdot dx}{x}$$

$$= \int_{x=r}^{x=r_1} \frac{Q}{2\pi \epsilon_0 \epsilon_1 x} \cdot dx$$

$$= \frac{Q}{2\pi \epsilon_0 \epsilon_1} \left[\ln(x) \right]_r^{r_1}$$

$$V_1 = \frac{Q}{2\pi\epsilon_0\epsilon_1} \ln\left(\frac{r_1}{r}\right).$$

$$V_1 = g_{max1} \cdot r \ln\left(\frac{r_1}{r}\right).$$

$$g_{max} = \frac{Q}{2\pi\epsilon_0\epsilon_2 r}$$

$$g_{max1} = \frac{Q}{2\pi\epsilon_0\epsilon_1 r}$$

• Potential difference across middle layer

$$g_{max2} = \frac{Q}{2\pi\epsilon_0\epsilon_2 r_1}$$

$$g_{max3} = \frac{Q}{2\pi\epsilon_0\epsilon_3 r_2}$$

$$V_2 = \int_{r_1}^{r_2} g_x \cdot dx.$$

$$= \int_{r_1}^{r_2} \frac{Q}{2\pi\epsilon_0\epsilon_2 x} \cdot dx$$

$$= \left[\frac{Q}{2\pi\epsilon_0\epsilon_2} \ln\left(\frac{r_2}{r_1}\right) \right]$$

$$= \left[\frac{Q}{2\pi\epsilon_0\epsilon_2 r_1} \right] r_1 \ln\left(\frac{r_2}{r_1}\right)$$

$$V_2 = g_{max2} \cdot r_1 \ln\left(\frac{r_2}{r_1}\right)$$

• potential difference across outer layer.

$$V_3 = \int_{r_2}^{R_0} g_x \cdot dx.$$

$$\Rightarrow \int_{r_2}^{R_2} \frac{Q}{2\pi\epsilon_0\epsilon_3} \ln\left(\frac{R}{r_2}\right)$$

$$= \frac{Q}{2\pi\epsilon_0\epsilon_3 r_2} \ln\left[\frac{R}{r_2}\right]$$

$$V_g = g_{max2} \cdot r_2 \ln\left(\frac{R}{r_2}\right)$$

when $\epsilon_1 r = \epsilon_2 r_2 = \epsilon_3 r_2$

$$g_{max1} = g_{max2} = g_{max3}$$

$$\begin{aligned} r < r_1 < r_2 \\ \epsilon_1 > \epsilon_2 > \epsilon_3 \end{aligned}$$

• Voltage b/w core and sheath.

$$V = V_1 + V_2 + V_3$$

$$V = g_{max} \left[r \ln\left(\frac{r_1}{r}\right) + r_1 \ln\left(\frac{r_2}{r_1}\right) + r_2 \ln\left(\frac{R}{r_2}\right) \right]$$

• capacitance of the cable.

$$C = Q/V$$

$$C = \frac{Q}{V_1 + V_2 + V_3}$$

$$= \frac{Q}{\frac{Q}{2\pi\epsilon_0\epsilon_1} \ln\left(\frac{r_1}{r}\right) + \frac{Q}{2\pi\epsilon_0\epsilon_2} \ln\left(\frac{r_2}{r_1}\right) + \frac{Q}{2\pi\epsilon_0\epsilon_3} \ln\left(\frac{R}{r_2}\right)}$$

$$= \frac{Q}{2\pi\epsilon_0} \left[\frac{1}{\epsilon_1} \ln\left(\frac{r_1}{r}\right) + \frac{1}{\epsilon_2} \ln\left(\frac{r_2}{r_1}\right) + \frac{1}{\epsilon_3} \ln\left(\frac{R}{r_2}\right) \right]$$

$$C = \frac{2\pi\epsilon_0}{\left[\frac{1}{\epsilon_1} \ln\left(\frac{r_1}{r}\right) + \frac{1}{\epsilon_2} \ln\left(\frac{r_2}{r_1}\right) + \frac{1}{\epsilon_3} \ln\left(\frac{R}{r_2}\right) \right]}$$


Date

26 Oct 15

Quesⁿ

Single core cable has a conductor of 10mm diameter and 2 layers of different dielectric, each of 5mm thickness. The relative permittivities are 3 and 2.5, determine the potential gradient at the surface of the conductor when the potential difference b/w conductor and sheath is 60KV.

Solⁿ

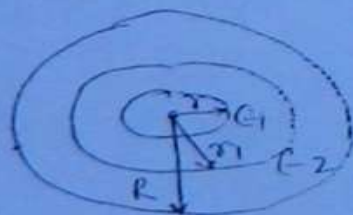

Radius of conductor = 10/2 = 5mm = 5×10^{-3} m

$\epsilon_1 = 3$

$\epsilon_2 = 2.5$

$R = t + t = 15$ mm

$r_1 = R$ and $r_2 = 15 + 10 = 25$ mm

now, max^m potential gradient at surface of conductor

$$g_{1\max} = \frac{Q}{2\pi\epsilon_0\epsilon_1\delta} \quad \text{--- (1)}$$

$$g_{2\max} = \frac{Q}{2\pi\epsilon_0\epsilon_2\delta_1} \quad \text{--- (2)}$$

on dividing,

$$\frac{g_{1\max}}{g_{2\max}} = \frac{\epsilon_1\delta}{\epsilon_2\delta_1}$$

$$\frac{\delta_1 g_{2\max}}{\delta g_{1\max}} = \frac{\epsilon_1}{\epsilon_2} \quad \text{--- (3)}$$

• potential difference between conductor and sheath

$$V = V_1 + V_2$$

$$60 = g_{1\max} \cdot \delta \ln \frac{R}{\delta} + g_{2\max} \delta_1 \ln \frac{R}{R_1}$$

$$\Rightarrow 60 = g_{1\max} \delta \left[\ln \frac{R}{\delta} + \frac{g_{2\max} \delta_1 \ln \frac{R}{R_1}}{g_{1\max} \delta} \right]$$

$$= g_{1\max} \delta \left[\ln \frac{R}{\delta} + \frac{\epsilon_1}{\epsilon_2} \ln \left(\frac{R}{R_1} \right) \right]$$

$$60 = g_{1\max} \cdot 5 \left[\ln \frac{15}{5} + \frac{3}{2.5} \ln \frac{35}{15} \right]$$


$$g_{1\max} = 70.1 \text{ kV/mm}$$

Quesⁿ:-

A single core cable is to be designed for 66KV to ground. The radius of conductor is 10mm. and insulating materials A, B and C have relative permittivities of 5, 4 and 3, and corresponding max^m stresses 5.8, 2.6 and 2 KV/mm. determine the minimum diameter of sheath.

Solⁿ

$$\begin{array}{l|l} 5.8 = g_{A \max} & \epsilon_A = 5 \\ 2.6 = g_{B \max} & \epsilon_B = 4 \\ 2 = g_{C \max} & \epsilon_C = 3 \end{array}$$

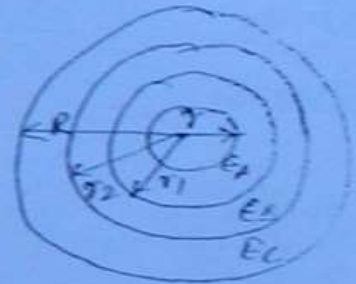

max^m dielectric stress of dielectric A

$$g_{A \max} = \frac{Q}{2\pi\epsilon_0\epsilon_A r}$$

$$5.8 = \frac{Q}{2\pi\epsilon_0 \times 5 \times 10 \text{ mm}}$$

$$\Rightarrow \frac{Q}{2\pi\epsilon_0} = 190$$

max^m dielectric stress of dielectric B.

$$= \frac{Q}{2\pi\epsilon_0\epsilon_B r_1}$$

$$2.6 = \frac{190}{4 \times r_1}$$

$$r_1 = 18.26 \text{ mm.}$$

• max^u dielectric stress of dielectric C

$$g_{c \max} = \frac{Q}{2\pi\epsilon_0\epsilon_c r_2}$$

$$Q = \frac{190}{3 \times r_2}$$

$$r_2 = 31.67 \text{ mm}$$

• Potential difference across inner layer.

$$V_1 = g_{A \max} \cdot r_1 \cdot \ln\left(\frac{r_1}{r}\right)$$

$$= 3.8 \times 10 \ln\left(\frac{18.3}{10}\right)$$

$$V_1 = 2256 \text{ KV}$$

$$V_2 = g_{B \max} \cdot r_1 \ln\left(\frac{r_2}{r_1}\right)$$

$$= 2.6 \times 18.3 \cdot \ln\left(\frac{31.67}{18.3}\right)$$

$$V_2 = 26.1 \text{ KV}$$

as $V = V_1 + V_2 + V_3$

$$V_3 = g_{C \max} \cdot r_2 \cdot \ln\left(\frac{R}{r_2}\right)$$

$$= 2 \times 31.67 \ln\left(\frac{R}{31.67}\right)$$

$$V_3 = 63.34 \ln\left(\frac{R}{31.67}\right)$$

$$66 \text{ kV} = 22.96 + 26.1 + 63.34 \ln\left(\frac{R}{31.7}\right)$$

$$\frac{16.51}{63.34} = \ln\left(\frac{R}{31.7}\right)$$

$$0.26 \quad 0.267$$

$$1.506 = \frac{R}{31.7}$$


$$R = 41.40$$

$$\text{Diameter} = 2R = 82.8 \text{ mm.}$$

INTER-SHEATH GRADING.

- In this method same insulating material is utilized through out the total thickness of the dielectric.
- The dielectric is divided in two or more sheaths layers by providing intersheaths.
- Intersheaths are thin metallic or cylindrical sheaths concentric with the conductor and placed b/w conductor and outside sheaths.
- Intersheaths are maintained at suitable potentials by connecting them to the

tappings from the supply lines.

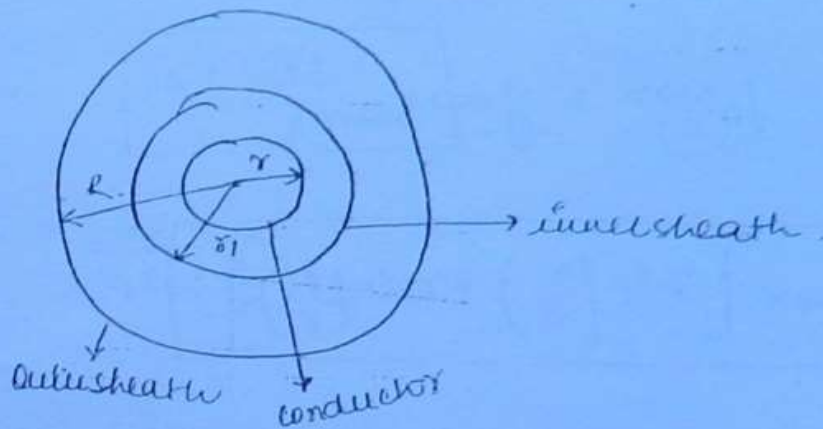

• Let $r \rightarrow$ radius of conductor

$r_1 \rightarrow$ radius of intersheath

$R \rightarrow$ radius of outer sheath.

$V_1 \rightarrow$ voltage b/w conductor and intersheath.

$V_2 \rightarrow$ voltage b/w intersheath and outer sheath.

$V \rightarrow$ voltage b/w conductor and outer sheath.

$$g_{1\max} = \frac{V_1}{r \ln(r_1/r)} \Rightarrow \boxed{V_1 = r g_{1\max} \ln\left(\frac{r_1}{r}\right)} \quad \dots (1)$$

$$g_{2\max} = \frac{V_2}{r_1 \ln\left(\frac{R}{r_1}\right)} \Rightarrow \boxed{V_2 = r_1 g_{1\max} \ln\left(\frac{R}{r_1}\right)} \quad \dots (2)$$

Potential difference b/w core and sheath

$$V = V_1 + V_2$$

$$= r g_{\max} \ln\left(\frac{r_1}{r}\right) + r_1 g_{\max} \left(\frac{r}{r_1}\right)$$

and $g_1 \max = g_2 \max = g_{\max}$.

$$\therefore V = g_{\max} \left[r \cdot \ln\left(\frac{r_1}{r}\right) + r_1 \ln\left(\frac{r}{r_1}\right) \right]$$

ECONOMICAL SIZE OF CABLE

According to dielectric grading

$$\frac{r_1}{r} = e = \frac{\text{Sheath radius}}{\text{conductor radius}} \quad \text{--- (1)}$$

now

$$g_1 \max = \frac{V_1}{r \ln\left(\frac{r_1}{r}\right)}$$

$$\left[g_{\max} = \frac{V_1}{r} \right]$$

Since $g_{\max} = g_{\max} = \frac{V_1}{r}$

$$\therefore r = \frac{V_1}{g_{\max}}$$

substituting in eqn. (1)

$$\Rightarrow r_1 = e\gamma = \frac{eV_1}{g_{max}}$$

$$\boxed{r_1 = \frac{eV_1}{g_{max}}} \quad \text{--- (2)}$$

• Since $g_{2max} = \frac{V_2}{r_1 \ln(R/r_1)}$

$$g_{2max} = \frac{V_2}{r_1 \ln(R/r_1)}$$

$$g_{2max} = \frac{V_2}{r_1 \ln(R/r_1)}$$

$$\frac{V_1}{\gamma} = \frac{V_2}{r_1 \ln(R/r_1)}$$

$$\Rightarrow \ln(R/r_1) = \frac{V_2 \times \gamma}{r_1 V_1}$$

$$\ln(R/r_1) = \frac{V_2}{V_1} \times \frac{1}{e}$$

$$\therefore \frac{r_1}{\gamma} = e$$

Since

$$V = V_1 + V_2$$

$$V_2 = V - V_1$$

Thus

$$\ln(R/r_1) = \frac{(V - V_1)}{V_1} \times \frac{1}{e}$$

$$\ln(R/r_1) = \frac{V}{eV_1} - \frac{1}{e}$$

$$\Rightarrow \frac{R}{r_1} = e^{\left[\frac{V}{eV_1} - \frac{1}{e}\right]}$$

$$R = r_1 e^{\left[\frac{V}{eV_1} - \frac{1}{e}\right]}$$

Substitute eqⁿ (2) in above eqⁿ

$$R = \frac{e V_1}{g_{max}} e^{\left[\frac{V}{eV_1} - \frac{1}{e}\right]}$$

$$R = \frac{V_1}{g_{max}} \cdot e^1 \cdot e^{\frac{V}{eV_1}} \cdot e^{-1/e}$$

$$R = \frac{V_1}{g_{max}} \cdot e^{1-1/e} \cdot e^{\frac{V}{eV_1}}$$

where $A = \frac{e^{1-1/e}}{g_{max}}$

$$R = A \cdot V_1 \cdot e^{\frac{V}{eV_1}} \quad \text{--- (3)}$$

Equation (3) represents the relation b/w the radius of interelectrode in terms of the potential difference across the interelectrode.

For minimum radius of outersheath differentiate eqn (3) w.r.t V_1 and equate to zero.

$$\frac{dR}{dv_1} = 0.$$

$$\therefore \frac{d}{dv_1} [A \cdot v_1 \cdot e^{v/v_1}] = 0$$

$$= A \cdot v_1 \frac{d}{dv_1} [e^{v/v_1}] = 0 + A \cdot e^{v/v_1} \cdot \frac{d}{dv_1} (v_1) = 0$$

$$\Rightarrow A \cdot v_1 \cdot e^{v/v_1} \cdot e^{v/v_1} + A \cdot e^{v/v_1} \cdot 1 = 0$$

$$\Rightarrow A \cdot e^{v/v_1} \left\{ \frac{-v v_1}{e v_1^2} + 1 \right\} = 0$$

The above expression is equal to zero for the following condition.

$$1 - \frac{v v_1}{e v_1^2} = 0$$

$$1 = \frac{v}{e v_1}$$

$$\boxed{e = v/v_1} \quad \text{and} \quad \boxed{v_1 = v/e}$$

$$\boxed{\text{voltage across sheath} = \frac{\text{total voltage}}{e}}$$

- for economical size of cable the voltage across inner layer is $1/e$ thus the voltage b/w conductor and sheath

- now dielectric stress across first layer.

$$g_{1\max} = g_{\max} = \frac{V}{r \ln(r_1/r)}$$

$$\Rightarrow g_{\max} = V/r$$

$$g_{\max} = \frac{V}{e \cdot r}$$

$$\boxed{r = \frac{V}{e \cdot g_{\max}}} \dots (4)$$

This should be radius of conductor so that size of cable decreases.

- now $r_{1/2} = e$

$$r_1 = r \cdot e$$

$$= V/g_{\max} \cdot e \dots$$

$$\boxed{r_1 = V/g_{\max}} \dots (5)$$

- the most economical size of cable.

$$R = A \cdot V_1 e^{-V_1/e}$$

$$R = \frac{V_1}{g_{\max}} \cdot e^{(1-1/e)} \cdot e^{V_1/e V_1}$$

$$R = \frac{V}{g_{\max}} e^{1-V/c} \cdot \frac{V}{e^{V/c} \cdot V/c}$$

$$R = \frac{V}{g_{\max}} e^{1-1/c}$$

$$R = 1.881 \frac{V_1}{g_{\max}} \dots \dots \textcircled{6}$$

Radius of outer sheath ↑

Questⁿ

A 60kV single core cable is graded by means of metallic intersheath. The safe electric stress of insulating material is 4kV/mm. Calculate

1) diameter of intersheath and voltage at which it must be maintained in order to obtain minimum overall diameter and the corresponding conductor diameter

2) compare the conductor diameter obtained in question ① with that of an ungraded cable working under same condition

Solⁿ 1) with intersheath

$$\text{Voltage across inner layer} = V_1 = V/c = \frac{60}{2.718} =$$

$$= 22.1 \text{ kV}$$

∴ economical radius of conductor

$$r \approx \frac{V}{E_{gmax}} = \frac{60}{2.718 \times 4}$$

$$r \approx 5.5 \text{ mm}$$

∴ economical diameter of conductor = 2×5.5
= 11 mm.

radius of inter sheath $r_1 = \frac{V}{g_{max}} = \frac{60}{4} = 15 \text{ mm}$.

∴ economical diameter of intersheath = $2 \times r_1 = D_1 = 30 \text{ mm}$

economical radius of outersheath or cable.

$$R = 1.881 \frac{V}{g_{max}} = 28.2 \text{ mm}$$


$$\text{So diameter} = 2 \times 28.2 = 56.43 \text{ mm}$$

now voltage across second layer = $(V - V_1)$

$$= 60 - 22.1$$

$$V_2 = 37.5 \text{ kV}$$

2) without intersheath

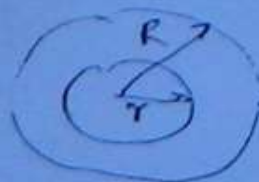

now $R/r = e$

$\Rightarrow R = e \cdot r = 2.718 \times r$

now operating voltage = 60kV, when sheath is not used the voltage totally operated at dielectric. Now voltage b/w conductor and sheath.

$$V = g_{max} \cdot r \ln(R/r)$$

$$V = g_{max} \cdot r \cdot 1$$

$\frac{60}{4} = 15 \text{ mm} = r$ and $d = 30 \text{ mm}$ (conductor diameter)

so $R = 2.718 \times 15 \text{ mm}$

$= 40.77 \text{ mm}$

; economical radius of cable $R = 40.77 \text{ mm}$

$D = 81.54 \text{ mm}$

CHARGING CURRENT IN CABLE


• the capacitance of a cable determines

- 1) charging current
- 2) Charging kVA
- 3) dielectric loss.


- charging current limits the use of cables on extra-high voltage lines.
- In a/c system the charging current depends on length of line and location of capacitance. The current carrying capacity of a transmission line increases when the locatⁿ of capacitance moves away from the sending end.
- In d/c system - the current carrying capacity of d/c cable is independent of the length.
 → b/c capacitor behaves like open circuit

CALCULATION OF CAPACITANCE IN 3-CORE CABLE


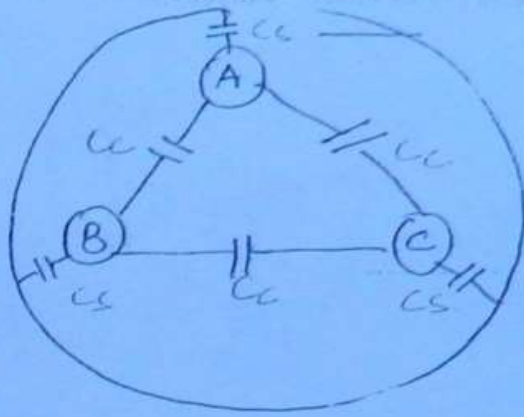
- Conductors in cable are separated from each other by dielectric. Similarly there is dielectric b/w conductor and sheath when potential difference is applied b/w conductors in a cable. The effect of combination of 6 capacitances must be considered.
- Capacitance b/w the conductors is denoted by ' C_c ' and capacitance b/w conductor and sheath is denoted by C_s



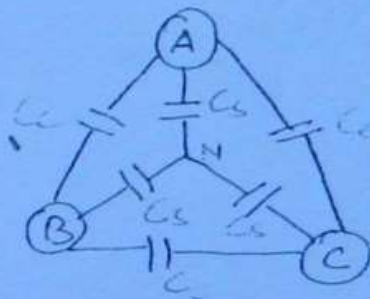- Sheath operates at zero potential. therefore the entire sheath is represented by a ground / neutral point.



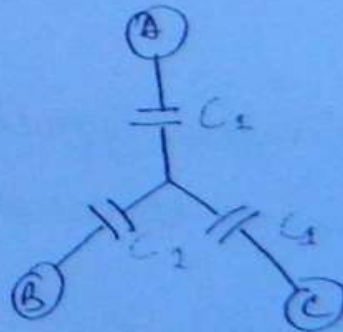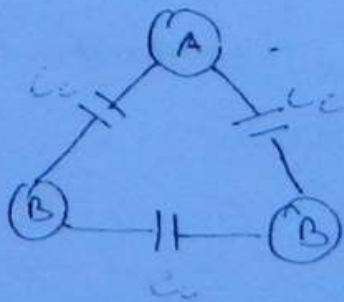- Conductor capacitance is in delta and capacitance between ^{conductor &} sheath is in star.
- Converting capacitances connected in delta into equivalent star.



$$\Delta \rightarrow C_{AB} = C_c + \frac{C_c}{2} = 1.5 C_c$$


$$Y \rightarrow C_{AB} = \frac{C_c}{2}$$

now

$$C_{AB} = \frac{Q}{2}$$

$$1.5 C_c = Q/2$$

$$C_1 = 3C_c$$

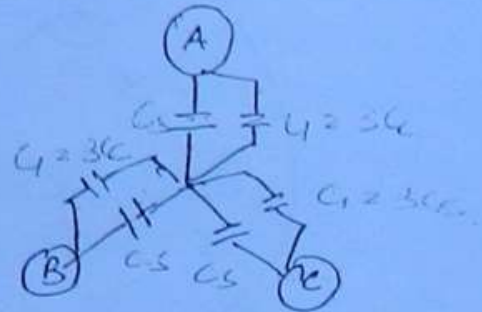

So

$$C_0 = C_{N-A} = C_1 + C_2 = 3C_c + C_c$$

$$C_0 = C_{N-B} = C_1 + C_3 = 3C_c + C_c$$

$$C_0 = C_{N-C} = C_2 + C_3 = 3C_c + C_c$$

$$C_0 = 3C_c + C_c$$

charging current $= \frac{V_{ph}}{X_c}$

$$= \frac{V_{ph}}{\frac{1}{\omega C_0}} = \omega C_0 V_{ph}$$

$$\text{charging current} = \omega C_0 V_{ph}$$


Ques

Determine the equivalent capacitance b/w two conductors A & B when conductor C is connected to the sheath


(A)

(B)

(C)

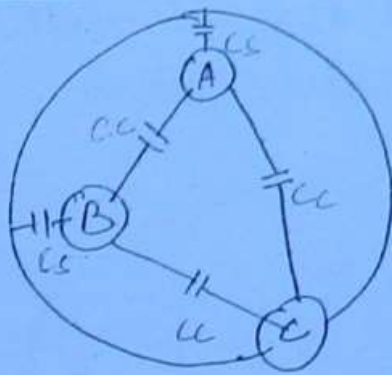

Solution:

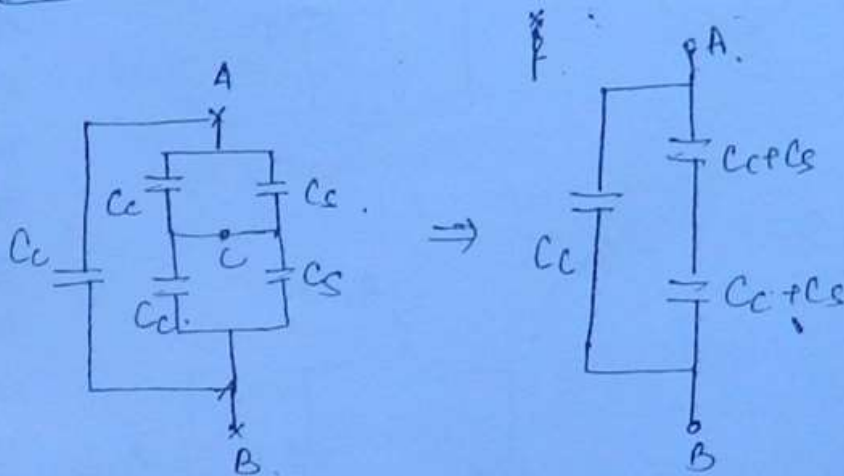

$$C_{AB} = C_c + \frac{(C_c + C_s)}{2}$$



$$= \frac{1}{2} [3C_c + C_s]$$

$$C_{AB} = \frac{1}{2} C_0$$

Quesⁿ

Determine the capacitance b/w conductor and sheath when all the 3 conductors are connected together.


Solⁿ

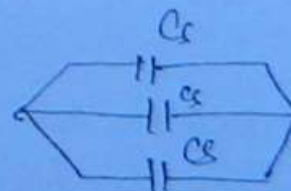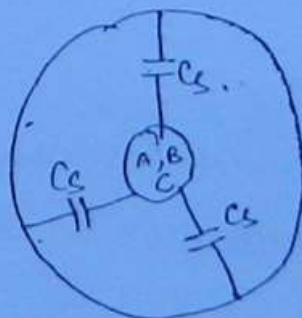

$$\Rightarrow 3C_s$$

Ques
Two conductors A and B are joined together determine the capacitance between the conductor A and C or conductor B and C.

Solutⁿ

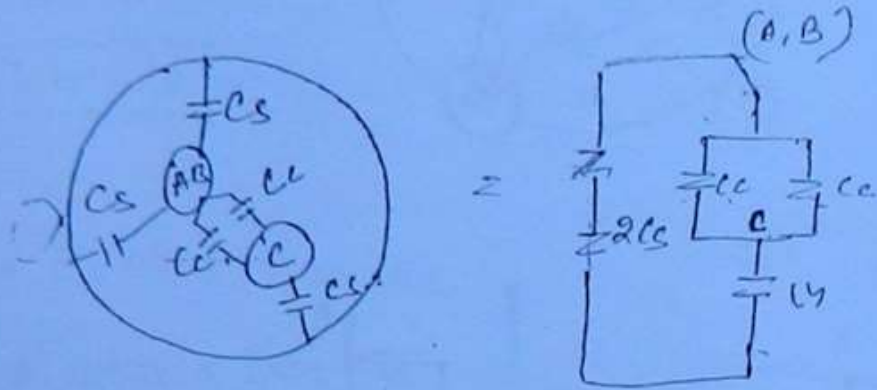

$$\frac{2C_s \times C/c}{3/c} = \frac{2}{3} C_s$$

$$\text{NOW} = 2C_c + \frac{2}{3} C_s$$


$$C_{A-C} / C_{B-C} = 2C_c + \frac{2}{3} C_s$$

$$2 \left(C_c + \frac{1}{3} C_s \right)$$

$$6 \left[C_c + C_s \right]$$

$$\frac{2}{3} [3C_c + C_s]$$




$$C_{A-C} / C_{B-C} = \frac{2}{3} C_0$$

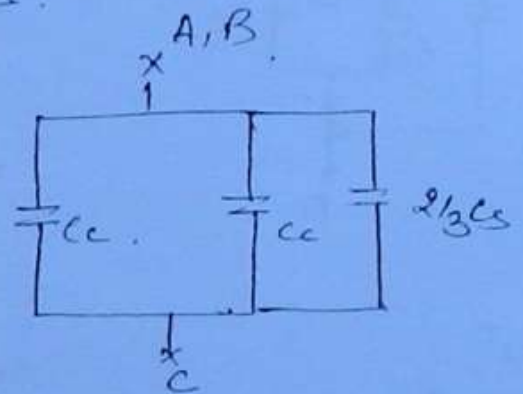

Ques

Two conductors A and B are connected to sheath determine the capacitance b/w 4 conductors A and B and third conductor C.

Solution:-

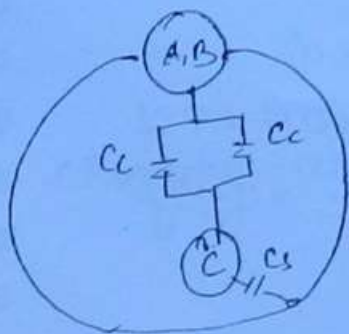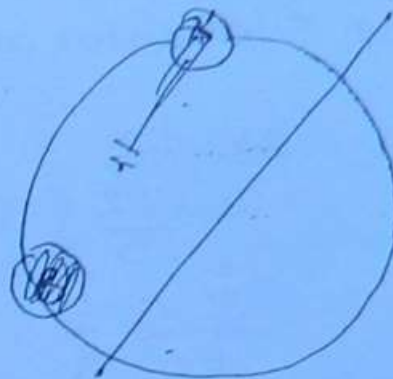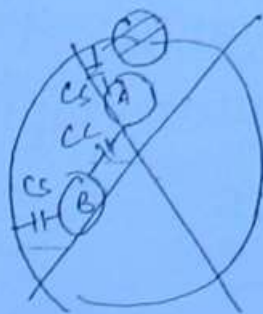

$$\begin{aligned} &2C_c + \\ &2C_c + C_s \\ &2(C_c + \end{aligned}$$

$$\begin{aligned} C_{A-C} &= 2C_c + C_s \\ &= (C_c + 2C_c + C_s) - C_c \\ &= (3C_c + C_s) - C_c \end{aligned}$$

$$C_{A-C} = C_c + C_s$$

Ques

The result of 1 km, 3- ϕ cable, give measured capacitance

0.74 F between 1 conductor and other 2 conductors

bunched together with earthed sheath and 1.24 F

measured b/w 3-bunched conductors and sheath. Calculate

1) capacitance b/w any pair of conductors, sheath being isolated.

2) charging current when cable is connected to 11 kV at 50 Hz supply.

Soln


Capacitance b/w 1 conductor and other 2 conductors bunched together.

$$2C_c + 2C_s = 0.74 \text{ F}$$

capacitance b/w 3-conductor and sheath.

$$Z_c = 1.2$$

$$C_s = \frac{1.2}{3} = 0.4 \mu F$$

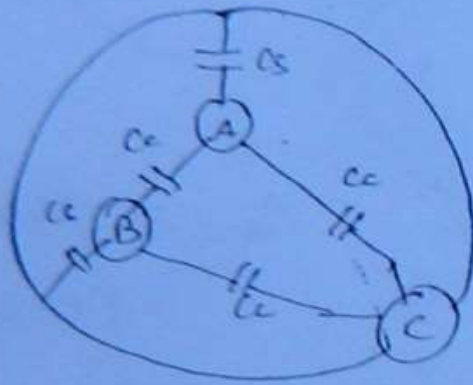

$$\therefore C_c + 0.4 = 0.7$$

$$C_c = 0.15 \mu F$$

$$1) \quad C_{AB} = C_0/2$$

$$= \frac{1}{2} [3C_c + C_s]$$

$$= \frac{1}{2} [3 \times 0.15 + 0.4]$$

$$C_{AB} = 0.425 \mu F$$

$$2) \text{ charging current} = \frac{11 \times 10^3 \cdot 2 \times \pi \times 50 \times}{\sqrt{3}}$$

$$= 1.69 \text{ A/phase}$$

Ans:

The capacitance measure b/w any two core of 3- ϕ cable is $0.3 \mu F/km$. Determine the charging reactive power taken by 5km length of this cable when connected to an 11kV, 50Hz supply.

When conductor 'c' is connected
the capacitance b/w conductors

$$C_{A-B} = C_0/2$$

$$\Rightarrow 0.3 \mu\text{f} \times 5 \text{ km} = C_0$$

$$C_0 = 3 \mu\text{f}$$

$$\text{charging current} = \frac{11 \times 10^3}{\sqrt{3}}$$

$$I_C = 5.98 \text{ A}$$

$$\text{reactive power} = I_C^2 X_C$$

$$= \sqrt{3} V_L I_C$$

$$= \sqrt{3} \times 11 \times 10^3 \times 5.98$$

$$= 114 \text{ KVAR}$$

Ques 7

A single core cable 5-km long has insulation resistance of 0.4 MΩ. The diameter of core is 20 mm. Diameter over insulation is 50 mm. Calculate the resistivity of insulating material.

Insulation resistance of cable

$$R_i = \frac{\rho}{2\pi l} \ln(R/r)$$

l → length of cable

r → radius of conductor

or inner radius of dielectric

$$R = 25 \text{ m}\Omega$$

$$R_i = 0.4 \text{ M}\Omega$$


$$0.4 \times 10^6 = \frac{8}{2 \times 13.14 \times 5000} \ln\left(\frac{25}{16}\right)$$

$$R_i = 13.42 \times 10^3 \text{ M}\Omega \cdot \text{m}$$

- the insulation resistance is inversely proportional to length of cable.

DIELECTRIC POWER LOSSES

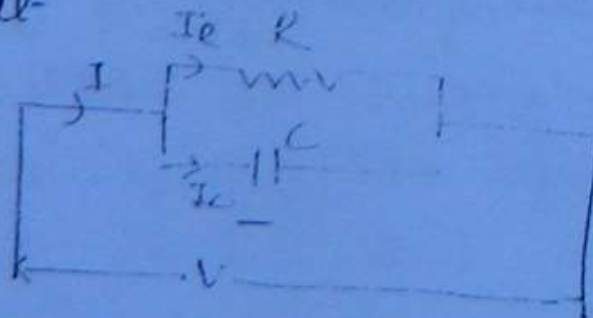- In a perfect cable resistance of dielectric is negligible
- All practical cables has dielectric resistance.
- The resistance are 'R' is connected in parallel to capacitance of cable.
- Equivalent circuit




Vector diagram :-

1) Perfect cable

open circuit.

$$R=0, I_R=0, I=I_C$$


$\therefore I_C$ leads V by 90°

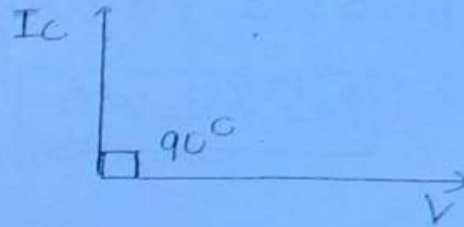

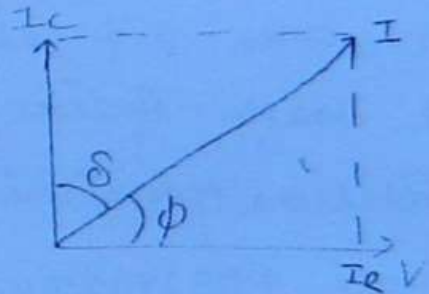2) Practical cable

- $I = I_R + I_C$
- I_R in phase with V
- I_C lead V by 90°

$\delta \rightarrow$ dielectric power loss angle.



- For a single phase line the dielectric power loss

$$\begin{aligned} P_d &= V \cdot I_R \quad \text{--- (1)} \\ P_d &= V I \cos \phi \quad \text{--- (2)} \end{aligned}$$

• On applying $\tan \delta = \frac{I_R}{I_C}$

$$I_R = I_C \tan \delta \quad \text{--- (3)}$$

$$I_C = V \omega \epsilon \quad \text{--- (4)}$$

So

$$I_R = \omega \epsilon V \tan \delta \quad \text{--- (5)}$$

⑤ → ⑥

$$P_d = V(\omega C V) \tan \delta$$

$$\text{Hence } \boxed{P_d = \omega C V^2 \tan \delta} \quad \text{--- (6) dielectric loss}$$

as $\tan \delta \approx \delta$ (δ very small)

$$\boxed{P_d = \omega C V^2 \delta} \quad \text{--- (7)}$$

• for 3- ϕ line

$$\boxed{P_d = 3 \omega C V^2 \delta} \quad \text{--- (8)}$$

Quesⁿ

A 33 kV, 50 Hz 3- ϕ cable has diameter 20 mm and internal sheath radius, 15 mm. If the dielectric has relative permittivity of 2.4 and dielectric loss angle 0.031 radian. Determine for 2.5 km length of cable.

- 1) Capacitance
- 2) Charging current
- 3) Generated reactive volt ampere
- 4) Dielectric loss
- 5) equivalent susceptance resistance

Sol

$$C = \frac{\epsilon_r}{18 \ln \left(\frac{R}{r} \right)} \quad \text{--- (9)}$$

$$= \frac{2.4}{18 \ln \left(\frac{15}{4} \right)} = 0.328 \mu\text{F}$$

$$\text{Magnetizing current} = V \cdot \omega \cdot C_0$$

$$= \frac{11 \times 10^3 \times 2\pi \times 2.14 \times 0.323 \times 2.5}{\sqrt{2}}$$

$$= 2.8 \text{ Amp / phase}$$

$$\text{Reactive power} = V_L I_L = 11 \times 10^3 \times 2.84$$

$$= 11 \times 10^3 \text{ KVAR}$$

$$\text{Dielectric loss} = \omega C_0 V^2 \tan \delta.$$

$$= 2\pi \times 50 \times 0.8225 \times 10^{-6} \times 11^2 \times \tan 0.03$$

$$\Rightarrow 968.75 \text{ W.}$$

$$5) \quad V I_R = P_d.$$

$$= V^2 / R = P_d.$$

$$R = V^2 / P_d$$

$$\Rightarrow \frac{(11000)^2}{968.75}$$

$$R = 0.125 \text{ M}\Omega$$

DISTRIBUTION SYSTEMS

- A distribution sys consists of 3-components.

1. Feeder [T.L]
2. Distributor
3. Service Mains.

FEEDER:

Feeder is a conductor of large current carrying capacity, carrying the current to the feeding points.

- A current carrying element, carrying uniform current through out the length of the conductor is known as feeder.
- Transmission lines are also known as feeder lines

DISTRIBUTOR:

Distributor is conductor from which current is tapped to supply to the consumer.

- A current carrying element carrying current for distance less than feeder is known as distributor

• SERVICE MAINS:

- The small cable located between distributor and consumer
- The size of feed, distributor or service main depends on current carrying capacity.

HV
EHV
CHV } criteria to select the feeder is
current carrying capacity.

- The selection of size of conductor for EHV line is based on current carrying capacity.
- The design of distributor size is based on voltage drop or percentage voltage drop

$$V = RI$$

$$V = \frac{\rho l}{A} \cdot I$$

$$VA = \rho l \cdot I$$

$$I < A$$

$$I \geq f A$$

$$\boxed{\text{Current density} = I/A}$$

current density equal $\rightarrow$ feeder
current density unequal $\rightarrow$ dist.

A feeder has ~~an~~ constant current density and distributor has variable current density.

Ques

For same power, same material and equal length the operating voltage of EHV line is increased by $\frac{n}{\sqrt{}}$ times. then the area of cross-section is

Solution

$$V_2 = nV_1$$

$$\text{at } V_1 \text{ : } P_1 = V_1 I_1 \cos \phi$$

$$\text{at } V_2 \text{ : } P_2 = V_2 I_2 \cos \phi$$

$$P_1 = P_2$$

$$V_1 I_1 \cos \phi = V_2 I_2 \cos \phi$$

$$V_1 I_1 = n V_1 I_2$$

$$\boxed{\frac{I_2 \cdot I_1}{I_1} = n} \quad \dots$$

$$I_1 \propto a_1$$

$$I_2 \propto a_2$$

$$\frac{a_2}{a_1} = \frac{I_2}{I_1}$$

$$a_2 = \frac{a_1 I_2}{I_1} = a/n$$

2) weight of conductor:

$$W \propto \frac{wt}{Vol}$$

$$wt \propto Vol$$

(current density is same)

$$wt \propto Vol$$

$$\propto (A \times L)$$

$$wt \propto (AL)$$

$$\% \eta = \frac{P}{P + I(J_{SE})} \times 100$$

and $P = VI \cos \phi$

$$\Rightarrow I = \frac{P}{V \cos \phi}$$

$$\therefore \% \eta = \frac{P}{P + \frac{P}{V \cos \phi} J_{SE}} \times 100$$

$$\% \eta = \frac{1}{1 + \frac{J_{SE}}{V \cos \phi}} \times 100$$

$$\% \eta = \left\{ 1 + \frac{J_{SE}}{V \cos \phi} \right\}^{-1} \times 100$$

$$\% \eta = \left\{ 1 - \frac{J_{SE}}{V \cos \phi} \right\} \times 100$$

now $P_2 = \frac{1}{n} P_1$; $I_2^2 R_2 = \frac{1}{n} (I_1^2 R_1)$

$$I_2^2 \frac{1}{a_2} = \frac{1}{n} (I_1^2 \frac{1}{a_1})$$

$$I_2 (J_2) = \frac{1}{n} (I_1) (J_1)$$

$$\boxed{I_2 = I_1 / n}$$

$$V_1 = I_1 R_1$$

$$V_1 = I_1 \frac{1}{a_1}$$

$$V_1 = J_1$$

$$V_2 = I_2 R_2$$

$$V_2 = I_2 \frac{1}{a_2}$$

$$V_2 = J_2$$

$$O_1 = J_2$$

$$\boxed{V_2 = V_1}$$

now for SE

$$S_1 = R_1 \frac{a_1}{l_1}$$

$$S_1 \propto R_1 \propto \frac{1}{I_1}$$

$$S_2 \propto R_2$$

$$\propto \frac{1}{I_2}$$

$$\boxed{\frac{S_2}{S_1} = \frac{I_1}{I_2} = \eta}$$

So

$$\% \eta = \left\{ 1 - \left(\frac{I_1}{V \cos \phi} \right) S_1 \right\} \times 100$$

$$\boxed{S_2 = \eta S_1}$$

$$\% \eta = \left\{ 1 - \left(\frac{I_1}{V \cos \phi} \right) (\eta S_1) \right\} \times 100$$

- the percentage efficiency increases as per above relation

Ques 17

In a distributor line the operating voltage is increased by n -times. Determine the new resistance.
 • R_2

Solution :-

$$\text{At } V_1 \text{ voltage drop} = \frac{I_1 R_1}{V_1}$$

$$\text{at } V_2 \text{ voltage drop} = \frac{I_2 R_2}{V_2}$$

$$\text{given } \boxed{V_2 = n V_1}$$

Based on the power equation

• voltage drop must be equal.

$$\frac{I_1 R_1}{V_1} = \frac{I_2 R_2}{V_2}$$

$$\frac{I_1 R_1}{V_1} = \frac{(1/n I_1) (R_2)}{n V_1}$$

$$\frac{I_1 R_1}{V_1} = \frac{I_1 R_2}{n^2 V_1}$$

$$R_2 = n^2 R_1$$

a) for above condition the cross-sectional area

$$R \propto \frac{1}{a^3}$$

$$R_1 \propto \frac{1}{a_1} \text{ and } R_2 \propto \frac{1}{a_2}$$

$$\frac{R_1}{R_2} = \frac{a_2}{a_1}$$

$$a_1 = a_2 \frac{R_2}{R_1} = a_2 \times \frac{n^2 R_1}{R_1}$$

$$a_2 = \frac{a_1}{n^2} \text{ --- distributor}$$

$$a_2 = a/n \text{ --- feeder}$$

• for the same power, same material, length, when the operating voltage increased by 'n' times

$$P_1 = V_1 I_1 \cos \phi$$

$$P_2 = V_2 I_2 \cos \phi$$

$$V_1 I_1 \cos \phi = V_2 I_2 \cos \phi$$

$$V_1 I_1 = n V_1 I_2$$

$$I_2 = \frac{1}{n} I_1$$

— area of the cross-section of feeder

$$A_2 = \frac{A_1}{n}$$

and of distributed

$$A_2 = \frac{A_1}{n^2}$$


Dated

27 Oct 2010

A two conductor feeder extending over a distance carries current of 120 A up at point C a 60 A up at point B. The point impedances of the sections AB and BC are

$Z_{AB} = (0.04 + j0.08) \Omega$ and $Z_{BC} = (0.08 + j0.12) \Omega$. Currents at

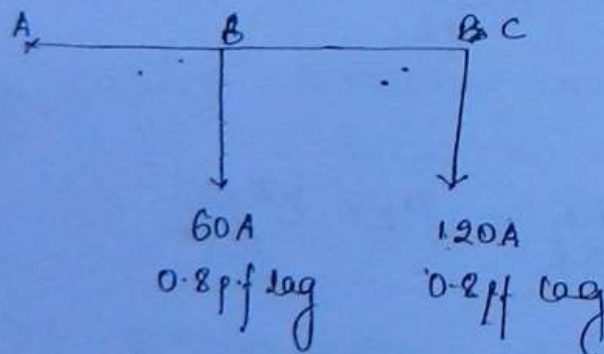point B and point C operates at power factor of 0.8 lagging the voltage at point C is 400 V. Calculate currents at point B and C.



Solⁿ current tapped at B

$$I_B = 60 \angle -\cos^{-1} 0.8$$

$$= 60 \angle -36.8^\circ \text{ A}$$

Current at point C

$$I_C = 120 \angle -\cos^{-1} 0.8$$

$$120 \angle -36.8^\circ \text{ A}$$

• current flowing in the section AB.

$$\begin{aligned} I_{AB} &= I_B + I_C \\ &= 60 \angle -36.8^\circ + 120 \angle -36.8^\circ \\ &= 179 \angle -36.8^\circ \text{ A} \end{aligned}$$

• current flowing in section BC.

$$I_C = 120 \angle -36.8^\circ \text{ A}.$$

Voltage drop in the section AB.

$$\begin{aligned} V_{AB} &= I_{AB} \cdot Z_{AB} \\ &= 179 \angle -36.8^\circ \cdot (0.04 + j0.08) \end{aligned}$$

$$V_{AB} = 16 \angle 26.6^\circ \text{ V}$$

voltage drop in the section BC.

$$\begin{aligned} V_{BC} &= I_{BC} \cdot Z_{BC} \\ &= 120 \angle -36.8^\circ (0.08 + j0.12) \end{aligned}$$

$$V_{BC} = 17.5 \angle 19.54^\circ \text{ V}$$

voltage at point B = $V_C + V_{BC}$

$$= 400 + 17.5 \angle 19.54^\circ$$

$$= 414.5 \angle 0.79^\circ \text{ V}$$

$$V_A = V_{AB} + V_B$$

$$416.4 \angle 0.79^\circ + 16 \angle 26.6^\circ$$

$$V_A = 450.8 \angle 1.72^\circ \text{ V}$$


Quesⁿ

A single phase A/c distributor 500m long, having impedance $(0.02 + j0.04)$ is fed with 250V at the extreme end. Currents are tapped at 3-points on the distributor

- 50Amp ~~up~~ UPF and 200m from extreme end.
- 100Amp 0.8 pf lag 300m from extreme end.
- 50Amp 0.6 pf lag 500m from extreme end.

Determine the voltage drop in each section and potential at the point where current 50Amp at 0.6 p.f lag is tapped.

Solⁿ

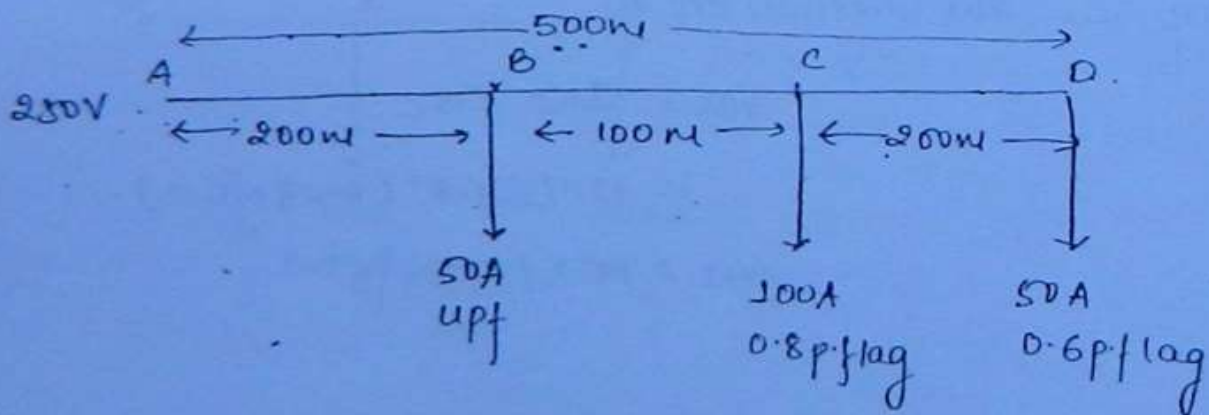

• Current tapped at point B.

$$I_B = 50 \angle 0^\circ \text{ Amp}$$

Current tapped at point C

$$I_C = 100 \angle -\cos^{-1} 0.8 = 100 \angle -36.8^\circ \text{ Amp}$$

$$I_D = 50 \angle -\cos^{-1} 0.6$$

$$= 50 \angle -53.2^\circ \text{ Amp.}$$

Section AB

Impedence of section AB

$$Z_{AB} = \frac{200}{500} (0.02 + j0.04)$$

$$= (0.008 + j0.016) \Omega$$

$$I_{AB} = I_B + I_C + I_D$$

$$= 100 \angle -36.8^\circ + 50 \angle -53.2^\circ + 50 \angle 0^\circ$$

$$= 188.6 \angle -31.9^\circ \text{ Amp}$$

~~V_{AB}~~

$$V_{AB} = I_{AB} \cdot Z_{AB}$$

$$= 188.6 \angle -31.9^\circ \times (0.008 + j0.016)$$

$$V_{AB} = 3.37 \angle 0.31^\circ \text{ Volt.}$$

Section BC

$$Z_{BC} = \frac{100}{500} (0.02 + j0.04)$$

$$Z_{BC} = (0.004 + j0.008) \Omega$$

$$I_{BC} = I_C + I_D$$

$$= 50 \angle -\cos^{-1} 0.6 + 100 \angle -36.8^\circ$$

$$I_{BC} = 148.5 \angle -42^\circ \text{ A}$$

$$V_{BC} = I_{BC} \cdot Z_{BC}$$

$$= 1.32 \angle -20.8^\circ \text{ V}$$

Section CD

$$Z_{CD} = \frac{200}{500} (0.008 + j0.016) \\ = (0.008 + j0.016)$$

$$I_{CD} = I_D \\ = 50 \angle -53.2^\circ \text{ A}$$

$$V_{CD} = I_{CD} \cdot Z_{CD} \\ \Rightarrow 50 \angle -53.2^\circ \times (0.008 + j0.016)$$

$$V_{CD} = 0.89 \angle 10.2^\circ \text{ V}$$

now

$$V_D = V - (V_{AB} + V_{BC} + V_{CD}) \\ = 250 - [5.37 \angle 0.31^\circ + 1.32 \angle 20.8^\circ + 0.89 \angle 10.2^\circ]$$

$$V_D = 245.08 \angle -0.5^\circ \text{ V}$$

Limitation of Radial System :-

- when a section of system is subjected to fault power is not supplied to the remaining sections. thereby interruption of power supply takes place for the consumers. To overcome this disadvantage and increase reliability of supply Ring Main system is adopted.

Question:

A two wire dc distributor ABCDEA is in the form of a ring main fed point A at 220V and is loaded as follows.


10Amp at point B, 20Amp at point C, 30Amp at point D and 10Amp at point E. The resistances of various sections are.

$$R_{AB} = 0.1\Omega; R_{BC} = 0.5\Omega; R_{CD} = 0.01\Omega$$

$$R_{DE} = 0.025\Omega; R_{EA} = 0.075\Omega. \text{ Determine}$$

- 1) Current flowing b/w point A and B
- 2) the point of minimum potential
- 3) Current in each section of distributor

Soln

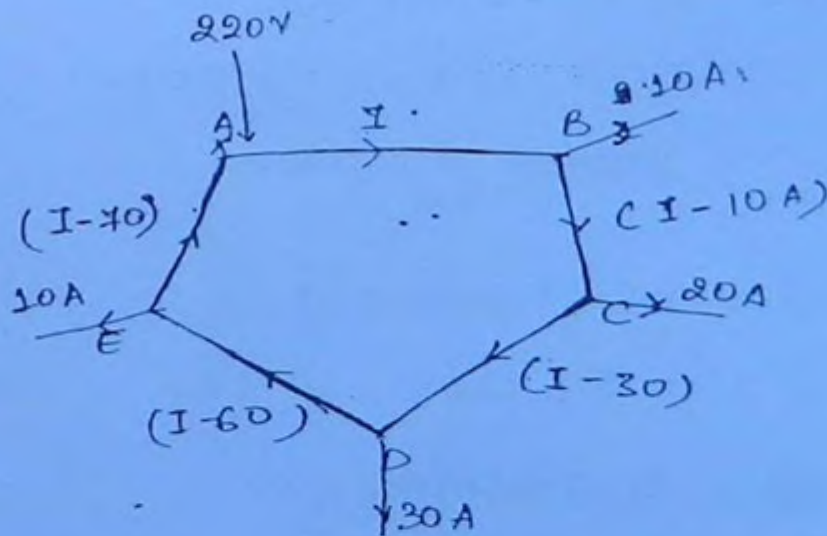

Applying

KVL to ring main system

$$= I(0.1) + (I-10) \times 0.5 + (I-30) \times 0.01 + (I-60) \times 0.025 + (I-70) \times 0.075\Omega.$$

$$= I(0.1 + 0.5 + 0.01 + 0.025 + 0.075) + 5 - 5 - 15 - 5$$

$$I = 29.04 \text{ A}$$

$$I_{AB} = I = 29.04 \text{ A}$$

• potential at point B

$$V_B = V_A - I(0.01)$$

$$= 220 - (29.04)(0.01)$$

$$V_B = 217.09 \text{ V}$$

p. now

$$V_C = V_B - (I-10)(0.05)$$

$$= \frac{208.48}{22}$$

$$V_C = V_B - (I-10)(0.05)$$

$$217.09 - (29.04-10)(0.05)$$

$$= \cancel{206.64} 216.158 \text{ V}$$

$$V_D = V_C - (I-30)(0.01)$$

$$= 216.128 \text{ V}$$

$$V_E = V_C - (I-60)(0.025)$$


$$V_E = 216.902 \text{ V}$$

✓

VOLTAGE CONTROL METHODS

- for the ~~safe~~ safe operation of power sys network the operating voltage of power sys components must be within the operating limits.
- Voltage control in power system equipment can be obtained by three methods.
 - 1) OFF-load tap changing x_{mtr} .
 - 2) On load tap changing x_{mtr}
 - 3) Auto x_{mtr} tap changing.

1) OFF-LOAD TAP CHANGING x_{mtr}

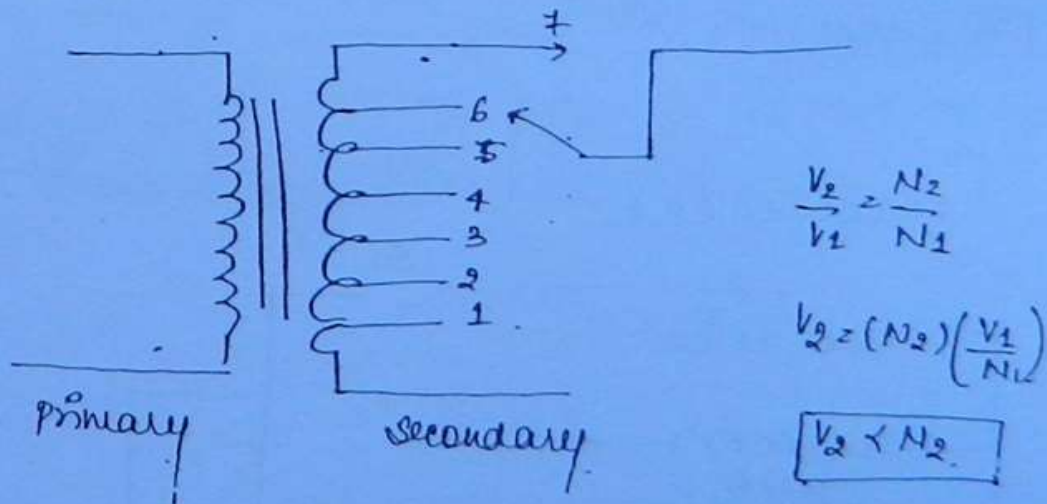

- $S \rightarrow 1$ position | $S \rightarrow 6$ position
 $V \rightarrow \min$ | $V \rightarrow \max$

the voltage is minimum when the switch is

is located at position 1.

- Voltage is max^m. when the switch is located at the position 7.


- By varying the position of the switch the required voltage can be obtained

- Voltage control is achieved by changing turns in secondary.

Limitation:-

- The thickness of the switch must be less so that the switch does not come into contact with two positions at the same time. which otherwise results in short-circuit of windings

2) ON-LOAD TAP CHANGING X^m % -

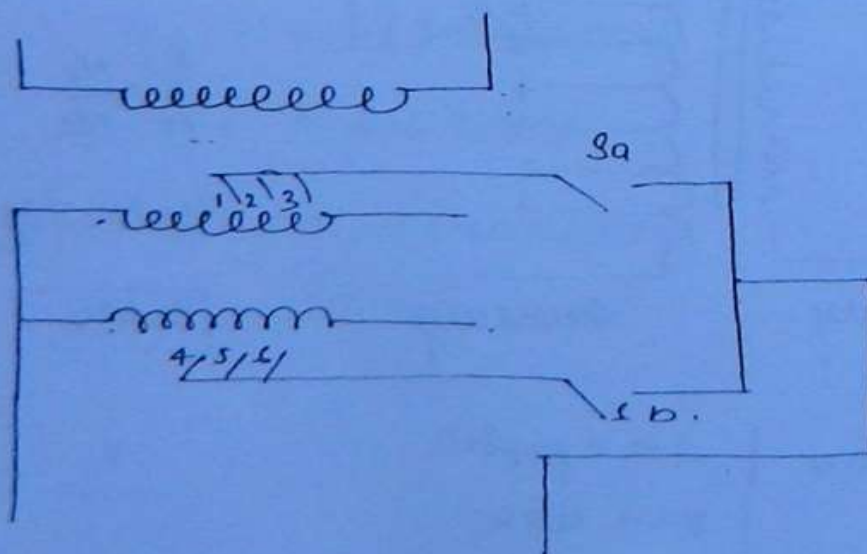

- Using this method required voltage is obtained without disconnecting load from S/W

Steps:

1) 2 secondary winding

2) $S_a \rightarrow \text{closed}$ $S_b \rightarrow \text{closed}$
 $\rightarrow 2$ $\rightarrow 5$

3) $V \uparrow$ $2 \rightarrow 3$ $5 \rightarrow 6$

4) $S_a \rightarrow \text{open}$, $S_b \rightarrow \text{closed}$

$2 \rightarrow 3$

$\downarrow$
carries twice previous current

$S_a \rightarrow \text{closed}$

$S_b \rightarrow \text{open}$

5) $S_a \rightarrow \text{closed}$

$S_b \rightarrow \text{open}$

$\downarrow$
carries twice previous current

6) $S_a \rightarrow \text{closed}$

$S_b \rightarrow \text{closed}$

- To decrease. In this method voltage control is achieved by means of the load current flowing through secondary winding of the S/M.
- The changes in the voltage depends on the changes in the load demand and load current

SUBSTATION

- Substation are located from the generating statⁿ to the consumer premises


Types of Substation:

1) Step-up substation: The step-up substation are located at ~~the~~ generating statⁿ.

- Step up substatⁿ, steps up the generated voltage.

- Power is transmitted at stepped up voltage through

T.L.

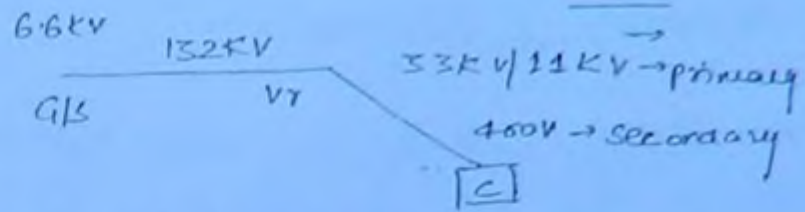

2) Primary substation:-

- Primary substation are located at load centers along primary T.L.
- the primary Transmission voltage is stepped down to a no. of secondary voltages.

3) Secondary substation:-

- A secondary substation the voltage level is further stepped down to sub transmission voltage and primary distribution voltage.

4) Distribution substation:-

- Distribution sub-station supply power to the consumer through distributor and service lines.

5) Industrial Substation:-

- Industrial substation regulate voltage levels of components in an industry.

6) Mining Substation:-

- Mining sub-station are the stand by sub-station which operates when one of the existing substation is subjected to abnormal conditions.

7) Mobile substation:-

- Mobile substation are utilized for the construction of

or an industry is completed.

- In the latest applications the mobile substations are used as the mining substatⁿ.
- The mobile sub-statⁿ is initial sub-statⁿ i.e. useful for completion of industry or generating statⁿ.

HVDC - TRANSMISSION

- North
 - Eastern
 - Central North
 - South
 - North Eastern
- } Grids in India

≠ A/c transmission takes place only when operating at same frequency.

≠ when a/c frequency same, known as synchronous Tx

≠ In India HVDC transmissions are mainly used.

- All the generating statⁿ, load centers and power s/w components in a grid operate at same frequency. Therefore within a grid a/c transmission takes place because the entire grid operates at same frequency.


- Two different grids may not operate at the same

same frequency.

- A/c power transmission b/w the grids operating at different frequencies is not possible.
- Since D/c transmission is independent of frequency power transfer b/w grids operating at different frequencies must be dc in nature.
- HVDC transmission is b/w the two grids operating at different frequencies. HVDC
- HVDC transmission line is located b/w one grid and another grid
- A/c transmission is known as synchronous transmission because A/c transmission takes place when frequency is same.
- HVDC transmission is known as asynchronous transmission, coz d/c transmission takes place for different frequencies.

• HVDC Application:-

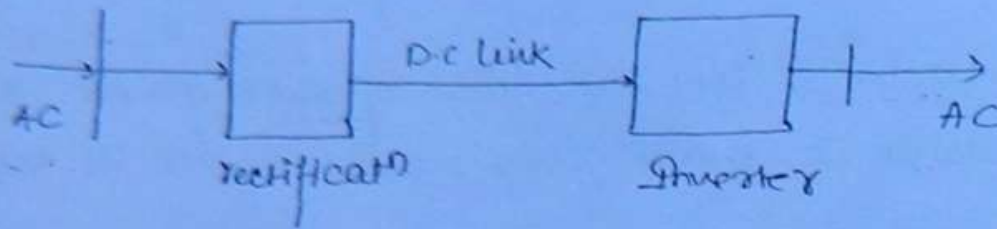
- HVDC transmission deals with transmission of power over long distances.
- Therefore HVDC transmission is distance constrained



- A rectifier is located b/w generating station and transmission line to convert generation which is in ac to dc transmission. Inverter is located b/w transmission line and load center to convert dc transmission to the ac distribution.

TYPES OF DC LINKS:-

1) Monopolar dc link:-

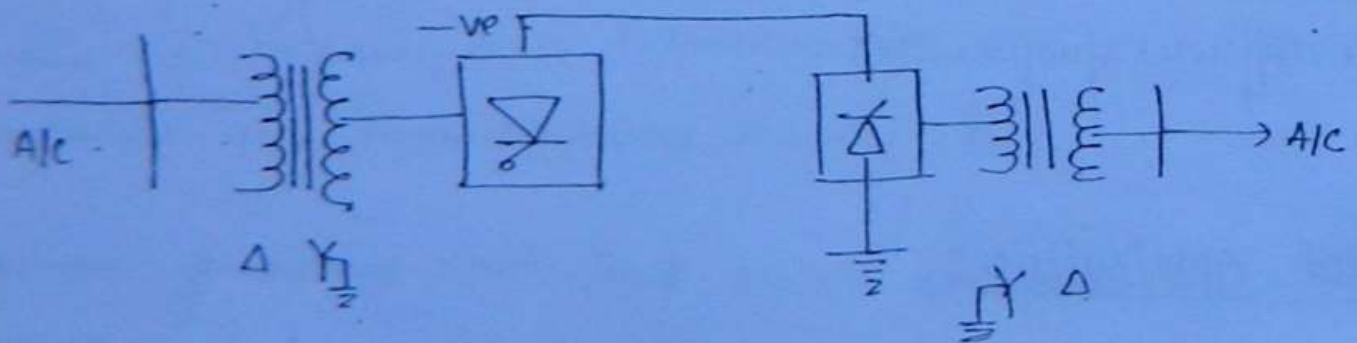


- A monopolar dc link consists of one conductor with w.r.t ground.
- Conductor operates at -ve polarity in order to

decrease corona loss.


- Skin effect does not exist for a dc link.
- Since stringing of solid conductor is difficult, stranded conductors are used.
- No. of strands depends on operating voltage.
- The power transformer on either side of dc link operates at 1:1 transformation ratio.
- The power transformer under normal operating conditions prevents power frequency harmonics to act on terminal equipments.
- The power transmission capacity is less due to the single conductor in the monopolar dc link.
- Therefore in the practical conditions monopolar dc link is not used.

2) Bipolar d/c link :-

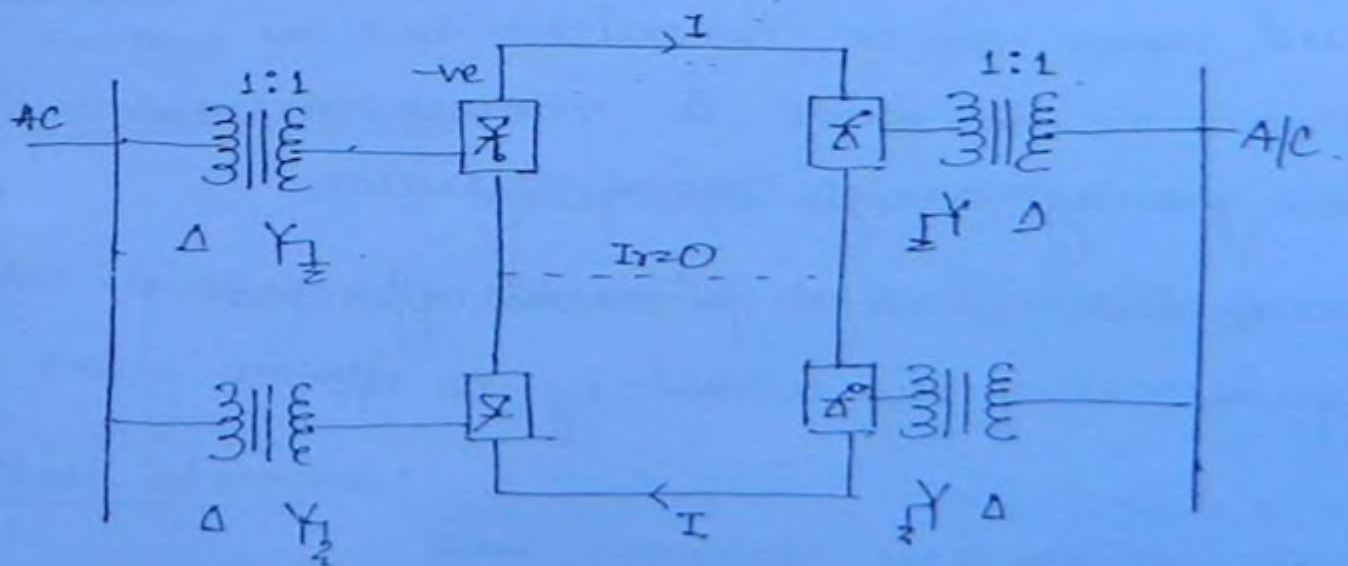

- In bipolar dc link the current carrying capacity is increased by the two conductors in the d/c link
- All practical HVDC d/c links operate with bipolar d/c link

5) Homopolar d/c link

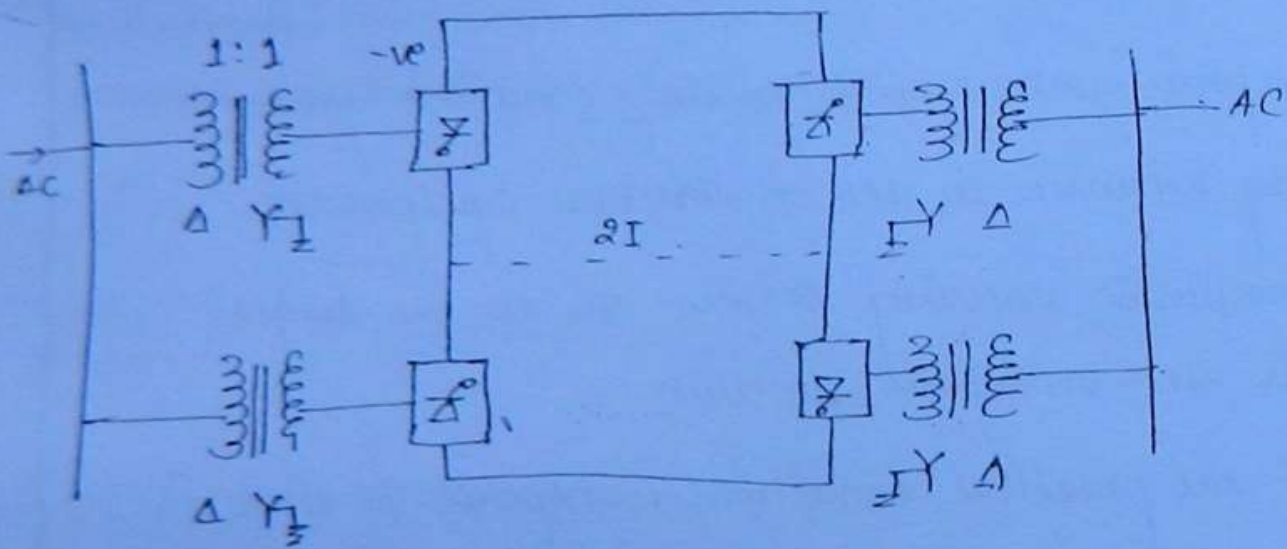

- By changing the position of thyristors of second conductors the required power can be transmitted and the current flowing between the two points is increased to 2 times the current flowing through either of conductors
- Homopolar d/c link is useful for certain applications like requirement of high current by d/c n/c.

Advantages of HVDC Transmission:-

- Power transmitted per conductor is increased.
- The power transferred in a circuit increases.

Disadvantage:-

- To convert a/c to d/c we require rectifier unit and to convert d/c to a/c we require inverter unit.

POWER FACTOR IMPROVEMENT

1) Static Capacitor:-

- Static capacitors are connected in parallel with the equipment operating at lagging power factor.
- Static capacitors improve power factor in industries and factories.

2) Synchronous Condenser:-

Synchronous condenser is a synchronous motor, operating with over excitation on load condition taking the leading current.

3) Phase advancers:-

Phase advancers improve the power factor of induction mtr. the low power factors in

induction motor is due to the stator winding which draws exciting current which lags behind the supply voltage by 90°

Quesⁿ


A synchronous glr is supplying load of 300 kW at p.f. 0.6 lag. If the power factor is increased to unity, the no. of kilowatts the synchronous glr can supply for the same KVA loading is

- a) 300 kW
- b) 200 kW
- c) 500 kW
- d) 700 kW

Solⁿ

$$KW = 300 \quad \cos \phi = 0.6$$

when pf $\rightarrow$ 0.6 lag

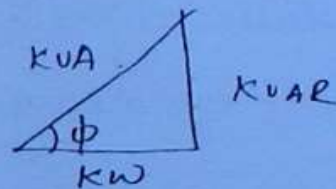

$$\cos \phi = \frac{KW}{KVA}$$

$$\frac{KW}{\cos \phi}$$

$$= \frac{300}{0.6}, 500 KVA$$

when pf $= 1$

$$KW = KVA \times \cos \phi$$

$$= 500 KW$$

When the pf is increased from 0.6 to 1 the synchronous glr has to supply 200 kW in excess.

Quesⁿ :

The following readings are obtained in a month of 30 days at a consumer location

KVAR meter - 83830

Kwh meter - 291940

Demand meter - 1400 KW.


The average monthly load factor and power factor at the consumer premises is.

Solutⁿ

$$\text{Average load factor} = \frac{\text{Energy generated in a month}}{(30 \times 24) \times \text{Max}^{\text{m}} \text{ demand (KW)}}$$

$$\Rightarrow \frac{291940}{30 \times 24 \times 1400} \times 100$$
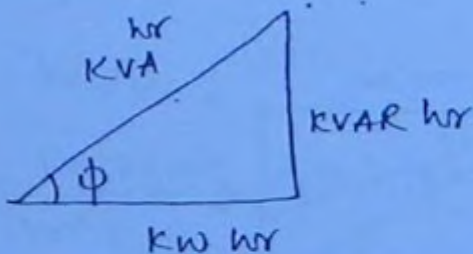
$$\Rightarrow 0.289 \times 100$$
$$28.9\%$$



$$\cos \phi = \cos \left[\tan^{-1} \left(\frac{83830}{291940} \right) \right]$$

$$\cos \phi = 0.961$$

Quesⁿ

A 3- ϕ , 50Hz, 30KV. T.L supplies a load of 5MW at a power factor 0.707 lag. to the receiving end. where the voltage is maintained constant at 1KV. the line resistance and inductance are 0.02 Ω and 0.84 mH/phase/km

a capacitor is connected across the load to rise the

p.f. 0.8 lag. calculate

1) capacitance / phase

2) voltage regulation

3)

Given length of the line $l = 30 \text{ km}$.

Load = 5 MW at 0.707 lag

$V_R = 11 \text{ kV}$

resistance of 30 km length: 0.02×30


$\Rightarrow 0.6 \Omega / \text{phase}$

Reactance of $3 \text{ km} = 1.2 \times 3.14 \times 50 \times 30 \times 0.84 \times 10^{-3}$

$= 4.9 \Omega / \text{phase}$

Impedance of line $Z = (0.6 + j4.9) \Omega / \text{phase}$.

$\cos \phi_2 = 0.8$

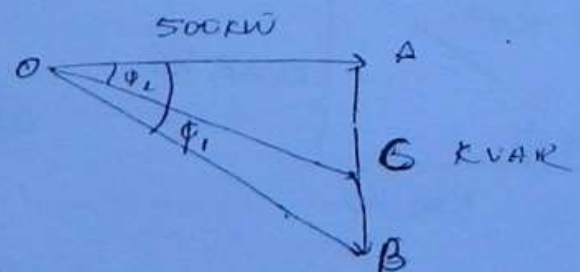

capacitive reactive power

$$BC = AB - AC$$

AB

$$\tan \phi_1 = \frac{AB}{OA}$$

$$AB = OA \tan \phi_1$$

$$AB = OA \cdot \tan \phi_1$$

$$= 5000 (\tan \{ \cos^{-1}(0.707) \})$$

$$5000 (\tan 45^\circ)$$

$$= 5000 \text{ KVAR} = AB.$$

$$\underline{AC}: \quad \tan \phi_2 = \frac{AC}{OA}$$

$$AC = OA \tan \phi_2$$

$$= 5000 \tan \{ \cos^{-1}(0.8) \}$$

$$= 3749.5 \text{ KVAR}$$

$$\therefore BC = AB - AC$$

$$= 1250 \text{ KVAR}$$

capacitive reactive power. $V_R \cdot I_C = 1250$

$$\sqrt{3} V_R I_C = 1250$$

$$\frac{\sqrt{3} V_R \cdot V_R}{\sqrt{3} X_C} = 1250$$

$$V_R^2 / X_C = 1250$$

$$\frac{1250 \times 10^3}{V_R^2 \times \omega} = 1250$$

$$\frac{1250 \times 1000}{(1100)^2 \times 2 \times \pi \times 50} = 3.289 \times 10^{-3} \text{ F.}$$

$$V_L = V_R + I_R \omega L \sin \phi_R + I X \sin \phi_Y$$

$$\Rightarrow \quad 500 \times 10^{-6} = \sqrt{3} \times 11 \times 10^{-3} \times I_L \times 0.8.$$

$$I_L = 32.80 \text{ A.}$$

$$V_s = 1 \times 10^3 + 32.80 \times 0.6 \times 10^3 \times 0.8$$

$$V_s = \frac{11000}{\sqrt{3}} + (57119.0)(0.6) \times 0.8 + (37119.0)(7.9) \times 0.6$$

$$= 200.1 \text{ kV}$$

$$\frac{V_s - V_r}{V_r} \times 100 = \frac{200.1 - 1000}{1000} \times 100$$


Quesⁿ An industry draws 100kW at 0.7 Pf lagging from a 3φ, 11kV supply. It is desired to increase the pf to 0.95 lag using series capacitor. The value of req. capacitor

a) 90 kVAR

b) 69 "

c) 50 "

d) 79 "

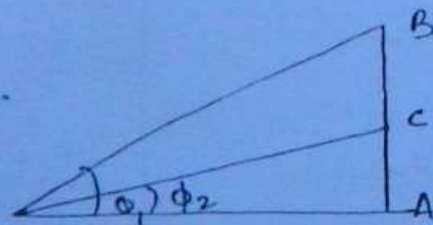

Sol

$$BC = AB - AC$$

$$AB =$$

$$\tan \phi = \frac{AB}{OA}$$

$$AB = OA \tan \phi_1$$

2)

$$BC = AB - AC = OA (\tan \phi_1 - \tan \phi_2)$$

$$= 100 \times 10^3 [\tan$$

=

$$69 \text{ kVAR}$$

$$\omega_1 \propto a_1 l$$

$$\omega_2 \propto a_2 l$$

$\therefore$ length is same.

$$\frac{\omega_2}{\omega_1} = \frac{a_2}{a_1} = \frac{1}{n} \cdot \omega_1$$

$$\boxed{\omega_2 = \frac{1}{n} \omega_1}$$

Gate

The operating voltage of a s/m is increased by 50%. The cost of the s/m increases by.

$$\text{earlier} = V_1$$

$$\text{new} = 1.5 = V_2$$

$$V_2 = 1.5 V_1$$

$$\omega_2 = \frac{1}{1.5} \omega_1$$

$$\boxed{\text{cost}_2 = \frac{1}{n} \text{cost}_1}$$

$$\frac{\text{cost}_2}{\text{cost}_1} = \frac{1}{n} = \frac{1}{1.5} = \frac{\omega}{15} = \frac{2}{3}$$

$$\Rightarrow 66.67\%$$

$\rightarrow$ cost₂ is increased by 66.67% of cost₁

5) BHEL-01

A current carrying elect. c equal current density has its current carrying capacity decreased by n times. the new power loss in feeder is

Sol.

$$I_2 = \frac{1}{n} I_1$$

$$P_2 = I_1^2 R_1$$

$$\text{at } I_2 = P_2 = I_2^2 R_2$$

$$\Rightarrow \frac{I_1^2 R_1}{n^2}$$

$$\boxed{P_2 = \frac{1}{n} P_1}$$

$$I_1 \propto \frac{1}{R_1}$$

$$I_2 \propto \frac{1}{R_2}$$

$$\Rightarrow \frac{I_1}{I_2} = \frac{R_2}{R_1}$$

$$R_2 = n R_1$$

the power losses in T.L are decreased by n times
[$P_2 = \frac{1}{n} P_1$] the efficiency of the s/w. increases by

$$\text{percentage } \eta = \frac{P}{P + P_{\text{loss}}} \times 100 = \frac{P}{P + I^2 R} \times 100$$

$$\therefore \frac{P}{P + I^2 \frac{R_1}{n}}$$

$$R_2 = R_1 / n$$

and current density $j = I/a \Rightarrow a = I/j$

$$= \frac{P}{P + I^2 \frac{R_1}{I/j}} \times 100$$

(Kamran)

LOAD FLOW STUDIES

- Network Modelling
- Mathematical Modelling
- Solution stage.


- Study means obtaining parametric values of s/c parameter.
- S/c parameter describe the condition of s/m.
- System parameters are of two type.
 - independent
 - dependent.
- Studies are carried under two stage of s/m
 - steady state
 - dynamic / transient
- In steady state of system, system parameters are described as time invariant funcⁿ and dynamic state of system they are represented as time variant function.
- In any study we have to pass through three stage.
 - Network Modelling
 - Mathematical Modelling
 - Solution stage.
- Network Modelling: Here various component of power system is represented by its electrical equivalent circuit component model. There by as overall

obtained.

• Mathematical Modelling: Here with the knowledge of n/w analysis the network model is converted into mathematical model. A mathematical model comprises of set of ~~exactly~~ algebraic or set of differential eqn depending upon type of study we carry.


• Solution stage: In this stage by using appropriate numerical techniques the mathematical equations are solved and system parameters are obtained. With the knowledge of system parameters we are able to analyse the s/n. This complete study.

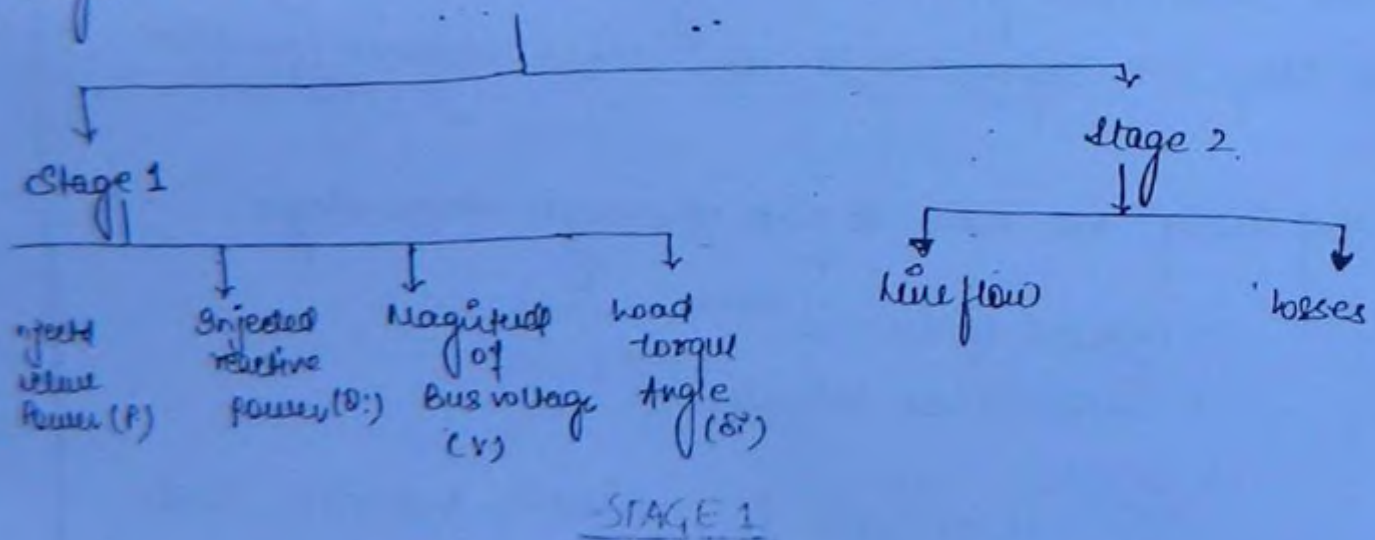• When a load flow study is performed it is connected in two stages.



$$S_{Gi} = P_{Gi} + jQ_{Gi} = \text{Complex power generated at } i^{\text{th}} \text{ bus}$$
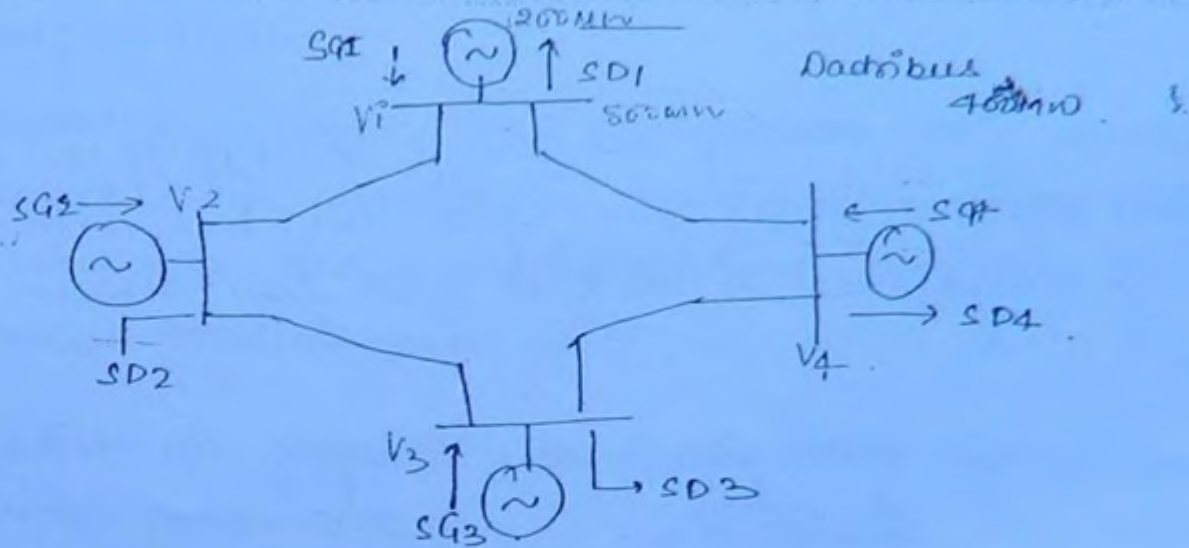
$$S_{Di} = P_{Di} + jQ_{Di} = \text{Complex power demand at } i^{\text{th}} \text{ bus}$$



- $S_i = S_{Gi} - S_{Di}$ = Complex power injected to i^{th} bus.

$$S_i = P_{Gi} + jQ_{Gi} - P_{Di} - jQ_{Di} = \underbrace{P_{Gi}}_{\text{active}} + j \underbrace{Q_{Gi}}_{\text{Reactive}}$$

- If $S_{Gi} > S_{Di} \rightarrow S_i > 0 \rightarrow$ Bus acts like exporting bus
- If $S_{Gi} < S_{Di} \rightarrow S_i < 0 \rightarrow$ Bus acts like importing bus

- Magnitude of bus voltage is measured by voltmeter.

- Load torque angle $\delta_i = \angle V_i - \angle V_{ref}$

Ex • $\delta_1 = \angle V_1 - \angle V_{ref} \rightarrow 0$ always true

$$\delta_2 = \angle V_2 - \angle V_1$$

$$\delta_3 = \angle V_3 - \angle V_1$$

$$\delta_4 = \angle V_4 - \angle V_1$$

- Based on value of injected power a bus may act like an exporting bus [$S_i > 0$] or importing bus [$S_i < 0$].
The power will flow from exporting bus to importer.

buses


- Active power flows leading bus voltage to lagging bus voltage. And reactive power flows from the bus with high voltage magnitude to the bus with low voltage magnitude.
- With same voltage, active power still transfers due to leading.

~~STAGE 2~~

Application:


- It data is used for planning of power system.
 - can be estimated to voltage profile.
 - Economic scheduling.
 - Steady state data.
- Load flow analysis is mainly used for planning power sys.

1. NETWORK MODELING

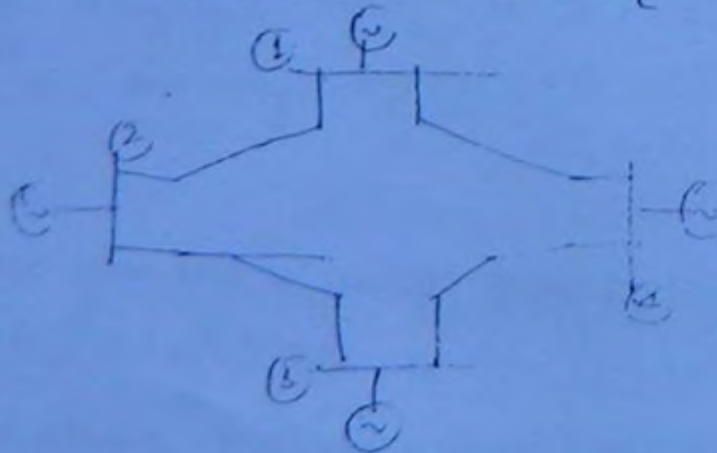

• In load flow studies

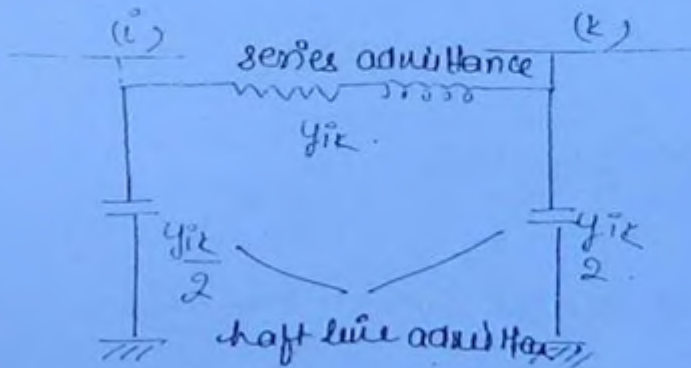- 1) Generators are represented as complex power sources, this means it is represented by complex no. where real no. indicates active power P & imaginary no. represent reactive power Q .
- 2) Similar to generator load are represented as complex power demand.
- 3) Transmission line are represented as π n/w. with series admittance & half line charging admittances.



• Data given

R_{ik}

X_{ik}


$\frac{Y_{ik1}}{2}$

$$Y_{ik} = \frac{R_{ik}}{R_{ik}^2 + X_{ik}^2} - j \frac{X_{ik}}{R_{ik}^2 + X_{ik}^2}$$


* T network is better than π n/w as, no. of buses of T n/w is less than π and T gives more good performance. Still in load flow we use π n/w coz of mathematical simplification.

$$Z = R + jX \quad \begin{array}{l} \text{inductive} \\ \text{capacitive} \end{array}$$
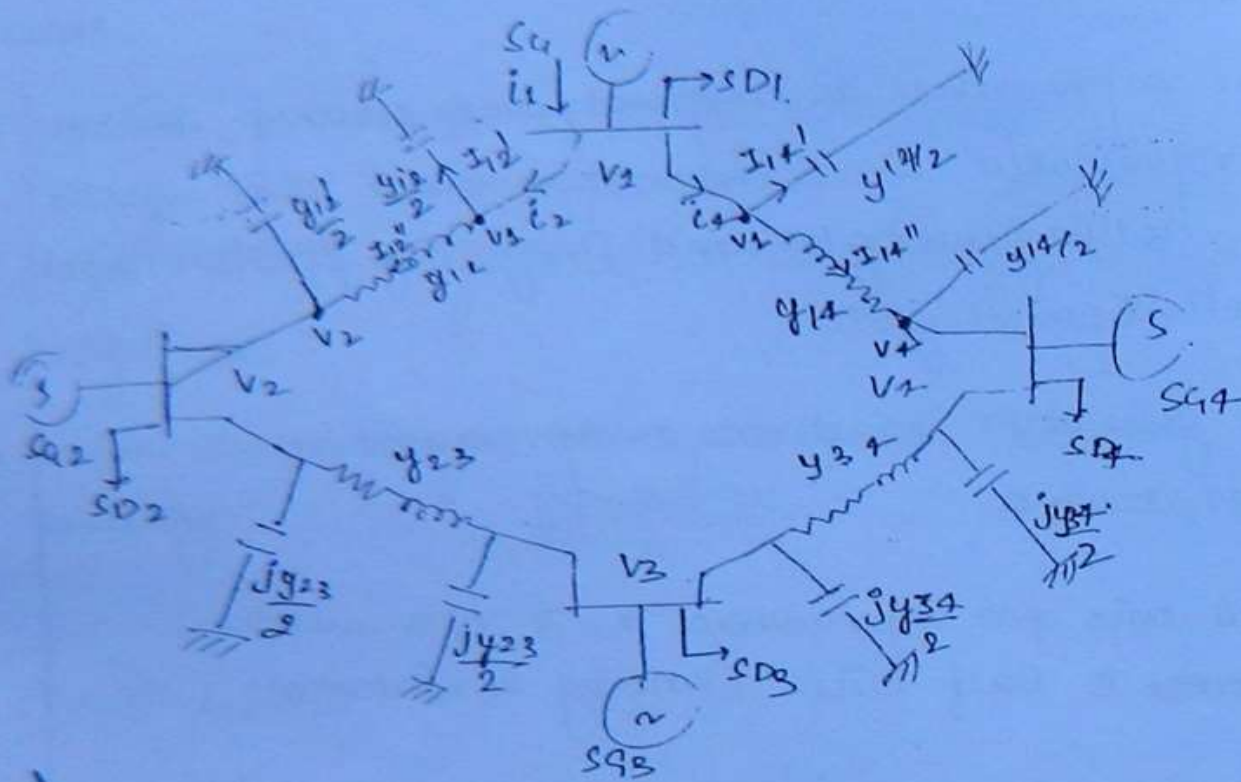
$$Y = G + jB \quad \begin{array}{l} \text{C} \\ \text{L} \end{array}$$




2) MATHEMATICAL MODELLING

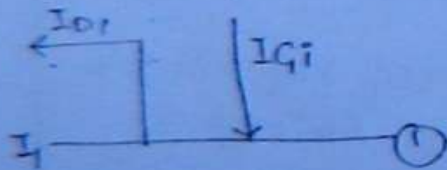

Injected current into 1st bus = I_1

$$I_1 = I_{12} + I_{14}$$
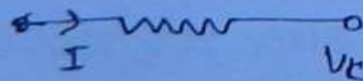
$$= (I_{12}' + I_{12}'') + (I_{14}' + I_{14}'')$$



$$I = (V_i - V_j) y$$

$$I_1 = \frac{V_1 y_{12}'}{2} + (V_1 - V_2) y_{12} + \frac{V_1 y_{14}'}{2} + (V_1 - V_4) y_{14}$$

$$= V_1 \left(\frac{y_{12}'}{2} + y_{12} + \frac{y_{14}'}{2} + y_{14} \right) + (-y_{12}) V_2 + (0) V_3 + (-y_{14}) V_4$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 + Y_{13} V_3 + Y_{14} V_4$$

and Y_{11} is total admittance connected to 1st bus.

$$Y_{11} = \frac{Y_{12}'}{2} + \frac{Y_{14}'}{2} + Y_{12} + Y_{14}$$

we see the directly connected admittances.

• Y_{12} = Negative value of series admittance connected b/w bus ① & ②

$$Y_{12} = -Y_{12}$$

• Similarly

$$Y_{13} = -Y_{13} = 0$$

$$Y_{14} = -Y_{14}$$

Now

$$I_2 = Y_{21}V_1 + Y_{22}V_2 + Y_{23}V_3 + Y_{24}V_4$$

$$Y_{21} = -Y_{12}$$

$$Y_{22} = \frac{Y_{12}'}{2} + \frac{Y_{23}'}{2} + \frac{Y_{24}'}{2} + Y_{12} + Y_{23} + Y_{24}$$

$$Y_{23} = -Y_{23}; Y_{24} = -Y_{24}$$

* Off diagonal terms gives information about the no of T.L.

similarly eqⁿ of I_3 and I_4 .

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} & Y_{14} \\ Y_{21} & Y_{22} & Y_{23} & Y_{24} \\ Y_{31} & Y_{32} & Y_{33} & Y_{34} \\ Y_{41} & Y_{42} & Y_{43} & Y_{44} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} I_{bus} \end{bmatrix}_{n \times 1} = \begin{bmatrix} Y_{bus} \end{bmatrix}_{n \times n} \begin{bmatrix} V_{bus} \end{bmatrix}_{n \times 1} \dots \dots \dots (1)$$

equation for injected current into i th bus of n -bus power s/n

$$I_i = Y_{i1}V_1 + Y_{i2}V_2 - \dots - Y_{in}V_n$$

$$\boxed{I_i = \sum_{k=1}^n Y_{ik}V_k} \quad \text{for } i, 2, \dots, n. \dots (2)$$

$$\underline{Y_{BUS}}$$


Y_{bus} can be developed by direct inspection method.

Load flow analysis can also using Z_{bus} .

Y_{bus} is preferred, coz it is sparsity matrix


sparsity matrix:- when elements ^{of matrix} are often zero is known as sparsity matrix. a null matrix has 100% sparsity.

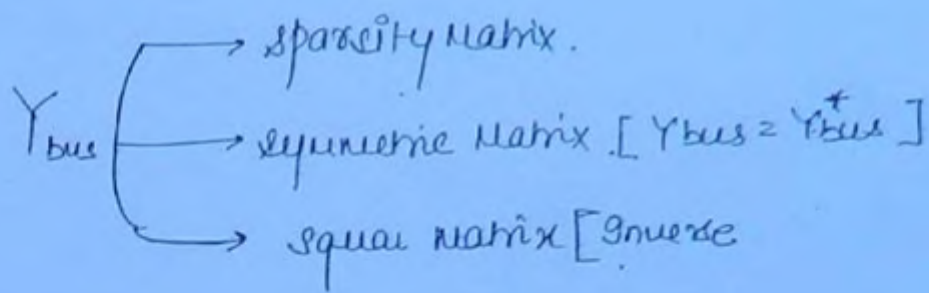As Y_{bus} is sparsity matrix the no. of elements are zero thus the memory required for storage decreases greatly






- In power system every bus is connected to 2-3 bus, in view of this Y_{bus} is dominated by zero, and hence said to sparsity matrix.
- As Y_{bus} is sparsity matrix its inverse Z_{bus} is full matrix.
- A matrix with less no of zero provide more information of the network therefore Z_{bus} is used in short-circuit studies.
- Y_{bus} can be obtained by two methods.
 - 1) Direct inspection Method.
 - 2) Singular Transformation Method.
- When the mutual inductance is present b/w the two line direct inspection method cannot be used to go for singular transformation method using A matrix.

Question: form Z and Y_{bus} ?

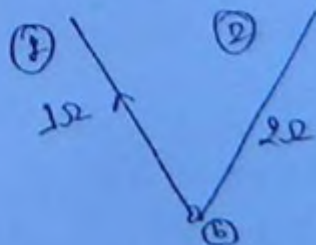

Solutⁿ: Z_{bus}

Step 1:

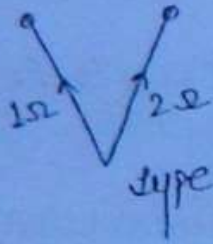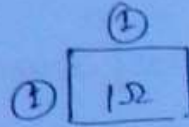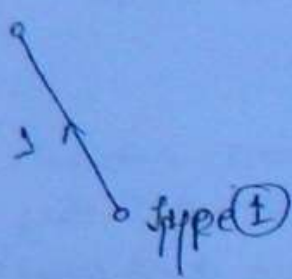

	①	②
①	1Ω	0
②	0	2Ω


Method 1: Y_{bus} through Z_{bus}^{-1}

$$Y_{bus} = \begin{bmatrix} 1 & 0 \\ 0 & 2 \end{bmatrix}^{-1}$$

$$= \frac{1}{2} \begin{bmatrix} 2 & 0 \\ 0 & 1 \end{bmatrix} \dots$$

$$Y_{bus} = \begin{bmatrix} 1 & 0 \\ 0 & 0.5 \end{bmatrix}$$

Method 2: Direct inspection Method.

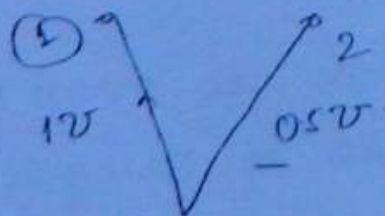

$$Y_{11} = 1 \text{ pu}$$


$$Y_{12} = 0$$

$$Y_{21} = 0$$

$$Y_{22} = 0.5 \text{ pu}$$

$$Y_{bus} = \begin{bmatrix} 1 & 0 \\ 0 & 0.5 \end{bmatrix}$$

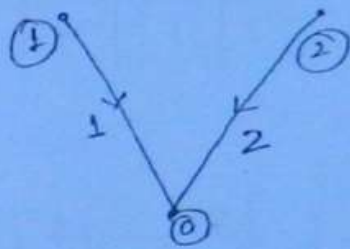Method 5^o - Single Transformation Method.



	①	②
1	1	0
2	0	2

$$A^T = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

primitive impedance MATRIX


$$Z = \begin{array}{c|cc} & 1 & 2 \\ \hline 1 & 1 & 0 \\ 2 & 0 & 2 \end{array}$$

$$Y = Z^{-1} = \begin{bmatrix} 1 & 0 \\ 0 & 0.5 \end{bmatrix}$$

$$Y_{bus} = [A^T][Y][A]$$

$$= \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & 0.5 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$
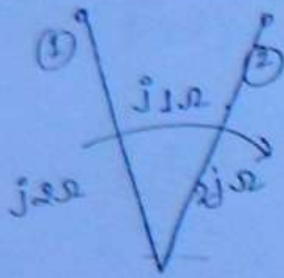
$$= \begin{bmatrix} 1 & 0 \\ 0 & 0.5 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 0.5 \end{bmatrix}$$



primitive impedance matrix

z_2

	1	2
1	$j2$	$j1$
2	$j1$	$j2$

primitive admittance matrix

-4x4

$$y = z^{-1} = \frac{1}{-3} \begin{bmatrix} j2 & -j1 \\ -j1 & j2 \end{bmatrix}$$

$$y_2 = \begin{bmatrix} -0.66j & -j1/-3 \\ -1/3j & -j0.667 \end{bmatrix}$$

$$y_2 = \begin{bmatrix} -j0.667 & +j0.33 \\ +j0.33 & -j0.667 \end{bmatrix}$$

$[A]_2$



$$\begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$


incidence matrix.

$$[A']_2 = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

$$Y_2 = [A']^T [y] [A] = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} -j0.667 & +j0.33 \\ +j0.33 & -j0.667 \end{bmatrix}$$

$$Y_{bus} = \begin{bmatrix} -j0.667 & +j0.33 \\ +j0.33 & -j0.667 \end{bmatrix}$$

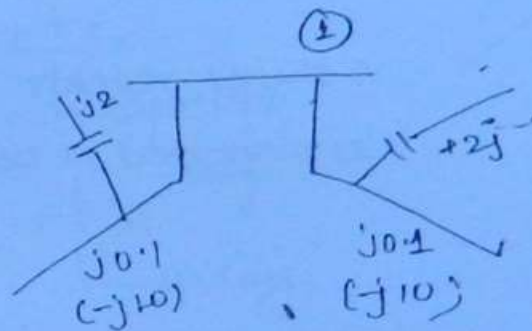Quesⁿ. In a pure imaginary Y_{bus} matrix which element of Y_{bus} are +ve imaginary and -ve imaginary



$$Y_{11} = +j2 + j2 - j10, j10 \\ = -j16$$

$$Y_{12} = -(-j10) = +j10$$

$$Y_{21} = -(-j10) = +j10$$

Ans + off diagonal $\rightarrow$ +ve


Diagonal = -ve.

The condition for convergence of load flow problem is all the diagonal element of Y_{bus} must dominate the off diagonal element.

In aft above example mag Y_{11} is 16

and mag of Y_{12} is 10. As $\text{mag } Y_{11} > \text{mag } Y_{12}$
problem converges.

(20)

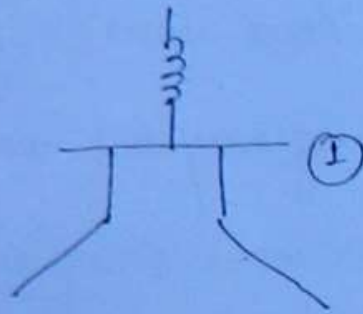

A shunt reactor $9-j10$
is connected to bus (1)

$$Y_{11} = -j16 - j10$$

$$= -j26$$

$$Y_{12} = +j10$$


$$Y_{14} = +j10$$

$$Y_{11} = -j16 + j10$$

$$= -j6$$

$$Y_{12} = +j10$$

$$Y_{14} = +j10$$

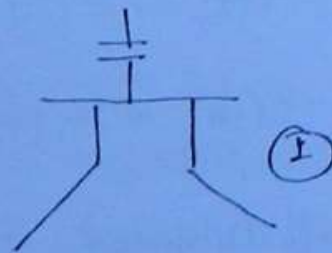

A load flow problem may converge or diverge can
be initially estimated by absorbing Y_{bus} . The
condition for convergence: all the diagonal
- element of Y_{bus} must dominate off-diagonal elements
otherwise diverges.

Shunt reactor in power sys improves the convergence condition where as shunt capacitor in power sys improves divergence of load flow problem.


Dated
29th Oct 2020

• $Z = R \pm jX$
 $\begin{matrix} \nearrow & \text{inductor} \\ \searrow & \text{capacitor} \end{matrix}$

• $S = P \pm jQ$
 $\begin{matrix} \nearrow & \text{lag} \\ \searrow & \text{leading} \end{matrix}$

$V \rightarrow$ is taken as reference vector.
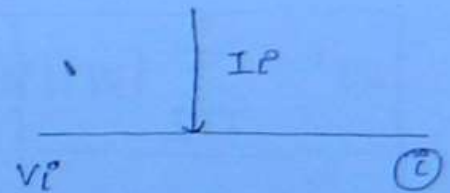
$$I_i = \sum_{k=1}^n Y_{ik} V_k \quad \text{--- (1)}$$



Pf is lagging $V = |V| \angle 0^\circ$
 $I = |I| \angle -\theta$

$$S_i = P_i + jQ_i$$

$$= V I_i^* *$$

• $S = VI^* = |V||I| \angle \theta$
 $= |V||I| \cos \theta + j |V||I| \sin \theta$
 $= P + jQ$

$$S = V_i \left[\sum_{k=1}^n Y_{ik} V_k \right]^*$$

• So we calculate $S_i^* = V_i^* I_i^* = P_i + jQ_i$

$$\boxed{\begin{matrix} P_i = \text{Real} \{ S_i^* \} \\ Q_i = -\text{Imag} \{ S_i^* \} \end{matrix}}$$

Let

$$V_i = |V_i| \angle \delta_i$$

$$V_i^* = |V_i| \angle -\delta_i$$

$$Y_{ik} = G_{ik} - jB_{ik}$$

$$= \sqrt{G_{ik}^2 + B_{ik}^2} \left[\tan^{-1} \left(\frac{-B_{ik}}{G_{ik}} \right) \right]$$

$$= |Y_{ik}| \angle -\gamma_{ik}$$

$$V_k = |V_k| \angle \delta_k$$

and

$$S_i^* = P_i + jQ_i$$

$$= |V_i| \angle -\delta_i \sum_{k=1}^n |Y_{ik}| \angle -\gamma_{ik} \cdot |V_k| \angle \delta_k$$

$$S_i^* = \sum_{k=1}^n |V_i| |V_k| |Y_{ik}| \angle -(\delta_i - \delta_k + \gamma_{ik})$$

and

$$P_i = \text{Re} \{ S_i^* \} = \sum_{k=1}^n |V_i| |V_k| |Y_{ik}| \cos(\delta_i - \delta_k + \gamma_{ik}) \quad \text{--- (A)}$$

$$Q_i = -\text{Imaginary} \{ S_i^* \}$$

$$Q_i = \sum_{k=1}^n |V_i| |V_k| |Y_{ik}| \sin(\delta_i - \delta_k - \gamma_{ik}) \quad \text{--- (B)}$$

Eqn (A) and (B) are known as static load flow equation.

• the load flow equations are non linear simultaneous algebraic equation.

• BUS VOLTAGE EQUATION :-

$$S_i^* = V_i^* I_i^* = P_i - jQ_i$$

$$I_i^* = \frac{P_i - jQ_i}{V_i^*}$$

$$\sum_{k=1}^n Y_{ik} V_k = \frac{P_i - jQ_i}{V_i^*}$$

$$Y_{ii} V_i + \sum_{k=1, k \neq i}^n Y_{ik} V_k = \frac{P_i - jQ_i}{V_i^*}$$

$$V_i = \frac{1}{Y_{ii}} \left[\frac{P_i - jQ_i}{V_i^*} - \sum_{k=1, k \neq i}^n Y_{ik} V_k \right]$$

for $i = 1, 2, \dots, n$

3. SOLUTION OF STAGE :-

1) GAUSS & SEIDEL METHOD

Let take

$$y_1 = f_1(x_1, x_2) = x_1^2 - \log x_1 x_2 + x_2^2 = 2$$

$$y_2 = f_2(x_1, x_2) = -2x_1^2 + \log x_1 x_2 + x_2^2 = 5$$

$$x_1 = \sqrt{2 + \log x_1 x_2 - x_2^2} \quad \dots \quad (1)$$

$$x_2 = \sqrt{5 + 2x_1^2 - \log x_1 x_2} \\ = f_4(x_1, x_2)$$

→ start with Guess of Guess.

$$x_1^0 = x_2^0 = 4$$

• first Iteration

$$x_1^{(1)} = f_3(x_1^0, x_2^0)$$

$$= \sqrt{2 + \log x_1^0 x_2^0 - (x_2^0)^2}$$

$$x_2^{(1)} = f_4(x_1^{(1)}, x_2^0)$$

$$= \sqrt{5 + 2(x_1^{(1)})^2 - \log x_1^{(1)} x_2^{(1)}}$$

Guess

→ check for convergence:-

$$\cdot |x_1^{(1)} - x_1^{(0)}| \leq \text{Error}$$

$$\cdot |x_2^{(1)} - x_2^{(0)}| \leq \text{Error}$$

NOTE:-

- Gauss method is not appropriate coz takes a very long process.


• Classification of Buses:-

→ load flow study has to be performed under online
CPU execution time is very important in this
aspect. In order to reduce the total no. of iterations

Out of four bus quantities of each bus, two bus quantities are specified.


- Depending upon which two bus quantities out of four bus quantities are specified, buses are classified into different type.

Classification of Buses

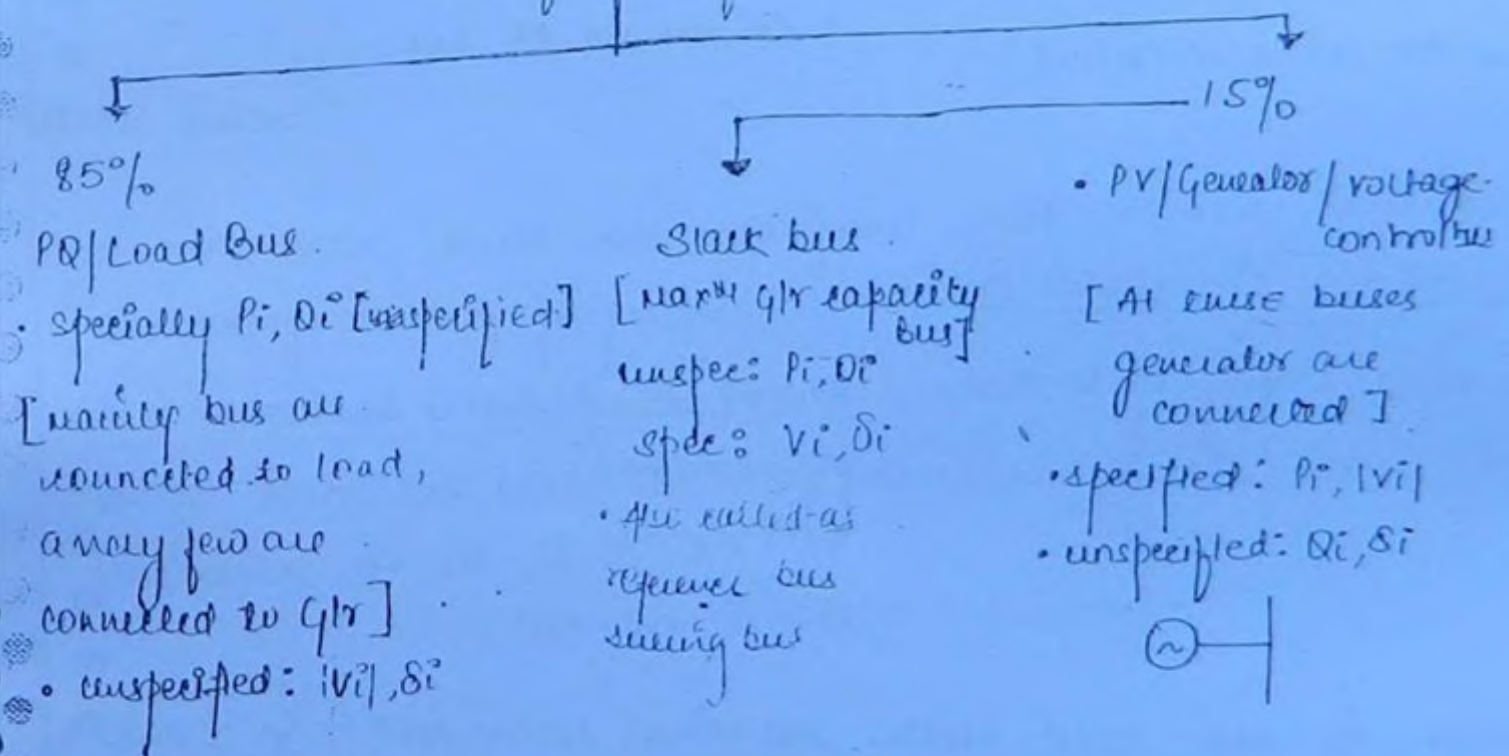


Every PV bus can be generator or voltage controlled buses but it cannot be that every generator or voltage controlled buses is a PV bus.

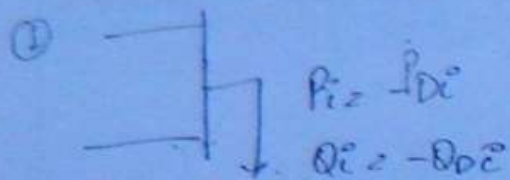
Slack bus is called as the reference bus.




• cannot be taken as PQ bus

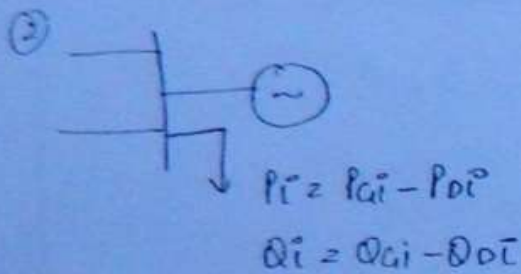

• can be taken as PQ bus

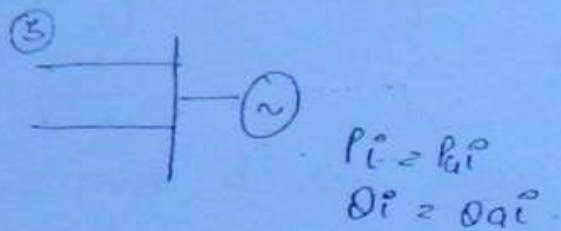


• can be taken as PQ bus

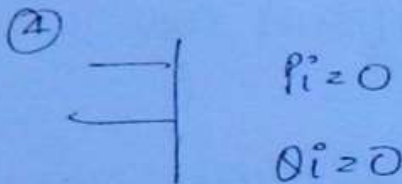

• cannot be PQ bus

• Pure VOLTAGE CONTROLLED Bus:-

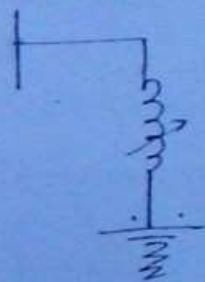

$P_i = 0$ (active power is known)

$V_i \rightarrow \text{constant}$

$Q_i = V^2/X$

$\therefore \delta \rightarrow \text{is unknown}$

• similar is the case with capacitor connected



WES

In order to conduct load flow study under online condition CPU execution time should be less.

By reducing the total no of unknown we can reduce the iteration, convergence need to be

PQ Buses :-

- If the values of P and Q are known the bus can be selected as PQ bus. By default all load buses are PQ bus.
- Buses connected with generators can be selected as PQ bus since the values of P and Q are known. Voltage controlled buses can be selected as PQ bus.


PV Buses :-

- A PV Bus must be equipped with either generator or voltage control equipment. At these buses $P_i = 0$, V is constant and Q can be estimated. Therefore a pure voltage controlled bus the only parameter which is unknown to us is ' δ '.





SLACK Bus :-

- A Generator bus with max^{im} generating capacity is chosen as ~~lag~~^{slack} bus. As the generator is connected to the bus voltage can be specified and this bus voltage is taken as reference vector. Load angle for this bus is zero. Without slack bus load flow problem never converges.





• Slack Bus

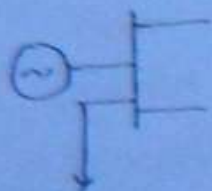

• PV Bus

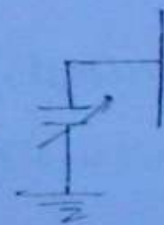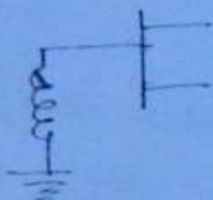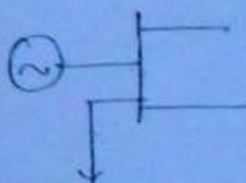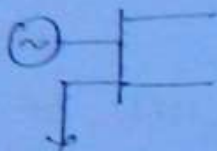


• PD bus

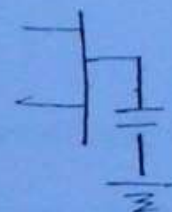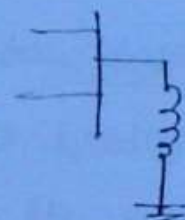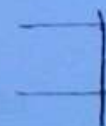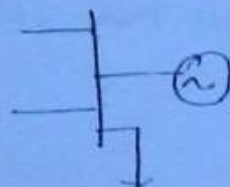

ALGORITHM

Case 1: PV buses are absent

Stage 1: to find bus quantities

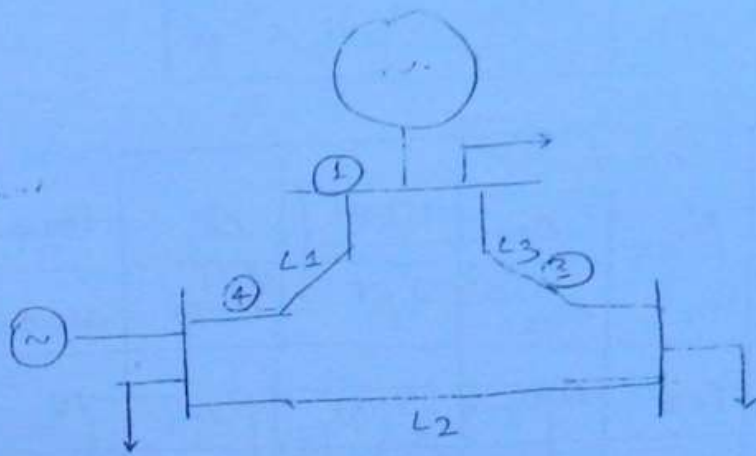

• line data.

line no	from bus (i) to Bus (k)	R_{ik}	X_{ik}	$\frac{y_{ik}'}{2}$
L_1	1-2	R_{12}	X_{12}	$y_{12}'/2$
L_2	2-3	R_{23}	X_{23}	$y_{23}'/2$
L_3	3-1	R_{31}	X_{31}	$y_{31}'/2$

Series Impedance $Z_{ik} = R_{ik} + jX_{ik}$

Series admittance $Y_{ik} = \frac{R_{ik}}{R_{ik}^2 + X_{ik}^2} - j \frac{X_{ik}}{R_{ik}^2 + X_{ik}^2}$

• from Y_{bus} by using Direct inspection Method.

$$Y_{bus} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} \\ Y_{21} & Y_{22} & Y_{23} \\ Y_{31} & Y_{32} & Y_{33} \end{bmatrix}_{3 \times 3}$$

$$Y_{11} = \frac{y_{11}'}{2} + y_{12}' + y_{13}'$$

$$Y_{12} = -Y_{12}'$$

• Bus Data:

Bus no. (i)	Generator		Load		V_i	δ_i	Remark
	P_{Gi}	Q_{Gi}	P_{Di}	Q_{Di}			
1	?	?	P_{D1}	Q_{D1}	V_1	$\delta = 0$	slack.
2	P_{G2}	Q_{G2}	P_{D2}	Q_{D2}	$V_2 = ?$	$\delta_2 = ?$	PQ
3	P_{G3}	Q_{G3}	P_{D3}	Q_{D3}	$V_3 = ?$	$\delta_3 = ?$	PQ

$$P_{G1} = P_1 + P_{D1}$$

$$Q_{G1} = Q_1 + Q_{D1}$$

Bus Synchronism:

Given: $V_1, \delta_1, P_2, Q_2, P_3, Q_3$.

or Given: P.Q, $V_2, \delta_2, V_3, \delta_3$.

$$P_i = \sum_{k=1}^n V_i V_k Y_{ik} \cos(\delta_i - \delta_k + \gamma_{ik})$$

$$V \angle \delta_i = \frac{1}{Y_{ii}} \left[\frac{P_i - jQ_i}{V_i^*} - \sum_{k=1, k \neq i}^n Y_{ik} V_k \right]$$

$$Q_i = \sum_{k=1}^n V_i V_k Y_{ik} \sin(\delta_i - \delta_k + \gamma_{ik})$$

• FLAT START:-

$$V_2^0 = V_3^0 = 1 \text{ p.u.}$$

$$\delta_2^0 = \delta_3^0 = 0 \text{ radians}$$

$$V_3^{(1)} = \frac{1}{Y_{12}} \left[\frac{P_2 - jQ_2}{1 \angle V_1^0 \angle -\delta_1^0} - Y_{21} V_1 - Y_{23} V_3 \right]$$

$$V_3^{(1)} = |V_2^{(1)}| / \delta_2^{(1)}$$

$$V_3' = \frac{1}{Y_{33}} \left[\frac{P_3 - jQ_3}{V_3^{(0)} \angle -\delta_3^0} - Y_{31} V_1 - Y_{32} V_2^{(1)} \right]$$

$$V_3' = |V_3^{(1)}| / \delta_3^{(1)}$$

• check for convergence.

$$|V_i^{(1)} - V_i^{(0)}| \leq \epsilon$$

$$| \epsilon_i | |V_i^{(n)} - V_i^{(n-1)}| \leq \epsilon$$

$$|\delta_i^{(n)} - \delta_i^{(n-1)}| \leq \epsilon \quad \therefore \text{when } \epsilon \text{ is current iteration } n$$

If convergence is occurred, then calculated ^{losses} slack bus power and then go to stage-2
If not repeat the process.

USE OF ACCELERATION

Example

↓ the 2nd iteration value

$$V_2^{(2)} = \frac{1}{Y_{22}} \left[\frac{P_2 - jQ_2}{|V_2^{(1)}| \angle -\delta_2^{(1)}} - Y_{21} V_1 - Y_{23} V_3^{(1)} \right]$$

$$= |V_2|^{20} \angle \delta_2^{(20)}$$

before using V_2 in the next cal.

accelerate V_2 first and then used it-

$$V_2^{\text{accelerated}} = V_2^{19} + \alpha (V_2^{20} - V_2^{19})$$


acceleratⁿ factor

$$\alpha = 1.6$$

acceleration of 20-30%

$$\delta_2^{20} = \delta_2^{19} + \alpha (\delta_2^{20} - \delta_2^{19})$$

STAGE-2: to find line flow / losses.

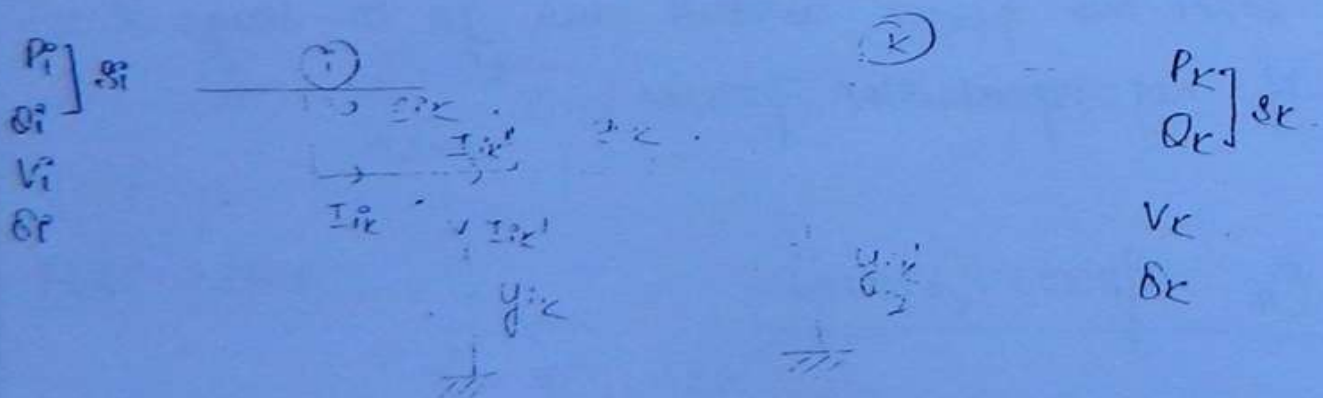

$S_{ik} = P_{ik} + jQ_{ik}$ = Complex power transferred from bus (i) to bus (k)

$$I_{ik} = I_{ik}^1 + I_{ik}^2 = V_i^0 \frac{y_{ik}^1}{2} + (V_i - V_k) y_{ik}$$

$$S_{ik} = V_i I_{ik}^* = V_i \left(V_i^* \frac{y_{ik}^*}{2} + (V_i^* - V_k^*) y_{ik}^* \right)$$

Similarly

$$S_{ki} = V_k I_{ki}^* = V_k \left[V_k^* \frac{y_{ki}^*}{2} + (V_k^* - V_i^*) y_{ki}^* \right]$$

$$S_{kp} = 1.1 + j0.9 \quad \rightarrow \text{sending (K to P) (importing)}$$

$$S_{pk} = -0.3 - j0.2 \quad \rightarrow \text{receiving (from P to K) (exporting)}$$

Dated

9 Nov 2010

Case 2: PV buses are present.

Stage 1: to find bus quantities



- using line data from Y bus

- Bus data:

Given: $V_1, \delta_1 = 0$

$P_2, V_2, Q_{2min}, Q_{2max}, P_3, Q_3$

Find:

P_1, Q_1, P_2, Q_2

V_3, δ_3

Init start:

$$V_2^{(0)} = 1 \angle 0$$

$$\delta_2^{(0)} = \delta_3^{(0)} = 0 \text{ radian}$$

= Step 1: calculate $Q_2^{(0)}$

$$Q_2^{(0)} = -|V_2||V_1||Y_{12}| \sin(\delta_2^0 - \delta_1^0 + \gamma_{12}) \\ + |V_2||V_3||Y_{23}| \sin(\delta_2^0 - \delta_3^0 + \gamma_{23})$$

= Step 2: check for reactive power limits

$$Q_{2min} \leq Q_2^{(0)} \leq Q_{2max}$$

= Step 3: update voltage magnitude and angle.

$$V_2^{(1)} = \frac{1}{Y_{22}} \left[\frac{P_2 - jQ_2^0}{|V_2| \angle -\delta_2^0} - Y_{21} V_1 - Y_{23} V_3 \right] \\ = |V_2|^{(1)} \angle \delta_2^{(1)}$$

const $|V_2|^{(1)}$, retain $\delta_2^{(1)}$

$$V_2^{(1)} = |V_2| \angle \delta_2^{(1)}$$

$$V_3^{(1)} = \frac{1}{Y_{33}} \left[\frac{P_3 - jQ_3}{|V_3|^0 \angle -\delta_3^0} - Y_{31}V_1 - Y_{32}V_2^{(1)} \right]$$

$$= |V_3|^{(1)} \angle \delta_3^{(1)}$$

Step 4 : check for convergence.


$$|\delta_1^n - \delta_1^{(n-1)}| \leq \epsilon$$

$$|V_3^n - V_3^{(n-1)}| \leq \epsilon$$

- If convergence occurs then calculate slack bus power, P_1, Q_1 and find value of Q_2 then goto stage 2 calculation
- If convergence do not occur repeat step 2 to 4 using current iteration values until convergence occurs.

REACTIVE-POWER LIMIT VIOLATION AT PV BUSES

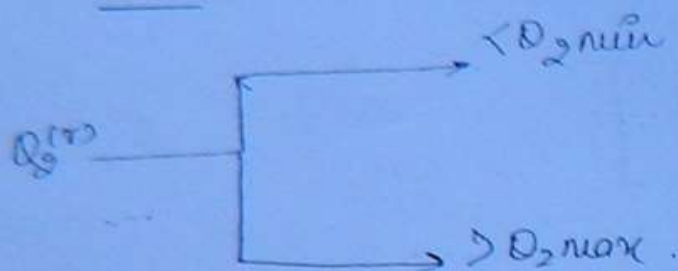- Let we have completed all no. of iteration, convergence could not be obtained even at the end of n^{th} iteration. Before going to $(n+1)^{\text{th}}$ iteration for updating voltages and load angle, $Q_2^{(n)}$ is calculated using n^{th} iteration values of (V) and (δ) - Now $Q_2^{(n)}$ has violated the limits. It can violate limit in two ways.



- Under these circumstances the voltage at the second bus may be more than or less than specified value.
- Treating second bus as PV bus is WRONG, it should be treated as PQ bus only.
- The true active power P_2 can be selected as specified value the reactive power Q_2 may be said $Q_2(\text{min})$ or $Q_2(\text{max})$ depending upon the case may be.

NEWTON-RAPHSON METHOD

(a) Single value function:

$$y_2 \quad f(x) = x^2 - \log x + 1$$

$$f(x) = 0$$

Let x, x^0 is the root

$$y^{(1)} = f(x^0) \neq 0$$

$$x^{(1)} = x^0 + \Delta x^0$$

$$y^{(1)} = f(x^{(1)}) = f(x^0 + \Delta x^0) = 0$$

expand the eqn by Taylor series approximates

$$y^{(1)} = y^{(0)} + \Delta y^{(0)} = f(x^0) + \left(\frac{\partial y}{\partial x}\right)^0 \Delta x^0 + \left(\frac{\partial^2 y}{\partial x^2}\right)^0 \Delta^2 x^{(0)} + \dots$$

$$f(x^0) + \left(\frac{\partial y}{\partial x}\right)^0 \Delta x^0 = 0$$

$$\Rightarrow \boxed{\Delta x^{(0)} = -\frac{f(x^0)}{\left(\frac{\partial y}{\partial x}\right)^0}}$$

175
x
345

$$\longrightarrow x^{(1)} = x^{(0)} + \Delta x^0$$

check for convergence.

$$|x^{(1)} - x^{(0)}| \leq \epsilon$$

$$x^{(2)} = x^{(1)} + \Delta x^{(1)}$$

$$\boxed{\Delta x^{(1)} = -\frac{f(x^{(1)})}{\left(\frac{\partial y}{\partial x}\right)^1}}$$

b) Multi value function:-

$$y_1 = f_1(x_1, x_2) = x_1^2 - \log x_1 x_2 + x_2^2$$

$$y_2 = f_2(x_1, x_2) = -2x_1^2 + \log x_1 x_2^2 - x_2^2$$

$$f_1(x_1, x_2) = 0$$

$$f_2(x_1, x_2) = 0$$

$x_1^{(0)}, x_2^{(0)} \rightarrow$ Initial guess

$$y_1^{(0)} = f_1(x_1^{(0)}, x_2^{(0)}) \neq 0$$

$$y_2^{(0)} = f_2(x_1^{(0)}, x_2^{(0)}) \neq 0$$

Newton's

$$x_1^{(1)} = x_1^{(0)} + \Delta x_1^{(0)}$$

$$x_2^{(1)} = x_2^{(0)} + \Delta x_2^{(0)}$$

$$y_1^{(1)} = y_1^{(0)} + \Delta y_1^{(0)} = f_1(x_1^{(1)}, x_2^{(1)}) = f_1(x_1^{(0)} + \Delta x_1^{(0)}, x_2^{(0)} + \Delta x_2^{(0)}) = 0$$

$$f_1(x_1^{(0)}, x_2^{(0)}) + \left(\frac{\partial f_1}{\partial x_1}\right)^0 \Delta x_1^{(0)} + \left(\frac{\partial f_1}{\partial x_2}\right)^0 \Delta x_2^{(0)} = 0 \quad \dots \textcircled{1}$$

$$f_2(x_1^{(0)}, x_2^{(0)}) + \left(\frac{\partial f_2}{\partial x_1}\right)^0 \Delta x_1^{(0)} + \left(\frac{\partial f_2}{\partial x_2}\right)^0 \Delta x_2^{(0)} = 0 \quad \dots \textcircled{2}$$

Put eqn's $\textcircled{1}$ and $\textcircled{2}$ in Matrix form.

$$\underbrace{\begin{bmatrix} \frac{\partial f_1}{\partial x_1} & \frac{\partial f_1}{\partial x_2} \\ \frac{\partial f_2}{\partial x_1} & \frac{\partial f_2}{\partial x_2} \end{bmatrix}}_{\text{Jacobian Matrix}} \underbrace{\begin{bmatrix} \Delta x_1 \\ \Delta x_2 \end{bmatrix}}_{\text{Increment Matrix}} = - \underbrace{\begin{bmatrix} f_1(x_1, x_2) \\ f_2(x_1, x_2) \end{bmatrix}}_{\text{Constant Matrix}}$$

$$\boxed{[J]^0 [\Delta X]^0 = -[f]^0} \quad \text{--- condensed form.}$$

so, $\boxed{[\Delta X]^0 = -[J^0]^{-1} [f]^0}$

After getting the increments update the values of $(x_1 \text{ and } x_2)$ using the increment value then check for convergence. If convergence is occurred take the solutⁿ of simultaneous algebraic equatⁿ otherwise repeat the process.

new roots : --- $x_1^{(2)} = x_1^{(1)} + \Delta x_1^{(1)}$
 $x_2^{(2)} = x_2^{(1)} + \Delta x_2^{(1)}$

$$\boxed{[\Delta X]^{(2)} = -[J^n]^{-1} [f^{(1)}]}$$

NR METHOD

$$P_i = f_i(\delta_i, |v_i|) \quad i = 1, 2 \quad n$$

$$Q_i = f_2(\delta_i, |v_i|) \quad i = 1, 2$$

$$\Delta P_i = \left(\frac{\partial P_i}{\partial \delta_1} \right) \Delta \delta_1 + \left(\frac{\partial P_i}{\partial \delta_2} \right) \Delta \delta_2 + \dots + \left(\frac{\partial P_i}{\partial \delta_n} \right) \Delta \delta_n + \left(\frac{\partial P_i}{\partial |V_1|} \right) \Delta |V_1| + \left(\frac{\partial P_i}{\partial |V_2|} \right) \Delta |V_2| + \dots + \left(\frac{\partial P_i}{\partial |V_n|} \right) \Delta |V_n|$$

$$\Delta Q_i = \left(\frac{\partial Q_i}{\partial \delta_1} \right) \Delta \delta_1 + \left(\frac{\partial Q_i}{\partial \delta_2} \right) \Delta \delta_2 + \dots + \left(\frac{\partial Q_i}{\partial \delta_n} \right) \Delta \delta_n + \left(\frac{\partial Q_i}{\partial |V_1|} \right) \Delta |V_1| + \left(\frac{\partial Q_i}{\partial |V_2|} \right) \Delta |V_2| + \dots + \left(\frac{\partial Q_i}{\partial |V_n|} \right) \Delta |V_n|$$

For slack buses δ_1 and V_1 are constant so the values like $\Delta \delta_1$ and ΔV_1 do not exist.

$$\begin{bmatrix} \Delta P_2 \\ \Delta P_3 \\ \Delta Q_2 \\ \Delta Q_3 \end{bmatrix} = \begin{bmatrix} \frac{\partial P_2}{\partial \delta_2} & \frac{\partial P_2}{\partial \delta_3} & \frac{\partial P_2}{\partial |V_2|} & \frac{\partial P_2}{\partial |V_3|} \\ \frac{\partial P_3}{\partial \delta_2} & \frac{\partial P_3}{\partial \delta_3} & \frac{\partial P_3}{\partial |V_2|} & \frac{\partial P_3}{\partial |V_3|} \\ \frac{\partial Q_2}{\partial \delta_2} & \frac{\partial Q_2}{\partial \delta_3} & \frac{\partial Q_2}{\partial |V_2|} & \frac{\partial Q_2}{\partial |V_3|} \\ \frac{\partial Q_3}{\partial \delta_2} & \frac{\partial Q_3}{\partial \delta_3} & \frac{\partial Q_3}{\partial |V_2|} & \frac{\partial Q_3}{\partial |V_3|} \end{bmatrix} \begin{bmatrix} \Delta \delta_2 \\ \Delta \delta_3 \\ \Delta |V_2| \\ \Delta |V_3| \end{bmatrix}$$

Increment of Matrix.

Power mismatch matrix.
 $(2n-2) \times 1$

Jacobian Matrix $[(2n-2) \times (2n-2)]$

$[(2n-2) \times 1]$

$$\begin{bmatrix} \Delta P \\ \Delta Q \end{bmatrix} = \begin{bmatrix} H & N \\ J & L \end{bmatrix} \begin{bmatrix} \Delta \delta \\ \Delta |V| \end{bmatrix}$$

$H, N, J, L \rightarrow$ submatrices of $[J]$

$$H = \frac{\partial P}{\partial \delta} ; N = \frac{\partial P}{\partial |V|} ; J = \frac{\partial Q}{\partial \delta} ; L = \frac{\partial Q}{\partial |V|}$$


ex -

$$H_{22} = \frac{\partial P_2}{\partial \delta_2} ; H_{23} = \frac{\partial P_2}{\partial \delta_3} ; L_{32} = \frac{\partial Q_2}{\partial |V_2|}$$

NR METHOD

Case 1: PV buses are ~~present~~ absent.

stage 1: to find the bus quantity.

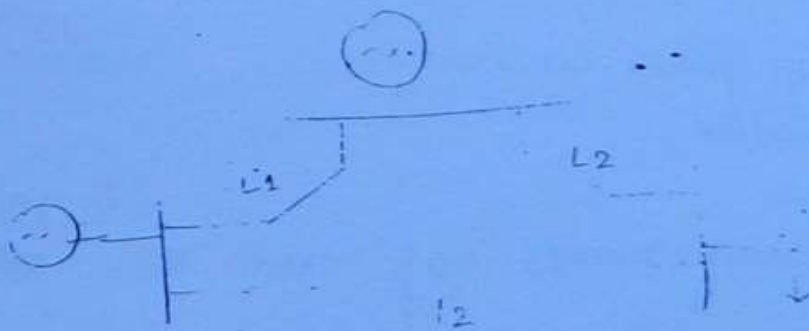

$\rightarrow$ using line data from Ybus.

Bus data:

Given: $V_1, \delta_1, P_2, Q_2, P_3, Q_3$

to find: $P_1, \delta_1, V_2, \delta_2, V_3, \delta_3$

* Flat start :-

$$V_2^{(0)} = V_3^{(0)} = 1 \text{ p.u.}$$

$$\delta_2^{(0)} = \delta_3^{(0)} = 0 \text{ radian}$$

* Step 1

- calculate P and Q values for PD buses.

$$P_2^{(0)} = |V_2|^{(0)} |V_1| |Y_{21}| \cos(\delta_2^{(0)} - \delta_1 + \gamma_{21}) \\ + |V_2|^{(0)} |V_2| |Y_{22}| \cos \gamma_{22} \\ + |V_2|^{(0)} |V_3| |Y_{23}| \cos(\delta_2^{(0)} - \delta_3 + \gamma_{23})$$

Similarly calculate $P_3^{(0)}$, $Q_2^{(0)}$, and $Q_3^{(0)}$

* Step 2

- calculate power mismatches

$$\Delta P_2^{(0)} = P_2^{(0)} - P_2 \parallel \text{fill up power mismatch matrix}$$

$$\Delta P_3^{(0)} = P_3^{(0)} - P_3$$

$$\Delta Q_2^{(0)} = Q_2^{(0)} - Q_2$$

$$\Delta Q_3^{(0)} = Q_3^{(0)} - Q_3$$

Step 3: Fill up $[J]^{(0)}$ elements

$$\left(\frac{\partial P_2}{\partial \delta_1} \right)^T = H_{21}^{(0)} = -|V_2|^{(0)} |V_1| |Y_{21}| \sin(\delta_2^{(0)} - \delta_1 + \gamma_{21}) \\ - |V_2|^{(0)} |V_3| |Y_{23}| \sin(\delta_2^{(0)} - \delta_3 + \gamma_{23})$$

$$\left(\frac{\partial P_2}{\partial |V_3|}\right)^0 = V_{23}^0 = |V_2|^0 |Y_{23}| \cos(\delta_2^0 - \delta_3^0 + \gamma_{23})$$

similarly all other elements can be found.

- after filling up the Jacobian elements and power mismatch elements the increments for delta and magnitude $|V|$ can be obtained as

$$\begin{bmatrix} \Delta \delta \\ \Delta |V| \end{bmatrix}^p = [J^0]^{-1} \begin{bmatrix} \Delta P \\ \Delta Q \end{bmatrix}$$

Step 5:


- Using the increments obtain update and magnitude of V values.

Step 6:

the check for convergence, if convergence occurs then calculate slack bus power P_1, Q_1 and go to stage 2 calculation, if not repeat the process.

stage 2: PV buses are present

stage 1: to find bus quantities

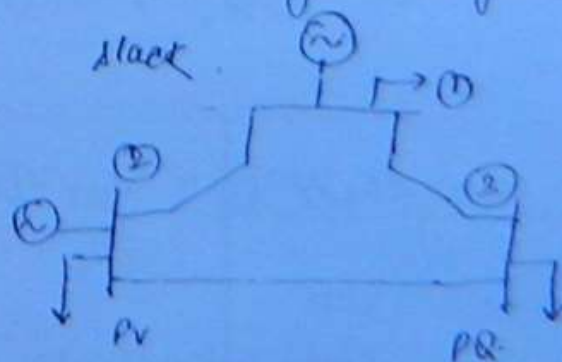

$$\begin{bmatrix} \Delta P_2 \\ \Delta P_3 \\ \Delta Q_3 \end{bmatrix}, \begin{bmatrix} \frac{\partial P_2}{\partial \delta_2} & \frac{\partial P_2}{\partial \delta_3} & \frac{\partial P_2}{\partial |V_3|} \\ \frac{\partial P_3}{\partial \delta_2} & \frac{\partial P_3}{\partial \delta_3} & \frac{\partial P_3}{\partial |V_3|} \\ \frac{\partial Q_3}{\partial \delta_2} & \frac{\partial Q_3}{\partial \delta_3} & \frac{\partial Q_3}{\partial |V_3|} \end{bmatrix} \begin{bmatrix} \Delta \delta_2 \\ \Delta \delta_3 \\ \Delta |V_3| \end{bmatrix}$$

Non-existing elements:

$J_{22}, J_{23}, L_{23}, L_{22}, N_{22}, N_{32}, L_{32}$

— using line from Y_{bus}

Bus data:

Given: $V_1, \delta_1, P_2, V_2, Q_{2min}, Q_{2max}, P_3, Q_3$

To find: $P_1, Q_1, Q_2, \delta_2, V_3, \delta_3$

Flat start:

$$V_3^0 = 1.0$$

$$\delta_2^0 = \delta_3^0 = 0 \text{ rad.}$$

Step 1:

check Q_3^0 for limits

Step 2:

that calculate b, l and Q values for PQ bus
and l values of PV buses

Step 3 calculate power mismatches ΔP_2^0 , ΔP_3^0 and ΔQ_3^0 and fill up the matrix.

Step 4 Evaluate Jacobian element and fill the matrix.

Step 5 calculate increment for δ and $|V|$ as follows.

$$\begin{bmatrix} \Delta \delta \\ \Delta |V| \end{bmatrix} = \begin{bmatrix} J^0 \end{bmatrix}^{-1} \begin{bmatrix} \Delta P \\ \Delta Q \end{bmatrix}$$

Step 6: using the increments update δ and $|V|$ values

Step 7: Check for convergence, if occurs calculate slack bus power P_1, Q_1 and final value of δ_2 if not repeat the process.

Label
10 Nov 20

= COMPARISON B/W NR AND GSM :-

Parameter of comparison	GS METHOD	NR METHOD
1. Time for each iteration	LESS	MORE —
2. Complexity of iteration	EASY	Very Difficult.

3. Type of convergence	Linear	Quadratic
4. Convergence rate	Slow	Fast
5. Total no. of iterations	Increases with size of P.S	Independent of size of P.S
6. Guarantee of Convergence	Not Guaranteed	Guaranteed
7. Acceleration	External	Internal
8. Selection of slack bus on convergence	more dependent	less dependent
9. Suitability	for small size P.S	for large size P.S
10. Accuracy	less	Highest

DECOUPLED LOAD FLOW METHOD

NR method

$$\begin{bmatrix} \Delta P \\ \Delta Q \end{bmatrix} = \begin{bmatrix} H & N \\ J & L \end{bmatrix} \begin{bmatrix} \Delta \delta \\ \Delta V \end{bmatrix}$$

$$H = \frac{\partial P}{\partial \delta} \begin{matrix} \nearrow 100 \\ \rightarrow 50 \\ \searrow 10 \end{matrix}$$

$$N = \frac{\partial P}{\partial |V|} \begin{matrix} \nearrow 0.1 \\ \rightarrow 0.1 \\ \searrow 0.001 \end{matrix}$$

$$J = \frac{\partial Q}{\partial \delta} \begin{matrix} \nearrow 0.1 \\ \rightarrow -0.1 \\ \searrow 0.001 \end{matrix}$$

$$L = \frac{\partial Q}{\partial |V|} \begin{matrix} \nearrow 100 \\ \rightarrow 50 \\ \searrow 200 \end{matrix}$$

Decoupled LF Method

$$\begin{bmatrix} \Delta P \\ \Delta Q \end{bmatrix} = \begin{bmatrix} H & 0 \\ 0 & L \end{bmatrix} \begin{bmatrix} \Delta \delta \\ \Delta |V| \end{bmatrix}$$

$$\Delta P = H \cdot \Delta \delta$$

$$\Delta Q = L \cdot \Delta |V|$$

Further assumption made :- (fast decoupled load flow method)

1) Neglect resistance of Generator, T/F, Transmission lines etc.

$$Y_{bus} = j[B] \quad \begin{matrix} \nearrow \text{Integer} \\ \searrow \text{Matrix} \end{matrix}$$

2) $\delta_i - \delta_k \approx 0 \text{ rad}$. [as the value of difference in radians is very small value.]

$$\begin{bmatrix} H_{ii} = L_{ii} \\ H_{ik} = -L_{ik} \end{bmatrix}$$

Advantages of Decoupled load flows method over NR Method:-

- 1) Instead of finding 100% of Jacobian element in NR method, in DCLF method we find 50% of J. element
- 2) Sparsity of Jacobian matrix is improved.
- 3) No. of calculations are reduced.

* Advantages of FDLF over DCLF Method:-

- 1) In contrast to 50% of Jacobian element in FDLF method we calculate only 25% of J. elements.
- 2) By neglecting the resistance Y_{bus} is stored as integer matrix.
- 3) Less memory space is required for storing J matrix.

NOTES:-

- For small size p/s or offline p/s GS method is used.
- For large size power sys and for online application no. of p/s is used.

- for evaluating sensitivity coefficients NR method is used.


WORK BOOK

1)

total admittance connected to bus 2

$$Y_{22} = -j10 - j5 - j5$$


$$Y_{22} = j20$$

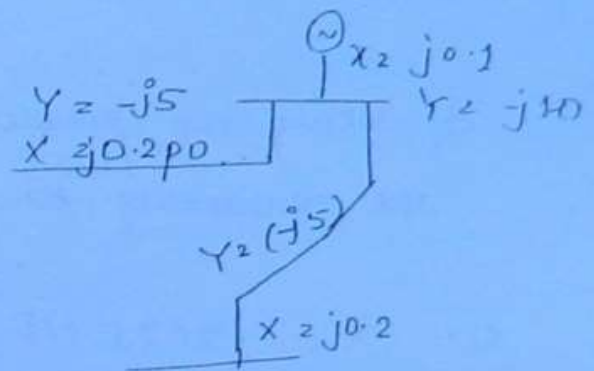


2) d.

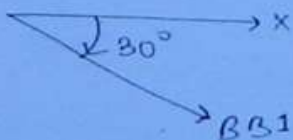- 3) Active power transfer from BB1 to BB2 is zero if busbar voltage are in phase

Reactive power transfer from BB1 to BB2 is zero if busbar voltage magnitude are same




BB1 voltage lag voltage by 30°

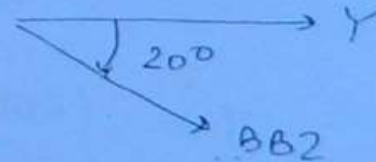

BB2 voltage lag Y by 20°

after series connection

A) Am

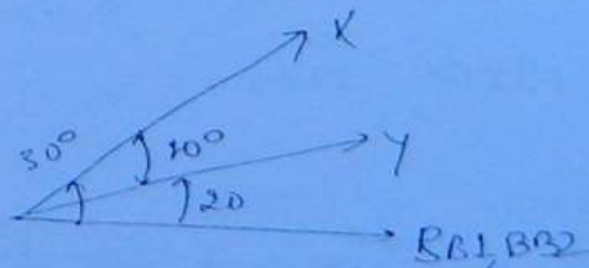

4)

$\eta = 30\%$

20 buses $\rightarrow$ 418 buses

25 buses $\rightarrow$ reactive power

15 buses $\rightarrow$ Shunt Capacities

240 buses $\rightarrow$ PQ buses

Size of Jacobian

Solution:

By taking one generator bus as the slack bus
the remaining 10 buses connected with $q/r = 19$.

Let $n = 19 + 25 + 15 = 59$ PV buses.

Jacobian

$$(2 \times 300 - 2 - 59)$$

$$\Rightarrow 539 \times 539$$

(i) Let 19 generator bus and 25 bus of reactive power
support are taken as PV buses

$$n = 19 + 25 = 44$$


$$J = (600 - 2 - 44)$$

$$\Rightarrow 554 \times 554$$

$$12) \quad 2 \times 12 - 2 - 3 = 19 \times 13$$

5) c

6)

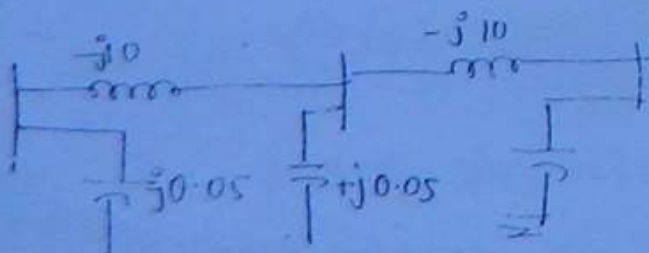

$$-j10 + j10 + j0.05$$

$$= 13.95j$$

$$4) \quad Z = \begin{bmatrix} 0.9 & 0.2 \\ 0.2 & 0.6 \end{bmatrix}$$

$$0.54 - 0.04$$

$$Y = \frac{1}{0.50} \begin{bmatrix} 0.6 & -0.2 \\ -0.2 & 0.9 \end{bmatrix}$$

$$\Rightarrow Y_{22} = 1.8$$

$$8) \quad Z_{bus, (new)} = Z_{bus} (old) - \frac{1}{Z_{22} + Z_3} \begin{bmatrix} 2' \end{bmatrix}$$

$$\begin{bmatrix} j0.3408 & j0.2586 \end{bmatrix} - \frac{1}{j0.3408 + j0.2} \begin{bmatrix} j0.2860 \\ j0.3408 \\ j0.2586 \\ j0.2414 \end{bmatrix} \begin{bmatrix} j0.2660 & j0.5408 \\ j0.2586 & j0.2414 \end{bmatrix}$$

$$Z_{22}^{(new)} = j0.3408 - \frac{1}{j0.5408} \times j0.3408 \times j0.3408$$

$$= 0.1266$$

$$Z_{33}^{(new)} = j0.2586 - \frac{1}{j0.5408} \times j0.3408 \times j0.2586$$

$$= j0.0956$$

9) b.

13) C

$$14) \quad \text{Total no of zero element} = 9000$$



$$\text{Total no of non-zero element} = 1000$$

total no of new few elements in the upper / lower triangle


$$= \frac{1000 - 100}{2} = 450$$

No of transmission line = 450

SWITCH GEAR PROTECTION.

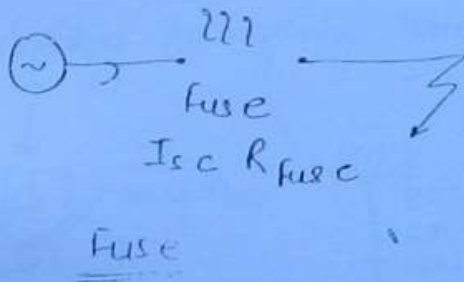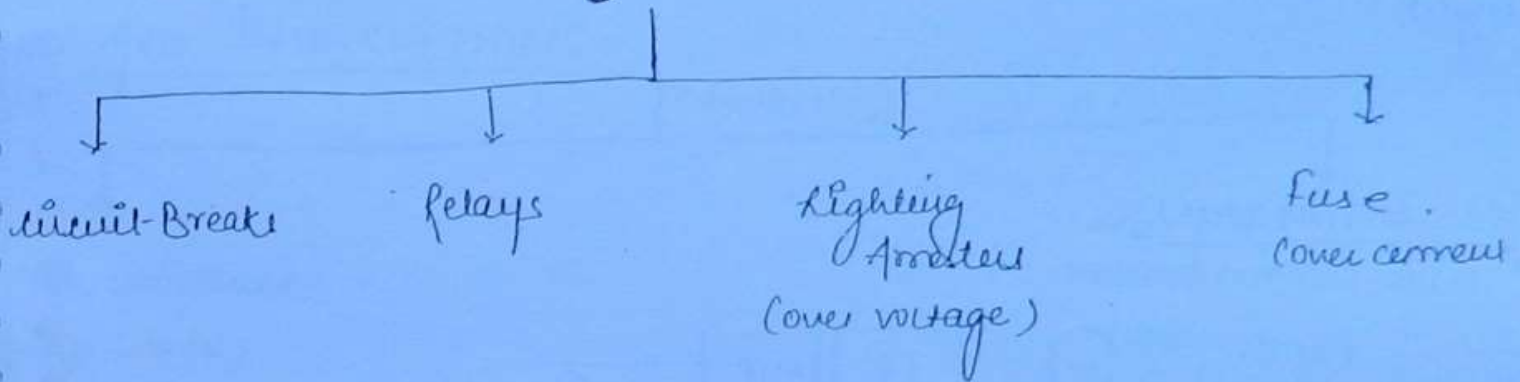

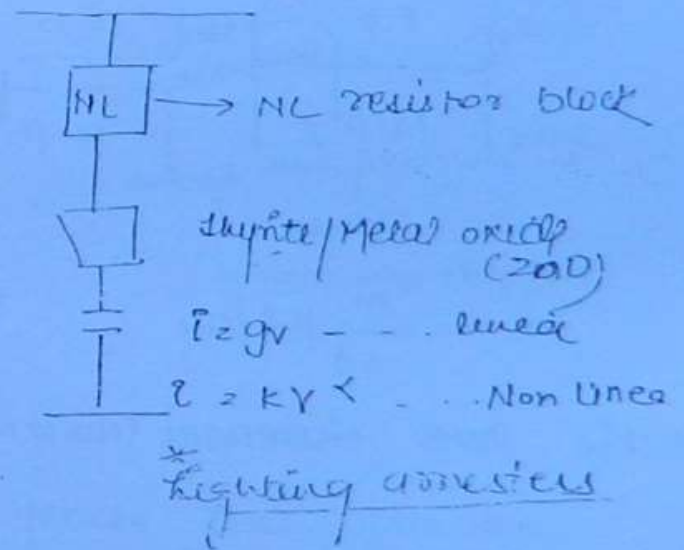* Every circuit breaker acts as a series switch




CIRCUIT BREAKERS

- The only difference arc and current is, if the flow of charges take place in conducting material like Al, Cu, we call it as current, if same flow of charges take place in medium

we call it an 'arc'

- During the time of arcing I^2 losses are very high and high heat is produced. This in turn produces light.

ARC INITIATION:-

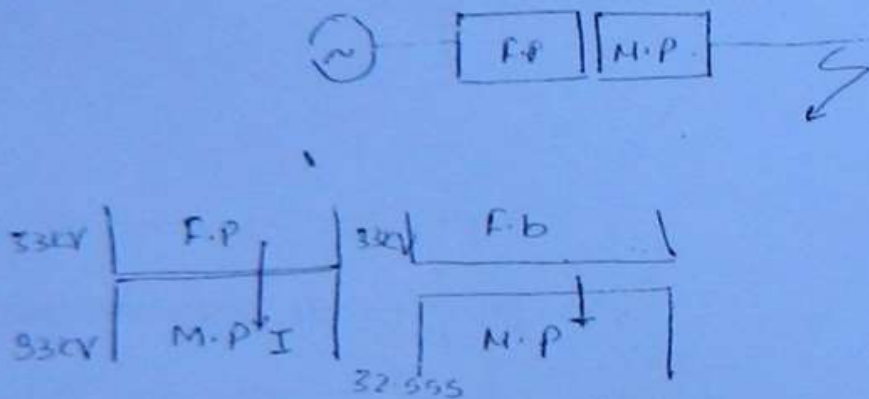

$$\frac{\Delta V}{\Delta d} \text{ kV/cm}$$

- Dielectric stress increases tremendously as distance is in micron.
- In circuit breaker arc is initiated because of field emission process, at the instant when two poles are separating a high dielectric stress will occur because of negligible time distance b/w two contacts. This dielectric stress is much near higher than the dielectric strength of any dielectric medium. Therefore ionisation begins / arc strikes. This process is known as field emission process.

- In circuit breakers arc is maintained because of thermionic emission process.


ARC INTERRUPTION:-

(Methods)


High resistance
(D/C Bus)

low resistance.
Natural current zero
(A/C Bus).

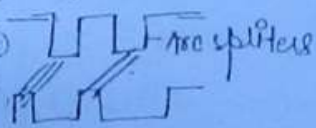
arc splitting Arc lengthening forced blast



* metal evaporates near arc

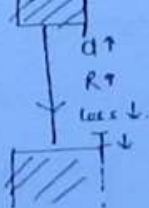

* size of C.B need to be big

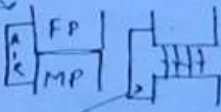

* High pressures compressor are needed.



- * low pressure is used.
- * Here arc itself goes to zero.



- In A/C CB arc interruptⁿ takes place only after the arc passes natural current zero.

Dated

13 Nov 2020

ARC RESTRICTION

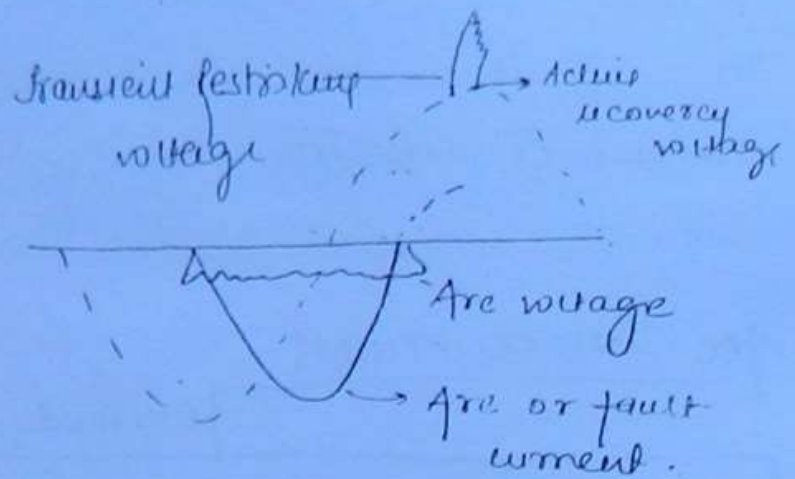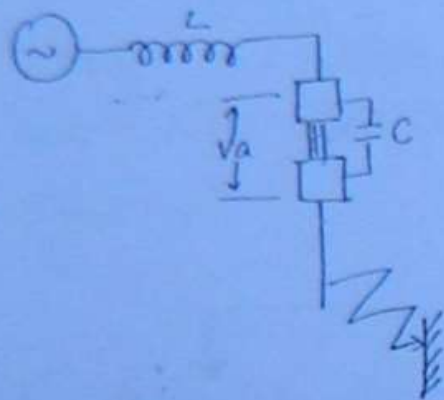Consider a power s/m with negligible resistance.




$L \rightarrow$ inductance of c/w upto fault resistance.

$$V_a = I_a R_a$$

(1) Arc has unity power factor*

2) characteristic of arc

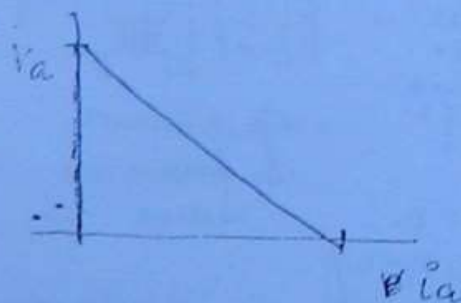

Arc has negative resistance characteristic

During the time of arcing the voltage across the breaker poles is the arc voltage which is generally a small value due to short circuit condition.

At the instant when the arc passes its natural current zero arc is interrupted. At this point of time some heat is present in gap.

- the system response is oscillatory coz a capacitance is appearing across the breaker poles due to open circuit condition.
- the arc may restrike or not will depend on behavior of restriking voltage. the behaviour of restriking voltage depends upon L and C . the values of L and C are such that restriking voltage is rising rapidly this means in this short time the heat in gap cannot be removed and contact cannot be cooled. therefore all the conditions in the gap helping restriking voltage to make arc restrike again; in other way the values of L and C are such the restriking voltage is rising slowly. this means ample of time is available to remove the heat and to cool the contacts. therefore no condition are helping the restriking voltage to make arc restrike again. Hence final arc interruption takes place.

Transient restriking voltage (Vr): -

The transient voltage that appears across breaker pole at instant of arc interruption is known as transient restriking voltage.


$$V_r = V_{max} \left[1 - \cos t \sqrt{\frac{1}{LC}} \right]$$

$V_{max} \rightarrow$ supply peak voltage.

$t \rightarrow$ time distance

$L, C \rightarrow$ line inductance and capacitance.

sample

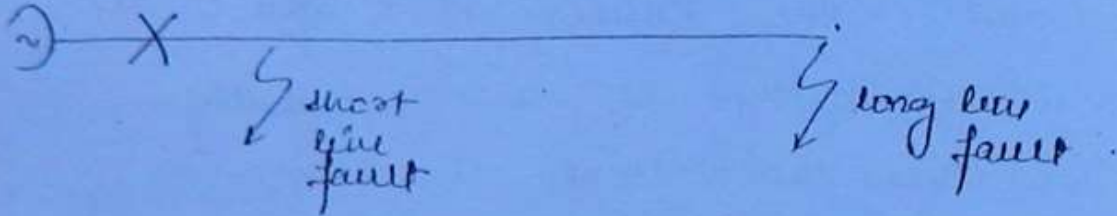

short line fault: L and $C \downarrow \frac{t}{\sqrt{LC}} \uparrow \cos \frac{t}{\sqrt{LC}} \downarrow 1 - \frac{\cos t}{\sqrt{LC}} \uparrow V_r \uparrow$

long line fault: L and $C \uparrow \frac{t}{\sqrt{LC}} \downarrow \cos \frac{t}{\sqrt{LC}} \uparrow 1 - \frac{\cos t}{\sqrt{LC}} \downarrow V_r \downarrow$

In view of restriking voltage a short line fault is more severe compare to long line fault.

Rate of Rise of Restriking voltage: - [RRRV]

for restriking free operation of CB RRRV should be less.

$$RRRV = \frac{dV_r}{dt}$$

$$RRRV = \frac{V_M}{\sqrt{LC}} \sin\left(\frac{t}{\sqrt{LC}}\right) \quad \text{KV/} \mu\text{sec}$$

$$\text{Maximum RRRV} = \frac{V_m}{\sqrt{2}C} \text{ kV}/\mu\text{sec}$$

• Natural frequency of oscillation $f = \frac{1}{2\pi\sqrt{LC}}$

• Average RRRV = (Max value of restriking voltage) / time taken to reach the value

$$\text{Average RRRV} = \frac{2V_{\max}}{\pi\sqrt{LC}} \text{ kV}/\mu\text{sec}$$

Objective:

If the rate at which heat is dissipated is less compared to RRRV then arc will not be otherwise arc is interrupted

Active Recovery Voltage:


The instantaneous voltage that appears across breaker for after fault are interruption is known as active recovery voltage.

Recovery voltage:

The rms voltage that appears across breaker for after fault are interruption is known as recovery voltage.

CURRENT CHOPPING PHENOMENON

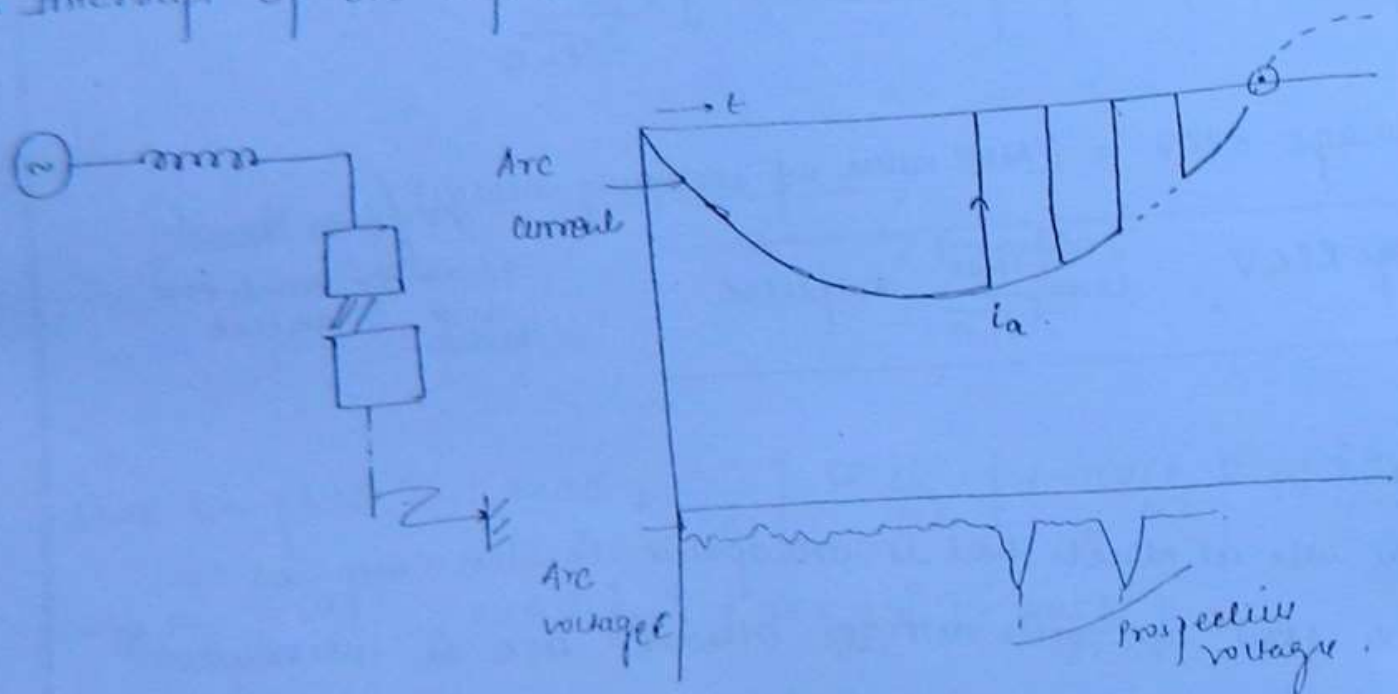"Interrupt" of arc before natural current zero.



i_a : Instantaneous current i.e. interrupted

energy stored by inductance $\frac{1}{2} L i_a^2$

• Energy balance equation

$$\frac{1}{2} C V^2 = \frac{1}{2} L i_a^2$$

$$V = i_a \sqrt{\frac{L}{C}}$$

prospective voltage.

• As the strength of driving deionizing force is so high and severity of p fault current is so so less, arc will be interrupted well before it passes its natural current zero.

the energy stored in the inductance will start converting into electro-static energy by the capacitor. When the capacitor is charging the voltage across breaker poles as well as dielectric stress starts increasing. At particular value of dielectric stress, an arc will restrike again. As the de-ionising force is still ~~on~~ the arc will extinguish again. This process repeats until arc passes natural zero.

Disadvantage:-



Transient off voltage known as switching overvoltage ^{will appear} s/w.

- the insulation requirement for EHV lines is designed based on switching over voltages.


RESISTANCE SWITCHING CIRCUIT BREAKER

- Resistance switching is employed in ckt breaker to avoid ω C C phenomena.

$$R = 0.5 \sqrt{\frac{L}{C}}$$

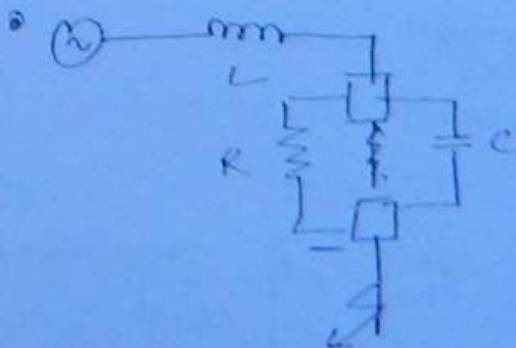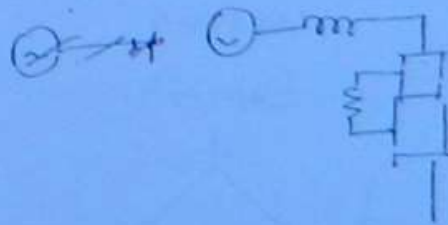

CIRCUIT BREAKER RATING

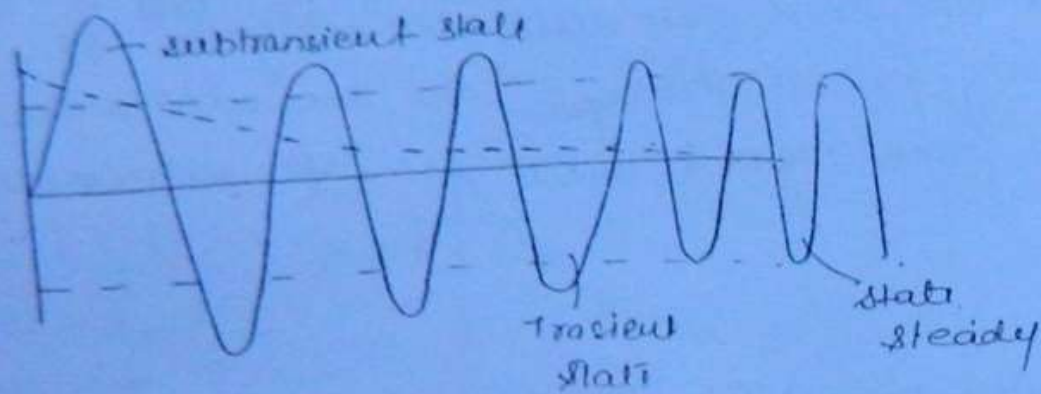

• Subtransient current $\rightarrow$ Breaking current

A CB can make the circuit during subtransient state or break the circuit during transient or steady state.

CB Rating

Breaking
Capacity

KV

MVA

Making
Capacity

KA

MVA

Short time rating
(Rated breaking capacity
for specified duration)

Symmetrical Asymmetrical

$$I_{break} = \frac{V}{\sqrt{2}}$$

$$I_{break} = \sqrt{\frac{2 \times V}{\sqrt{2}}}$$

$$\boxed{\text{Making Capacity} = 2.55 \times \text{Breaking Capacity}}$$

Numerical:-

A 33KV 33⁰⁰MVA, 15kVA, 3sec, SDH2 1- ϕ oil CB has

1) Rate normal current = 1500 A

2) Rate breaking capacity 3300MVA


3) Rated breaking capacity in kVA = $\frac{3300}{23} = 100 \text{ kVA}$

4) Rated making capacity in kA = $\frac{2.55 \times 100}{1} = 255 \text{ kA}$

5) Short time rating = $\frac{3300 \text{ MVA}}{1.5 \text{ sec}}$
or $\frac{6600 \text{ MVA}}{1.5 \text{ sec}}$

Classification based on dielectric:-

Oil Circuit Breaker

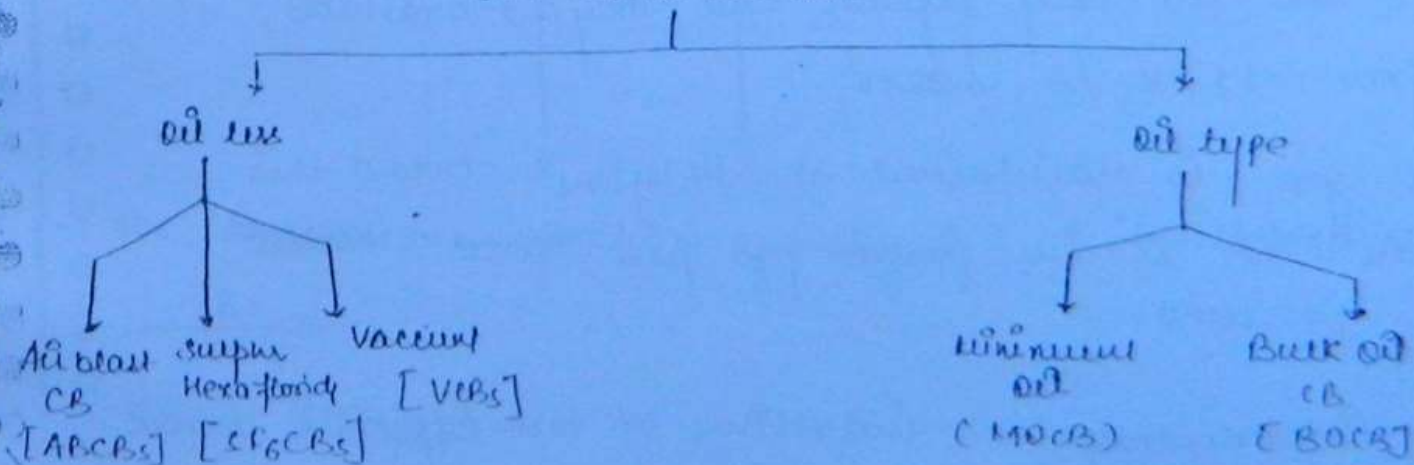

• current chopping phenomenon is more severe in case of air blast ABCBS

- Resistance switching is mainly employed in ABCBs.
- Resistance switching reduces the severity RRRV.
- Air pressure in ABCBs is maintained around 30 kg/cm^2 .
- ABCBs are not suitable for high speed and repeated operation.
- ABCBs are more suitable for EHV and UHV application [400kV range].
- Both arc energy and arcing time are least in case of ABCBs.
- SF_6 gas is 3 to 5 times better than air due to its electronegativity properties. Electronegativity means affinity of electrons.




- Because of its low molecular weight SF_6 gas has excellent thermal conducting properties.
- SF_6 CBs are very popular and they are available from 11 kV to 800 kV.
- SF_6 gas is maintained at 14 kg/cm^2 below this pressure it is in powder form. Hence heaters may be used.
- For interrupting low inductive or low capacitive current without resistance switching the CB employed is SF_6 CBs.
- Transformer oil in DCBs has two applications.

FUNCTIONAL CHARACTERISTICS:-

1) Sensitivity:-

Relay is able to produce sufficient operating torque to close the trip ckt even for small change in operating quantity

2. Selectivity (Zone of protection)

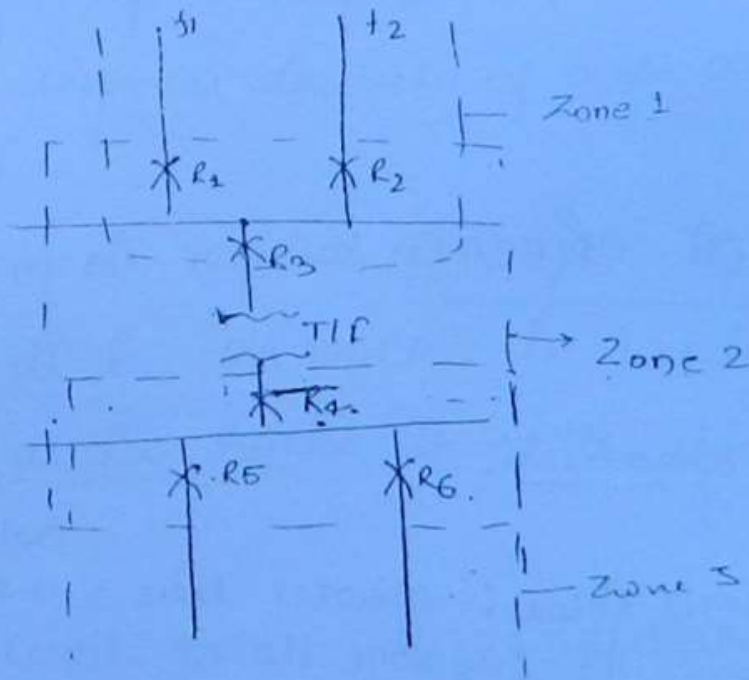

the simultaneous operation of Relay 1, 2, 3, fault occurs at BB:-

3) Speed:-

clear the fault in time < 5 cycles time
 $5 \times 0.02 \text{ sec} = 0.1 \text{ sec.}$

④ Simplicity:-

↳ design of the relay must be simple

⑤ Cost:-

20% of the cost of the equipment can be spend on protectⁿ.

⑥ Reliability:-

:- when fault occurs relay should operate

TYPE OF RELAY


1) Based on type of operation:-

a) Instantaneous relay:- operates time $\leq 0.1 \text{ sec}$

used for generator protection

made up of balanced beam and induction cup.

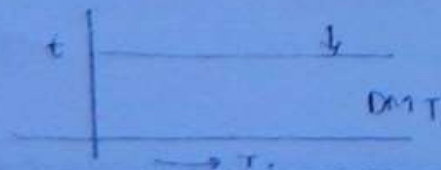b) Definite Minimum time: time is constant



1) It acts as dielectric medium [dielectric strength of T/r 50kV,
in air 30kV
in oil 1mV]

2) At 658°K xnu oil decomposes and produces various gases, out of these gases $\approx 70\%$ of gas is Hydrogen which act like coolant.

- In oil CB the strength of deionising force shall adjust in accordance to severity of fault current. Thus for current chopping phenomenon is least in this case.
- The chance for an interruption in subsequent natural current zero improves in case of OCB's but reduces in other types.
- The volume of oil required for MOCB's is only 10% of BOCB's as oil in BOCB's is used for arc extinction only whereas in MOCB's it is used for insulating line parts also.
- OCB's are used for all voltage applications from 11 kV to 132 kV.
- The vacuum pressure in VCB's is maintained around 10^{-8} to 10^{-6} Torr.
 $1 \text{ Torr} = 1 \text{ mm Hg}$
- The principal of arc interruption in VCB's is condensation of arc products like copper vapours etc.


maintenance is least in case of VCB's

VCB's are suitable for remote and rural electrification
for interrupting high current and low voltage (11KV
range) VCB's are used.

AUTO-RECLOSEING FEATURES


used for over current protection of Induction Motor.

c) Inverse Relays:-

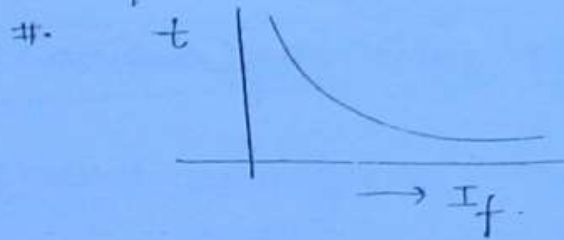

generally not used.

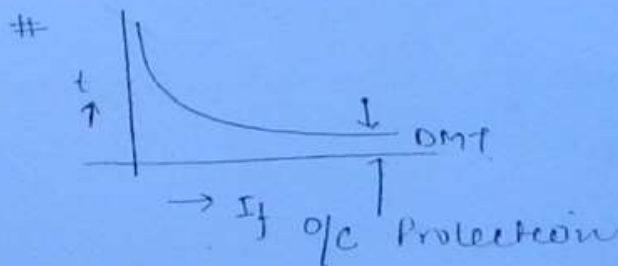d) IDMT relay:- [combination of Inverse and DMT relay]



Commercially used.

Over current relay.

2) Based on the construction / operating principle:-

a) Electromagnetic attraction type:-

Balanced beams [differential protection]

Attracted armature

Moving plunger

b) Electromagnetic Induction Type

- # Shaded pole
- # Wattmeter [o/c protection]
- # Induction Cup: fastest relay [distance relay]

c) Gas protected Type:-

- # Buchholz relay [used for protecting oil immersed ~~xm~~ from internal / incipient faults]

d) Thermal Relays:-

- # Overload protection.

e) Static / microprocessor base relays

- # Not widely used as need much precaution.

OVER-CURRENT PROTECTION

Definition:-

1) PICK-UP VALUE:- It is the minimum value of operating quantity at which relay is 'WEDGE' of operation of

② RESET VALUE:- It is a maximum value of operating quantity at which relay is at the wedge of non-operation.

$$\boxed{\text{wedge condition} \Rightarrow \text{operation force} = \text{restraining force}}$$

- Reset and Pick values are different because of hysteresis error.
- For well-designed relays ratio of Reset to pick up value is unity. However for induction type relay it is 0.9.

③ TIME MULTIPLIER SETTING:-

$$TMS_{\text{required}} = \frac{\text{Time of operation required}}{t_{ms} = 1} \cdot \frac{t_{\text{required}}}{t_{ms} = 1}$$

Example:-

1) A relay operates in 5 sec when $TSM > 1$, to operate relay in 2 sec, TMS should be adjusted to.

$$TMS_{\text{required}} = 2 \cdot \frac{2}{5} = 0.4 \text{ sec}$$

2) A relay operates in 4 sec when $TSM > 1$. To operate relay in 1.98 sec, TMS should be adjusted to

$$TMS = \frac{1.98}{4} \cdot 0.495 \approx 0.5 \text{ sec}$$

$$= \text{time taken by relay} = 0.5 \times 4 = 2 \text{ sec}$$

Delay takes more time to react. delay of 0.02 sec
so take value as = 0.4 sec.

NOTE:-

Ans should always be rounded to nearest lower values always.

$$\frac{TMS_2}{TMS_1} = \frac{t_2}{t_1}$$

Q. A relay operates in 3-sec when $TMS = 0.7$ when T is adjusted to 0.2, the relay operates in — sec


2nd

$$\frac{0.2}{0.4} = \frac{t_2}{63}$$

$$\begin{array}{r} 0.6 \\ 0.7 \end{array} \quad 2 \pm 2$$

$t_2 = 0.857 \text{ sec}$

③ PLUG SETTING MULTIPLIER (PSM).

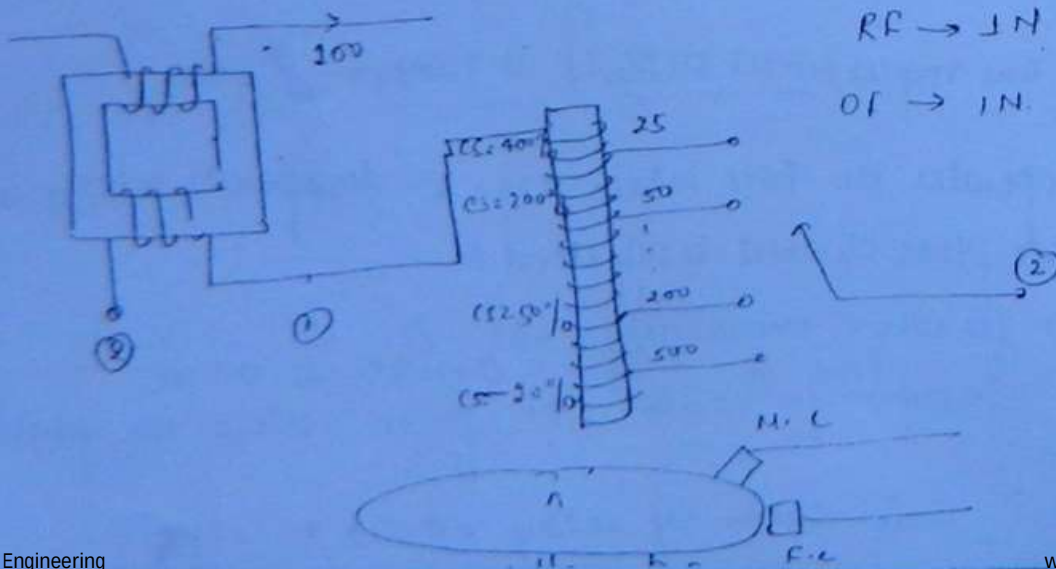

• relay normal current

$$= CT \text{ sec rated current} = 5A$$

• relay operating current = 20A
= 4x5

$$\text{relay operating current} = \text{current setting} \times \frac{CT \text{ secondary rated current}}{CT \text{ ratio}}$$

$$\text{relay operating current} = \text{current setting} \times \frac{CT \text{ secondary rated current}}{CT \text{ ratio}}$$

related to CT primaries

$$PSM = \frac{\text{Fault current}}{\text{Current setting} \times \frac{CT \text{ secondary rated current}}{CT \text{ ratio}}}$$

$$PSM = \frac{\text{Fault current}}{\text{Current setting} \times \frac{CT \text{ secondary rated current}}{CT \text{ ratio}}}$$

Example:

1) current setting = 40%, fault current 2000A, CT = $\frac{100}{5}$, then PSM

$$PSM = \frac{2000}{\frac{40}{100} \times 5 \times \frac{100}{5} \times 5} = 50$$


PSM increases with fault current

- Higher the fault current lower is time of operation.

• $PSM \uparrow I_f \uparrow$ • $I_f \uparrow PSM \uparrow t \downarrow$ • $PSM \uparrow t \downarrow$

- Higher the PSM higher the speed of disc.

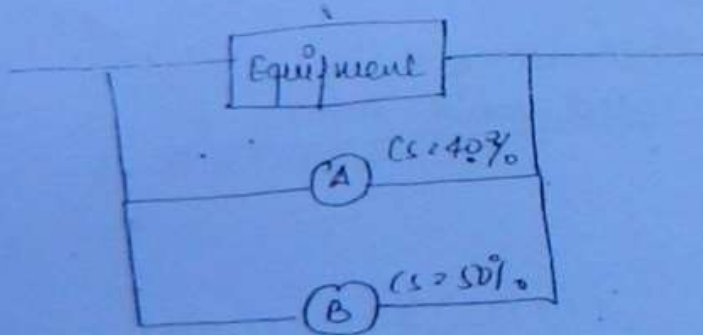- if $PSM < 1 \rightarrow$ will not operate
- $PSM = 1 \rightarrow$ wedge of operation
- $PSM > 1 \rightarrow$ Relay operates.



as

$$\# PSM_A > PSM_B$$

relay A acts like primary relay.

$$\# P_s \quad \boxed{PSM < \frac{1}{CS}}$$


NOTE :-

- The time for primary relay is less than backup relay.

- Current setting for primary and back up relay is generally same.
- Except the protecting equipment, there should not be anything common b/w primary and back-up relays.

OVER CURRENT RADIAL FEEDER PROTECTION

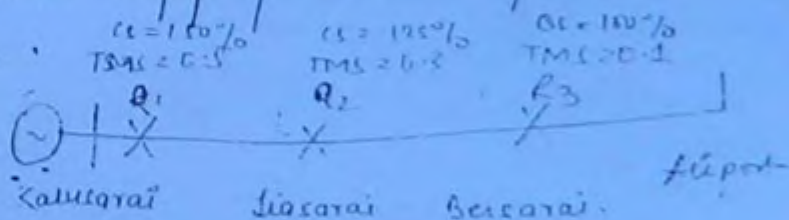- The feature required in o/c radial feeder protection is if fault occurs at the far end from the supply we should clear the fault there itself, this leaves minimum no. of customers are given interruption and majority of customers are continued to be given w/d supply. This improves reliability of radial feeder.



Methods used:

1) Time graded Method:

According to this method for the relay farthest from the source minimum TMS is set. As we are approaching towards the source the TMS is gradually increased.

Disadvantage:

The disadvantage of this method is if the fault occur near the source the magnitude of fault current is very high. This high magnitude fault current is over cleared in more time.

b) current graded method:-

According to this method for the relay furthest from the source minimum current setting is set, as we are approaching towards the source the over current setting is gradually increased.


- the disadvantage is as we have only four over current setting viz 125, 150, 175 and 200%. we can make the radial feeder section. However by adopting time current graded method we can make the radial feeder into more no. of section & improve the reliability further.

c) Time-current graded method:-


According to this method for the relay furthest from the source minimum PMS and as we set as we are approaching towards the source these setting are gradually increased.

Example:-

the CS and TMS for relay zone

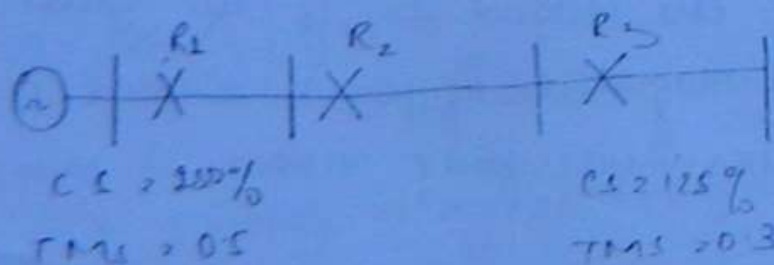


PROTECTION OF PARALLEL LINES

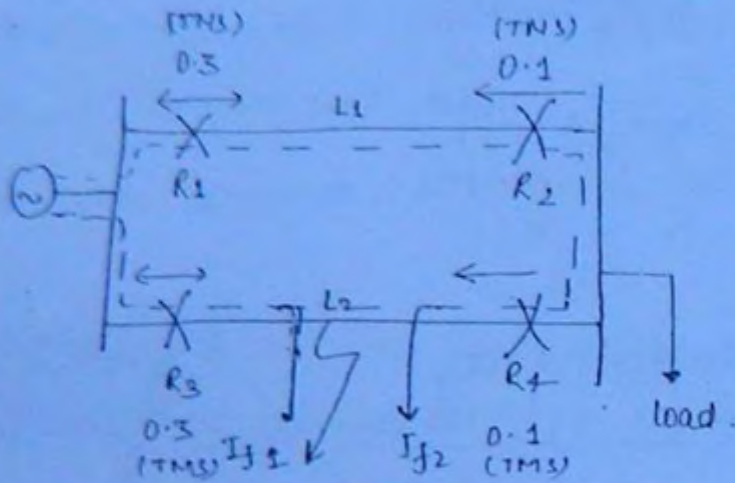

$I_{f1} : R_3$ ↗ directional relay
 $I_{f2} : R_1, R_2, R_4 \rightarrow 0.1$ (R_4 operate first)
0.3

O/C PROTECTION OF RING MAIN FEEDER

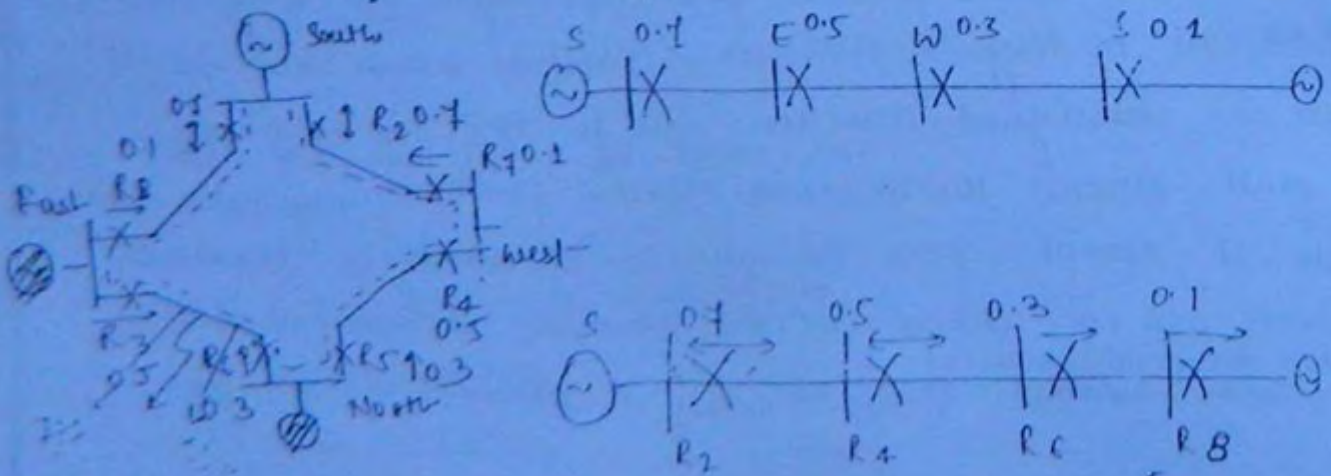= while providing over current protection for ring main feeder
It is treated as two radial feeders.




$$I_{f1}: R_1 \xrightarrow{\text{directly}} R_3 \text{ [operates]}$$

$\downarrow$ $\downarrow$
 0.4 0.5

$$I_{f2}: R_2 \xrightarrow{\text{0.4}} R_4 \xrightarrow{\text{0.5}} R_6 \text{ [operates]}$$

OVERCURRENT PROTECTION OF G/R


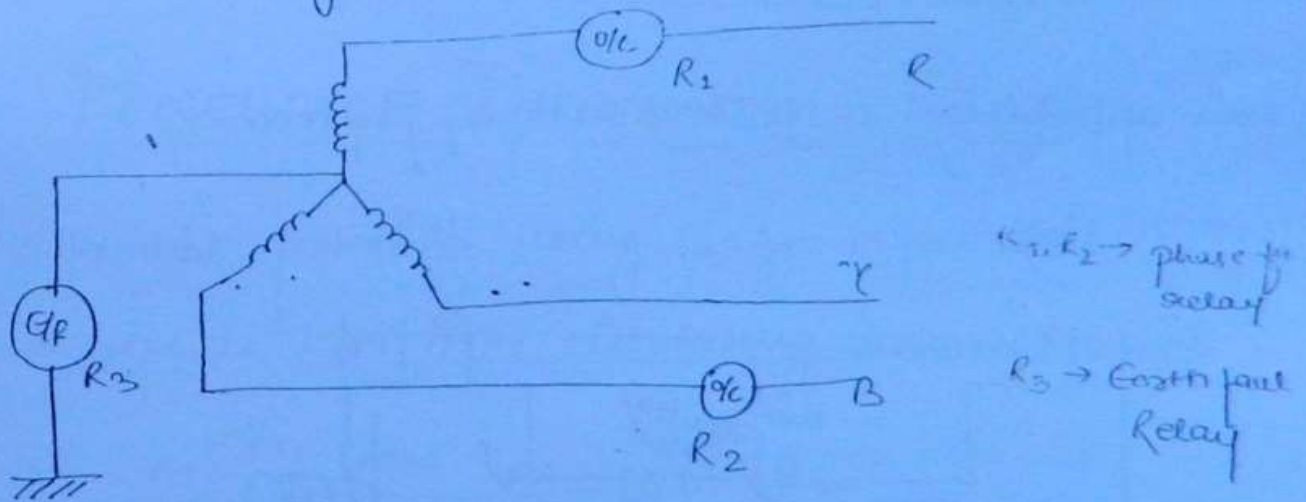
For complete overcurrent protection of generator ~~two~~ we need two overcurrent relay and one earth fault relay.



• The R_3 is known as earth fault relay since it can detect only earth fault, in addition to earth fault this relay also detects unbalanced condition. Therefore setting for this relay will of minimum like 20% - 40% etc.

3 ϕ faults $\rightarrow$ R_1 and R_2 operates

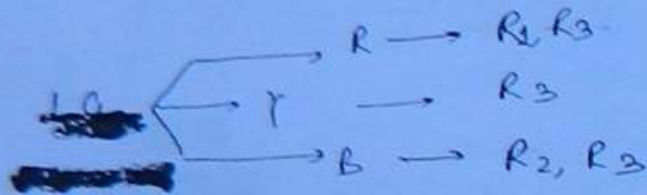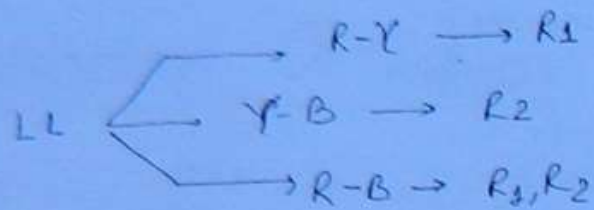
$L-L$ $R-\gamma \rightarrow R_1, R_3$
 $L-B$ $\rightarrow R_2, R_3$
 $L-G$ $\rightarrow R_1, R_2, R_3$



unbalanced condition $\rightarrow R_3$

DIFFERENTIAL PROTECTION

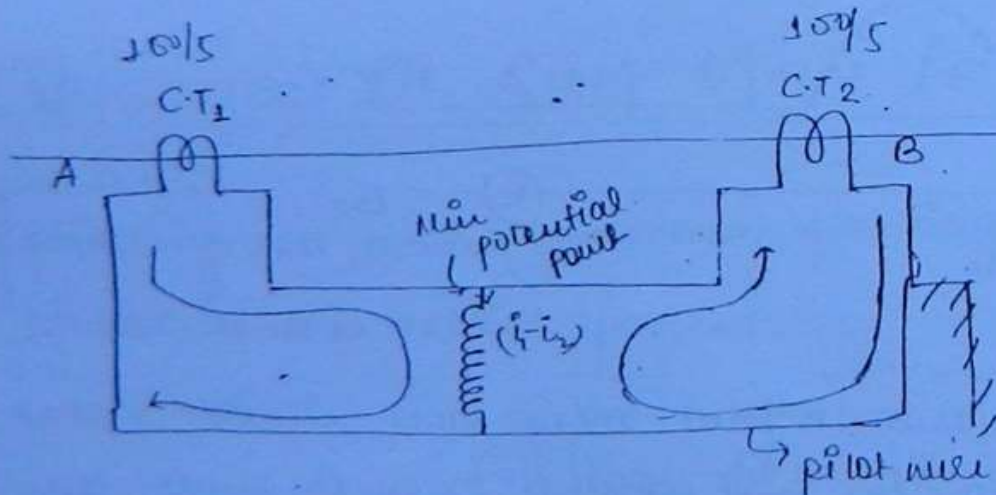→ Main application is to have zone of protection



→ A differential relay operates well when the difference of two same electrical quantities [$i_1 - i_2$, or $V_1 - V_2$ but not $P_1 - P_2$] exceed the set of designed value.


→ this relay operates only for internal fault and provide zone of protection, it cannot operate for external or through fault condition.

→ A differential protection comparing voltage is known as Translay Protect?

→ A differential relay may "not operate" either due to unequal saturation level of two CTs or due to CT error. To avoid this mal operation ordinary differential relay is modified to percentage differential relay.

PERCENTAGE DIFFERENTIAL RELAY

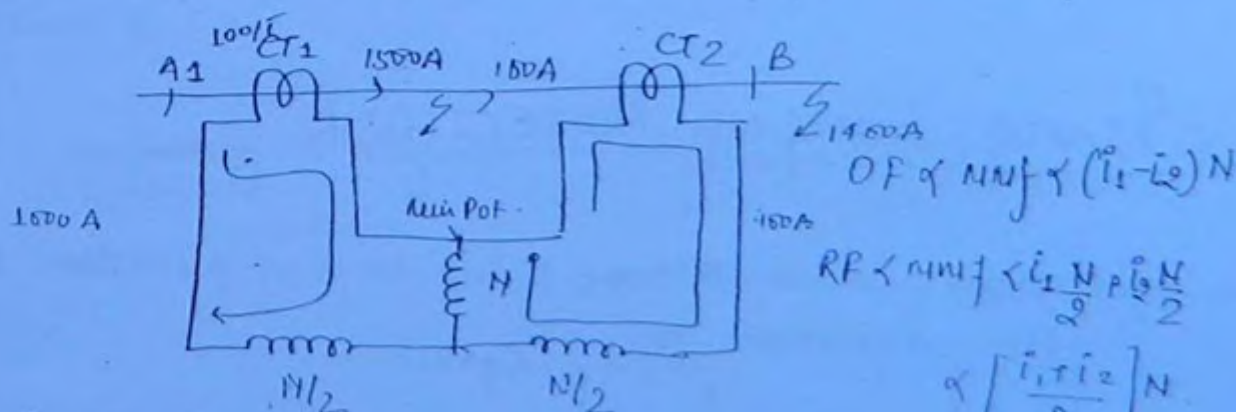→ A differential protection using %age differential relay is known as Mery Price circulating current method.



$$I_1 = 50, I_2 = 45$$

$$OP \propto (I_1 - I_2) N$$

$$RF \propto \frac{(I_1 + I_2) N}{2}$$

$$\propto 47.5 N$$


$$I_1 = 50, I_2 = 45$$

$$OP \propto (50 - 45) N$$

$$\propto (5) N$$

$$RF \propto (50 + 45) / 2 \propto 47.5 N$$

Characteristic:-

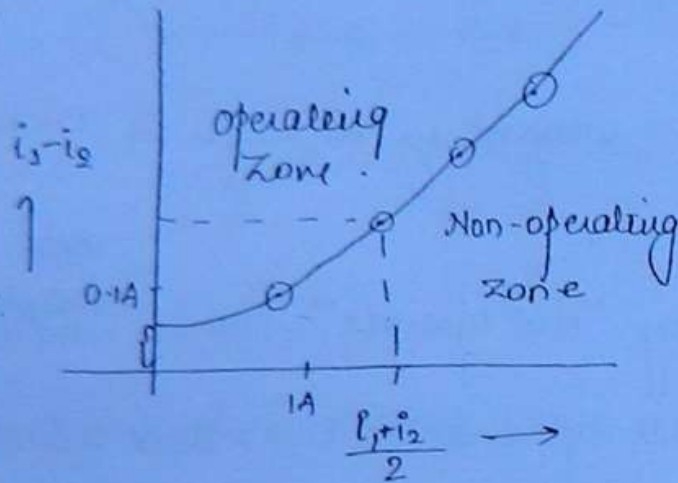


→ The characteristic of differential relay starts above origin due to essential problems.

$$\% \text{ slope} = \frac{i_1 - i_2}{\left(\frac{i_1 + i_2}{2}\right)} \times 100$$

10% slope, means if operating force is 10% of restraining force the relay is on wedge of operation.

STATOR WINDING PROTECTION

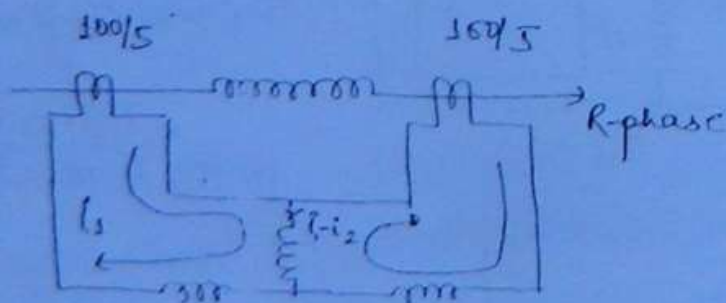

Quest 1 : $CT, CT_2 \rightarrow 100/5$

$$\% \text{ slope} = 10\%$$

$$I_f = 10A$$

1) for the fault of $10A$, with $\% \text{ slope } 10$, will relay operate CB or not.

$$1) \quad I_1 = 110A \Rightarrow \hat{I}_1 = 110 \times \frac{5}{100} = 5.5A$$


$$I_2 = 100A \quad \hat{I}_2 = \frac{100 \times 5}{100} = 5A$$

$$O.C = \hat{I}_1 - \hat{I}_2 = 0.5A$$

from $\% \text{ slope}$

$$\frac{\hat{I}_1 - \hat{I}_2}{\frac{\hat{I}_1 + \hat{I}_2}{2}} = 0.1$$
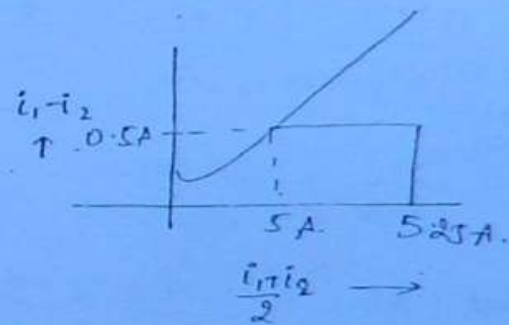
$$\frac{\hat{I}_1 + \hat{I}_2}{2} = \frac{0.5}{0.1} = 5$$



for an operating current of $0.5A$, the restraining current at which current at which the relay is at the wedge operation is $5A$.

Now ~~original~~ $R.C$ Original $R.C = \frac{\hat{I}_1 + \hat{I}_2}{2} = \frac{5.5 + 5}{2} = 5.25A$

as restraining force at $5.25A$ at $5A$, the relay will not operate

Quest 2

$$CT_1, CT_2 = 100/5$$

$$\% \text{ slope} = 5\%$$

$$I_f = 10A$$

Soln

$$I_1 = 110 \text{ A}$$

$$I_2 = \frac{110 \times 5}{100} = 5.5 \text{ A}$$

$$I_2 = \frac{100 \times 5}{100} = 5 \text{ A}$$

$$O.C = I_1 - I_2 = 0.5 \text{ A}$$

$$\frac{I_1 - I_2}{(I_1 + I_2)/2} = 0.05$$

$$\Rightarrow \frac{0.5}{0.05} = \frac{I_1 + I_2}{2}$$

$$= \frac{1}{0.01} = 10 \text{ A}$$

$$\text{original RC} = \frac{I_1 + I_2}{2} = 5.25$$


$5.25 \text{ A} < 10 \text{ A}$ so relay will operate

NOTE:-


the relay sensitivity is increasing with decreasing % slope

PERCENTAGE WINDING PROTECTED/UNPROTECTED


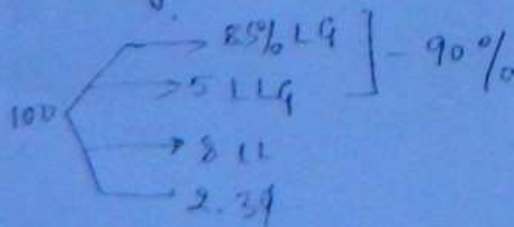
→ Out of 100% generator total 100% are star connected




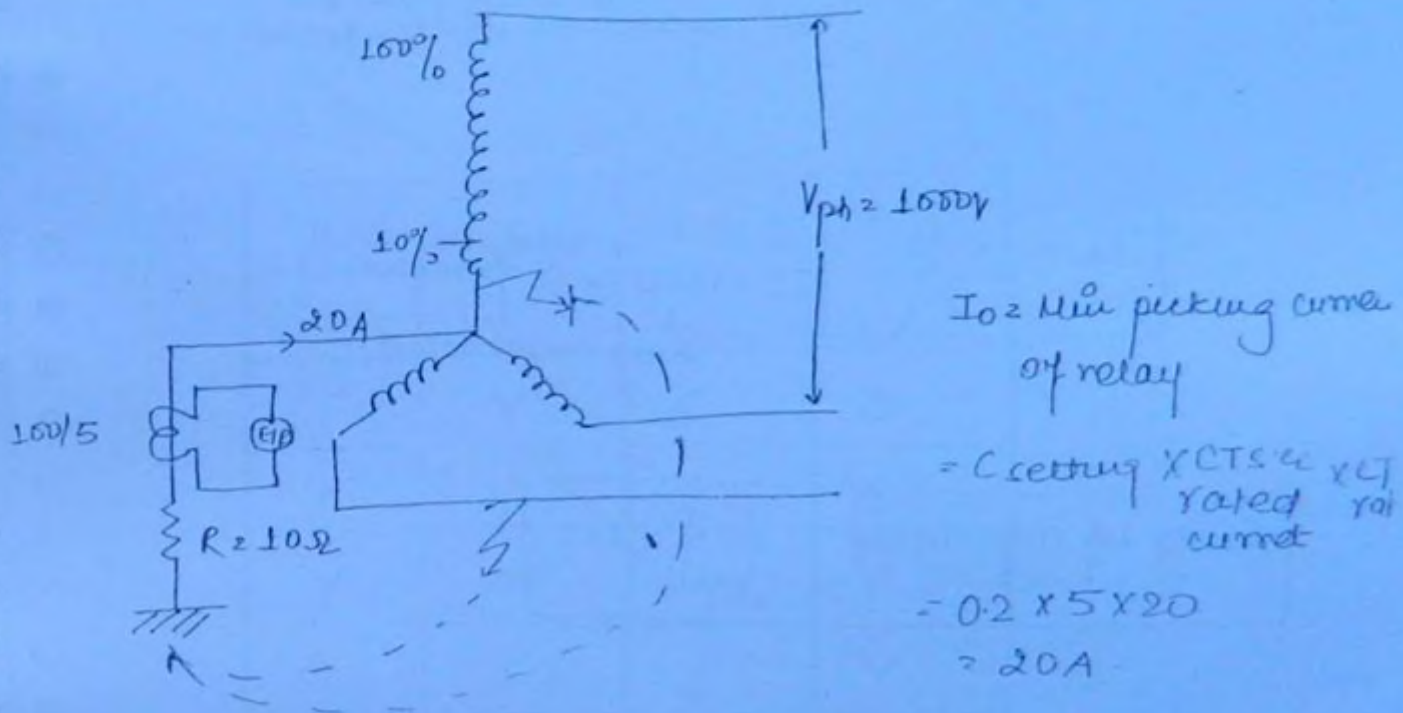- At 0% winding 0% voltage induced and with 100% winding 100% voltage is induced.




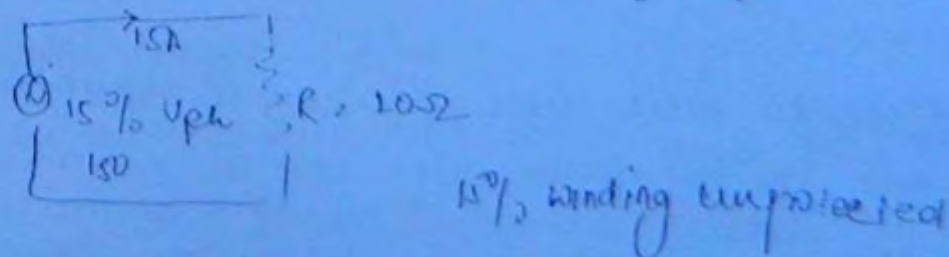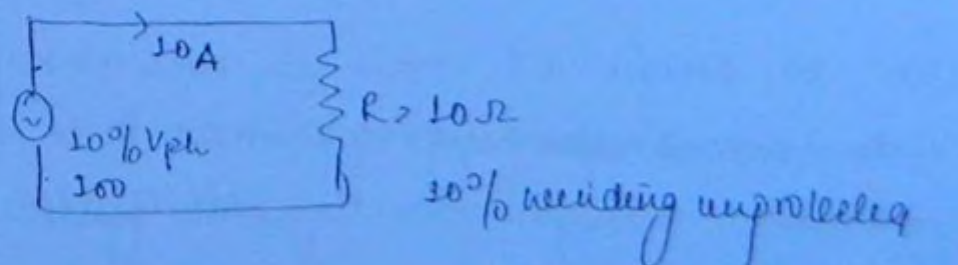- To minimize most frequently occurring fault (earth), the neutral of g/r is grounded with resistance 'R'
- Generally for detecting unbalance current the current setting of earth fault relay is set to minimum say 20%



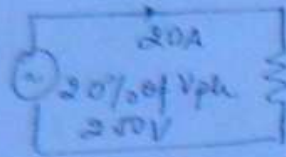

20% wdg protected

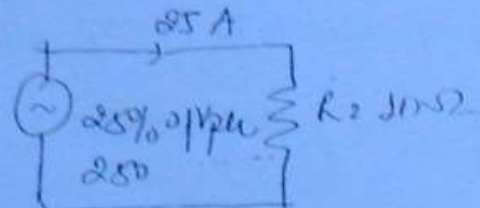

25% wdg protected

$$I_0 = \frac{x V_{ph}}{R}$$

where x is fraction of wdg unprotected.

$$\% \text{ wdg unprotected} = \frac{I_0 R \times 100}{V_{ph}}$$

DIFFERENTIAL PROTECTION OF TRANSFORMER

→ Before providing differential protection to power transformer, there are two issues to resolve.

1) How to design CT ratio in such a way that under normal operating condition the current flowing through operating coil is zero.

2) How to avoid mis operation of differential relay due to 30° phase shift b/w line currents of star-delta and delta-star power transformer.

1. To avoid the 'mal operation' of differential relay due to 30° ratio between line currents of star-delta, delta-star power xmr. the secondaries of the CTs must be connected as per following table.

Power Transformer		CT's secondary	
LV	HV	LV	HV
Y	Y	Δ	Δ
Δ	Y	Y	Δ
Y	Δ	Δ	Y
Δ	Δ	Y	Y


Numerical:

A 8MVA, 33/11KV, star Y- Δ power xmr is protected by Mergence circulating current method. Design the CT ratio for a nominal CT-secondary current of 5Amp

Sol:

- 1) CT ratio means it is a ratio of primary winding current to secondary winding current
- 2) CT primary winding current = line current of power xmr
- 3) If CT secondaries are connected in Y then pilot wire current = line current = phase current - CT secondary winding current.

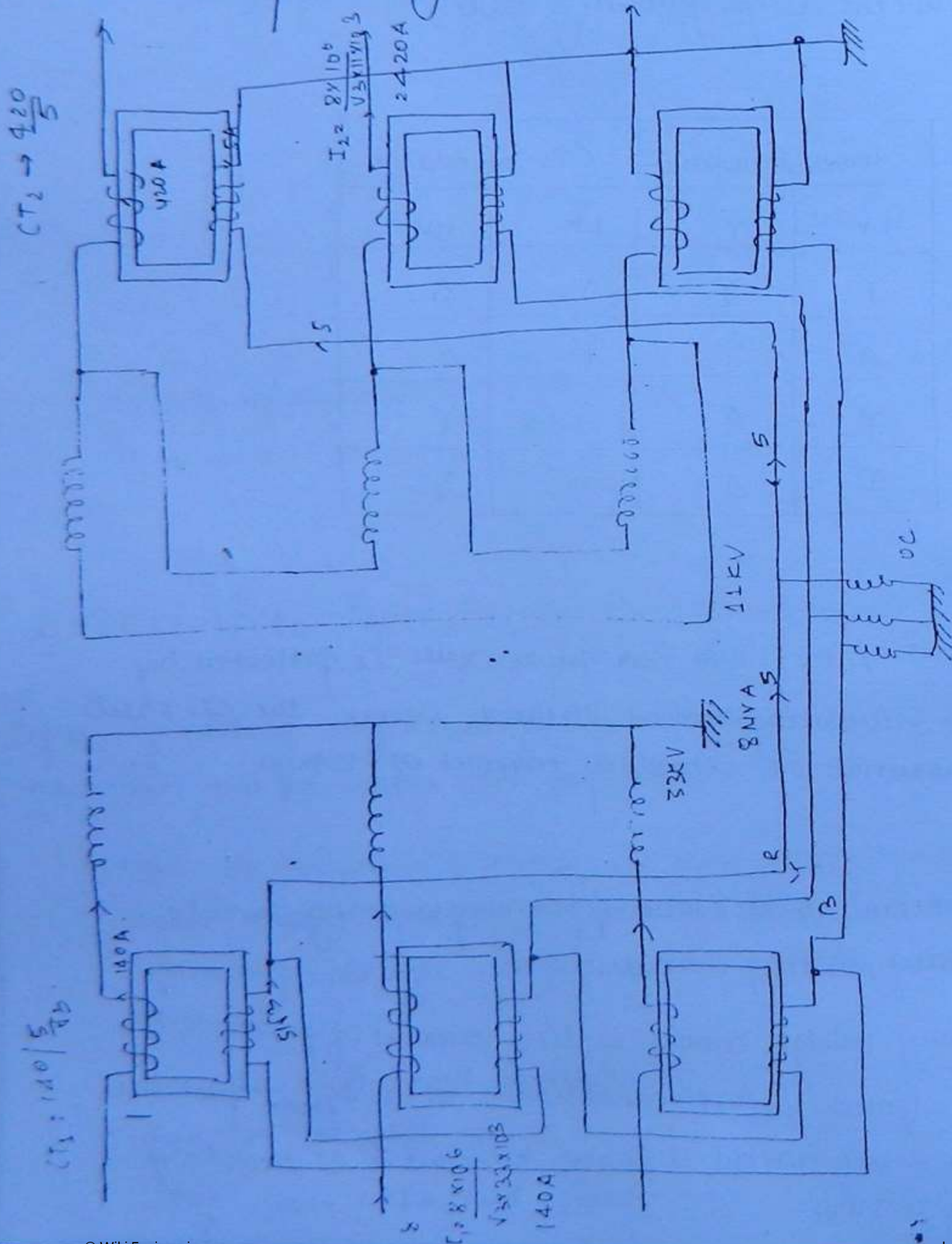
4) If CT secondaries are connected in delta then
 pilot wire current is equal line current = $\sqrt{3}$ phase current
 = $\sqrt{3}$ Secondary winding current.



DISTANCE PROTECTION

- can not be used for xmer protectⁿ.
- can be used for generator and Transmission line protect^r
- Main application is protectⁿ of T.L
- used as primary protection for long lines.
- In this type of relay operating force is produced due to CT secondary and restraining force is produced due to PT secondary.
- Known as Double actuating quantity relay.
- If induction type relay are used
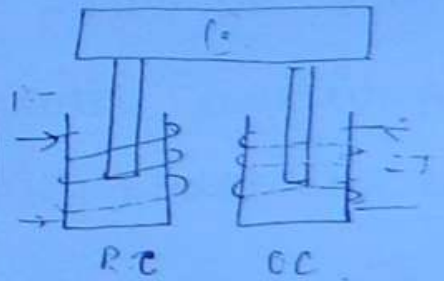
$$\begin{aligned} \text{operating force} &\propto I^2 \Rightarrow OF = K_1 I^2 \\ \text{Restraining force} &\propto V^2 \Rightarrow RF = K_2 V^2 \end{aligned}$$



- Relay will operate when

$$RF < OF$$

$$K_2 V^2 < K_1 I^2$$

$$\frac{V^2}{I^2} < \frac{K_1}{K_2}$$

$$\frac{V}{I} < \sqrt{\frac{K_1}{K_2}}$$

→ The relay is operating when ratio of voltage to current seen by the relay is less than some set or designed value. K_1, K_2 are design constant.

This relay is known as Ratio relay. as well as Impedance relay. [$\because V/I = \text{Impedance}$]

→ As impedance and distance are proportional quantities this relay is also known as distance relay.

→ REACH :- It is the distance at which a distance relay is at the wedge of operation.

→ A distance relay operates for all the faults occurring below the reach.

→ A distance relay has a problem of under reach or over reach due to dc offset current.

Dated
14 Nov 2010

DEFINITE DISTANCE, DEFINITE TIME DISTANCE PROTECTION
(3-zone of protection)

1st disc - $Z < 85\%$

→ Instantaneously


2nd disc - $Z < 15\% \text{ and } t > 0.3 \text{ sec}$

- exclusively Z ^{values} at which exclusive 2nd disc alone operates at 8-15 Ω .

- 3rd disc — $2 < 20\Omega$ $t_2 = 0.05\text{sec}$

exclusive Z values at which 3rd disc alone operates 15-20 Ω .

Example:

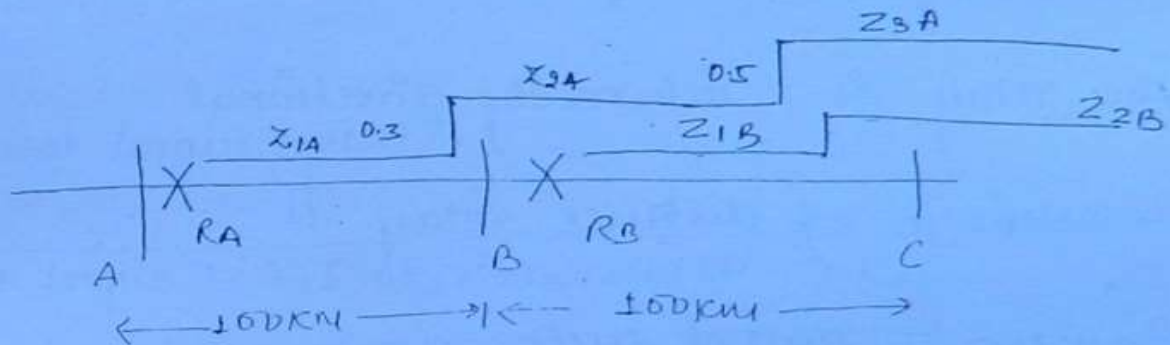

Relay - A has 3 zones

Z_{1A} : 80% distance of section

Z_{2A} : 20% remain distance of section AB + 50% distance of adjacent section BC

Z_{3A} : Remaining 50% distance of adjacent section BC

Comments:

Distance relay are 3 types

- 1) Impedance Relay
- 2) Reactance Relay
- 3) Admittance / Mho relay

3) An impedance relay with voltage restrained or over current relay.

3) The ^{restrained} distance relay is directional restrained over current relay.


4) the MHO relay is voltage restrained directional relay

5) A MHO relay is inherently directional

6) The characteristic of distance relay is

$$C^2 = a^2 + b^2 \quad \text{--- eqn of circle}$$


$$Z^2 = R^2 + X^2$$

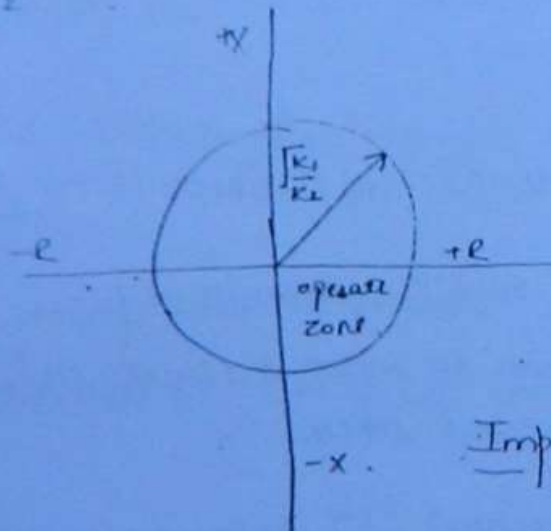

A circle having origin as center


Impedance Relay

→ X-relay

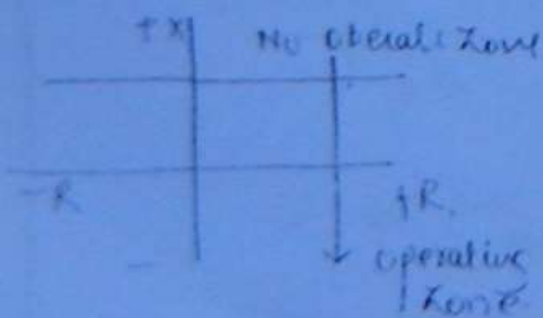


A straight line parallel to real axis

MHO Relay

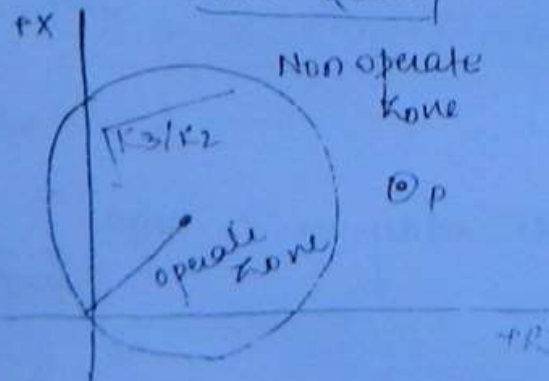

A circle passing through origin

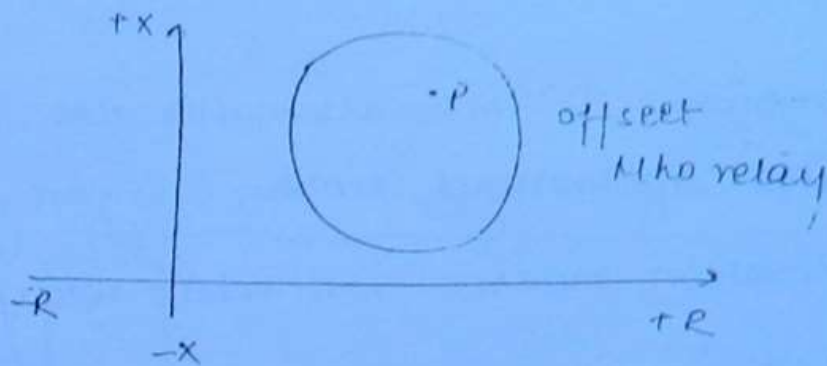

Universal Torque equation:

$$\text{Net Torque } T = K_1 I^2 + K_2 V^2 + K_3 VI \cos(\theta - \tau) + K_4$$

• Overcurrent $\rightarrow T = K_1 I^2 - K_4$

• Overvoltage $\rightarrow T = K_2 V^2 - K_4$

1) For earth fault zero reactance relay are normally used.

2) For phase faults.

Short line $\rightarrow$ X-relay

Medium line $\rightarrow$ X-relay

Long line $\rightarrow$ Mho relay.

3) Where the power swings are high Mho relay is used.

4) For ~~some~~ over load protectⁿ of Gtr thermal relays are used.

5) For severe unbalance condition of alternator negative.

sequence relay is used to

When prime mover/turbine is lost alternator acts like induction generator. synchronous motor.

for this problem direction reverse wattmeter relay is used.

3) when the excitation is lost alternator acts as synchronous motor for this problem offset Mho relay is used.

4) for ~~in-tur~~ inter-turn fault differential fault protection can not be used. for this problem split-phase relay is used.


5) for stator winding protection differential protection is used.

6) A differential protection comparing voltages is known as translay relay.

7) to avoid the 'mal operation' of relays due to initial inrush currents of vacuum harmonic restrain relay is used.

8) Pilot wire relaying is not economical for the protection of long line. for such line differential protection is provided using carrier communication.

#

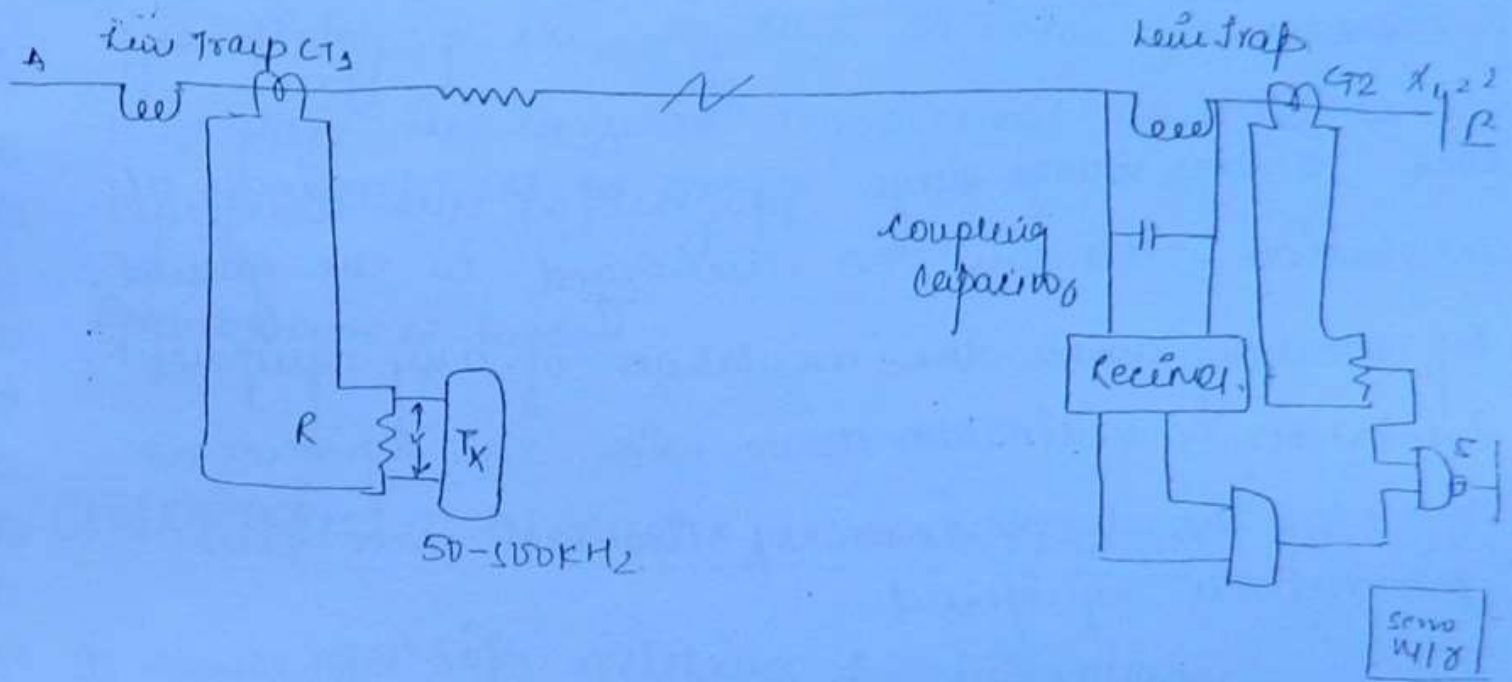


- The frequency of ~~any~~ carrier signal will be in range $50 \times 500 \text{ KHz}$ and some times it may go to GHz depending upon distance of T.L.
- A line or wave trap is a resonant LC circuit, shall & resonate for carrier frequency and ~~pi~~-passes 50 Hz signal. In other words they offer high resistance for carrier signal and low resistance for 50 Hz .
- A coupling capacitor blocks the 50 Hz signal and transmits the carrier signal.


INSULATION Co-ordination CONDITION

When a over voltage surge appears ^{on} the terminals of substation this can be discharged to the ground by breaking down the insulation of any equipment. Insulation co-ordination deals with the sequence at which the break down of insulatⁿ take place for various equipment.

Breakdown characteristic:

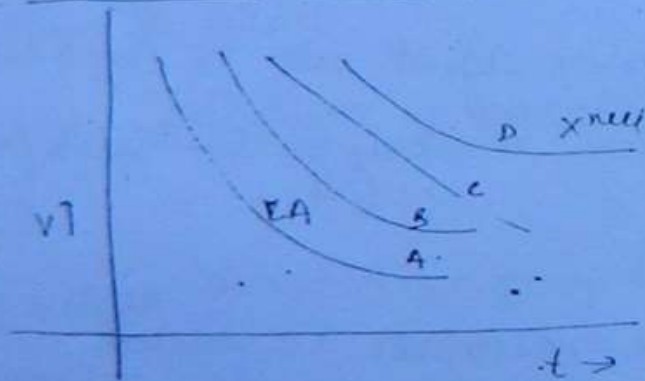

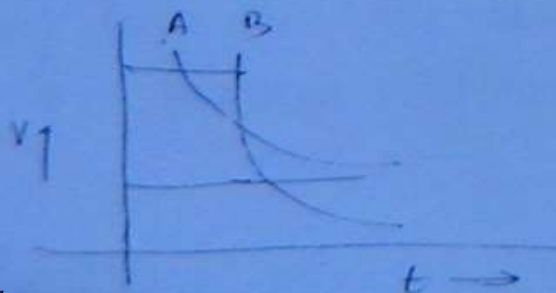- For proper insulation coordinatⁿ of lightning arrestor must be found below than any other equipment breakdown characteristic and the breakdown characteristic of most important equipment should be place above all other equipment.




- For proper insulation co-ordinatⁿ, the breakdown charac. should not cut and overlap each other.

After fixing up the sequence at which breakdown take place. the insulatⁿ requirement for various equipment will be designed.


Requirements of such

CHARACTERISTIC OF SURGE DIVERTOR / LIGHTING ARRESTOR

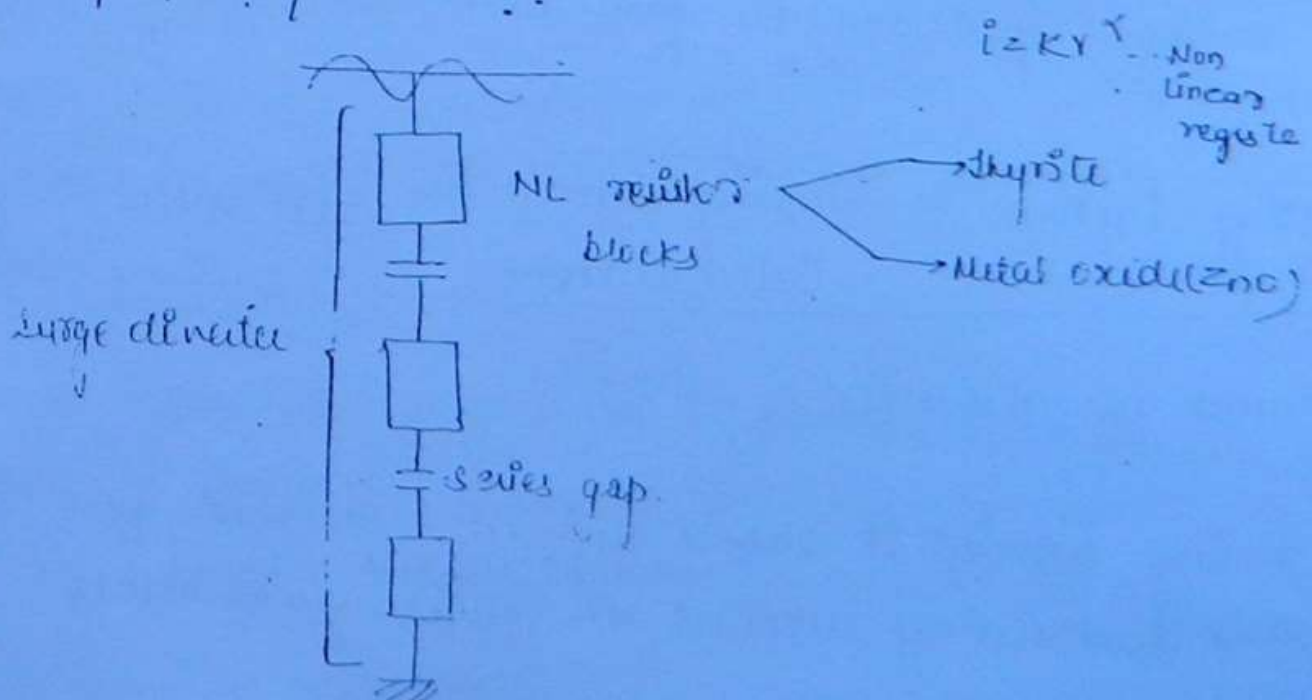- 1) It should offer high resistance for low voltages
- 2) It should offer low resistance for high voltage.
- 3) Arcing should not be continued due to power frequency follow currents.



Types of lightning arrestors:-

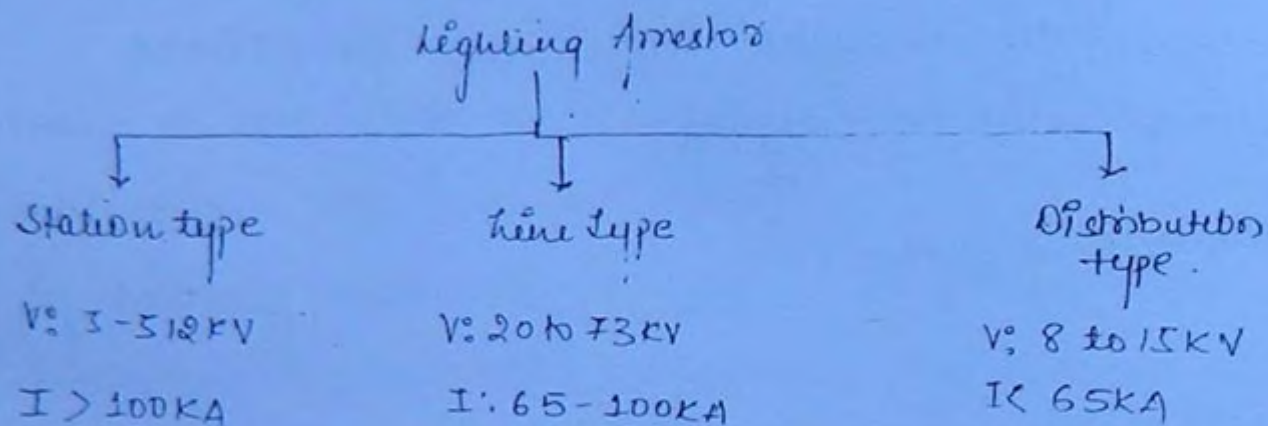

- These voltages are r.m.s. phase voltages of switching voltage.
- In descending order of cost of fused material the various fused material are Platinum, gold, silver, copper, Aluminium, Tin, lead.
- For current up to 10A Tin fuse, above 10A Copper fuses are used.
- $\text{Fusing Factor} = \frac{\text{Fusing Current}}{\text{Rated Current}}$

, this value should be around 2.
- Fusing current is rated current at which fuse melts and cut-off current, ^{actual current} at which fuse melts.
- Fuse should have melting point temp.

- A fuse protect equipment from prospective current.

ECONOMIC SCHEDULING

- the problem of economic scheduling first began with unit commitment. A unit commitment problem suggest the schedule of the unit must be kept on or off. Unit commitment problem is more complex because of variety of constraints present in the problem. Following the schedule, the economic scheduling problem allocate the load among the unit in service in such a way the total cost of generation is minimum.
- Optimum power flow problem is similar to economic scheduling problem. The only difference is OPF is very complex due to concentration of large variety of constraints.

Dated
15 Nov 2020

Economic scheduling Problem:-

→ is an optimization problem.

→ objective function

$$\min [C_T(P)] = \min \left[\sum_{i=1}^n C_i(P_i) \right]$$

→ Subject to the satisfaction of ~~equation~~ equality/inequality constraint.

Constraint

Equality

1) Load flow solution must be obtained

$$2) \sum P_i - P_D = 0$$

--- without losses

$$3) \sum P_i - P_D - P_{loss} = 0$$

--- with losses

Inequality

1) Generator power limits
 $P_{i\min} \leq P_i \leq P_{i\max}$


2) Transformer tap setting
 $t_{\min} \leq t \leq t_{\max}$

3) Voltage limits.

4) T.L thermal capabilities

CHARACTERISTIC OF THERMAL UNIT


1) HEAT CURVE:

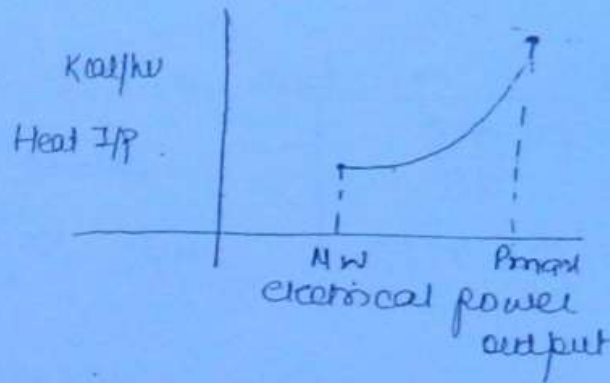

- Slope of this graph is known as "Heat rate"

$$\text{slope} = \text{Heat rate} = \frac{df_i}{dP_i}$$

2) COST CURVES:-

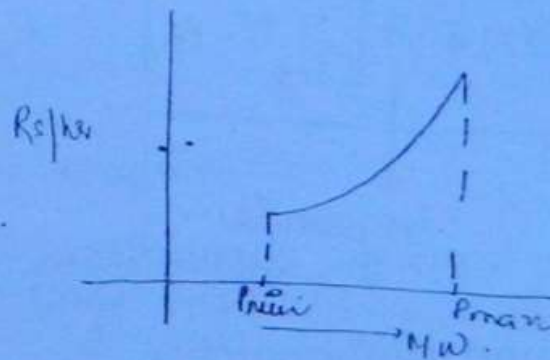

— using the parabolic eqn, the equation of cost curve is

$$C_i = \alpha_i + \beta_i P_i + \gamma_i P_i^2$$

α_i β_i γ_i --- cost coefficient of i^{th} M/C

for $i = 1, 2, \dots, n$

- the slope of this curve is known as "Incremental cost of production (IC)".

$$\text{slope} = IC_i = \frac{dC_i}{dP_i} = \beta_i + \gamma_i P_i$$

unit- Rs/Wh.

Economic scheduling problem by neglecting losses? - (Method of Lagrangian)

- we define Lagrangian funcⁿ as

$$L = \sum_{i=1}^n C_i(P_i) + \lambda \left[\sum_{i=1}^n P_i - P_D \right]$$

↓
Lagrangian multiplier.

- for objective function minimization

$$\frac{dL}{dP_i} = 0 \quad i = 1, 2, \dots, n.$$

$$\frac{dL}{dP_i} = \frac{dC_i}{dP_i} - \lambda [1] = 0$$

condition of cost minimization is

$$\frac{dQ}{dh} \quad \boxed{\frac{dC_1}{dh} = \frac{dC_2}{dh} = \dots = \frac{dC_n}{dh} = \lambda} \quad \text{coordinate eqn}$$

- the unit of $\lambda \rightarrow \text{Rs/MWh}$, and it is also known as cost of received power.

Algorithm -

1. start with $\lambda = \lambda^0$

2. $P_D = P_1 + P_2 + \dots + P_n$

3. solve for using

$$\frac{dC_i}{dP_i} = \lambda^0 = B_i + X_i P_i \quad \text{for } i = 1, 2, \dots, n$$

3. Check $\left| \sum_{i=1}^n P_i - P_D \right| \leq \epsilon$ $\epsilon = \text{error}$

Give solution

If $\sum P_i - P_D \rightarrow$ (demand more, fr less) large negative $\dots$ increase λ

Or $\sum P_i - P_D \rightarrow$ (cgr more demand less) large positive $\dots$ decrease λ

4. Repeat problem

- In the iteration process if any unit violates the limit then set the generation of that unit as $P_i = P_{\text{min}} \text{ or } P_{\text{max}}$

$P_i = P_i^{\text{min}}$ at the remaining load $P_D - P_i$ is optimally allocated in the remaining $(n-1)$ units (generating).

Numerical*

Increment cost of production in rupees/MWh for a plant consisting of two unit

$$\begin{array}{r} 1 \\ 56 \\ 0.2 \\ \hline 172 \end{array}$$

$$IC_1 = \frac{dC_1}{dP_1} = 0.2P_1 + 40 \quad \text{--- (1)}$$

$$IC_2 = \frac{dC_2}{dP_2} = 0.25P_2 + 30 \quad \text{--- (2)}$$

Assume both the unit in operation vary, a total load varies from 40 to 250 MW

$$P_D = 40 \rightarrow 250 \text{ MW}$$

$$P_i^{\text{min}} = 20 \text{ MW}$$

$$P_i^{\text{max}} = 125 \text{ MW for } i=1, 2$$

Solution:-

how will the load is shared when the load varies from 40 MW to 250 MW.

$$1) P_D = 40 \text{ MW}$$

$$\text{Let } P_1 = P_2 = 20 \text{ MW}$$

$$IC_1 = 0.2 \times 40 + 40 = 48 \text{ Rs/MWh}$$

$$IC_2 = 0.25 \times 20 + 30 = 35 \text{ Rs/MWh}$$

P_1	P_2	P_D	Plant A
—	40 MW	40 MW	—
—	60 MW	60 MW	—
20 MW	56 MW	76 MW	44
33.33	66.66	100	46.6
61.11	88.88	150	52.2
88.89	111.11	200	57.7
106.95	143.05	250	61.25

→ Beginning of economic dispatch

→ Economic dispatch

- for minimum load we start plant (2)

- When a minimum load of 20 MW

$IC_1 = 44 \text{ Rs/MWh}$ for what load of

P_2 $IC_2 = 44 \text{ Rs/MWh}$

$$44 = 0.25 \times P_2 + 30$$

$$P_2 = 56 \text{ MW}$$

8) $P_D = 100 \text{ MW}$

i.e. $P_1 + P_2 = 100 \text{ MW}$

$$\rightarrow IC_1 = IC_2$$

$$\text{SO } 0.2P_1 - 0.25P_2 = -10$$

$$P_1 = 83.33 \text{ MW}$$

$$P_2 = 66.66 \text{ MW}$$

120	125	245	—
125	125	250	—

* When any plant reaches 125 MW the economic control stops.

With 125 MW

$$IC_1 = 0.2 \times 125 + 40 = \text{Rs } 65/\text{MWh}$$

$$IC_2 = 0.25 \times 125 + 30 = \text{Rs } 61.25/\text{MWh}$$

Question 2 -

The Incremental generating cost of two generating unit are given by

$$IC_1 = 0.1x + 20$$

$$IC_2 = 0.1y + 18 \text{ Rs/MWh}$$

In a total load demand of 3000 MW the value

value of x and y ?

$$x + y = 360$$

$$0.1x + 20 +$$

$$0.1x - 0.15y = -2$$

$$x = 172 \text{ MW} \quad y = 188 \text{ MW}$$

the incremental cost of production of ~~two~~³ units are.

$$IC_1 = 0.00284P_1 + 7.2$$

$$IC_2 = 0.00388P_2 + 7.85$$

$$IC_3 = 0.00364P_3 + 7.97$$

find optimum scheduling for total load of 850 MW.

$$P_1 + P_2 + P_3 = 850 \quad \text{--- (1)}$$

$$IC_1 = IC_2$$

$$IC_3 = IC_1$$

$$0.00284P_1 + 7.2 = 0.00388P_2 + 7.85$$

$$\frac{0.00284P_1 + 7.2 - 7.85}{0.00388} = P_2$$

$$\frac{0.00284P_1 + 7.2 - 7.97}{0.00364} = P_3$$

$$P_1 + (0.731P_1 - 16.52) + (0.234P_1 - 79.875) = 850$$

$$P_1 = 541.92 \text{ MW}$$

$$P_2 = 228.62 \text{ MW}$$

$$P_3 = 794.4 \text{ MW}$$

Economic power solution (considering the losses)

• objective function

$$\min \left(\sum_{i=1}^n C_i \cdot P_i \right)$$

• subject to

$$\sum_{i=1}^n P_i - P_D - P_{\text{loss}} = 0$$

Lagrangian fn is defined as

$$L = \sum_{i=1}^n C_i(P_i) - \lambda \left[\sum_{i=1}^n P_i - P_D - P_{\text{loss}} \right]$$

objective function is minimised when

$$\frac{dL}{dP_i} = 0 \Rightarrow \frac{dC_i}{dP_i} - \lambda \left[1 - \frac{dP_{\text{loss}}}{dP_i} \right]$$

Let $\frac{dP_{\text{loss}}}{dP_i}$ = Incremental T.L losses

Penalty factor $L_i = \frac{1}{1 - \frac{\partial P_{\text{loss}}}{\partial P_i}}$ for $i = 1, 2, \dots, n$

then

$$L_1 \frac{dC_1}{dP_1} = L_2 \frac{dC_2}{dP_2} = \dots = L_n \frac{dC_n}{dP_n} = \lambda$$

-- co-ordinate equation

penalty factor of i^{th} u/c is

$$L_i = \frac{1}{1 - \frac{\partial P_{loss}}{\partial P_i}}$$

the loss equation for a two plant system is

$$P_{loss} = \sum_{m=1}^n \sum_{n=1}^n B_{mn} P_m P_n$$

when

$P_m, P_n \rightarrow$ generation of two units

$B_{mn}, B_{nn} \rightarrow$ loss coefficients

$\rightarrow$ let $m=1$

$$\begin{aligned} n=1 \quad P_{loss} &= B_{11} P_1 P_1 \\ &= B_{11} P_1^2 \end{aligned}$$

$n=2$

$$P_{loss} = B_{12} P_1 P_2$$

$n=2$


$$\begin{aligned} n=1 \quad P_{loss} &= B_{22} P_2 P_2 \\ &= B_{22} P_2^2 \end{aligned}$$

Total loss

$$P_{loss} = B_{11} P_1^2 + 2 B_{12} P_1 P_2 + B_{22} P_2^2$$

$$B_{12} = B_{21}$$

Case 1: Load connect near plant 1:

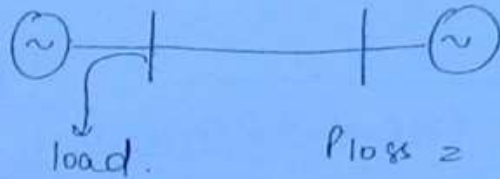


$$P_{loss} = B_{22} P_2^2$$

$$B_{11} = B_{12} = B_{21} = 0$$

Penalty factor $L_1 = \frac{1}{1 - \frac{\partial P_{loss}}{\partial P_1}} = \frac{1}{1-0} = 1$

$$L_2 = \frac{1}{1 - \frac{\partial P_{loss}}{\partial P_2}} = \frac{1}{1 - 2B_{22}P_2} > 1$$

Case 2: Load connected near plant 2

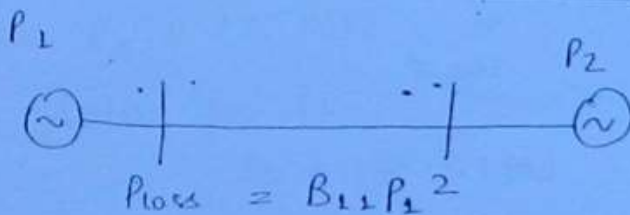

$$P_{loss} = B_{11} P_1^2$$

$$B_{22} = B_{21} = B_{12} = 0$$

$$L_1 = \frac{1}{1 - 2B_{11}P_1} > 1$$

$$L_2 = \frac{1}{1-0} = 1$$

Case 3: Load connected near both plants. Plants




$$P_{loss} = b_{11} P_1^2 + 2B_{12} P_1 P_2 + B_{22} P_2^2$$

$$L_1 = \frac{1}{1 - \frac{\partial P_{loss}}{\partial P_1}} = \frac{1}{1 - (2B_{11} P_1 + 2B_{12} P_2)} > 1$$

$$L_2 = \frac{1}{1 - \frac{\partial P_{loss}}{\partial P_2}} = \frac{1}{1 - (2B_{22} P_2 + 2B_{12} P_1)} > 1$$

Numerical

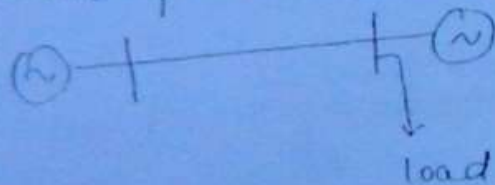A two bus sys is shown in figure, if 100MW power is transfer plant 1 to load. a 100 transmission loss 10MW is accrued. Find the required gen for each plant and the power reached by the load when sys is



P

$$P_1 = 0.02 P_2 + 16 \text{ Rs/MWh}$$

$$P_2 = 0.02 P_2 + 20 \text{ Rs/MWh}$$

soln

$$P_{loss} = B_{11} P_1^2$$

$$10 \text{ MW} = B_{11} \times 100^2 \text{ MW}$$

$$B_{11} = \frac{10}{100 \times 100}$$

$$= 0.001 \text{ MW}^{-1}$$

$$P_{loss} = 0.001 P_1^2$$

$$L_1 = \frac{1}{1 - \frac{\partial P_{loss}}{\partial P_1}} = \frac{1}{1 - 0.002 P_1} \quad \text{--- (1)}$$

$$L_2 = \frac{1}{1 - 0} = 1 \quad \text{--- (2)}$$

co-ordinate eqn.

$$L \frac{dC_1}{dP_1} = A \quad \text{--- (3)}$$

$$> \frac{1}{1 - 0.002 P_1} \times (0.02 P_1 + 16) > 25$$

$$L_2 \frac{dC_2}{dP_2} = A$$

$$= 0.04 P_2 + 20 > 25 \text{ Rs/MWh}$$

$$0.04 P_2 > 5 \text{ Rs/MWh}$$

solving P_2

$$P_2 > 125 \text{ MW}$$

Solve for P_1

$$P_1 > 128.5 \text{ MW}$$

$$P_{loss} > 0.001 P_1^2$$

$$= 0.001 \times 128.5^2$$

~~Solving $P_1 > P_2$~~

$$P_0 > P_1 - P_2 > P_{loss}$$

$$> 231.04 \text{ MW}$$

Given the incremental product cost 2nd unit

$$IC_1 = P_1 + 85 \text{ Rs/MW}$$

$$IC_2 = 1.2P_2 + 72 \text{ Rs/MW}$$

Given the B matrix

$$B = \begin{bmatrix} 0.015 & -0.001 \\ -0.001 & 0.02 \end{bmatrix}$$

for $\lambda = 150 \text{ Rs/MW}$

find P_1, P_2, P_{loss}, P_D

Soln

$$P_{loss} = 0.015 P_1^2$$

$$= -2 \times 0.001 P_1 P_2 + 0.02 B_{22} P_2$$

Ans

$$P_1 = 12.4 \text{ MW}$$

$$P_2 = 11.3 \text{ MW}$$

$$P_{loss} = 4.64 \text{ MW}$$

$$P_D = 19.88$$

$$\frac{\partial P_{loss}}{\partial P_1} = 0.03 P_1 = 0.002 P_2$$

$$\frac{\partial P_{loss}}{\partial P_2} = -0.002 P_1 + 0.04 P_2$$

$$L_1 = \frac{1}{1 - \frac{\partial P_{loss}}{\partial P_1}} = \frac{1}{1 - 0.03 P_1 - 0.02 P_2}$$

$$L_1 \frac{dC_1}{dP_1} = L_2 \frac{dC_2}{dP_2} =$$

$$\frac{1}{1 - 0.03P_1 + 0.002P_2} \times (P_1 + 85) = 150$$

$$\frac{1}{1 + 0.02P_1 - 0.04P_2} \times (1.2P_2 + 72) = 150$$


POWER System Stability

→ power of any m/c $\propto D^2 n_s$ where $D \rightarrow$ diameter
 $L \rightarrow$ length of shaft
 $n_s \rightarrow$ speed.

- power sys stability refers to the ability of power sys machines working in power sys to maintain synchronism after the disturbance.
- Whenever there is imbalance in the mechanical input and electrical power output the rotor of alternator may start accelerating or decelerating. If all the machines are accelerating or decelerating at the same rate then they form a coherent group. Coherent group of machines will not pose a problem of synchronism. Practically ^{owing to} differences in inertias, size and rating the machines can not form a coherent group.

- If the synchronism is lost there will be wild fluctuations in voltage and currents. That may lead to tripping of machine and collapse of the machine.
- Power system stability problem is also known as angular stability problem, is occurring mainly due to generator dynamics
- Voltage stability problem is due to load dynamics whereas angular ~~stang~~ stability problem is due to generator dynamics

FORMS OF STABILITY

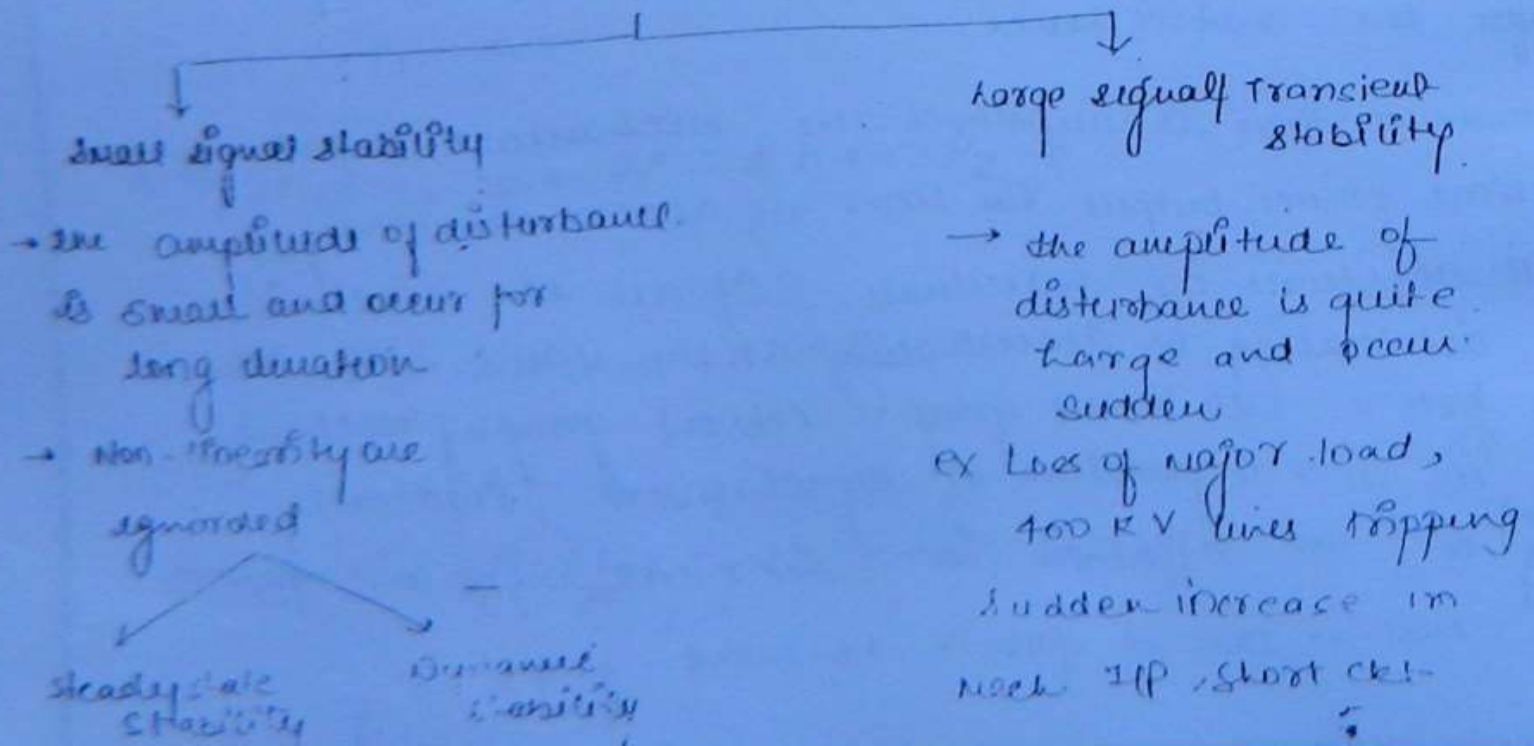

→ steady state stability

- the action of control $\frac{AVR}{exciter}$ d.c. are not included.

- Pessimistic Results.

→ Dynamic stability

- the control $\frac{AVR}{exciter}$ components are considered.
- optimistic Results.

→ Non-linearities are considered and they play vital role in this

→ Study is completed in 1 sec

→ the action of AVR, exciter are not included since these are slow acting devices

Steady state stability

Dynamic stability

Transient stability

- study period is from several min to hours

- study period $< 1 \text{ sec}$

NOTE :

Dynamic study is evaluated by developing the matrices

$$\dot{x} = Ax + Bu, \text{ where } [A] \text{ is s/m matrix, after developing}$$

the system matrix A we find the eigen values of A

for s/m to be stable the values must be found on left hand side of the s-plane. Various types of stabilizers and controllers are designed to maintain stability

As these stabilizers used the linearized power s/m model their effectiveness for transient stability problem is less



STABILITY LIMIT:-

- ~~security~~ The amount of power that will be transferred to the point of disturbance to maintain the stability is known as stability limit.
- Compare dynamic stability limit is highest and transient stability limit is lowest.
- Transient stability limit can be improved up to steady state stability limit but beyond this is not possible.

Q. system highest steady state stability limit is guaranteed for high transient stability?

- No, because system non-linearity plays a vital role.
- [A sys. with high transient stability guarantees the high steady state stability]

MODELLING ISSUES

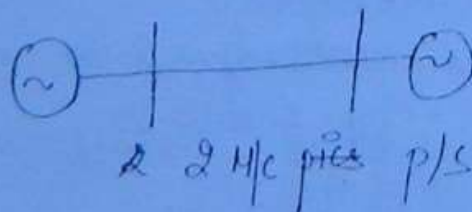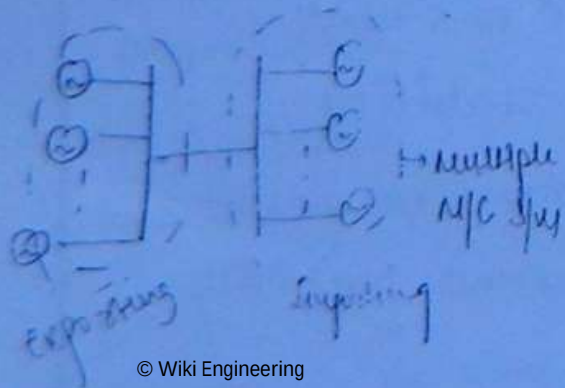

If an alternator is connected to Induction M/C, system may become unstable, but stability (synchronism) is never lost. However if an alternator is connected to synchronous M/C, system may become unstable or it may lose the stability (synchronism).

A two M/C system can be further reduced to a single M/C a single machine connected to infinite bus system. In such SMIP sys., if the disturbance is present it affects only generated dynamics.

SWING EQUATION

- this equation describes rotor dynamics of synchronous M/C
- whenever there is an imbalance bt mech. input to electrical power output, the rotor of alternator either accelerates or decelerates.

Acceleration Torque

$$T_a = T_m - T_e = \frac{I}{\omega_s} \frac{d^2\delta}{dt^2} \rightarrow \text{acceleration}$$

T_a → accelerating torque
 T_m → mechanical input
 T_e → mech equivalent torque

I → Inertia constant in Kg-m^2

multiplying on both sides with ' ω '

$$T_a \omega = T_m \omega - T_e \omega = I \omega \cdot \frac{d^2 \delta}{dt^2}$$

i.e

$$P_a = P_m - P_e = M \frac{d^2 \delta}{dt^2}$$

M = Inertia constant

M can be obtained from $M = I \omega$ eqn.

or by using another inertia constant ' H '

$$H = \frac{\text{stored KE (in MJ)}}{\text{Rating of M/C G (MVA)}}$$

from above stored K.E = $G \cdot H$.


from Law of Mechani

$$\text{* Stored K.E} = \frac{1}{2} I \omega^2 = \frac{1}{2} M \omega$$

$$\text{Stored KE} = \frac{1}{2} M \omega = G H.$$

$$M = \frac{G H}{\pi f} \frac{\text{MW-sec}}{\text{elect-rad.}}$$
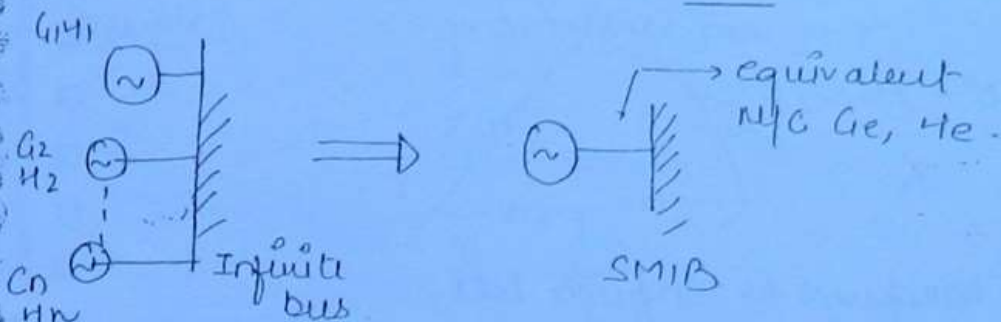
$$\rightarrow \frac{G H}{180 f} \frac{\text{MW-sec}}{\text{elec-rad degree}}$$



multiple M/Gs

$$\text{shorted KE} = G_e H_e$$


$$= G_1 H_1 + G_2 H_2 + \dots + G_n H_n$$

$$H_e = \left(\frac{G_1 H_1}{G_e} \right) + \left(\frac{G_2 H_2}{G_e} \right) + \dots + \left(\frac{G_n H_n}{G_e} \right)$$

if $G_e = G_{base}$

$$H_e(\text{imp.u}) = \frac{G_1 H_1}{G_{base}} + \frac{G_2 H_2}{G_{base}} + \dots + \frac{G_n H_n}{G_{base}}$$

POWER ANGLE CURVE AND TRANSFER REACTANCE

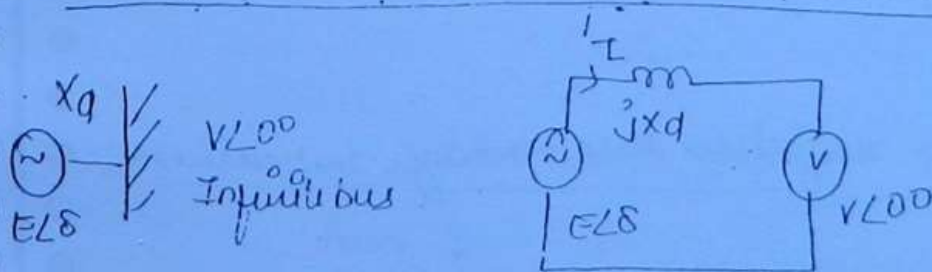

$$I = \frac{E\delta - VL00}{jX_d} = \frac{E\delta - VL00}{jX_d} \times \frac{j}{j}$$

$$= \frac{(E\delta - VL00) \times j}{j^2 X_d}$$

$$I = \frac{j VL00 - E\delta}{X_d}$$

$$= \frac{VL90^\circ - E \angle \delta + 90^\circ}{X}$$

Complex power transferred to infinite bus.

$$S = VI^* = VE \times \left[\frac{VL90^\circ - E \angle \delta + 90^\circ}{X_d} \right]$$

$$S = \frac{V^2 \angle -90^\circ - EV \angle (\delta - 90^\circ)}{X_d}$$


$$S = \frac{-jV^2 - EV(\cos(\delta + 90^\circ) - j\sin(\delta + 90^\circ))}{X_d}$$

$$\Rightarrow \frac{-jV^2 - EV[-\sin\delta + j\cos\delta]}{X_d}$$

$$S = \frac{EV}{X_d} \sin\delta - j \left[\frac{V^2}{X_d} - \frac{EV \cos\delta}{X_d} \right]$$

$$S = P - jQ$$

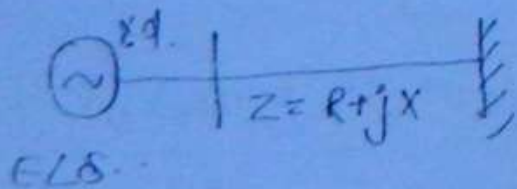Generator connected to infinite bus through impedance:-





$$P_e = \frac{EV}{X} \sin\delta$$

$$X = X_d + X'_{dr}$$

© Wiki Engineering it is the reactance that appears at sending end and receiving end terminal www.raghul.org

Example:

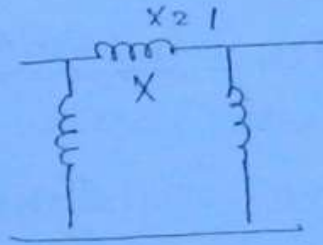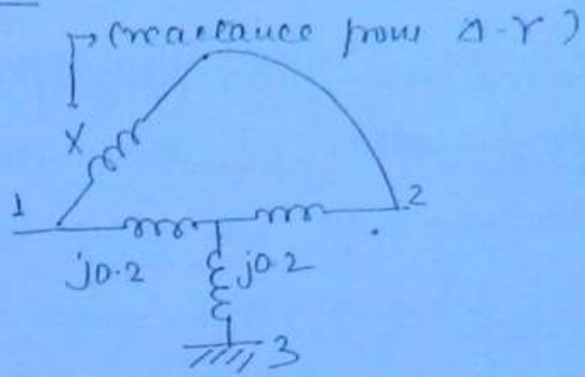

$$X = X_1 + X_2 + \frac{X_1 X_2}{X_3}$$

at $X = \sqrt{3}R \rightarrow \text{max}^{\text{m}}$ power transfer


Power angle curve:-

$P_e = \text{electrical power transferred}$

$$= \frac{E V \sin \delta}{X}$$

$\frac{E V}{X} \rightarrow \text{steady state power limit}$

$X \propto \text{transfer reactance}$

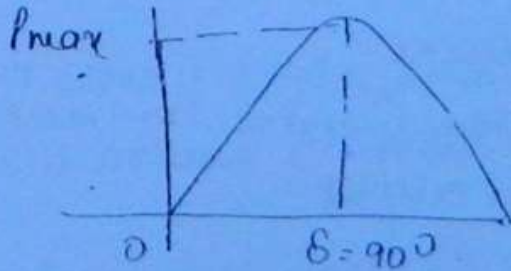


- In ac TL for transfer of electrical power reactance is compulsory, resistance is not required

the condition for maximum power transfer in a short T.L is $X = \sqrt{3}R$.

STABILITY STATE



Steady state stability: EVALUATION TECH

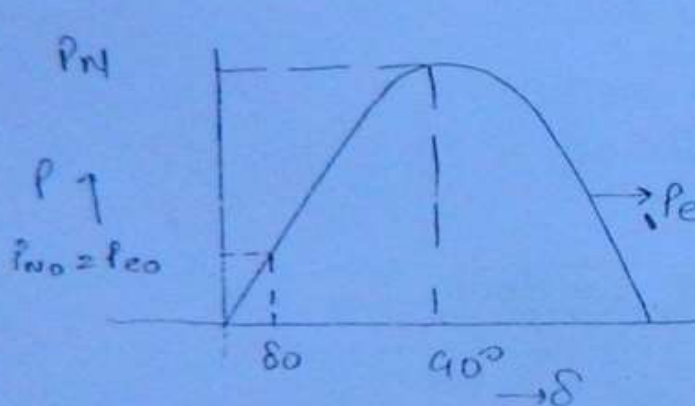

$$\frac{dP}{d\delta} > 0 \text{ at } \delta < 90^\circ$$

$$\frac{dP}{d\delta} = 0 \text{ at } \delta = 90^\circ$$
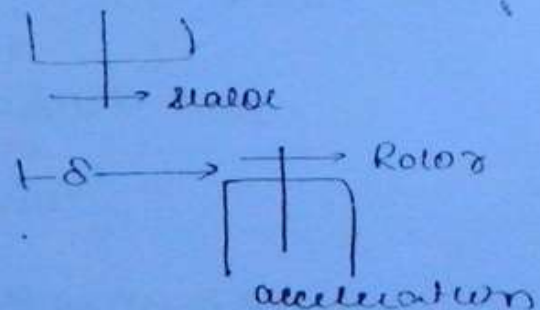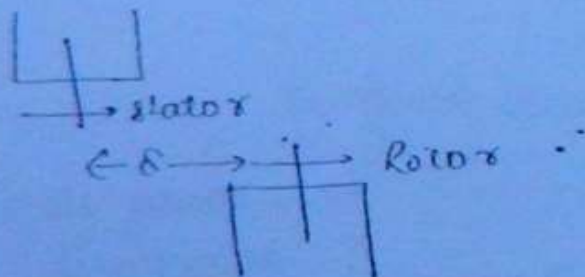
$$\frac{dP}{d\delta} < 0 \text{ at } \delta > 90^\circ$$



- when δ increases P_e increases
- when δ crosses 90° , any further increase in mech. HP decreases the electrical output.
- $\frac{dP_e}{d\delta}$ - synchronizing power coefficient (diff. of electrical w/c)
- $P_m \cos \delta$

when δ is changing from $0-90^\circ$, the electrical power output increase and for delta above 90° , the electrical power output decreases. If a mechanical input is increased, when rotor angle $[\delta = 90^\circ]$ say, the extra mechanical input store as K.E in the rotor, the rotor start accelerate and delta increases. The increase in delta reduces electrical power output this gives further acceleration and increase in δ . finally the system will reach the point when $P_e = 0$


NOTE:

- System has steady state stability as long as $\frac{dP}{d\delta} > 0$
- system loss stability when $\frac{dP}{d\delta} < 0$
- $\frac{dP}{d\delta} > 0$ when $0 < \delta < 90^\circ$, beyond $\delta = 90^\circ$, $\frac{dP}{d\delta}$ is -ve.
- system cannot have steady state stability beyond $\delta = 90^\circ$, In power system in order to have good steady state stability margins, δ is maintained around 30° to 40°

Eq Evaluation Technique-2:

$$\frac{\Delta P_{ec}}{\Delta \delta_0} \approx \frac{dP_e}{d\delta}$$

- linearized diff. eqn -

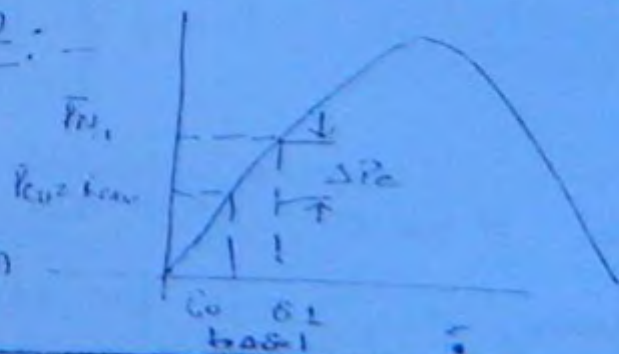

$$\Delta p_{e0} = \left(\frac{dp_e}{d\delta} \right) \cdot \Delta \delta_0 \quad \text{--- (1)}$$

accelerating energy

$$p_a = p_{m0} - (p_{e0} + \Delta p_{e0})$$

$$p_a = p_{m0} - (p_{e0} + \Delta p_{e0}) = \frac{M d^2 \delta}{dt^2}$$

$$\cancel{p_{e0}} - \cancel{p_{e0}} - \Delta p_{e0} = \frac{M d^2 \delta}{dt^2}$$

$$\frac{M d^2 \delta}{dt^2} = -\Delta p_{e0} \quad \text{--- (2)}$$

substitute eqn (2) in (1)

$$\frac{M d^2 \delta}{dt^2} + \left(\frac{dp_e}{d\delta} \right) \cdot \Delta \delta_0 = 0$$

let operator $p = \frac{d}{dt}$; $p^2 = \frac{d^2}{dt^2}$

$$(M p^2 + \frac{dp_e}{d\delta}) \Delta \delta = 0$$

roots of characteristic equation are

$$p = \pm \left[\frac{-\left(\frac{dp_e}{d\delta} \right)}{M} \right]^{0.5} = \pm j \omega_n$$

- When $\frac{dp_e}{d\delta} > 0$, s/m has 2 conjugate poles on imaginary axis for this condition system is


stable with undamped frequency of oscillation. However the inertial force are considered. These accelerations will be damped after some time.

- when $\frac{dP}{d\delta} < 0$, the system has two real poles, one on right axis and other on left axis. Indication of poles on R.H.S is indication for loss of stability.

•# Improvement of Steady state & stability:-

$$P_e = P_{max} \sin \delta$$

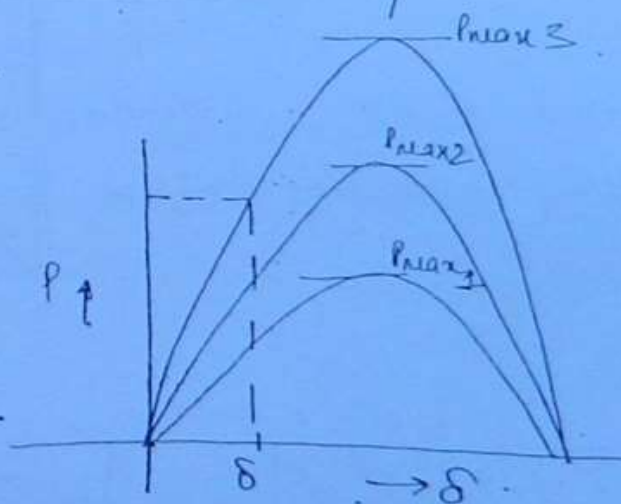- By improving ss power limit as for given value of δ we can transfer more electrical power.




$$P_{max} = \frac{EV}{X}$$

- 1) Operate T.L at high voltage
- 2) Reduce the reactance X .

for bundle

$$L = 2 \times 10^{-7} \ln \frac{D_m}{D_s}$$

$P_s \uparrow L \downarrow$

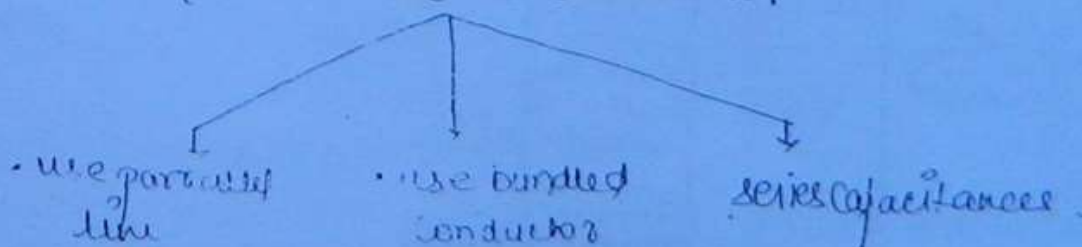


series → capacitor → improve steady state power line
 → reactor → Isc ↓

shunt reactor → to reduce ferranti effect
 → capacitor → to improve

Dated
 17 Nov 2010

TRANSIENT STABILITY:-

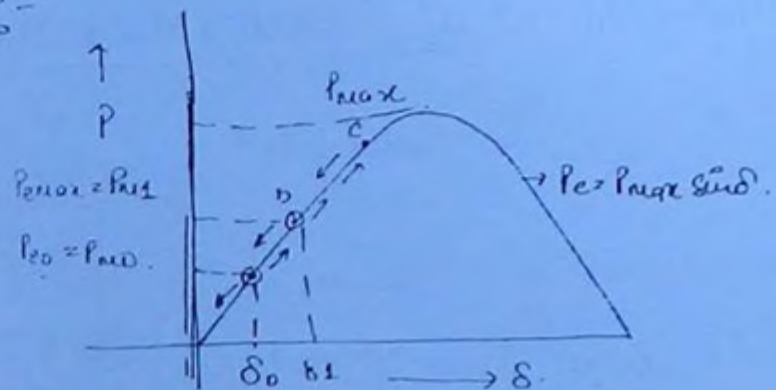

Operating Point	δ value	Load angle	Acceleration & Deceleration	P_a	Remark
a	$\delta = \delta_0$	$N_r = N_c$	None	$P_a = 0$	equilibrium [mechanical suddenly raised]
a-b	$\delta \uparrow$	$N_r > N_c$	Accelerat ⁿ	$P_a > 0$	-
b	$\delta = \delta_1$	$N_r > N_c$	Accelerat ⁿ stops	$P_a = 0$	-
b-c	$\delta \uparrow$	$N_r > N_c$	Decelerat ⁿ	$P_a < 0$	Subsides auto induction
c	$\delta = \delta_2$	$N_r > N_c$	Decelerat ⁿ	$P_a < 0$	Inertia absent
c-b	$\delta \downarrow$	$N_r > N_c$	-do-	-do-	

b	$\delta = \delta_1$	$N_A < N_C$	Decelerat ⁿ STOP	$P_a > 0$	—
b-a	$\delta \downarrow$	$N_A < N_C$	Accelerat ⁿ	$P_a > 0$	due to inertia
a	$\delta = \delta_0$	$N_A = N_C$	do —	$P_a > 0$	Inertia absent

CS speed here increases.

cycle repeats further.

NOTE:


- During this transient period, $\frac{d\delta}{dt}$ for some time it is positive and for another type time it is negative.

When these oscillations are died, system restores ~~from~~ stability condition, in other words transient stability is achieved when:

$$\boxed{\frac{d\delta}{dt} = 0}$$

LIMITING CASE:-

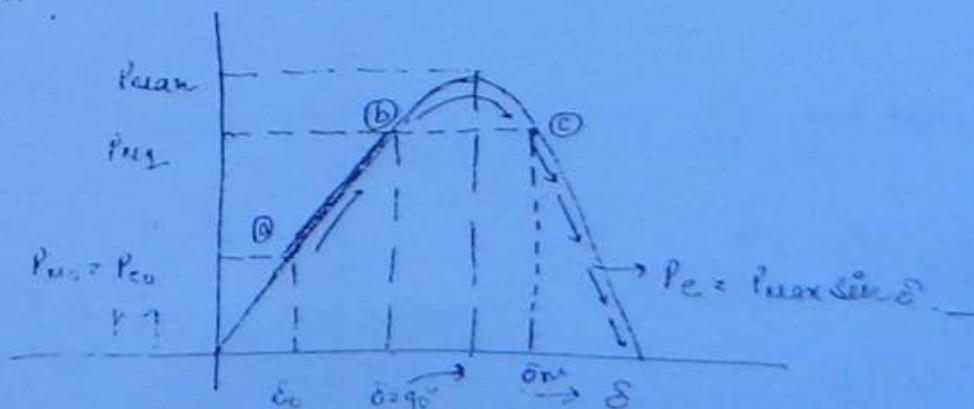From the present value of mechanical I/P to any value?



• electrical power input at point B and C are same.

$$\boxed{P_{max} \sin \delta_2 = P_{max} \sin \delta_1}$$

$$\sin \delta_2 = \sin \delta_1$$

$$\boxed{\delta_2 = \pi - \delta_1}$$

critical angle.

• &

If the mechanical input raised corresponding to $(\delta = \delta_c)$ the system is critically stable. During first swing rotor will travel upto δ_2 and may likely come back. During the first swing if δ crosses δ_c , then system is unstable.

EQUAL-AREA CRITERION

swing equatⁿ


$$M \frac{d^2 \delta}{dt^2} = P_a$$

$$\frac{d^2 \delta}{dt^2} = \frac{P_a}{M}$$


multiply both side by $\frac{d\delta}{dt}$

$$\frac{d\delta}{dt} \cdot \frac{d\delta}{dt} = \frac{P_a}{M} \cdot \frac{d\delta}{dt}$$

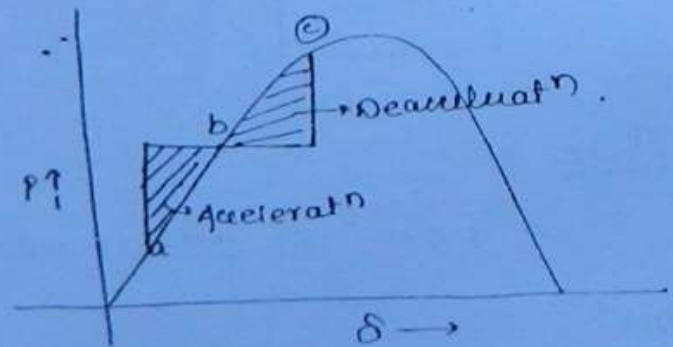
$$\frac{1}{2} \left[\frac{d}{dt} \left(\frac{d\delta}{dt} \right)^2 \right] = \frac{P_a}{M} \cdot \frac{d\delta}{dt}$$



during fault:

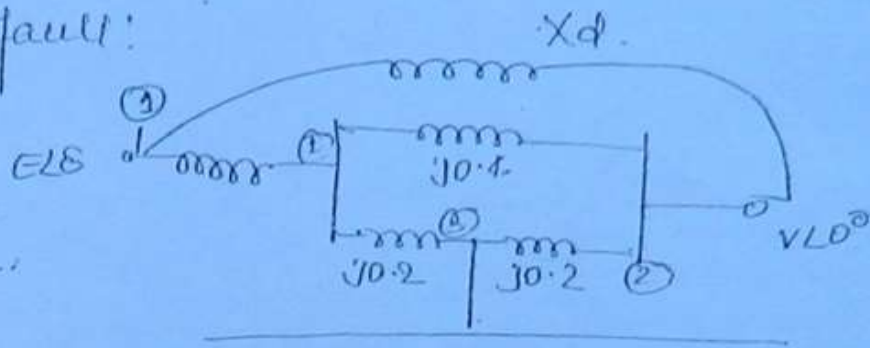

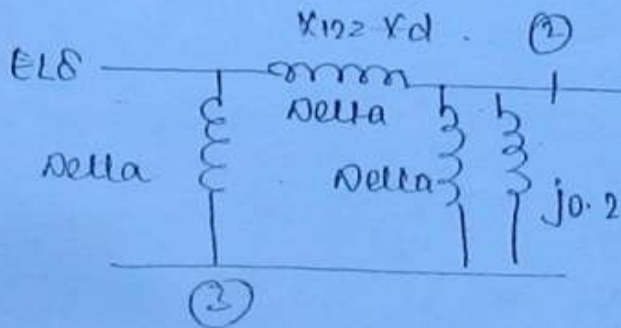convert star reactance bl- (1)(2), (2)(3) and (3)(1)



$$X_{12} = X_1 + X_2 + \frac{X_1 X_2}{X_3}$$

$$= j0.2 + j0.4 + \frac{j0.2 \times j0.4}{j0.2}$$

$$= j1$$

$$P_{maxd} = \frac{1.2 \times 1}{1} = 1.2 \text{ p.u.}$$

$$P_{ed} = 1.2 \sin \delta.$$



68.53

after fault

$$X_a = X_d + X_1 = 0.6 \text{ p.u.}$$

$$P_{maxa} = \frac{1.2 \times 1}{0.6}$$

$$P_{ea} = 2 \sin \delta.$$

$$\delta_m = \pi - \sin^{-1} \left(\frac{P_{mo}}{P_{maxa}} \right)$$

$$= \pi - \sin^{-1} \left(\frac{1.5}{2} \right)$$

$$= 131.4^\circ$$

$$\delta_0 = 30^\circ$$

POWER SYSTEM-II